

# Nuts & Volts

Exploring Electronics And Technology For The Hobbyist And Professional

[www.nutsvolts.com](http://www.nutsvolts.com)

August 1999 Vol. 20 No. 8

Ever wondered why your electric bill is so high?

Build the  
**Watts Showing™**  
digital meter kit,  
and you can  
accurately  
measure power  
consumption  
and calculate  
operating costs  
on anything that  
plugs into a  
120VAC outlet.

**EDISON**  
Customer Service Address  
T & PUBLISHING  
430 E PRINCETON RD  
CORONA CA 91719


Southern California Edison Company  
An EDISON INTERNATIONAL™ Company  
P.O. Box 600, Rosemead, CA 91771-0001

Date Bill Prepared  
July 01, 1999  
Next Meter


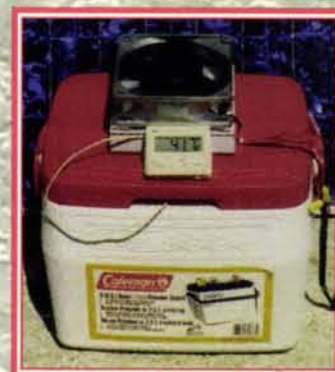
## HIGH "TEC" REFRIGERATOR

Build your own electric cooler for a quarter  
of the price you would normally pay,  
**plus** make it solar-powered.



U.S. \$3.50 CANADA \$5.00


08>



0 74470 89295 3



# MONSTER 47GB SCSI DRIVE

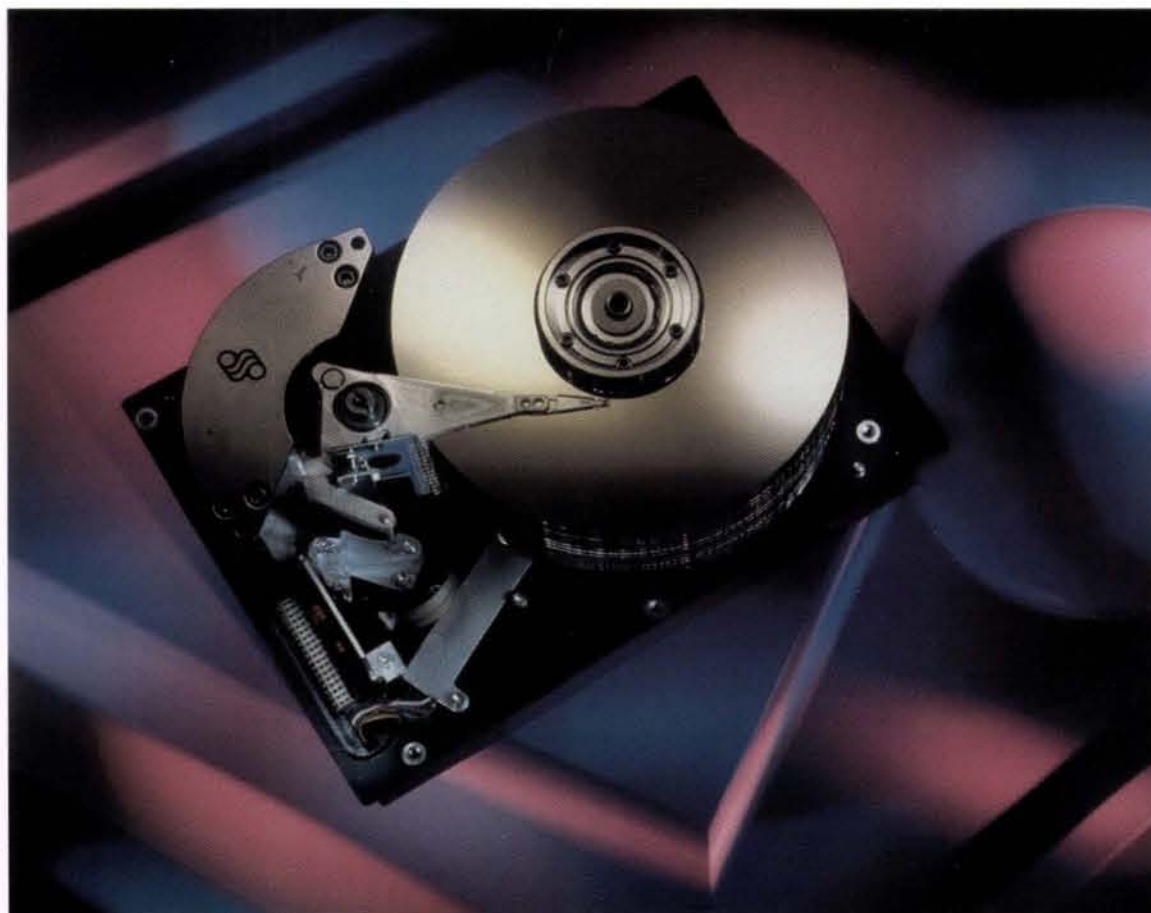

**\$895!**

**FREE SCSI ENCLOSURE  
408 330-5523**

Open Windows instantly. Process huge graphic and database files with ease. Make your file server scream with speed.

The 47GB Seagate Elite is the drive you need for serious performance. It features 14 disks and 28 heads for blazing performance 3.5" drives can't touch. The Ultra Wide interface makes installation a snap. A 4MB cache buffer accelerates data transfers.

A special volume purchase brings you brand new drives at low, low PC prices. Shop around. Compare price. No one else can match this deal.

Buy just one drive and build the ultimate workstation. Or add several to take advantage of NT RAID performance. Let us custom-build your multi-drive disk array at no extra charge. Redundant rack-mount trays stack to build arrays bigger than 1,000GB per rack!

Get the speed you need and the reliability you deserve. Get rock solid Seagate quality backed by a warranty of up to six years! Call now! Try your 47GB monster drive risk-free.



**CORPORATE SYSTEMS CENTER**  
3310 WOODWARD AVE., SANTA CLARA, CA 95054  
[WWW.SCSIDRIVES.COM](http://WWW.SCSIDRIVES.COM)

Seagate ST446452W drives are PC, Mac, SGI, and Sun compatible. 5 1/4" Elite drives are sold only in OEM enclosures and disk array trays. CSC carries low-cost, top-quality PCI controllers and SCSI accessories. If you haven't already upgraded to SCSI, call us for help. No-risk guarantee refunds your entire purchase price (less shipping) if you're not completely satisfied within 15 days. Call for your free catalog of hard drives, duplication equipment, and accessories.



# HSC Electronic Supply

Serving  
Silicon Valley  
since 1964!

...brings you a potpourri of high-tech goodies for the techno-tinkerer!  
For thirty years we have been your source for Silicon Valley exotica!

## Voltage Controlled Crystal Oscillators!

- ◆ +5VDC +/- 0.25V @ 40 mA
- ◆ Voltage Range: 1 - 4 VDC, frequency range: +/- 30 ppm
- ◆ Phase noise, -70 dBc @ 10 Hz to -140 dBc @ 100 KHz offset
- ◆ +/- 20 ppm @ -40 to +85 C, +/- 10 ppm aging over 10 yrs.
- ◆ Output power: 0 dBm +/- 2 dBm into 50 ohm load

SKU#	Frequency - MHz	1 - VC
HSC#18002	119.0625	2 - N/C
HSC#18003	77.86621	3 - VCC
HSC#18004	119.3710	4 - RF
HSC#18005	121.1210	5 - GND
HSC#18006	105.1562	
HSC#18007	103.9895	
HSC#18008	117.8958	

0 5	1 0
0 4	2 0
	3 0

New...90-day Warranty.....\$19.95

## SMD Voltage Controlled Crystal Oscillator!

- ◆ Frequency range: 1.205 - 1.315 GHz
- ◆ Model No. ID7F1
- ◆ VCC: +5VDC, Supply Current <= 10.0 mA
- ◆ Control Voltage Range: 0.5VDC - 4.5VDC
- ◆ Control Voltage Sensitivity: 35.0 +/- 5.0 mHz/V
- ◆ Stability: +/- 4000 kHz, -20C ~ +70C
- ◆ Pushing Fig: +/- 1000 kHz, 5.0, +/- 0.25 VDC
- ◆ Pulling Fig: +/- 1000 kHz, VSWR=2.0

HSC# 18001 \$19.95

## Power Supply

- ◆ LITEON 145W fan-cooled supply
- ◆ Perfect for bench use or motherboard test/development!
- ◆ Note: this is not standard tower-case form-factor.
- ◆ Input: 100-127VAC - 5A/200-240V - 2.5A, 50-60Hz
- ◆ Output: +5VDC/18.5A, -5VDC/0.3A, +5Vs/0.02A, +12VDC/4A, -12VDC/0.3A, +3.3VDC/7A
- ◆ Standard ATX-motherboard, disk drive power connectors
- ◆ Measures 2.75" x 4.125" x 6"
- ◆ New, 90-day warranty



HSC#17973 \$12.50

## Tiny Color CCD Camera!

- ◆ Last batch of these popular cameras found in warehouse!
- ◆ Camera-on-a-board measures 1.87" x 1.3", 1" thick!
- ◆ Has glass micro-lens element, not pinhole lens
- ◆ DSP on board for auto white-balance, shutter
- ◆ Standard NTSC composite video output
- ◆ 350 lines horiz. resolution, good low-light sensitivity
- ◆ Uses 4 - 5 VDC, only 150 mA! Three AA batteries would power it for over six hours!
- ◆ New in OEM pkg. (no box), 90-day HSC warranty



HSC#17736 \$89.95

## Rechargeable Battery Buy!

Three types of rechargeable battery for a variety of uses!

Amazing power in a small package! Nickel-Metal Hydride (Ni-MH) batteries have the capacity of Nicads without the "memory" effect. These are factory-new, not pulls!



- ◆ Toshiba 8TH-F5-F1-AIR, 9.6VDC at 600 mA, measures 4.5" x 1.875" x .25" thick (8 cells in series)
- ◆ Appears to have a thermal fuse for over-current protection

HSC#17871 \$17.50

...Or you can choose a NiCad battery pack in a similar form-factor. These are a flat array of cells, like the battery above, with handy solder tabs for connection.

- ◆ Thin NiCad pack, 8.4VDC at 450 mA, measures 4.5 x 1.875 x .25" thick (7 cells in series)

HSC#17872 \$12.50

...Or you may need the power of a lead-acid battery. These are all new batteries with tab terminals. Perfect for hobbies, security systems, battery back-up, garden equipment, etc.

- ◆ TR1.2-12, 12VDC at 1.2 AH, measures 3.75 x 1.875 x 2"

HSC#17197 \$4.95

- ◆ TR4-6, 6VDC at 4 AH, measures 2.75 x 1.75 x 4"

HSC#17588 \$4.95

- ◆ BAT-0063 (x2), 12VDC at 10AH, 4" x 6" x 4", this is two 6-volt batteries packaged in series by Best Power

HSC#17810 \$17.50

## Get the Right Touch with ALPS Input Devices!

Get name-brand quality at bargain-basement prices with these premium pointing devices -- all are new and have a 90-day HSC warranty. Some quantities limited!

### Alps Adjustable Mouse

- ◆ For Macintosh computers
- ◆ The first mouse that adjusts to you!
- ◆ Three programmable buttons!
- ◆ Sleek design for comfort, easy handling
- ◆ Chording -- Program multiple button combinations!
- ◆ Requires Mac OS 6.04 or later, available ADB port
- ◆ 400 dpi resolution, Made in U.S.A.

HSC# 17827 \$17.50

### Alps 2-Button Mouse

- ◆ Two-button type with PS/2 plug
- ◆ Ergonomic shape for comfort, easy handling
- ◆ Ultima Driver software v1.3 diskette included
- ◆ 400 dpi resolution
- ◆ New, OEM package, 90-day warranty

HSC# 17830 \$3.95

## ATX-Style Mid-Tower!

- ◆ ATX-style mid-tower cabinet
- ◆ Power supply included
- ◆ Three 5.25" and two 3.5" front bays
- ◆ 16.5" H x 8.25" W x 16.5" D
- ◆ Brand new!, 90-day warranty



HSC# 80459 \$59.50

## Price Breakthrough on Variable Transformers!

You say you've wanted one of these in the past, but the price kept you away? Now you can afford a brand-new variable AC supply for your work-bench! All have enclosed cases, knob and dial.

- ◆ Model AICVR-500W, 110/220 VAC input
- ◆ 0 - 250 VAC output, 500 watts
- ◆ Measures 5" dia., 6" tall
- ◆ Features meter, binding post terminals for input, output
- ◆ New in box, made in China



HSC#80474 \$50.00

- ◆ Model AEEC-1090VR, 110 VAC 60 Hz input
- ◆ 0 - 110 VAC output, 1 KVA
- ◆ Measures 6.5" dia., 8" tall
- ◆ Features meter, illuminated switch, line cord, fuse
- ◆ New in box, made in China



HSC#80481 \$85.00

- ◆ Model AEEC-2090VR, 110 VAC 60 Hz input
- ◆ 0 - 110 VAC output, 2 KVA
- ◆ Measures 8" x 10" x 8" tall
- ◆ Features meter, illuminated switch, line cord, fuse
- ◆ New in box, made in China



HSC#80461 \$125.00

## Oil Extractor!



- ◆ SAVE MONEY!
- ◆ For autos, yachts, forklifts, tractors, textile machines, lawn mowers...any large or small engine!
- ◆ Pumps 4 liters in 3 minutes
- ◆ Model R602A, 12VDC powered!
- ◆ Air compressor option NOT included or available
- ◆ Many uses...wherever you need a small, portable pump!
- ◆ New...includes manual, hoses and molded carrying case

HSC# 17999 \$19.95

## S-3 Aurora Video!

- ◆ 64-bit DRAM base graphic engine MPEG accelerator!
- ◆ Smooth video playback up to 30 frames per second
- ◆ Integrated 24-bit RAMDAC w/135 MHz output rate
- ◆ Glueless PCI 2.1 compliant, VESA DDC 2.0B support
- ◆ New, W3.x & W95 comp., CD install, 90-day warranty.



HSC#80458 \$17.50

## Laptop Carrying Cases

- ◆ Measures 12.5" x 10" x 2" inside dim.
- ◆ Velcro-sealed outer pouch, padded shoulder strap with heavy-duty swivel hooks, zipper closure.
- ◆ Handsome black vinyl "leather-grain" exterior
- ◆ Cushiony plush interior protects your laptop's case
- ◆ Quantity discounts available



HSC#17662 Large size case \$17.50

## ISA to SCSI Adapter!

- ◆ Model AVA-1505AI
- ◆ Single, complete PC connection
- ◆ For single non-bootable SCSI2 peripheral
- ◆ New, OEM pack, with install diskette & manual



HSC# 17995 \$17.50

Special!...w/DB25 adapter & cable....\$19.95

## 38 GHz Converters!

- ◆ High-quality, precision by Philips
- ◆ Up converter is marked 2/4 band, #ML202938-001
- ◆ Down converter marked 1/3 band, #ML 203038-002

HSC#18009 Up converter \$75.00

HSC#18010 Down converter \$75.00

## Pentium II/Celeron 440 LX MOTHERBOARD!

- ◆ Part Number: HOT367
- ◆ Intel 440 LX chipset
- ◆ Supports 266-400 (at 66 MHz bus) Celeron CPUs
- ◆ Supports Pentium II processors from 233-333 MHz
- ◆ Award BIOS, ATX Form Factor
- ◆ 1 AGP, 4 PCI & 3 ISA slots, 4 DIMM skts.
- ◆ Integrated EIDE/Floppy cont, 2 USB, 1 PIO, 2 SIO, 1 PS/2 mouse, and 1 PS/2 keyboard
- ◆ Supports up to 512 MB EDO OR SDRAM
- ◆ Modern Ring Power-on
- ◆ Includes CPU retention bracket, IDE cable, Floppy cable, CD-Rom driver and manual

HSC#18016 \$47.50

## Chiantech ATX Socket 7 Motherboard with Intel TX Chipset!

- ◆ Part Number: 5TTM-M201
- ◆ Original Intel TX Chipset
- ◆ General Specifications:
  - Standard ATX Form Factor - single rack
  - 512K Cache on board
  - Supports EDO/FPM DRAM, 256 MB max
  - Standard IDE I/O on board
  - 4-16 bit ISA and 4 PCI slots
  - 4-5V, 72-pin SIMM sockets, 3-3.3V 168-pin DIMM sockets
- ◆ CPU Compatibility List:
  - Intel MMX 200 to 233 MHz
  - Cyrix/IBM 6x86 (rev 2.7+), 6x86L, PR120+ to PR166+ and 6x86 MMX, PR166+ to PR200+
  - AMD-K5 PR75 to PR166 and up to 233 MHz AMD K6 CPUs
  - Supports 55/60/66/75 MHz system clock speeds
  - ZIP Socket7, 321-pin
- ◆ Comes with cables, drivers, utility CD

HSC#18015 \$47.50

## Sidewinder Slashed!

- ◆ Microsoft "Sidewinder" game controller ... Wow!
- ◆ New OEM package, high quality for fast action!
- ◆ Download drivers from Microsoft.com
- ◆ Eight programmable action buttons, two fire buttons



HSC#80486 \$17.50

**HALTED**  
specialties co.

**HSC**

**Electronic  
Supply**

Toll Free (Orders Only) 1-800-4 HALTED  
Internet World Wide Web:  
3500 Ryder St., Santa Clara, CA 95051  
4837 Amber Ln., Sacramento, CA 95841  
5681 Redwood Dr., Rohnert Park, CA 94928

(1-800-442-5833)  
http://www.halted.com  
(408) 732-1573  
(916) 338-2545  
(707) 585-7344

FAX your orders to:  
(408) 732-6428



## Visit HSC's Website!

- ◆ Pay us a virtual visit on the World Wide Web!
- ◆ Simply point your browser to <http://www.halted.com>
- ◆ Site is constantly being revised, please visit often!
- ◆ Check out the amazing "Gizmo of the Week" feature!

## HSC Catalog online!

- ◆ That's right, get HSC's catalog on the World-Wide Web!
- ◆ Simply go to [www.halted.com](http://www.halted.com) and follow the big red link.
- ◆ Adobe .PDF files are available for download and viewing.
- ◆ Or drop on by and pick one up...we'd love to see you!

Terms: Some quantities limited; all items subject to prior sale. Minimum order: \$10.00 plus shipping. Orders under \$20.00 subject to \$2.00 handling fee, in addition to shipping. All orders shipped FOB Santa Clara, CA (this means you pay freight!) by UPS Surface (no P.O. Boxes) unless otherwise specified, in which case prevailing carrier rate plus \$5.00 handling fee applies. Prepaid orders that don't include shipping charges will be shipped freight COD. There is a \$5.00 UPS charge added to shipping charges for COD shipments. If you have questions about your order, please call Customer Service at (408) 732-1854 M-F 9AM to 5PM PST.



# SCANTASTIC!



## This is no ordinary PC controlled Receiver



### TRUNKER

Using two Optocom receivers, Trunker software may be used for control channel trunk following of Motorola®. Also use TrunkTrac® with one Optocom for control channel monitoring.



### REACTION TUNE®

Use the popular Scout/Mini Scout/Super Scout to capture and instantly Reaction Tune the Optocom to the frequency captured. Ideal for mobile use and finding unknown frequencies.

The Optocom computer controlled receiver is no ordinary receiver. The Optocom provides solutions to applications that previously required multiple receivers, external decoders, and receiver modifications. Some features of the Optocom have never before been seen on a communications receiver. Ever! With an Optocom, you'll be poised to meet the changing scanning world.

### FEATURES

- Frequency range 25-520, 760-823.995, 849.005-868.995, 894.005-1300MHz (cellular blocked)
- Triple conversion GRE receiver board
- Scan conventional frequencies at 50 channels per second
- Trunk track Motorola and LTR on any frequency band
- Scan conventional and trunked frequencies simultaneously
- Track EDACS systems with additional third party program (E-Trax)\*
- Built-in data slicer for decoding of FSK data
- Discriminator audio input and output
- Reaction Tune with Scout/Mini Scout/Super Scout
- Decode CTCSS, DCS, LTR and DTMF
- Motorola control channel monitoring with Trunker software and two Optocoms\*
- Motorola control channel monitoring with Trunk Trac\*
- Palm Pilot support for frequency and tone display\*
- Store and Scan 100 frequencies for use away from computer
- Supported by other third party scanning programs
- Optocom includes: Trakkstar software, Palm Pilot software, Radio Manger for Windows, antenna, serial cable, and power supply



### PALM PILOT™

Interface the popular Palm Pilot™ Connected Organizer to display the frequency being scanned as well as decoding of CTCSS, DCS, and DTMF while in Store and Scan Mode. Software included. Ideal for mobile applications



### TRAKKSTAR®

Using the supplied Trakkstar software the Optocom has the ability to scan conventional frequencies, as well as trunk follow both LTR and Motorola Trunk systems.

Order Now!  
**\$499**

OPTODIRECT 800-327-5912

## OPTOELECTRONICS®

5821 NE 14th Avenue • Ft. Lauderdale, FL 33334

Telephone: (954) 771-2050 Fax: (954) 771-2052 Email: sales@optoelectronics.com

Prices and Specifications are subject to change without notice or obligation

Order Online at [www.optoelectronics.com](http://www.optoelectronics.com)

\*Trunker, Trunk Trac, E-Trax, Scout, Computer, and Palm Pilot Connected Organizer not included.



# Contents

VOLUME 20 • NO. 8 • AUGUST 1999



## Columns

### AMATEUR ROBOTICS NOTEBOOK

The birth of Breadbot's power switch board, more on I2C, and loving Linux. *Robert Nansel*

### ELECTRONICS Q & A

*TJ Byers*

### OPEN CHANNEL

Notes on vibration detectors and seismographs — Part 2, plus a note on lightning and WWV clocks. *Joe Carr*

### STAMP APPLICATIONS

A Stamp-controlled high power H-Bridge. This circuit can be used for controlling high current motors, driving relays, controlling lamps, and powering heating elements, just to name a few possible applications. *Lon Glazner*

## Departments

Advertiser's Index ... 68  
Classified Ad Info ... 68  
Dealer Directory ... 67  
Events Calendar ... 23  
New Product News ... 93  
News Bytes ... 16  
NV AdMart ... 80-82  
NV Bookstore ... 9  
Prize Drawing ... 54  
Reader Feedback ... 16  
Tech Forum ... 28

## Classified Ad Index

10. Ham Gear for Sale .....	33	120. Components .....	41
20. Ham Gear Wanted .....	0	125. Microcontrollers .....	42
30. CB/Scanners .....	33	130. Antique Electronics .....	42
40. Music & Accessories .....	0	135. Aviation Electronics .....	42
50. Computer Hardware .....	33	140. Publications .....	42
60. Computer Software .....	34	145. Robotics .....	42
70. Computer Equip. Wanted .....	35	150. Plans/Kits/Schematics .....	56
80. Test Equipment .....	35	155. Manuals/Schematics Wanted .....	0
85. Security .....	37	160. Misc. Electronics For Sale .....	57
90. Satellite Equipment .....	38	170. Misc. Electronics Wanted .....	58
95. Military Surplus Electronics .....	38	175. BBS & Online Services .....	0
100. Audio/Video/Laser .....	38	180. Education .....	59
110. Cable TV .....	39	190. Business Opportunities .....	59
115. Telephone/Fax .....	41	200. Repairs/Services .....	59

### THREE-AXIS CHOPPER, STEP MOTOR CONTROLLER FOR COMPUTER NUMERICAL CONTROL (CNC) APPLICATIONS — PART 4

Retrofitting a desktop milling machine for CNC. *Dan Mauch*

6

### BUILD A DIGITAL WATT AND WATT-HOUR METER

Ever wondered why your electric bill is so high, or how much electricity your freezer, blow dryer, or air conditioner consumes? With the Watts Showing™ digital meter kit, you can accurately measure power consumption and calculate operating costs on anything that plugs into a 120VAC outlet. *Dan Harrison*

10

### TOP 10 SOLAR PV POWER APPLICATIONS

Just in time for summer ... Look at 10 terrific solar power applications that will show positive cost benefits. *Kenton Chun*

43

### HIGH "TEC" REFRIGERATOR

Build your own electric cooler for a quarter of the price you would normally pay, plus make it solar-powered. *Kenton Chun*

46

### DC-TO-LIGHT RADIOS: YAESU AND ICOM COMPARISONS

Two brand new ham transceivers from these major manufacturers undergo side-by-side comparisons, along with some torture tests. *Gordon West*

49

### SERVOS, STEPPERS, AND OPTICAL ENCODERS — PART 1

Which one works best in your robotic or R/C project? Here's everything you need to know. *TJ Byers*

84

### BUILD AN LED DIGITAL THERMOMETER

Construct this under-\$38.00 kit for an LED digital display thermometer that can measure temperatures in all kinds of environments from either -040° to +100° Centigrade, or from -040° to +212° Fahrenheit. *Fred Blechman*

87

Published Monthly By  
**T & L Publications, Inc.**  
430 Princeland Court  
Corona, CA 91719  
(909) 371-8497  
FAX (909) 371-3052

Copyright 1999

by  
**T & L Publications, Inc.**  
All Rights Reserved

E-Mail — editor@nutsvolts.com  
URL —  
http://www.nutsvolts.com

Subscription  
Order ONLY Line  
1-800-783-4624

PUBLISHER  
Jack Lemieux N6ZTD

EDITOR  
Larry Lemieux KD6UWV

MANAGING EDITOR  
Robin Lemieux KD6UWS

ON-THE-ROAD EXHIBIT  
COORDINATOR  
Audrey Lemieux N6VXW

SUBSCRIPTIONS  
Abby Madain

CLASSIFIED ADS  
Natalie Sigafus

DISPLAY ADS  
Mary Gamar

All advertising is subject to publisher's approval. We are not responsible for mistakes, misprints, or typographical errors. Nuts & Volts Magazine assumes no responsibility for the availability or condition of advertised items or for the honesty of the advertiser. The publisher makes no claims for the legality of any item advertised in Nuts & Volts. This is the sole responsibility of the advertiser. Advertisers and their agencies agree to indemnify and protect the publisher from any and all claims, action, or expense arising from advertising placed in Nuts & Volts. Please send all subscription orders, correspondence, UPS, overnight mail, and artwork to: 430 Princeland Court, Corona, CA 91719.

NUTS & VOLTS MAGAZINE IS PUBLISHED MONTHLY FOR \$19.00 PER YEAR BY T&L PUBLICATIONS, INC., 430 PRINCELAND COURT, CORONA, CA. POSTMASTER: SEND ADDRESS CHANGES TO NUTS & VOLTS MAGAZINE, 430 PRINCELAND COURT, CORONA, CA 91719.



## ***This article will describe the steps necessary to convert a desktop milling machine to CNC.***

A desktop milling machine is a great addition to the home shop. It will help make your electronic projects look professional and to accomplish tasks that would be difficult with hand tools. By adding Computer Numerical Controls (CNC) to the milling machine, new horizons will be available to the home shop.

Imagine drilling your printed circuit boards using an automated machine. Think about the project panels you could make if you had a CNC machine to do the work. Think about all the robotic parts you could finally build if you had a machine that could machine the parts that you need. If any of these ideas appeal to you, then a CNC retrofit of a desktop milling machine may be just what you are looking for.

This article will describe the steps necessary to convert a desktop milling machine to CNC. You will find that there are several retrofit kits available from various suppliers. Most of them use similar methods for mounting the stepper motors and connecting the lead screws on the machine to the stepper motors. I found that these retrofit kits tended to be very expensive, so I decided to design and build my own.

The desktop milling machine that I chose

to retrofit to CNC was the Sherline Mill model 5000. I selected the Sherline because it is an excellent quality machine capable of doing very good work. Unlike many imported machines, the Sherline has minimum backlash in the lead screw to axis drive nut. This quality makes machining arcs and circles possible.

the Y axis. The Z axis is slightly different.


### **The general steps are:**

- Remove the X, Y, and Z hand wheels from each axis lead screw.
- Place the mounting plate over the lead

## **Three-Axis Chopper, Step Motor Controller for Computer Numerical Control (CNC) Applications**

### ***Part 4***
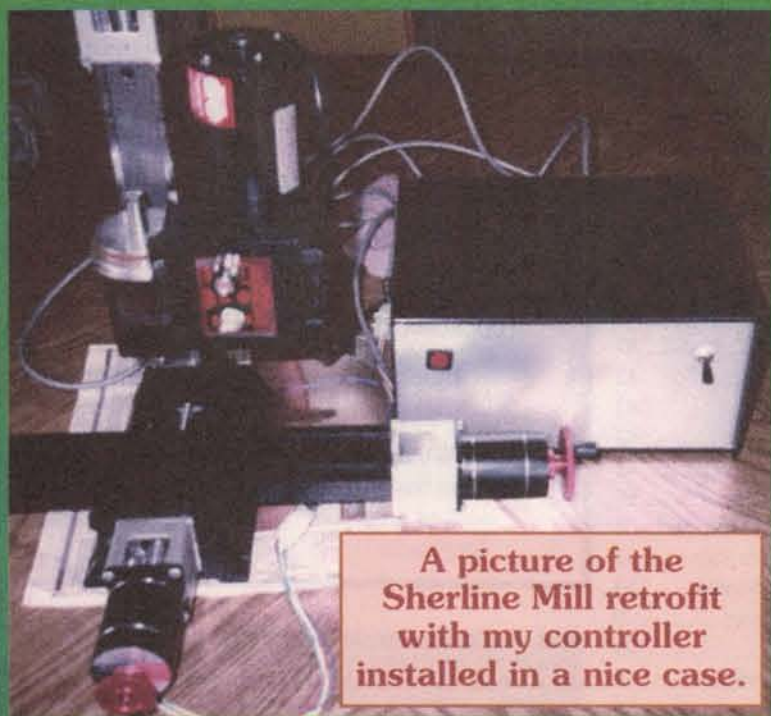
# ***At Home with CNC — Retrofitting a Desktop Milling Machine for CNC***



**A picture of the Sherline Mill retrofit with my controller installed in a nice case.**

Additionally, there is less chance for tool chatter when you have a close tolerance machine that is well made. The last consideration, but most important, is cost. Here too, the Sherline wins. When all factors are added up, the Sherline lathes and mills are a clear winner in my mind.

If you already have a Sherline mill or lathe, but it is a different model, then the following explanation of the retrofit installation may differ, but the principles should be the same. With that in mind, let's convert our Sherline model 5000 to CNC!

Retrofitting a Sherline is really easy once the mounting plates, extruded spacers, and shaft couplers are in hand. These are available from the source listed elsewhere in this article. The process for installing the parts is similar for the X and

screw thrust collar.

- Locate the mounting plate square to the axis.
- Use the mounting plate as a template to scribe and spot the holes to be drilled.
- Remove the mounting plate, then drill and tap.
- Install the mounting plate.
- Slip a thrust bearing over the lead screw.
- Slip a lead screw to the stepper motor coupling onto the lead screw.
- Install the stepper motor on the spacer and secure to the mounting plate
- Check for alignment.

### **Here are the detailed instructions:**

- Remove the X axis (moves left to right) lead screw handle by loosening the Allen set screw.
- Slide the handle off.
- Check that the collar retaining screw is tight. Use an Allen wrench. Do not over tighten.
- Place the X axis mounting plate over the 1" nominal, .997" actual size thrust collar. Do not force it on. It should be a snug fit, but not overly tight.
- Dress the inside of the mounting plate




- Test the alignment by rotating the handle, making sure that none of the leads on the stepper motor are shorted together. The axis should turn freely with only the cogging of the stepper motor felt. Adjust as necessary to achieve this alignment.

- That the PC is connected to the controller.



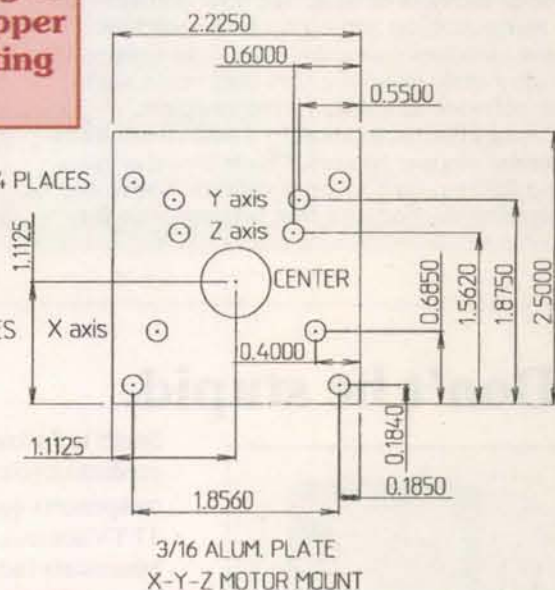- Boot up your computer and configure the software for



- That the PC is connected to the controller.

Nuts &amp; Volts Magazine/AUGUST 1999 7



your parallel port. Set the parameters used for the Sherline Mill. With the controller set in the half-step mode for each axis, the number of steps per unit should be 8000, thus, a resolution of .000125" per step.

- Measure the backlash and divide the backlash by .000125, thus .002" backlash will be .002/.000125=16 steps. Place that value in the backlash location on the set-up menu.

- Run the G code interpreter program. (Desknc for Dos)

- Turn on the controller.
- Jog the X axis left and right.
- Jog the Y axis front and back.
- Jog the Z axis up and down.
- Adjust the configuration file as needed.
- Enter the command G00X1. The X axis should move rapidly 1.000" in the X positive direction.

- Enter the command G01X0F1. The X axis should move back to the X = 0.000 location at a slow feed rate.
- Accomplish the same on each axis.

Note that the dials will not come back to zero because the backlash compensation will offset the dial locations by the amount of backlash compensation added into the configuration file.

Micro switches to limit the maximum travel for the X, Y, and Z axis should be installed on your first CNC machine. This will help prevent damage to the machine caused by operator error or faulty G coding. See your software files for instruction on setting up limit switches. Home switches can reduce the time needed to set up a task. Read the files that come with your software to set up home switches.

Avoid the temptation to install much more powerful stepper motors. I have heard of guys using 250 oz. inch stepper motors. These are professionals. For your first attempt, use the

~60 oz. inch motors from the source listed. They should reduce the chance of damage to the machine should there be a mistake in your tool path file. The Z axis motor, however, can safely be upgraded to 125 oz. inches. I installed these type motors on the three axes of my machine because I have extensive experience with them.

## Troubleshooting

If any axis seems to lack power, check that the configuration file is set up correctly. Ensure that the maximum feed rate is not excessive. Set it so that each axis will accept the G00 (X), (Y), or (Z) commands without any axis losing steps. Adjust as necessary.

If the stepper motors sound fine, then make sure the set screws are securely tightened. Replace the set screws at the first sign that they are rounding off. The stepper creates a lot of vibration. The set screws may come lose in time. After the machine is operating correctly, a drop of locktite in each set screw hole will prevent further loosening of the screws.

If you notice lost step during one of the arc or circular G code commands, such as G02 or G03, then your feed rate for that particular arc is too fast. Slow the feed rate down during arc and circular moves.

If you continue to lose steps during circular moves after you have reduced the feed rate, then you may be seeing stepper motor resonance. If your controller is in the full-step mode, shift to the half-step mode. Alternatively, a slight drag on the X, Y, Z slides will also eliminate/

reduce resonance problems. You can adjust the gibs on each axis accordingly.

## Safety

- **Never let a machine operate unattended.**


- **Always wear safety glasses when running the machine.**

- **Keep children away from the area while operating.**


- **Read, understand, and follow the safety instructions provided with the Sherline Mill, the software, and the controller.**

CNC may be addictive (humor). Once you successfully create your first perfect part, you will be inspired to accomplish even more challenging tasks. That is when CNC becomes addictive. We all have our faults. This would be a great fault to have. This concludes this series of articles. Look for a future article on more advanced projects using the CNC Sherline Mill. If you have any questions, you may E-Mail me at dmauch@seanet.com. NV

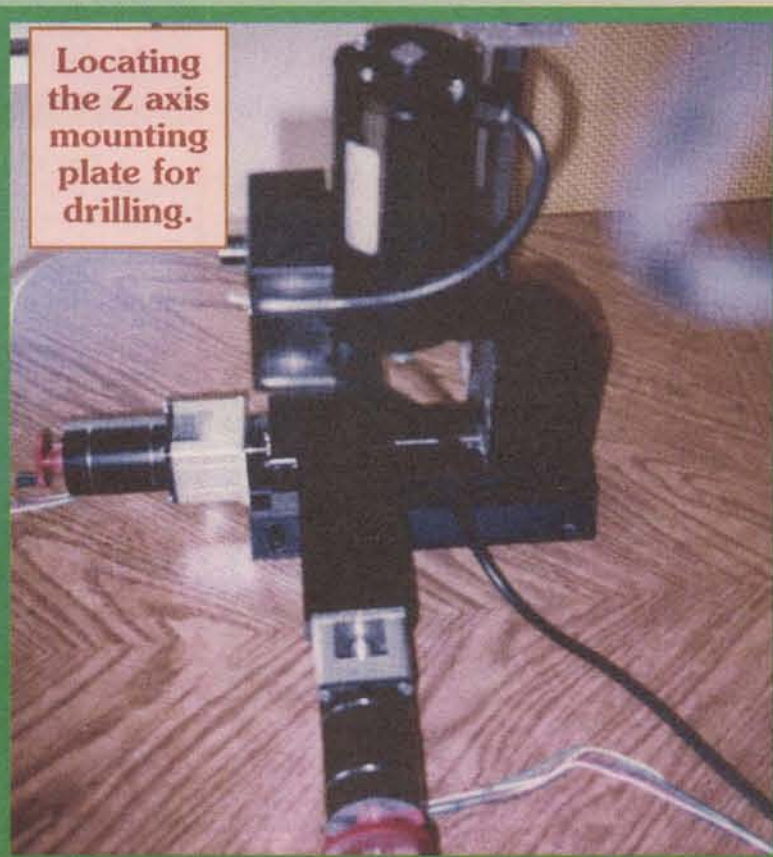Locating the Z axis mounting plate for drilling.



## Don't be stupid.

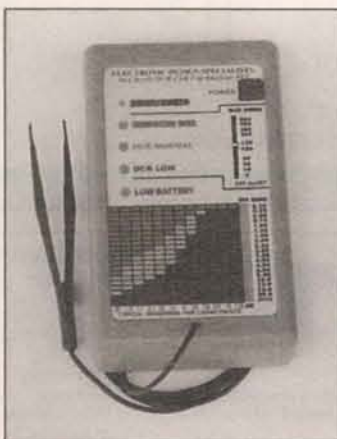

Smart techs know that to be productive you need to find defective components quickly. Maybe that's why 37 TV stations, General Motors, Matsushita Industrial, Sears Service, Pioneer Electronics, Panasonic Authorized Service, and thousands more independent service technicians have chosen the **CapAnalyzer 88** over all of the other capacitor checkers. Check [www.eds-inc.com/88users.html](http://www.eds-inc.com/88users.html) for actual **CapAnalyzer** users' comments as they compare their **CapAnalyzer** to the "wizards" and "z-meters" they already own. They all prefer the **CapAnalyzer 88** because it

does what you expect it to do: check electrolytic capacitors, in-circuit, with 100% accuracy. Period. No unsoldering to check out-of-circuit, no mistaking a shorted or leaky cap as good, as other "ESR" meters do, no guessing about whether a value is good or bad. With our exclusive three-color chart right on the front panel, auto-discharge, multi-beep alert, and one-handed tweezer test probe, even your pet monkey could find defective caps in that problem TV, monitor or VCR in a few seconds. 55% of sales of **CapAnalyzers** are from recommendations by other **CapAnalyzer** owners, and 9% of sales are from previous customers buying a second unit. So get smart and buy one for yourself. It's only \$179. With our exclusive 60-day satisfaction-or-money-back guarantee, you risk nothing. Your only problem will be running out of work as you take care of all of those "dogs" that you've been sitting on. We're EDS. We make test equipment designed to make you money. Available at your distributor now. **561-487-6103**

[www.eds-inc.com](http://www.eds-inc.com)

Sherline Mill — **Sherline Products**, 170 Navajo St., San Marcos, CA 92069-2593; (Tel) 1-800-541-0735; (Internet) Model 5000 — \$500.00; [www.sherline.com/sherline](http://www.sherline.com/sherline)

The following are available from **Camtronics, Inc.** — Three-axis, two-amp chopper driver kits are \$145.00 plus \$9.00 S/H. Dual shaft stepper motors are \$25.00 per axis plus \$4.00 S/H per motor.

A limited number of three-axis stepper motor mounting kits designed for the Sherline Model 5000 are available for \$150.00 plus \$6.00 S/H. Hardware kits include the shaft coupling, extruded spacers, mounting plates, fasteners, and thrust bearings.

Send check or money orders to:

**Camtronics, Inc.**  
18230 130th PL N.E.  
Bothell, WA 98011-3118

## SOURCES

Or send E-Mail to [dmauch@seanet.com](mailto:dmauch@seanet.com) for additional information.

Desknc for Dos may be obtained from <http://www.deskam.com>.



# Get **Hot Deals** On Great Electronic Titles through the **Nuts & Volts Bookstore**

*As a paid subscriber to Nuts & Volts, you'll receive a 10% discount off the listed price shown here!!*



**\$34.95**

"Programming and Customizing the BASIC Stamp Computer" by S. Edwards

Build smart electronics projects with the inexpensive, simple-to-use, surprisingly powerful BASIC Stamp.



**\$44.95**

"Handbook of Radio and Wireless Technology" by S. Gibilisco

A comprehensive compendium on the entire field of radio and wireless technology.



**\$39.95**

"Encyclopedia of Electronic Circuits" Vol. 7 by R. Graff

An extensive library of 1,000 circuits from the bestselling, seven-volume "Encyclopedia of Electronic Circuits."



**\$54.95**

"Handbook of Microcontrollers" by M. Predko

This much-needed reference is the first to cover all the most common types of eight-bit microcontrollers.



**\$34.95**

"Electronic Troubleshooting" by D. Tormat and N. Widmer

Troubleshoot and repair any type of electronics with this comprehensive guide.



**\$39.95**

"Programming and Customizing the 8051 Microcontroller" by M. Predko

This tutorial/disk package details the features of the 8051 and demonstrates how to use these embedded chips to access and control many different devices.



**\$39.95**

"Circuit Troubleshooting Handbook" by J. Lenk

This handbook gives full descriptions of the operation of important circuits, and how each circuit's characteristics may figure in its failure or poor performance.



**\$24.95**

"How Electronic Things Work... and What to Do When They Don't" by R. Goodman

Never again be flummoxed, flustered, or taken for a ride by a piece of electronic equipment with this fully illustrated, simple-to-use guide.

## Other Available Titles ...

"Practical Antenna Handbook" by J. Carr **\$39.95**

"Secrets of RF Circuit Design" by J. Carr **\$29.95**

"The Illustrated Dictionary of Electronics" by S. Gibilisco **\$39.95**

"TAB Encyclopedia of Electronics for Technicians and Hobbyists" by S. Gibilisco **\$69.50** (Hard Cover)

"The Robot Builder's Bonanza" by G. McComb **\$18.95**

"Programming and Customizing the PIC Microcontroller" by M. Predko **\$34.95**

"How Radio Signals Work" by J. Sinclair **\$24.95**

"Making Printed Circuit Boards" by J.L. Axelson **\$22.95**

"How to Read Electronic Circuit Diagrams" by R.M. & Lawrence Brown **\$19.95**

"Build Your Own Test Equipment" by H.L. Davidson **\$22.95**

"Radio Receiver Projects You Can Build" by H.L. Davidson **\$21.95**

"Troubleshooting and Repairing Consumer Electronics Without a Schematic" by H.L. Davidson **\$24.95**

"Amateur Radio Encyclopedia" by S. Gibilisco **\$50.00** (Hardcover Only)

"Basic Electronics Theory" by D.T. Horn **\$26.95**

"Ready-to-Build Telephone Enhancements" by D.T. Horn **\$17.95**

"The Benchtop Electronics Handbook: 260 Most Common Popular Electronics" by V. Veley **\$65.00** (Cloth Cover)

**Build your electronics library at a price you can afford!!  
Order now!!**

BOOKS PUBLISHED BY MCGRAW HILL

**Call 1-800-783-4624 today!**  
WE ACCEPT VISA AND MASTERCARD

Send check or money order to Nuts & Volts, 430 Princeland Court, Corona, CA 91719. Include a complete shipping address (no P.O. Boxes, please). Shipping & handling \$4.50. CA residents add 7.75% sales tax. Or, call our toll-free order-only line at 1-800-783-4624 and use your MasterCard or Visa. ALL ORDERS MUST BE PREPAID.



# Build a Digital Watt and Watt-Hour Meter

by Dan  
Harrison

*Have you ever wondered why your electric bill is so high? How much electricity does your freezer, blow dryer, or air conditioner consume? Most people really have no idea how much each appliance costs to operate each year.*

**W**ith the 'Watts Showing™', a digital watt and watt-hour meter kit you can build, data on electrical power consumption can be accurately measured and operating costs calculated on anything that plugs into a 120VAC outlet.

Virtually every house and most apartments in the US are connected to an AC watt-hour meter that the power company or apartment complex uses to measure the amount of electricity consumed. A watt-hour is the equivalent of consuming one watt of power for one hour, or two watts of power for 30 minutes, or six watts of power for 10 minutes, and so on.

Traditional watt-hour meters are electro-mechanical devices, which use a small amount of the electrical power going through it to spin a wheel, which drives clock-like meter dials. I'm sure that everyone reading this magazine has seen them. [An interesting thought. Just like a mechanical clock with moving wheels, the power company's watt-hour meter can be inaccurate, too. How long has it been since the calibration on your meter was checked?]

Watts Showing is an all solid-state digital version of the watt and watt-hour meter with an LCD display. Any standard AC power voltage or frequency (90-240VAC, 50/60Hz) can be accommodated, making the Watts Showing useful around the world.

## Measuring AC Electrical Power

From elementary circuit theory, we know electrical power is the product of voltage times current,  $P = I \times E$ . For direct current (DC) circuits, power measurements can be made with a simple voltmeter and ammeter. When we get into complex AC circuits, the measurement is not so simple or straightforward.

To understand power measurement in complex circuits, a review of basic Alternating Current (AC) theory is in order.

The electrical power coming into your home has the shape of a sinewave and a frequency of either 50 or 60Hz, depending on where you live. The period for a 60Hz sinewave is  $P = 1/60 = 16.67\text{ms}$ . In the US, the standard frequency is 60Hz and that will be used for all calculations in this article.

A sinewave and its characteristics are shown in Figure 1. The amplitude of a sinewave is constantly changing with time, so when we refer to an AC voltage, we need to define whether it's the peak value or the RMS value we're speaking of. The peak value is the most distant displacement from the zero line, either positive or negative in a true sinewave. The Root-Mean-Square, or RMS, value is the value that you would read on an AC voltmeter.



The RMS value is always .707 of the peak value for sinewaves. Why .707 times the peak value and not 50% instead?

The reason is that a sinewave completes a full cycle in 360 degrees. In each 90-degree quadrant ( $4 \times 90 = 360$ ), the voltage changes by the delta of Vpeak; quadrant 1 is 0V to Vpeak, quadrant 2 is Vpeak to 0V, quadrant 3 is 0V to -Vpeak, and quadrant 4 is -Vpeak to 0V. Knowing that each quadrant is 90 degrees 'long' in angular displacement, then 50% of the rotation is 45 degrees. If you think that half way through the rotation of each quadrant would be the average, or effective voltage you're right! It's the sin (45 deg.), .707, times the Vpeak that we use for RMS voltage.

RMS is the DC equivalent in terms of calculations for power. In other words, a 115VAC (RMS) source driving a 100-ohm load would produce the same power as a 115VDC source driving a 100-ohm load. For a voltmeter (RMS) reading of 115VAC, the actual peak voltage is 162.6V and the peak-to-peak value is 325.2V.

Example: Assume a trivial case of delivering power to a resistive load like an incandescent light bulb. We assume the bulb is rated at 60 watts with nominal 120VAC power input. Given the formula  $P = I \times V$  and using a little algebra, we can determine that current (I) equals  $P/V$ , which is 0.5amp in the case of a nominal 120VAC source. In the resistive case (P) power, is the product of IRms and VRms.

Figure 2 illustrates the relationship of voltage and current in a resistive circuit. We know from basic circuit theory that when inductance and/or capacitance is added to an AC circuit, the phase relationship between current and voltage changes, making measurement of power consumption more difficult. Now it becomes necessary to sum the instantaneous product of voltage and current over time to calculate actual, or real, power.

When RMS voltage and RMS current are multiplied, it is called Apparent Power. This is what you would get, for example, when you use a clamp-on

ammeter to measure air conditioner compressor current and multiply that number by the operating voltage to determine power consumption. The number you calculate is not real power, it's apparent power.

It's critical to understand that power cannot be accurately determined by multiplying RMS current by RMS voltage due to the phase difference that exists in a non-resistive AC circuit. This can best be illustrated by the perfect circuit which only contains an inductor and assumes zero resistance in the wires, see Figure 3a. In a purely inductive circuit, current is said to lag the voltage by 90 degrees. The voltage leads the current because it depends on the rate of change of current through the inductor, and inductors resist a change in current flow. This is explained as follows.

At some instant in time, the current will equal zero and will begin to increase in value. When the current is increasing — in the first 90-degree quadrant — the counter electromotive force of the inductor opposes the applied voltage and energy is expended countering this force. During the second 90-degree quadrant, the current begins to decrease from its peak value and voltage is again induced in the inductor, but this time energy is added in the same quantity that was used opposing the voltage. Averaging this power results in a zero net power consumed even though large currents and voltages would be measured!

In the real world, nothing is perfect though, and the electrical resistance of the wires will have the effect of reducing the angle of lag. Let's assume that the inductor has a resistance of 10 ohms and an inductance of 100 Mh. See Figure 3b. The impedance of the inductor at 60Hz is about 38 ohms. To determine current, we find the total impedance

$$Z = \sqrt{R^2 + XL^2} = \sqrt{10^2 + 38^2} = 39.2\Omega$$

The phase angle is



$$\theta = \frac{XL}{R} = \frac{38}{10} = 75.25^\circ$$

The value of the current would be

$$I_t = \frac{V}{Z} = \frac{120V}{39.2} = 3.06A$$

giving an apparent power of 367 watts. Only the power dissipated by the resistance is true power and it is determined by

$$P = I^2 R = 3.06^2 \times 10 = 93.6W$$

or

$$P = \cos\theta(EI) = 96.3W.$$

Remember, in an inductive circuit, true power is always less than apparent power. The ratio of true power to apparent power is called the Power Factor. In the example shown, the power factor would equal

$$\frac{P_{true}}{P_{app}} = .255.$$

Watts Showing uses an analog quadrature multiplier, actually a Gilbert Cell derivative, to calculate true power. This circuit continuously produces the product of instantaneous voltage and current.

## How It Works

The Watts Showing's four main functional blocks are (Figure 4): the optically-isolated AC current and voltage measurement, the quadrature multiplier and summer circuit, the MC68HC705P6 microprocessor, and the LCD display. All four blocks are contained on two circuit boards and housed in a single assembly.

## Optically-Isolated AC Current and Voltage Measurement

Refer to the schematic in Figure 5 for the following description. The current and voltage measurement is composed of R1, POT1, Shunt1, and half of U1 (the LEDs). When an AC voltage is applied to the AC input terminals, current flows through either the D1-D3 pair or the D2-D4 pair, depending on the polarity of the voltage. In the no-load case, current flow through all diodes is equal since no voltage is dropped across the shunt, S1. When a load is applied to the AC output, there is a voltage drop across the shunt and slightly less current will flow in D3 and D4 than D1 and D2. The decrease in current flow makes a small change in the light output also. The amount of light output is therefore dependent on both voltage and current (remember that the product of voltage and current is power) at any given time.

\*\*\*\*\*  
\* put the LCD cursor in the position specified by  
\* the contents of ACC  
\* lcd map 80 81 82 83 84 85 86 87 C0 C1 C2 C3 C4 C5 C6 C7  
\*\*\*\*\*

```
put_cursor      ;acc=cursor position 0-15
add      #80      ;add offset to get address
cmp      #88      ;if >88 then add 38h
blo      do_cursor
add      #38
do_cursor
jsr      put_ctl   ;write character address to LCD control reg.
rts
```

Listing 1. Put\_Cursor

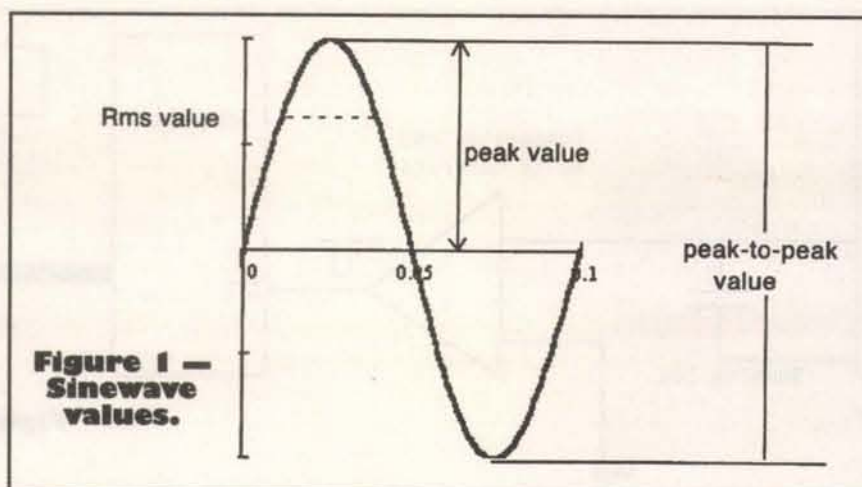


Figure 1 — Sinewave values.

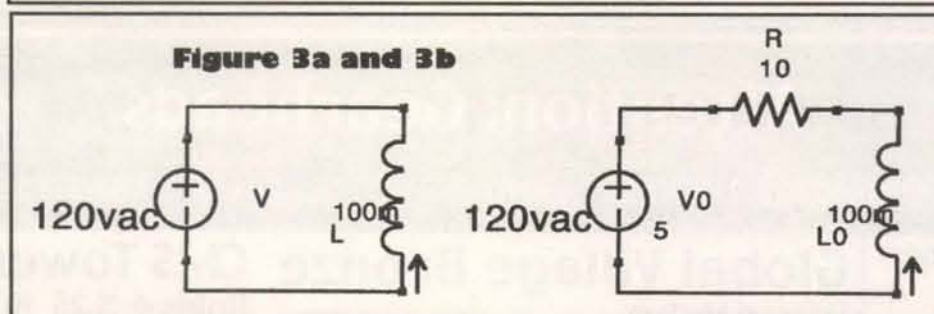
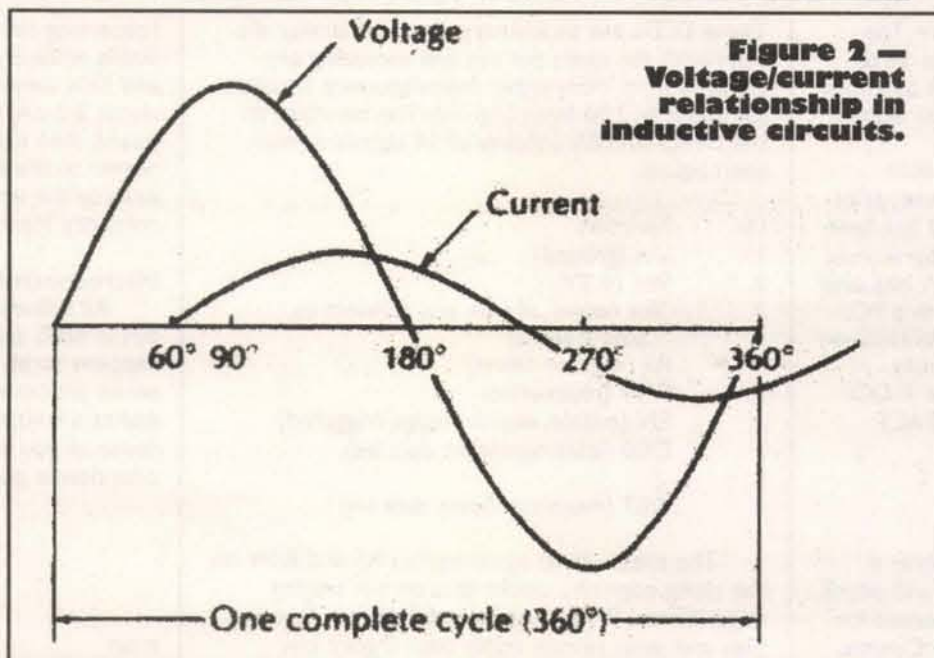


Figure 3a and 3b

The 500k ohm pot (Pot2) in series with R1, is used to control the bias current through the LEDs in the optocoupler. This bias current sets the rate of discharge of C1, which determines the scaling factor of the watt meter. As the voltage across the shunt increases, it results in a lower voltage across D3, D4, Pot2, and R1. This means less current flow, and lower light output as the power being measured increases. For 220-240VAC operation, R1 and POT1 values must be changed. I've never operated this circuit above 120VAC so, while it should work, I can't say exactly what value resistors will be needed to keep the watt measurement correct.

## Quadrature Multiplier and Summing Circuit

The multiplier and summer are made up of all the components inside the dashed block on the schematic. The transistors in U3 form two stacked differential amplifiers, in a modified Gilbert Cell arrangement. The output is proportional to the difference in light output from the LEDs, which we remember is a product of voltage and current (power). This is fed into C1 where it accumulates (sums).

When the voltage on C1 goes below the threshold set by Pot1 (approximately 0.4V, depending on capacitor and resistor tolerances), the output of U2A, pin 1, goes high. This, in turn, takes the inverting input of U2b to a high state, forcing the output, pin 7, to go low. This results in Q1 being turned on which charges the capacitor, C1 through R2.

When the voltage on C1 again crosses the threshold going positive, set by Pot1, U2a will switch back to a low output, driving U2b back to a high output and turning off Q1 which stops charging C1. The values shown will produce a 1-pulse/joule, which is 1Hz/watt. The output pulse width is set to approximately 400uS.

This configuration allows a full-scale measurement of greater than 1,000 watts. One thing to keep in mind about this circuit is the stacked differential amplifiers are extremely sensitive and must be precisely balanced in terms of gain across the four transistors. The gain, or Beta, of a transistor will vary with temperature. So long as all transistors are at the same temperature, the temperature coefficient of the copper shunt helps to cancel out a change in transistor gain as temperature changes. Where you can run into a problem is when a temperature gradient exists across OPT1 and not all transistors are the same temperature. This condition results in erroneous readings and makes it impossible to calibrate. Believe me, I learned this the hard way. Always keep OPT1 away from air currents or heat sources when calibrating.

## The MC68HC705P6

As is true with all microcontrollers, there are two parts to this story: hardware and software. First, a discussion of the hardware configuration will be presented, followed by a description of the software that makes it all work.


## Microcontroller Hardware

The Motorola MC68HC705P6 is an EPROM version of the MC68HC05P6 microcontroller. It is a low-cost combination of a generic 68HC05 CPU with a 16-bit timer, 176 bytes RAM, 4672 bytes EPROM, and 21 general-purpose I/O lines. A block diagram is shown in Figure 6.

The output pulses from the quadrature multiplier and summing circuit are input to the interrupt pin on the microprocessor. The processor can use this to count the number of pulses and, because it's on an interrupt, the counting process can occur in the background without constant attention from the main program. The interrupt pin must be programmed to be edge-sensitive rather than level-sensitive. Since the pulses generated by the summing circuit are 400uS wide, a level sensitive interrupt will cause the processor to be interrupted many times during the pulse.

The clock generation consists of a 4.00MHz crystal, two 22pF caps, and an 8.2 meg resistor. It's important to include R3 in the clock circuit if you're building this from scratch. This small amount of load helps to get the internal oscillator started; without it you may have trouble getting the processor to operate. The same is true for the Power On Reset circuit (POR), consisting of C6 and R13. The power on reset must be long enough for the crystal and power supply to stabilize. The



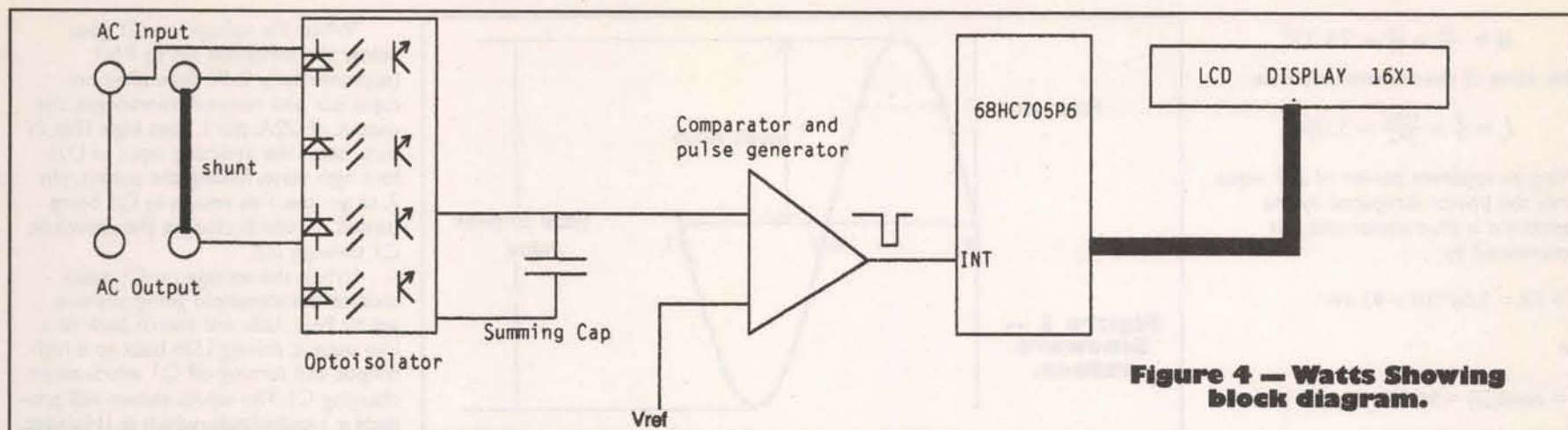

**Figure 4 — Watts Showing block diagram.**

values shown work well over temperature. The LCD interface is straightforward and uses 11 of the processor's general-purpose I/O lines to implement the data/control path. The serial data output PC0 is for serial data out.

Since the MC68HC705P6 has no built-in UART, and we want this design to be as cost-effective as possible, a "bit-banged" serial port has been implemented in software. This port is programmed to be 9600 baud, eight data bits, two start bits, and no parity. If you want to use this port with a PC, the interface needs to be converted to RS232C or RS422, whichever suits your needs. A sample RS232 interface circuit is shown in Figure 7. DO NOT CONNECT TO AN RS232 INTERFACE WITHOUT THE PROPER CIRCUIT.

#### LCD Interface

A 16-character-by-one-row LCD display is interfaced to the processor using portA and portB through J1, a 14-pin header. The LCD selected for the interface is a DMC-16117A made by Optrex.

These LCDs are an industry standard; similar displays with the exact pin out and mounting are available from many other manufacturers. It sells for about \$12.00 from Digi-Key. The interface to the DMC-16117A consists of 14 signals, as outlined below.

Pin	Function
1	Vss (ground)
2	Vcc (+ 5V)
3	Vee (wiper of a 5k pot connect to pins 1 and 2)
4	RS (register select)
5	R/W (read/write)
6	EN (enable, negative-edge triggered)
7	DB0 (least-significant data bit)
14	DB7 (most-significant data bit)

The enable (EN) signal latches RS and R/W on the rising edge and clocks data on the trailing edge. RS and R/W must be stable before E goes high and must remain stable until E goes low

(observing set-up and hold times). Data must be stable while E goes low (again, observing set-up and hold times). Power consumption should be about 2-3mA. If you're building this without the PC board, then care should be taken when connecting power to the LCD. Reversing +5V and GND will destroy the unit. Read your data sheet carefully to correctly identify pins 1 and 2.

#### Microcontroller Software

All software for the Watts Showing was written in 6805 assembly language. Assembly language happens to be my language of choice for the '05 series processors. At least one software company makes a limited 'C' compiler for this processor for those of you who prefer 'C.' The software overview is outlined in the following pseudo-code:

```

Power-on Reset
Initialize processor I/O, timers,
and A/D
Initialize LCD display
Print start-up message
main
  
```

We accept Visa,  
Mastercard, AmEx,  
and Discover

## Attention: Gearheads

www.shrevesystems.com

To Order Call 1-800-227-3971

Fax: 318-424-9771



**PowerMac 7200**  
75 Mhz PPC 601  
4 168 pin DIMM slots  
Build your own Mac!  
**\$99 Brand New!**

**Global Village Bronze**  
External Modem  
2400 Bps/9600 Fax  
**\$1 Each**

**CMS Tower SCSI Case**  
Holds 4 5.25 full height drives  
**\$99**



**Peltier Junction**  
with heat sink  
1 3/16" x 1 3/16"  
**\$10 each or 3 for \$25**



**Texas Instruments**  
Color Composite  
Display  
Great for Surveillance  
**Refurbished \$99**



**Apple IIE Logic Board**  
**\$19**



**LC Power Supply**  
+5V, -5V, +12V Output  
**\$5 New**

**Logic Boards**  
Q610 Logic **\$99**  
Q660 Av Logic  
Q650 Logic  
Q800 Logic  
Q840 Logic  
**No Processor**



**MacAllly ADB Keyboard**



**\$10**

**PDA Genuine**  
Leather Carry  
Case  
Let your palm  
pilot lead the life  
of luxury!

**Power Supplies**  
Apple IIE \$59  
Apple IIGS \$69  
Mac IICX, Ci \$99  
Mac II, X, FX \$49  
Mac IISi \$49  
Q610, 660AV, 6100 \$149

**Newton 130**  
Without Lid **\$179**  
Newton Carry Bags \$19  
Newton Fax Modems \$19  
16 MB Flash Cards \$79  
20 MB Flash Cards \$99  
24 MB Flash Cards \$129

**RAM**  
1 MB 30 Pin 4 For \$1  
4 MB 72 Pin 2 For \$5



**Claris Works**  
3.0 For  
PC/Mac  
EDOCS **\$29**

**Miscellaneous**  
Apple 8 bit Video Card \$19  
LaserWriter IINT \$199  
Apple ADB Keyboard \$19  
1.44 Super Drive \$49  
Clone ADB Mouse \$19  
Quicktake 100 Camera \$129  
Bernoulli 90 MB EXT \$10



**Membrane**  
Track Pad for  
laptop **\$2**

**\$25 minimum  
order**

**Shreve Systems**  
1200 Marshall St  
Shreveport, La 71101

Returns subject to a 15% restocking fee.  
Prices are subject to change without notice. We accept Visa,  
Mastercard, AmEx, Discover



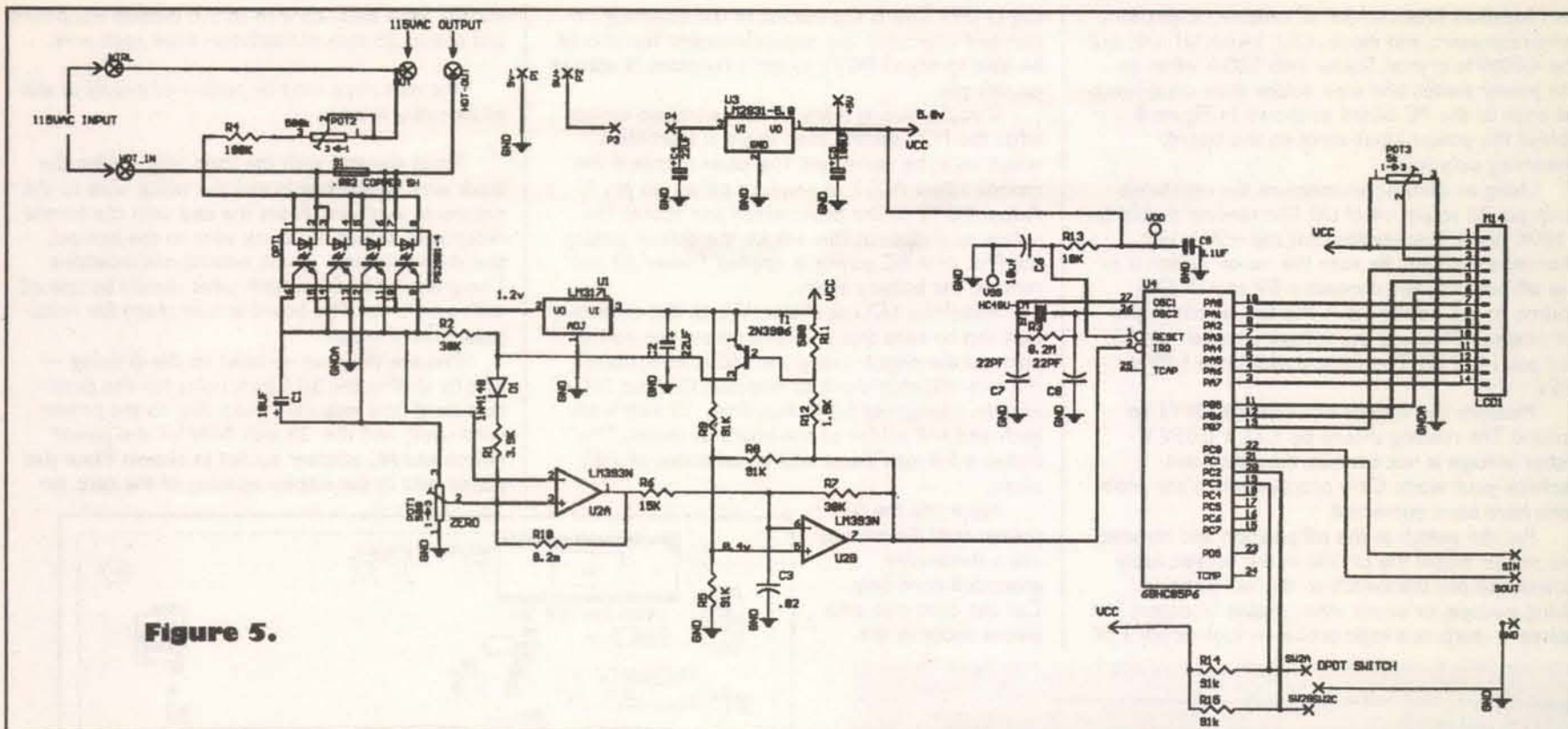


Figure 5.

Start clock

One\_second\_loop

Wait on clock for 10 "tics"  
(One second total time)  
Get accumulated one-watt/  
second  
pulses  
Write to display  
Add to accumulated watt/  
seconds  
Convert to watt hours  
Write to display  
Output watts and watt-hours  
to serial port  
branch to main

This is a simple structure and programmers should always strive to keep program structures simple. When the program structure is too complex, then the structure should be decomposed to keep each element of your design simple.

## LCD I/F Routines

The following LCD initialization was taken from the Optrex LCD data sheet.

Initialization:

set RS and R/W to logic 0  
data = 38h for 4ms  
data = 0fh for 500ns

data = 38h for 4ms  
data = 01h for 500ns  
data = 38h for 4ms  
data = 06h for 500ns

The display should be cleared with the cursor in the far left position. To send characters to the display, set 'RS' to logic '1' then send the ASCII code for the character. The cursor will automatically increment to the next position, but only for the first eight locations. This is because the 16x1 uses the following memory map:

80:81:82:83:84:85:86:87:C0:C1:C2:C3:C4:C5:C6:C7

The cursor starts out on address 80, increments to 81, 82, 83, etc. When the cursor is in position 87, it will increment to 88, not C0. So you must keep track of the current cursor position in software and change the internal character address for positions 9-16. Listing 1 is an example of this function. Routines for writing data and control words to the LCD are PUT\_DATA and PUT\_CTRL. For the control words, the app note instructs us to perform the following sequence:

1. Set R/W = 0 to write to the LCD.
2. Set RS = 0, for an instruction byte.
3. Place data on DB0-DB7.
4. Toggle EN (low-high-low).

Data is latched on the falling edge of EN. Two types of control instructions require extra delay time between the writing of the command and writing data to be displayed. The DMC-16207 supports the instructions shown in Listing 2. These routines were taken from the Motorola HC05 Applications guide. These are the same routines that are used in the Watts Showing.

## Timer Routines

Obviously, a watt hour accumulation cannot be accurately made without an internal clock. For the digital watt meter, we use a clock that 'ticks' at 10Hz, for a resolution of 0.1sec. This is accomplished by utilizing the internal 16-bit programmable timer of the 68HC705. A complete description of this timer is found in the MC68HC705P6 data book and the Motorola HC05 applications guide, both available from Motorola. Listing 3 demonstrates how to set up a 100mS loop for timekeeping. The basic form of this routine is taken from the HC05 applications guide.

## Building and Testing the Watts Showing

I like the build a little, test a little approach, starting with the printed circuit board. Install and solder all the IC sockets, observing the proper

PRODUCTS FEATURES ORDER NEWS LINKS

**Black Feather ELECTRONICS**

Black Feather Electronics  
10841 Noel St. #106  
Los Alamitos, Ca. 90720

DIRECT DIAL: (714) 236-1776 FAX: (714) 236-1778 E-MAIL: bifea@juno.com

**WWW.BLKFEATHER.COM**

WEBUT EXCESS/SURPLUS ELECTRONIC SUPPLIES

Write In 70 on Reader Service Card.

## SATELLITE TV - HACKERS 'BIBLE'!

### The SECRETS are REVEALED!

- The principles of security
- Descrambler building blocks
- Smart cards, information wars & stupid mistakes
- Cracking codes (includes DirecTV source code)
- Installing and hooking up descramblers
- Video manipulative systems...and much more...

**www.baylin.com**  
or... call 800-483-2423

ORDER via Internet or Send \$60 plus \$5 s/h to:  
Baylin Publications, 1905 Mariposa, Boulder, CO 80302  
MASTER, VISA & AMEX /COD orders accepted

FREE CATALOG - Satellite TV books, videos and software



576 pages, 6" x 8-1/2"

**NEW!**  
5th Edition

Telephone: 303-449-4551  
FAX: 303-939-8720

Write In 71 on Reader Service Card.

Nuts & Volts Magazine/AUGUST 1999 13



pin 1 location. Next, solder all resistors, capacitors, potentiometers, and diode, CR1. Install U1, U2, and the 4.00MHz crystal. Solder two 22GA wires to the power switch and then solder their unconnected ends to the PC board as shown in Figure 8. Solder the power input wires to the board, observing polarity.

Using an ohmmeter, measure the resistance from pin 28 to pin 14 of U4. The reading should be >100K ohms. This verifies that the +5V is not shorted to ground. Be sure the on-off switch is in the off position, and connect a 6V to 12V DC source to the power input. Put the switch in the on position. Measure the voltage between pin 28 and pin 14 of U4. The voltage should be 5.0V  $\pm$  .25V.

Measure the voltage from pin 10, OPT1 to ground. The reading should be 1.22  $\pm$  0.05V. If either voltage is not correct, then stop and recheck your work. Only proceed when any problems have been corrected.

Put the switch in the off position and remove the power. Install the LM393 in the socket, apply power, and put the switch to the 'on' position. Using a scope, or some other means to detect fast pulses — such as a logic probe — look at pin 7 of

the LM393. This is the output of the summing circuit and interrupts the microcontroller. You should be able to adjust POT2 to get a constant hi voltage on this pin.

If you're seeing many 400uS pulses no matter what the POT setting, then there is a problem which must be corrected. The same is true if you cannot adjust POT2 to produce pulses on pin 7. Adjust POT2 to the point which just causes the pulses to disappear. This will be the default setting the first time AC power is applied. Power off and remove the battery again.

Install the LCD as shown. Watch the orientation and be sure that it is level across the entire plane of the display. Using the 16GA wire, make the two milliohm shunt as directed. Cut the 16GA wire to a length of 6.3 inches. Strip .25 inch from each end and solder to the board as shown. This makes a 5.8 inch shunt with a resistance of .002 ohms.


Now add the AC power cord. Be sure to use a three-wire grounded cord only. Cut the cord into two pieces about in the

middle. Strip back 2.5 inch of the outside insulation and about .25 inch of insulation from each wire.


The next steps must be performed exactly as stated for safety reasons.

From the end with the male plug, solder the black wire to the hot-in and the white wire to the neutral-in locations. From the end with the female receptacle, solder the black wire to the hot-out and the white wire to the neutral-out locations. The green wires from both sides should be spliced with a wire nut. The board is now ready for installation into the case.

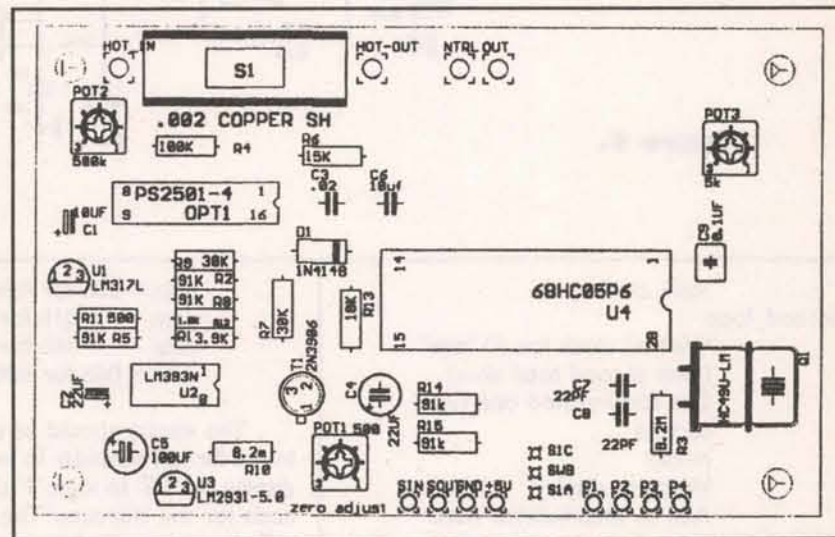
Prepare the case — refer to the drawing — first by drilling the 5/16 inch holes for the extension cord (this may vary according to the power cord used) and the .25 inch hole for the power switch and AC adapter socket as shown. Place the plastic lens in the display opening of the case, on



SILKSCREEN

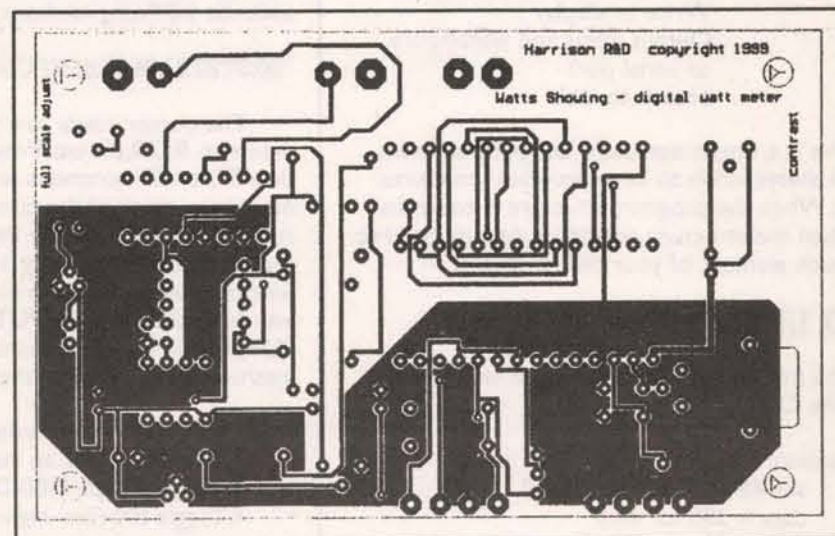

TOP LAYER

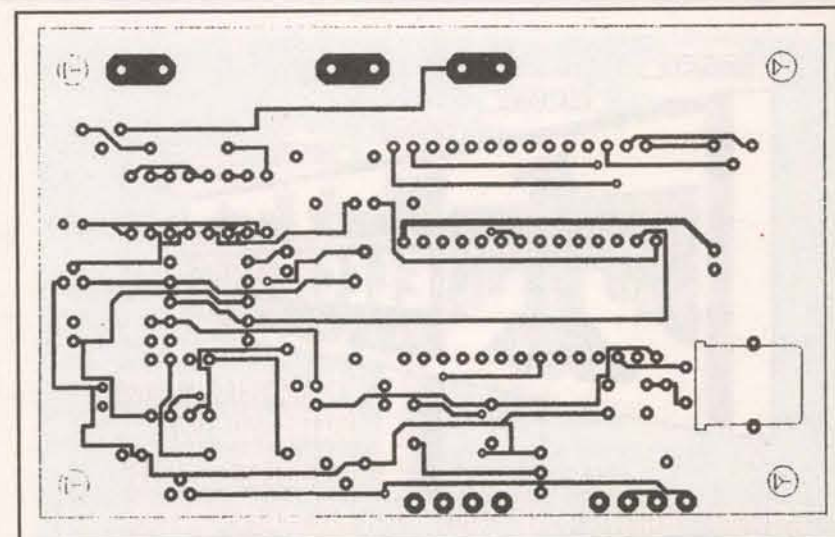

BOTTOM LAYER

#### Code Instruction

```
01H Clear display
38H Set 8-bit data, 2-line display, 5x7 font
02H Cursor to home position
06H Increment cursor, do not shift display
0CH Display on, cursor off, blink off
80H Move to beginning of line 1
COH Move to beginning of line 2
```

```
*****
* PUT_CTRL - Write control word to LCD peripheral *
* Enter with control word in accumulator *
* Return with original value of X *
* Delay ~4.5mS if A=$01 or $02 else delay ~120uS *
*****
```

#### PUT\_CTRL

```
STX TEMPX ;Save X
STA PORTA ;Write control word to LCD
BCLR 7,PORTB ;RW->0 WRITE ENABLE
BCLR 6,PORTB ;RS->0 SELECT COMMAND
BSET 5,PORTB ;E->1
BCLR 5,PORTB ;E->0
LDX #40 ;20*6~1uS/~120uS

L120U DECX ;Delay loop ~120uS
BNE L120U ;20-19,19-18...1-0
CMP #$02 ;Commands $01 & $02 req extra delay
BHI ARN5M ;If command > $02 skip long delay

L5M JSR ANRTS ;JSR+RTS TAKES 12~ (just want delay)
DECX ;TAKES 3~ (X=0->1 on first pass)
BNE L5M ;3~ Loop 256*18~1uS/~4.608mS Delay
ARN5M LDX TEMPX ;Restore X

ANRTS NOP
NOP
NOP
NOP
RTS ;** RETURN **
```

```
*****
* PUT_LCD - Write data word to LCD peripheral *
* Enter with data word in accumulator *
* Return with original values of X & A *
* Delay ~120uS after data write *
*****
```

#### PUT\_LCD

```
STX TEMPX ;Save X
STA TEMPX ;Save A
STA PORTA ;Write data word to LCD
BSET 6,PORTB ;RS->1
BSET 5,PORTB ;E->1
BCLR 5,PORTB ;E->0
BCLR 6,PORTB ;RS->0
LDX #40 ;20*6~1uS/~120uS

L120 DECX ;Delay loop ~120uS
BNE L120 ;20-19,19-18...1-0
LDA TEMPX ;Restore A
LDX TEMPX ;Restore X
RTS ;** RETURN **
```

Listing 2. Put\_CTRL & Put\_LCD



At this point, it's time to connect Watts Showing to 120VAC. With the top half of the case laying face down — so the PCB is facing up — plug the power cord into a convenient outlet.

**SAFETY NOTICE:** There is 120VAC on the circuit board, so please use *extreme* caution. Use an AC voltmeter to measure the potential of the PCB ground to AC ground on an outlet. There should be no more than a few volts differential. If you read over 20VAC, then your circuit is not isolated and **MUST** be fixed before continuing. In some cases, a 'ghost' voltage reading of more than 20VAC could exist. To know if it's real, put a 100k resistor across PCB ground and AC ground and apply AC power. If it's a 'ghost' voltage, then it will drop to near zero VAC. If the voltage holds, it's real.

Disconnect AC power and connect a scope to the anode end of D1. Reconnect AC power and adjust POT2 up and down, using an insulated screwdriver, to a point where the pulses just stop. Now connect a 60W light bulb to the output cord. Turn on the light and the pulses should reappear on the anode of D1. Turn the light off and stand up the case so that the LCD is visible, and also with POT1 and POT2 accessible.

Turn the light on and adjust POT1 for a Watt reading of  $60 \pm 1$  watts. Reset the zero point again by turning off the light and adjusting POT2 to the point at which the Watts display just goes to a 000 reading. Turn the light back on and readjust POT1 for  $60 \pm 1$  watts. This time when the light is turned off, POT2 won't require much adjustment, if any, to reach the point of just zeroing the Watts display.

Try to keep any breeze away from the opto-isolator when calibrating. The stacked differential pairs are extremely sensitive to temperature gradients across the part. It will be impossible to properly calibrate if air currents are moving across UI.

Let the unit sit with power on for about 10 minutes and do one more series of adjustments for a final calibration. Keep in mind the thermal sensitivity of the opto-coupler and be sure it's

**Figure 6 —  
MC68HC705P6  
block diagram.**

- \* Beginning of main timing loop
- \* Loop is executed once every 10mS (exactly)
- \* A pass through all major task routines takes
- \* less than 10mS and then time is wasted until
- \* the output compare flag gets set (every 100mS).
- \* When an output compare triggers, the flag is
- \* cleared & 50000 is added to the compare reg
- \* so the next trigger will occur in exactly 100mS
- \* ( $50000 \times 2\mu\text{S}/\text{cnt} = 10\text{mS}$ ).

The variable TIC keeps track of 100mS periods when TIC increments from 9 to 10 it is cleared to 0 and seconds are incremented.

MAIN1

```
BRCLR 6,TSR,MAIN1 ;Loop here till OCF flag set
LDA    OCMP+1 ;Low byte of OC register
ADD    #$88    ;Low half of 50000
STA    TEMPA   ;Save till high half calculated
LDA    OCMP     ;High byte of OC register
ADC    #$13    ;High half of 50000 (+carry)
STA    OCMP     ;Update OC reg
LDA    TEMPA   ;et low half of updated value
STA    OCMP+1  ;Update low half of OC reg
```

\* OC now = old OC + 50000, and OCF flag is clear

LDA	TIC	;Get current TIC value
INCA		;TIC=TIC+1
STA	TIC	;Update TIC
CMP	#10T	;10th TIC ?
BLO	ARNC1	;if not, skip next clear
CLR	TIC	;Clear TIC on 10th

ARNC1 EQU

- \* End of synchronization to 10mS TIC; Run main tasks and
- \* branch back to main within 100mS. Sync OK as long as
- \* no 2 consecutive passes take more than 200mS.


### Listing 3. 10Ms Timing Routine

shielded from air currents or direct incandescent light which might warm the part.

Turn off Watts Showing and unplug it from the 120VAC outlet. Put the strain relief's on the power cords and put both halves of the case together around each strain relief. Use the four screws to tighten the case halves and you're done.

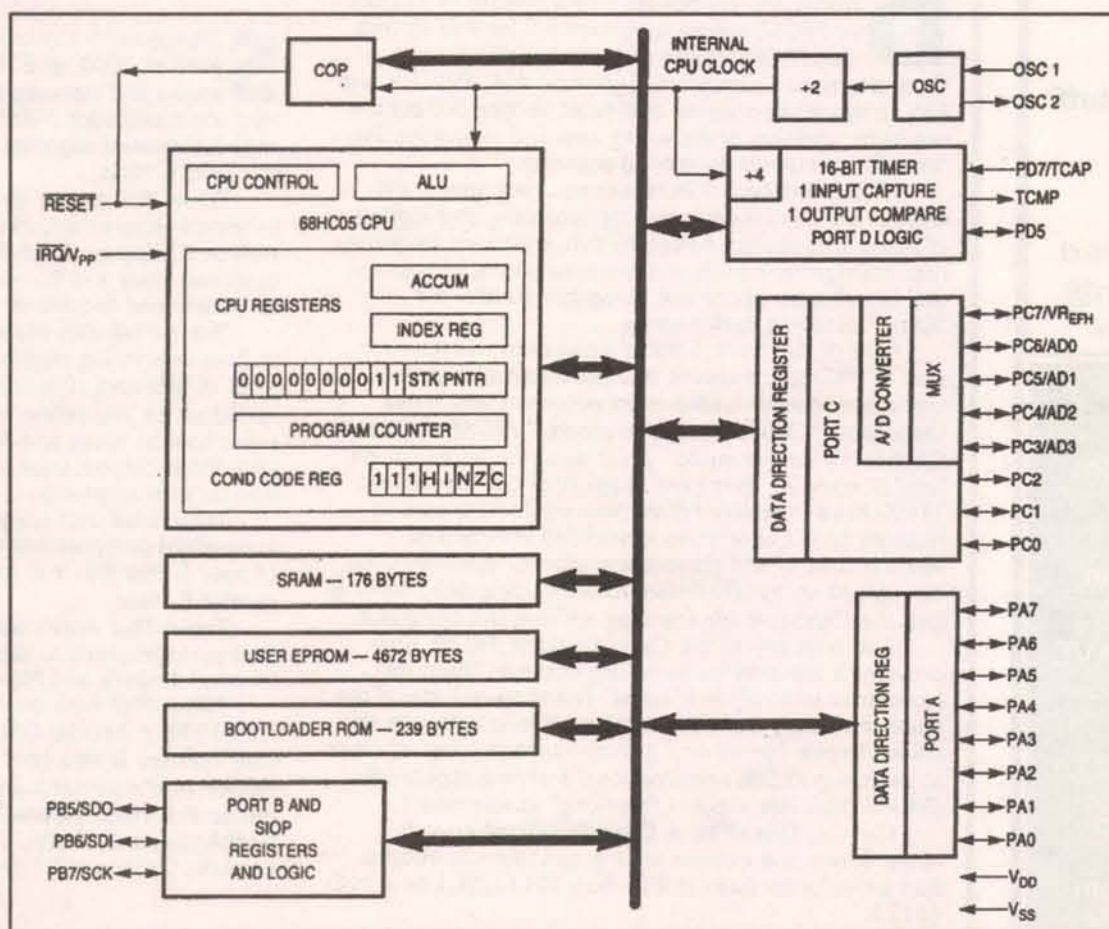
## Using Watts Showing

You can use Watts Showing to collect data on energy usage costs for appliances around your



**Learn MICROCONTROLLERS  
EMBEDDED SYSTEMS and  
PROGRAMMING...**

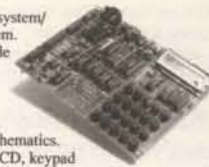with the AES learning system/  
embedded control system.  
Extensive manuals guide  
you through your  
development project.  
All programming  
and hardware details  
explained. Complete schematics.  
Learn to program the LCD, keypad,  
digital, analog, and serial I/O. for  
your applications.



**THREE MODELS AVAILABLE.**  
Choose from an Intel 8051,  
Intel 8088, or Motorola 68HC11  
based system.  
All models come with:

- 32K Byte ROM, 32K Byte RAM • 2 by 16 Liquid Crystal Display • 4 by 5 Keypad • Digital, Analog, and Serial I/O • Interrupts, timers, chip-selects • 26 pin expansion connector • Built-in Logic Probe • Power Supply (can also be battery operated) • Powerful ROM MONITOR to help you program • Connects to your PC for programming or data logging (cable included) • Assembly, BASIC, and C programming (varies with model) • Program disks with Cross Assembler and many, well documented, program examples • User's Manuals: cover all details (over 500 pages) • Completely assembled and ready to use • Source code for all drivers and MONITOR • Optional Text Book

**Everything you need. From \$279**  
**Money Back Guarantee**

Call for Free Info Pack, or see  
WEB at <http://www.aesmicro.com>  
714-979-1091, FAX 714-979-1093

**Call 1-800-730-3232**

**AES**  
Advanced Educational Systems

AES 2110 S. LYON ST., STE. C, SANTA ANA, CA 92705 USA

home or office or make sure that a power-strip's ratings won't be exceeded by all of the devices plugged into it. Take a freezer, for example. A typical household freezer will require 200-400 watts when the compressor is running. But the compressor only runs when its inside temperature exceeds the thermostatically-controlled value. At any given

time, it may or may not be running. If you connect the freezer to 120VAC through Watts Showing, and let it run for a day, you can see the total watt hours accumulated over time. After allowing it to run for 24 hours, you can multiply the watt-hours accumulated by your local power provider's rate to get cost-per-day of freezer operation.

Electric rates average about \$0.085 per kilowatt hour in the U.S. If your freezer used 2000 W/hr a day, the cost would be \$.17 or \$.5.10 per month. Of course, the duty cycle will vary with the amount of insulation in the freezer and the ambient temperature where the freezer is located.

Finally, I would like to thank Steve Woodward for his design of the modified Gilbert Cell power measurement circuit. **NV**



## PICmicros & BASIC

### PicBasic Compiler - \$99.95

Put BASIC Stamp I programs right into a PIC microcontroller - no BS1 module necessary! The programs run faster and can be longer. You also get more variables and extra instructions. For mid-range PIC12C67x, 16C55x, 6xx, 7xx, 8x, 9xx.

### PicBasic Pro Compiler - \$249.95

PicBasic Pro is BASIC Stamp II compatible, and like the standard compiler above, eliminates the need for a BS2 module. Pro adds built-in LCD support, interrupts in BASIC, arrays, program size to 16K, real If..Then..Else and I/O to any PIC pin. For mid-range PIC12C67x, 16C55x, 6xx, 7xx, 8x, 87x, 9xx and high-end 17Cxxx.

### New! PIC-XI Experimenter/ Lab Board

Bare PCB only - \$49.95  
Kit with parts - \$139.95  
Assembled - \$199.95



### EPIC Plus PIC Programmer - \$59.95



Programs PIC12C5xx, 67x, 14Cxxx, 16C505, 55x, 6xx, 7xx, 8x, 87x and 9xx.  
Optional ZIF adapters for DIP, SOIC, MQFP, PLCC.

Runs off two 9-volt batts or optional AC adapter. Includes programming software and assembler.

### PICProto Prototyping Boards

Get it wired quicker! High-quality blank prototyping boards for PICmicros. Holds 5V reg. caps, osc, DB9-25, large proto area.  
\$8.95 - \$19.95



microEngineering Labs, Inc.

Box 7532 Colorado Springs CO 80933  
(719) 520-5323 (719) 520-1867 fax  
<http://www.melabs.com>

Write in 189 on Reader Service Card.

## ON-LINE AUCTION [www.gosam.com](http://www.gosam.com)

HP  
WAVETEK  
FLUKE  
TEKTRONIX  
Other electronic "stuff"  
Auctions every  
2nd & 4th week

Can't wait till your next  
swap meet? log-on@  
[www.gosam.com](http://www.gosam.com)


## PRINTERS

[samelectronics.com](http://samelectronics.com)

Canon, HP, Epson,  
Lexmark  
Order on-line & SAVE

MONITORS  
ACER, NEC, etc.

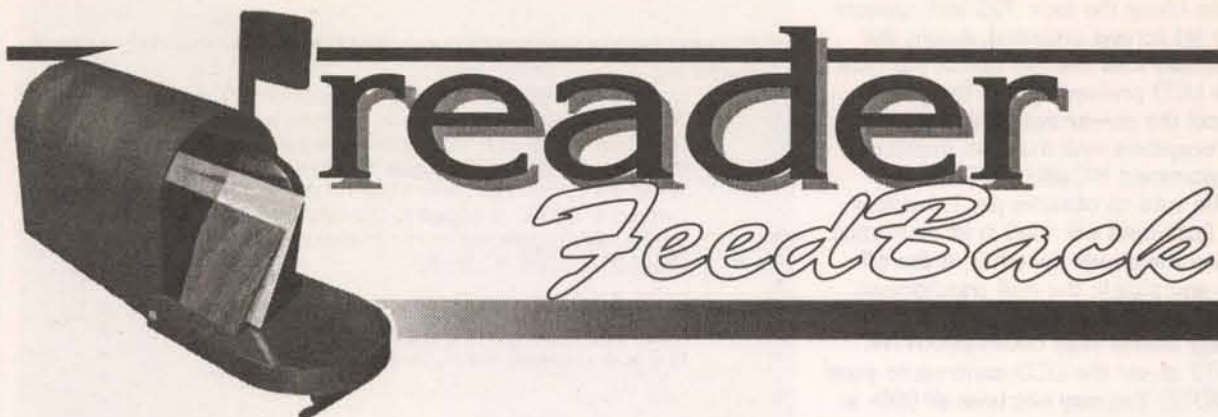[samelectronics.com](http://samelectronics.com)



Dear Nuts & Volts:

I just received my first subscription issue of *Nuts & Volts*, June '99, and I just had to say how impressed I am with the wealth of information contained within.

As an electronics technician, it is very important to me to stay current with the changes in technology.

Your writers and contributors are very knowledgeable and seem eager to solve any reader problems with an enthusiasm that has driven me to want to expand my knowledge into other areas of electronics.

As I have not yet had the opportunity to send you a problem (my questions seem to get answered before I ask them), it is reassuring to know that there is such a knowledge base to seek advice from.

Case in point: I work for a Christian-run electronics repair facility in NY, and the owner built a cross 12' x 7' with flashing LEDs and in the center of the cross bar is the name JESUS in super bright LEDs. We have requests to build others,

but needed to develop a self-contained power supply so the cross could be just plugged into a 110 VAC source.

On pages 22, 23 of June '99 was my answer for a low-voltage, high-current power supply.

Just for that reason, you have a reader for life. Keep up the great work.

Edward C. Anderson, Jr.  
[ecajr@acmenet.net](mailto:ecajr@acmenet.net)

Dear Nuts & Volts:

A reader asked how to change the receive frequency of a Plectron monitor (Tech Forum question 5998). The advice given was correct, but a little incomplete.

While it is true that all you need to do is use a crystal of a different frequency, there is much more that you need to specify about the crystal besides its frequency.

For example, the crystal will almost certainly be an overtone unit, or one which oscillates readily at the third, fifth, or seventh harmonic.

Continued on page 86

# Newsbytes

## NEW RELEASE OF PROBE VERSION 5.0 SOFTWARE

**D**ataFile, Inc. announces a new release of its popular *PROBE* software, Version 5.0, now in its fifth year. *PROBE* works exclusively with Optoelectronic's Optocom, Optoscan 456, 456 Lite, and 535 computer-to-scanner interfaces. Version 5.0 continues in its tradition of delivering new and innovative features for computer-controlled scanning.

*PROBE* Version 5.0 increases accuracy, speed, and control for unattended scanning, searching, and logging of active frequencies. Added to that, enhanced frequency data management tools and more functions to improve the overall ease of use and computer control for "Opto" scanning performance.

One of the more notable features in this new version of *PROBE* is support of Optoelectronic's new Optocom scanner. Unlike most programs which use Optocom's "OS535 Emulation mode," *PROBE* V5.0 uses Optocom's "native mode" which provides an enhanced level of scanning speed and support of the Optocom's 38400 baud capability. *PROBE* also supports access to features such as computer-controlled volume and squelch control and stand-alone scanner operation. You can upload up to 100 frequencies including delay settings into the Optocom for scanning without the computer.

And with any of the Opto products, *PROBE* now provides a function for switching between "Remote" (computer control) and "Local" (stand-alone) use of the scanner directly from the scanning screen with one simple keystroke. No other Optocom software comes close to matching *PROBE*'s conventional scanning capabilities. (*PROBE* does not support "trunking" at this time.)

Contact DataFile at [Datafiles@aol.com](mailto:Datafiles@aol.com) for more details and current pricing, and upgrade information or write to them at P.O. Box 20111, St. Louis, MO 63123.

## USING TALK-N-MAIL TO BRING E-MAIL COMMUNICATION TO LIFE

**S**oftApproach Corporation has released Talk-n-Mail version 2000, an E-Mail software that brings multimedia and Internet technologies together for E-Mail communication. With Talk-n-Mail, you use a microphone, animated pictures, and other cool stuff to create and send E-Mails.

Talk-n-Mail is easy to learn and fun to use. It offers animated pictures and Mail Templates to cover areas such as Christmas, Birthday, Computer, Sports, Kids Only, and Love and Romance. Its documentation is easy to understand and full of attractive pictures.

Talk-n-Mail uses objects instead of an entire picture to hold everything together. An object can be an animal, a set of billboard-style text playing frame by frame, or a sound script. You define how an object looks like, and tell it how to move and how to respond to your mouse click. With objects, your imagination is the only limitation to your creativity.

Talk-n-Mail uses unique techniques plus the industrial standard compression technology to reduce the size of your E-Mail files and thus reduce the time to send or receive E-Mails.

Talk-n-Mail works seamlessly with other popular E-Mail packages, such as Yahoo! Mail, America Online Mail, Hotmail, Eudora, and Microsoft Outlook.

Talk-n-Mail runs on Windows 95/98/NT and costs US \$39.98. It has the Gift Pack discount for multiple user licenses. It also contains a fully functional Free Edition in the same package. For more information, please visit <http://www.Talk-n-Mail.com> or contact SoftApproach Corp., 38 Brahm's Ave., Toronto, Ontario, Canada, M2H 1H4.

Continued on page 86



# We've Got It!

## MCM Electronics®

Prices effective  
July 16, through  
August 31, 1999.

For over 20 years, MCM has been the leading supplier to the electronics service industry. Huge inventory, rapid delivery and competitive prices have made MCM the choice for:

- Hobbyists
- Service Technicians
- Educators
- Installers

### Aluminum Tool Case

•Constructed with durable lightweight aluminum •Adjustable dividers •Tool palate with 17 tool pockets •Dimensions: 18" x 13" x 6 1/2" •Regular price \$39.95

Order #  
#22-3875  
\$29.50



### 8" Rubber Surround Polypropylene Woofer

#### MCM AUDIO SELECT™

Popular woofer design is the foundation of many home and auto speaker systems. 70W/100W RMS/peak capacity, frequency response 30Hz-3.5KHz. 8ohm. Other sizes available. Regular price \$13.50

Order #  
#55-1180  
\$9.95




### Regulated 13.8VDC Power Supplies

Choose the size that best suits your needs. All models have binding post connections, 4A, 7A and 10A versions include a cigarette lighter receptacle. Ripple voltage: <50mV, full load.



Order #	Continuous/Current	Surge (ea.)
72-6621	4A/6A	\$29.95
72-6622	7A/10A	49.95
72-6623	10A/14A	64.95
72-6624	15A/20A	84.95
72-6625	20A/25A	99.95

### Pre-Assembled Circuit Modules

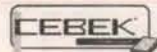

Ideal for repairing old equipment, prototype work or your latest project. These well constructed PC boards are fully assembled, tested and ready to use. Supplied with application instructions and technical specifications. All operate from a single 12VDC source. Call your MCM Sales Representative for more information on over 120 available modules.



Order #	Description	Reg.	Sale
28-4795	1W audio amplifier	\$7.49	\$5.99
28-4796	5W audio amplifier	13.95	11.15
28-4800	5W x 2 stereo amplifier	24.95	19.96
28-4801	15W x 2 stereo amplifier	39.95	31.96
28-4851	88-108MHz FM transmitter	24.95	19.96
28-4785	2 digit LED counter	14.95	11.96
28-5115	Flip-flop relay	16.50	11.96
28-4825	VOX relay	17.95	14.36
28-4815	Electric guitar preamplifier	8.95	7.16

### Ultra Compact CCD Camera

•Measures only 1 1/2" square •3.6mm lens •92° viewing angle •Requires 12VDC, 100mA •NTSC composite video output •75ohm •Regular price \$79.95

Order #  
#82-3890  
\$69.95



### Multi-Voltage Power Supply

Great for projects or as a battery eliminator. Provides 2A output on any of the following voltages: 3, 4V, 6, 7V, 9 and 12VDC. Regular price \$16.95

Order #  
#28-2200  
\$10.50



### 85 Channel Cable Converter

Includes last channel recall, channel memory, switched AC outlet and sleep timer. Remote requires two "AA" batteries (MCM #290-070). Regular price \$61.75.

Order #  
#33-2065  
\$49.95



### Multiple DC Outlet Strip

Great for use with any benchtop power supply. Allows easy connection and disconnection of multiple accessories. •DC voltage meter •15A fuse •Power switch •Eight pairs of RF bypassed binding posts •Regular price \$44.95

Order #  
#111-2874  
\$39.95



### Subwoofer Amplifier Module


Ideal for anyone interested in building their own powered subwoofer. •Isolated left/right speaker level inputs •Single line level input •40W/50W RMS/peak output •Auto turn-on •Continuously variable 40Hz-180Hz crossover •Adjustable level control

Order #  
#50-6270  
\$69.95


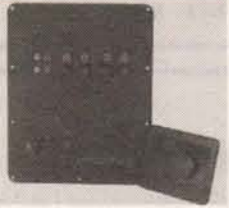
### 70 Watt Subwoofer Amplifier Module

A step-up from or #50-6270, this power amplifier features speaker level inputs, satellite outputs and line level inputs. •70W RMS output •Auto turn-on •12dB continuously variable 60Hz-160Hz crossover •Remote mount adjustable level control •Note: AC power cord not included, must be purchased separately.



Order #	Description	(ea.)	(2-9)
50-6275	Amplifier module	\$89.95	\$79.95
23-145	3' power cord	2.59	-
23-130	6' power cord	2.99	-
23-200	10' power cord	3.99	-

To take advantage of special pricing on the items listed, please provide this code: **NVM26**

### DMM W/Logic Function

**TENNA** 3 1/2 digit DMM measures AC/DC voltage from 200mV-600V, resistance to 2000Mohm, capacitance to 20uF, transistor hFE gain and audible continuity test. Requires 9V battery (#290-080) not included. Dimensions: 2 1/2" (W) x 5 1/4" (H) x 1 1/2" (D). Regular price \$65.95.

Order #  
#72-4025  
\$39.95



### Sealed Lead Acid Battery

**CS** 12 volt, 4.5 Amp/hour battery is ideal for security and other power backup applications. 0.25" tabs accept standard quick-disconnects. Dimensions 3 1/2" x 2 1/4" x 4". Regular price \$26.95

Order #  
#28-1335  
\$14.95



### 20MHz Oscilloscope

#### TENNA

Dual channel, dual trace scope offers external triggering functions for increased flexibility. 20MHz bandwidth is ideal in the classroom or for general service applications. Includes two 10:1 test probes. Regular price \$395.00

Order #  
#72-3055  
\$350.00



### Remote Control A/B Switch

Remote controlled RF switch allows selection from two sources for output to TV or VCR, via infrared remote. Frequency range: 5MHz-8900MHz. "F" type in/out connections. Remote requires two "AA" batteries not included (#290-070). Regular price \$25.75

Order #  
#32-4425  
\$19.95



### NTSC/PAL Video System Converter

Ideal when TVs or VCRs are to be connected with overseas models. Accepts NTSC signal and provides PAL output. Connects between VCR video line out and TV video line in. Requires television with vertical hold control. Includes 120/240V switchable AC adaptor. Regular price \$49.95

Order #  
#32-5180  
\$39.95



**FREE Literature**

Same Day Shipping!

In stock orders received by 5:00 p.m. (YOUR TIME), are shipped the same day.




**MCM ELECTRONICS®**  
650 CONGRESS PARK DR.  
CENTERVILLE, OH 45459  
A PREMIER FARNELL Company

For complete ordering information on the items listed, or a free catalog, Call...  
**1-800-543-4330**  
www.mcmelectronics.com  
SOURCE CODE: NVM26



# STAMP APPLICATIONS

by Lon Glazner

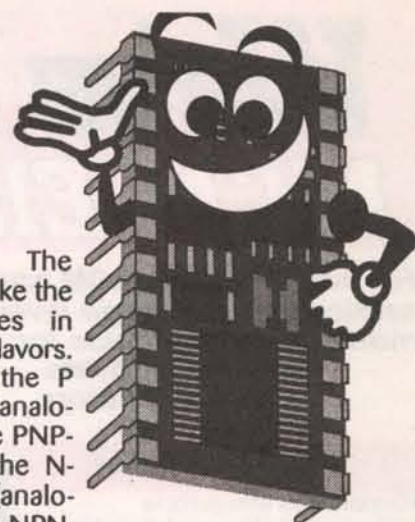

## Putting the Spotlight on BASIC Stamp Projects, Hints, and Tips

### Stamp-Controlled High Power H-Bridge

It seems like quite a few people are using BASIC Stamps as the brains in low-level robotics. Because of simplicity, ease of use, and versatility, it's no wonder that the BASIC Stamp is finding wide spread use with hobbyists and amateur robotics groups.

#### Overview

On the Stamp List — an informative E-Mail list provided by Parallax — I routinely see questions about how to bridge the gap between power devices and the BASIC Stamp. Often times, the applications require relatively high power motors for robotics, or other more industrial needs. I thought it might be interesting to share my experiences with an IC that I've used several times in the past.

This circuit can be used for controlling high current motors, driving relays, controlling lamps, and powering heating elements, just to name a few of the possible applications.

#### Defining the Design

The first thing that needs to be defined is what I mean by "high power." For the purposes of this article, I think we should limit it to about 30V and no more than 30A (so anything in the area of 900W). In the real world of hydroelectric dams and power utility companies, 900W is minuscule. But here, in the land of BASIC Stamps, I feel pretty comfortable using the "high power" moniker for this circuit.

One of the first concerns a designer has to face when confronted with high power require-

ments is the question of power dissipation. Any voltage drop across a device carrying current is accompanied with power being dissipated in the device as heat. In high current applications, any voltage drop can create significant needs for heatsinks and other means of removing the heat from the current carrying device.

For instance, take a power diode with a forward voltage drop of 0.5V. This diode carrying a load current of 1A would be required to dissipate 0.5W of power ( $\text{Power} = \text{Voltage} \times \text{Current}$ ;  $P=VI$ ). That is not too big of a deal. But increase the diodes load current to 30A and you've got a problem, a 15W problem.

For this reason, designers will often attempt to reduce the voltage drops that might be found in a high current application. A device that is ideal for this — metal-oxide-semiconductor-field-effect-transistor, which can be considered a voltage-controlled switch. Like the BJT (bipolar-junction-transistor, such as a 2N3904), the MOSFET can be biased into its active region (not all the way on, or all the way off). But in power switching applications, that is rarely done. In this design, the MOSFETs will be used either in the on or off state. Many applications require a load to be "turned on/off." This often means closing (on) or opening (off) a current path to your load, and MOSFETs are ideal for this purpose.

Previously, I defined high power as meaning about 900W. In a perfect system, we would lose no power in our MOSFETs as they switch our load into or out of the circuit. Therefore, all of the 900W would be dissipated by our load. But, of course, this isn't the case.

A little bit of information about MOSFETs would probably be helpful at this point. As I mentioned earlier, a MOSFET can be considered a voltage-controlled switch. This differs from a BJT which is a current-controlled

switch. The MOSFET, like the BJT, comes in two basic flavors. They are the P channel (analogous to the PNP-BJT) and the N-channel (analogous to the NPN-BJT). A MOSFET typically has three points of connection. They are: the gate, drain, and source (similar to the base, collector, and emitter of a BJT).

All MOSFETs have an "on resistance." This can be considered a resistor in series with your load. In a particular MOSFET data sheet, this

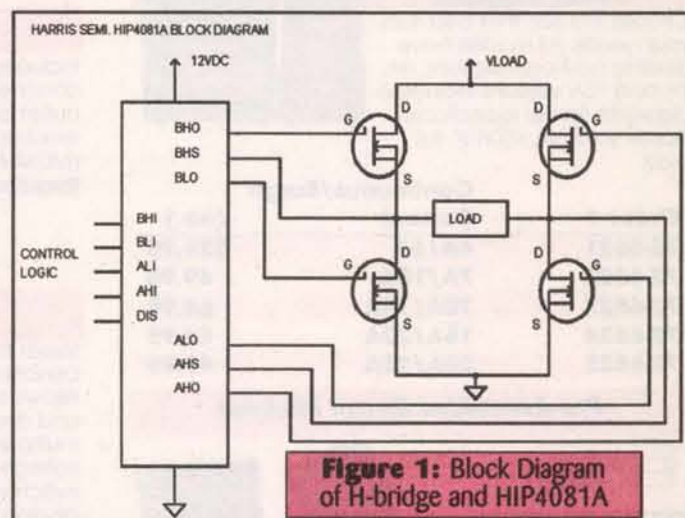


Figure 1: Block Diagram of H-bridge and HIP4081A

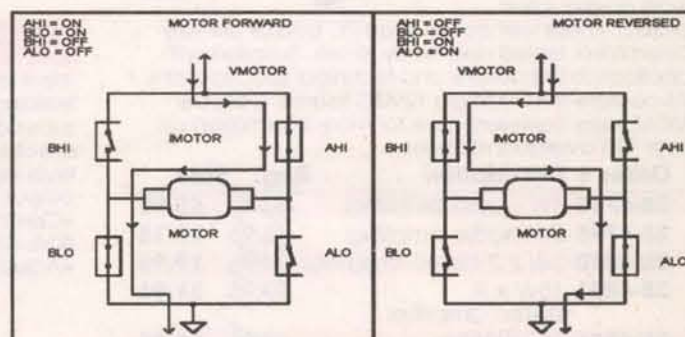


Figure 2: Current Flow Through an H-bridge

### Explore Fuzzy Logic with the AL220 device and

#### Fuzzy Logic Applications Expert (FAE) Development System.

The AL220 Device is a complete Single Chip Fuzzy Logic microcontroller which contains 4 analog inputs and 4 analog outputs. It was voted the most innovative product of 1994 by EDN magazine. Now it is available with a complete PC based development system, programmer, and real time hardware Emulator for hobbyist as well as professionals! Check out our web site at [www.BasiConcepts.com](http://www.BasiConcepts.com) for free data sheets, application notes, and additional product information.

Order	Description	Price Each
AL220	18 Pin Dip AL220 Device	\$12
FAE	FAE Dev System for Win 95/98 on CD	\$65
Hobby Pack	AL220, FAE, and Printer Port Programmer	\$95
Professional Pack	AL220, FAE, Programmer, and Real Time Hardware Emulator System	\$495

BasiConcepts, Inc. 312 W. First St. Suite 201, Sanford, FL 32771  
Tel: (407)322-5608 Fax: (407)322-5609 Email: [info@BasiConcepts.com](mailto:info@BasiConcepts.com)

## Professional 10 HOUR RECORDER

Factory Direct

"BUILT LIKE A BATTLESHIP"

- Heavy duty commercial recorder - NOT improvised from consumer models
- 12, 14, and 16 hour models also available
- BUILT-IN voice activation (add \$30)
- Applications information included
- Dimensions: 11.5 x 7.0 x 2.75"

SPECIAL Nuts & Volts Price..

**\$159**

COD's OK. Sorry, no credit cards. Free catalog USA only; other countries \$5. Price Includes UPS to 48 States on Pre-Paid Orders

Viking International 150 Executive Park Blvd. #4600 San Francisco, CA 94134  
Phone: (415) 488-2066 • Fax: (415) 488-2067 • Web: [www.vikingint.com](http://www.vikingint.com)



# STAMP APPLICATIONS

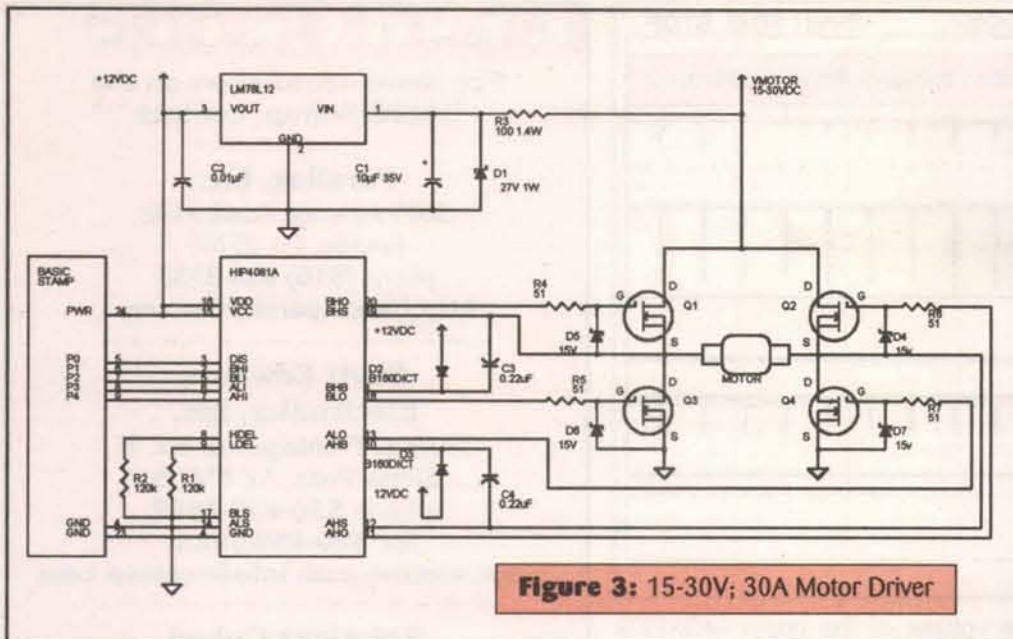


Figure 3: 15-30V; 30A Motor Driver

that allows you to change the direction of current flow through a load. This is done by selecting which pair of switches are on and which pair are off. This is particularly useful for controlling bi-directional motors.

We'll assume that our load is a motor for this design, although many types of loads could be controlled with the circuit that will be defined here. An H-bridge requires that there be two switches located between the system voltage supply and the load, and two switches located

between the load and the system ground return. To reduce power dissipation, it is desirable to use N channel MOSFETs for each of the four switches. This creates a significant problem. To fully turn on an N channel MOSFET, the gate drive voltage should be about 12V above the voltage at that MOSFET's source. In an H-bridge, the high side switches will have their source pins at the system voltage level when they are on. For example, in the system being designed here, I'll be using 18-20VDC for the system voltage. That means I'll need roughly 30-32V to drive my high side N channel MOSFETs. Things are definitely getting complicated!

## Connecting the Parts

Have you ever looked at an engineering problem before and said "Hey, this should definitely be easier than it is turning out to be?" Well, I think the people at Harris Semiconductor ([www.semi.harris.com](http://www.semi.harris.com)) did just that when they designed the HIP4081A H-bridge

value is typically listed as  $R_{ds(on)}$  (resistance from drain to source while the device is on). N channel MOSFETs typically have a lower  $R_{ds(on)}$  resistance as compared to the P channel types. Most power dissipated by a MOSFET is due to the  $R_{ds(on)}$  value. The  $R_{ds(on)}$  value is also dependent on the "gate drive voltage" (voltage on the gate when referenced to the source).

Therefore, for high power applications, you would want to do several things to minimize power dissipation in your circuit. You would use N-channel MOSFETs with low  $R_{ds(on)}$  values. It is desirable to maximize the gate drive voltage in order to minimize the  $R_{ds(on)}$  of your MOSFET. You would also ensure that when you turn your MOSFET on, the gate drive voltage would have a fast rise time to minimize the amount of time that the MOSFET is in its active region (the fall time of the gate drive voltage is also important when turning a MOSFET off).

This brings us to the concept of an H-bridge. The H-bridge is a configuration of four switching devices

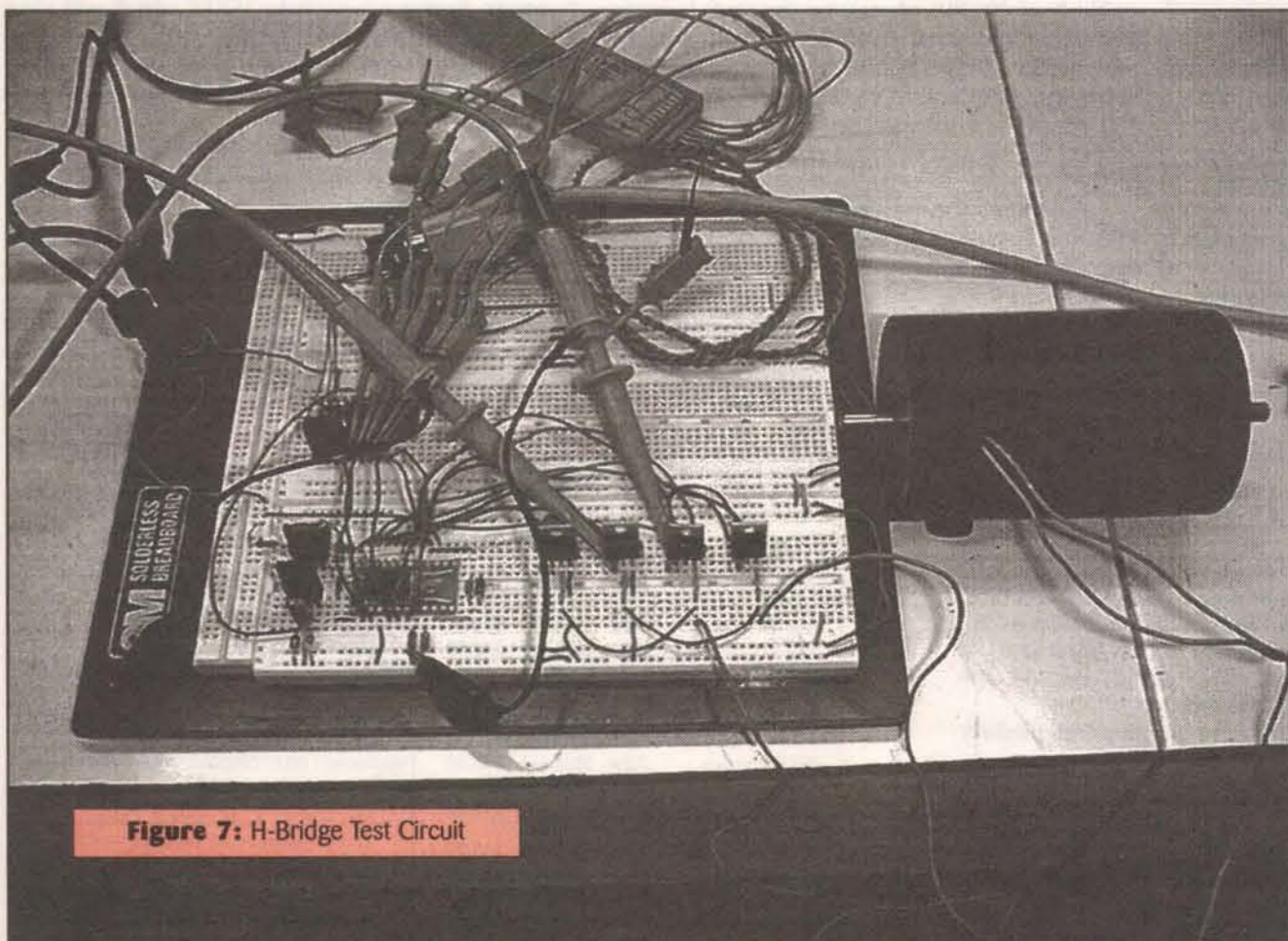


Figure 7: H-Bridge Test Circuit

## JFETS

ULTRA LOW NOISE  
LS843 - 3nV/Hz typ

TIGHT MATCHING  
LS843 - 1 mV max

- ◆ N & P Channel
- ◆ Duals & Singles
- ◆ Custom Screening
- ◆ Die, SMT, Thru-Hole
- ◆ No Order Minimum
- ◆ COD's Accepted

Second Source for Domestic  
& Foreign JFETs & Bipolars

Full Service U.S. Manufacturer  
of Specialty Linear Products

## LINEAR SYSTEMS

4042 Clipper Court  
Fremont, CA 94538  
510-490-9160/510-353-0261(Fax)  
E-mail: 3623671@MCIMAIL.COM

Write In 74 on Reader Service Card.



The RF Connection  
213 North Frederick Ave.  
Suite 11NV  
Gaithersburg, MD USA  
20877

<http://www.therfc.com/>

Complete Selection of MIL-Spec Coax, RF  
Connectors and Relays

UG-21B/U N Male for RG-213/214.....\$5.00  
UG-21D/U N Male for RG-213/214.....\$3.25

N Connectors for 9913/Flexi4XL/9096

UG-21B/9913.....\$6.00 Pins Only.....\$1.50  
UG-21D/9913.....\$4.00 Extra Gasket......75

Amphenol 83-1SP-1050 PL-259.....\$0.90  
UG-176/U Reducer RG-59/8X .25 or 5/1.00  
UG-175/U Reducer RG-58/58A .25 or 5/1.00  
Silver Teflon PL-259/Gold Pin.....\$1.00 or 10/\$9.00

MIL-Spec Coax Available (Teflon, PVC IIA)

New Product: Belden 9913F. 9913 with  
High Density PE Foam dielectric, stranded  
center cond. and Duobond III Jacket.....  
.....80/ft or \$76.00/100ft

Also New: 9092, RG8X with Type II Jacket  
Intro Price.....\$23.00/100ft

Call for Specials of the Month

Full Line of Audio Connectors for Icom,  
Kenwood, and Yaesu

8 Pin Mike Female.....\$2.50  
8 Pin Mike Male Panel.....\$2.50  
13 Pin DIN for Kenwood.....\$2.75  
8 Pin DIN for Icom.....\$1.00  
8 Pin DIN for Kenwood.....\$1.50

Prices Do Not Include Shipping

Orders 800/783-2666  
Info 301/840-5477  
FAX 301/869-3680

Write In 75 on Reader Service Card. 19



# STAMP APPLICATIONS

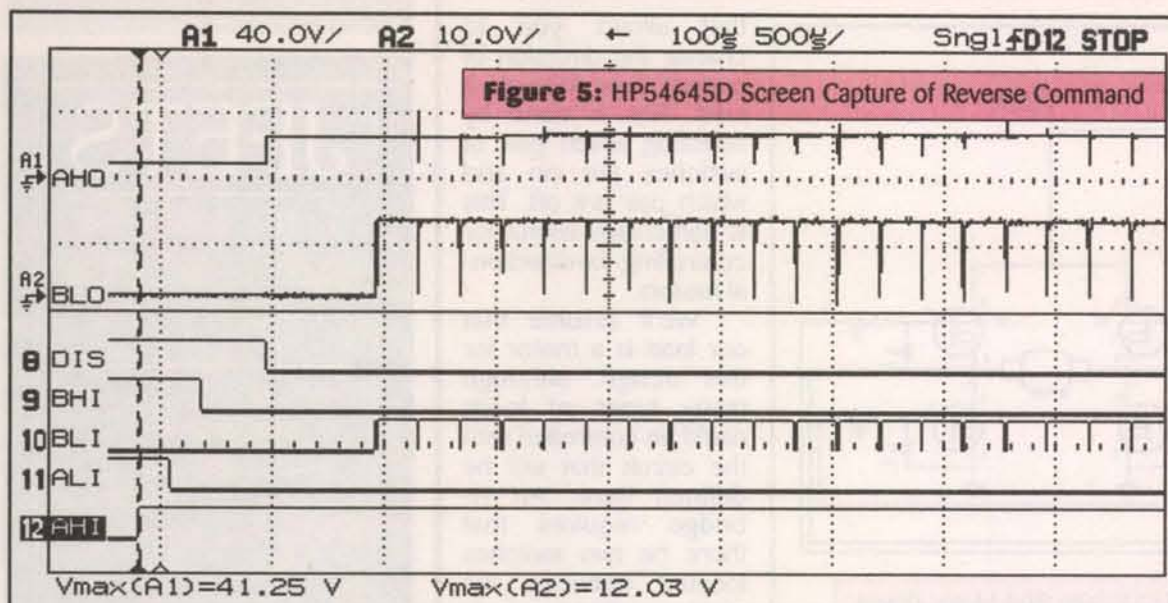


Figure 5: HP54645D Screen Capture of Reverse Command

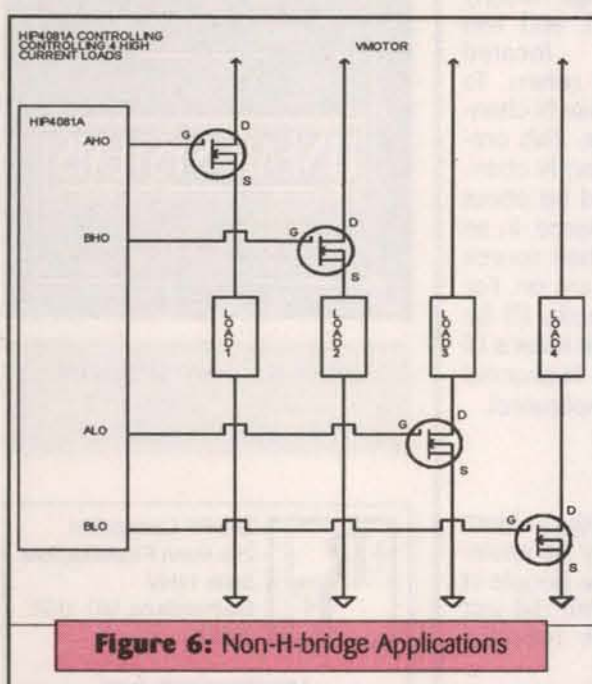


Figure 6: Non-H-bridge Applications

driver chip.

This device provides a logic level interface to an all N-channel MOSFET H-bridge. It also prevents things like shoot-through (inadvertently turning on the wrong switches and shorting your supply to ground through your H-bridge, usually resulting in transistors with cracks, missing legs, and that funny melted electronics smell).

The HIP4081A has on-board charge-pumps and upper bias supplies that are used to raise

the gate drive voltage of the upper MOSFETs above the system bus voltage when they are turned on. This is routinely called a "high-side driver;" two of which are required for an N-channel H-bridge. Figure 2 shows the logic states required for changing the current flow in an H-bridge. In many loads, the amount of current passing through the load is required for control, as well as the current direction. With a motor as your load, this translates to controlling both motor speed and direction. To control speed you can turn on the appropriate high side switch, and then pulse width modulate (PWM) the low side switch.

For the HIP4081A, the control pins are considered high for assertion, meaning that a logic high enables that function. For instance, a logic high (+5V) at the ALI and BHI pins would turn on the B high side driver, as well as the A low side driver.

Component selection for the HIP4081A is relatively simple. I selected the Harris HRF3205 MOSFET which has an  $R_{ds(on)}$  of about eight milli-ohms (0.008 ohms) for the four H-bridge switches. The charge-pump diodes selected were from Digi-Key, but virtually any 60V Schottky diode would work for this application. The charge-pump capacitor (C3,C4) should be at least 10 times the input capacitance of your MOSFET.

The HRF3205 has an input capacitance of 4000pF. I used 0.22uF capacitors, which are oversized but worked fine. The HRF3205 is rated for 55V and 75A. At 30V and 30A, I think we're well within its safe operating range.

## RESOURCES

For more information on the BASIC Stamp, contact:

### Parallax, Inc.

3805 Atherton Road, #102  
Rocklin, CA 95765  
phone (916) 624-8333  
<http://www.parallaxinc.com>

### Scott Edwards

#### Electronics, Inc.

1939 S. Frontage Rd. Ste. F  
Sierra Vista, AZ 85635  
phone 520-459-4802  
fax 520-459-0623

[www.seetron.com](http://www.seetron.com) [info@seetron.com](mailto:info@seetron.com)

### Solutions Cubed

Lon Glazner

3029 Esplanade Suite F  
Chico, CA 95973

E-Mail: [lon@solutions-cubed.com](mailto:lon@solutions-cubed.com)

[www.solutions-cubed.com](http://www.solutions-cubed.com)

Phone: 530-891-8045

Fax: 530-891-1643

I included a power supply circuit that is required for powering the HIP4081A with the motor voltage. This was also used to provide power to the BASIC Stamp. Some additional protection should be added to any noisy circuit to help protect the logic components. In this case, a bi-direction transient voltage suppressor (TVS) could be placed across the motor. Furthermore, RC snubbers, additional suppressors, zener diodes, and poly-fuses could be used to reduce or contain transient voltage spikes.

There are protective gate resistors and zener diodes on each MOSFET which will slow the rise and fall times of the gate drive voltage but they do not have much effect on the performance of this particular circuit. Figure 3 shows the finished schematic.

Power dissipation for this circuit at 30A is around 15W. Additionally, this power dissipation is split between two semiconductors ( $7.2W = 30A^2 \cdot 0.008\Omega$ ;  $P=I^2R$ ). This makes heatsinking easier. At 10A, virtually no heatsinking would be required.

MOSFETs are also ideal for paralleling. They

## WIDGETS

Sensors to RS232, 422 or 485

Starting at \$199

PRESSURE  
THERMOCOUPLE  
RTD  
VOLTAGE  
CURRENT  
MOTION  
GASES  
RH  
And more

Each system comes complete with one sensor, 10, 12 or 14 bit resolution w/ 7 extra channels of A/D, 30k of remote data storage, power supply, serial cable and WINLP-Lite data acquisition software (trending, storing and display)

1-888-597-3588

(530) 647-2028

LEMON-PLADD INC. FAX (530) 647 8951  
PO Box 1683 POLLOCK PINES CA. 95726  
[WWW.LEMONPLADD.COM](http://WWW.LEMONPLADD.COM)

## Mr. NiCd

## AUGUST 1999 SUPER SPECIALS!

THE BEST BATTERIES IN AMERICA!

Packs & Charger for YAESU FT-50R / 40R / 10R:			
FNB-40xh (5w NiMH)	7.2v	650mAh	\$41.95
FNB-47xh (5w NiMH)	7.2v	1800mAh	\$49.95
FNB-41xh (5w NiMH)	9.6v	1000mAh	\$49.95
For YAESU FT-51R / 41R / 11R:			
FNB-38 pack (5w)	9.6v	700mAh	\$39.95
For YAESU FT-530 / 416 / 816 / 76 / 26:			
FNB-26 pack (NiMH)	7.2v	1500mAh	\$32.95
FNB-27s (5w NiMH)	12.0v	1000mAh	\$45.95
For YAESU FT-411 / 470 / 73 / 33 / 23:			
FNB-11 pack (5w)	12.0v	600mAh	\$24.95
FBA-10 6-Cell AA case			\$14.95
Packs for ALINCO DJ-580 / 582 / 180 radios:			
EBP-20ns pack	7.2v	1500mAh	\$29.95
EBP-22nh pk (5w)	12.0v	1000mAh	\$36.95
EDH-11 6-Cell AA case			\$14.95
For ICOM IC-21A / T22-42A / W31-32A / T7A:			
BP-180xh pk (NiMH)	7.2v	1000mAh	\$39.95
BP-173 pack (5w)	9.6v	700mAh	\$49.95
For ICOM IC-W21A / 2GXAT / V21AT: (Black or Gray)			
BP-132s (5w NiMH)	12.0v	1500mAh	\$49.95

For ICOM IC-2SAT / W2A / 3SAT / 4SAT etc:			
BP-83 pack	7.2v	600mAh	\$23.95
For ICOM 02AT etc & Radio Shack HTX-202 / 404:			
BP-8h pack	8.4v	1400mAh	\$32.95
BP-202s pack (HTX-202)	7.2v	1400mAh	\$29.95
For KENWOOD TH-79A / 42A / 22A:			
PB-32xh pack (NiMH)	6.0v	1000mAh	\$29.95
PB-34xh pack (5w NiMH)	9.6v	1000mAh	\$39.95
For KENWOOD TH-78 / 48 / 28 / 27:			
PB-13 (original size)	7.2v	700mAh	\$26.95
For KENWOOD TH-77, 75, 55, 46, 45, 26, 25:			
PB-6x (NiMH, w/charging plug)	7.2v	1200mAh	\$34.95

Mail, phone, & Fax orders welcome! Pay with Mastercard / VISA / DISCOVER / American Express  
Call 608-831-3443 / Fax 608-831-1082  
Mr. NiCd - E. H. Yost & Company  
2211-D Parview Road, Middleton, WI 53562  
CALL OR WRITE FOR OUR FREE CATALOG!  
Cellular / Laptop / Videocam / Commercial & Aviation packs too!  
E-mail: [ehyost@midplains.net](mailto:ehyost@midplains.net)



# STAMP APPLICATIONS

'NV\_SEP99.BS2 - This BASIC Stamp 2 program runs a high current motor one direction, stops the motor, and runs it in 'the other direction. This is repeated until power is removed.

```
DISpin  CON  0      'Disable input, logic high disables all outputs
        BHIpin CON  1      'B high side control pin, a logic high turns on B high side driver
        BLIpin CON  2      'B low side control pin, a logic high turns on B low side driver
        ALIpin CON  3      'A low side control pin, a logic high turns on A low side driver
        AHIpin CON  4      'A high side control pin, a logic high turns on A high side driver

        PWMreg VAR  BYTE  'Pulse width modulation duty cycle register
        DURreg VAR  BYTE  'Pulse width modulation duration register
        Loop   VAR  BYTE  'FOR...NEXT loop variable

        HIGH  DISpin      'Disable H-bridge on power up
        PAUSE 500

        DURreg =100      'Duration = 100
        PWMreg =250      'Duty cycle is 98%

FORWARD
HIGH  DISpin      'Disable all driver outputs(stops motor)
PAUSE 1000        'Wait 1s then set input values
HIGH  BHIpin      'Enable B high side driver
LOW   BLIpin      'Disable B low side driver
LOW   AHIpin      'Disable A high side driver
LOW   ALIpin      'Disable A low side driver(will PWM it below)
LOW   DISpin      'Enable all driver outputs(only B high side in this case)

FOR    Loop = 1 to 25
PWM    ALIpin,PWMreg,DURreg  'PWM A low side driver
NEXT

REVERSE
HIGH  DISpin      'Disable all driver outputs(stops motor)
PAUSE 1000        'Pause 1s then set input values
HIGH  AHIpin      'Enable A high side driver
LOW   ALIpin      'Disable A low side driver
LOW   BHIpin      'Disable B high side driver
LOW   BLIpin      'Disable B low side driver(will PWM it below)
LOW   DISpin      'Enable all driver outputs(only A high side in this case)

FOR    Loop = 1 to 25
PWM    BLIpin,PWMreg,DURreg  'PWM B low side driver
NEXT
GOTO  FORWARD      'Change direction again

END
```

work well in current sharing applications. The current that the device passes is based, to a degree, on the  $R_{ds(on)}$  value of the MOSFET (and, of course, on the load resistance and bus voltage). In addition to being dependent on the "gate drive voltage," the  $R_{ds(on)}$  value will increase as the MOSFET's junction temperature increases. So, if a MOSFET gets hot, it will pass less current because of a increasing  $R_{ds(on)}$  value. Therefore, if two (or more) MOSFETs are connected in parallel, and one begins to heat up, it will eventually begin drawing less current than the cooler MOSFET of the pair, and subsequently cool down. This is assuming that all of the MOSFETs paralleled are of the same type; 100A plus H-bridge circuits can be realized with

parallel MOSFETs and an H-bridge driver like the HIP4081A.

## Writing the Code

The BASIC Stamp has limited PWM capability. The PWM command works just fine, but you can't have it run in the background (perform serial communication, etc., while doing PWM). Many applications will require a separate PWM generating device external to the BASIC Stamp. This application simply controls the HIP4081A by running the motor in one direction, stopping the motor, and then running it in the other direction. This should give most people insight into the simplicity of H-bridge control with a

logic level device.

In the code example in Figure 4, the DISpin (disable pin) was used to shut down the H-bridge driver. You can see in Figure 4 that the gate drive voltage on the A high side switch stayed at about 30V. The system was running with an 18VDC bus. Since the HIP4081A was powered by a 12VDC regulator, you would expect the gate drive voltage to be 12VDC + 18VDC = 30VDC, which it was. There is quite a bit of noise in this system as it stands. This can be seen as voltage spikes and noise coupling from scope probe to scope probe. Most of this noise would go away if the design were on a PCB and not on a solderless breadboard. The PWM signal can be seen on both the logic level BLI pin, and the low side driver output, BLO.

You can also see that, although the AHO output is enabled in the BASIC Stamp code via the AHIpin, the A high side driver is not enabled until the DISpin is taken low (0V), thus enabling individual control of the various output drivers.

Harris Semiconductor makes a part similar to the HIP4081A, the HIP4080A. The HIP4080A is designed specifically for H-bridge control. For that reason, it would require fewer I/O lines to interface to. But I felt that the HIP4081A provided for a multitude of high current applications other than H-bridge control. So, I felt it might have wider appeal to the readers of this column. The parts are so similar, though, that virtually all information on the HIP4081A that was provided in this article holds true for the HIP4080A. Figure 4 gives an idea of how some non-H-bridge applications might appear.

## In Closing

It's pretty difficult to come up with circuits that will have mass appeal, and fit them into a monthly article format. But I think this is a good one. There are quite a few parts out there in the electronics market that take a lot of anguish out of what would otherwise be a bear of a design. The Harris Semiconductor parts that I detailed here are great examples of the work many semiconductor manufacturers are doing these days.

Stop by and take a look at their web site. And, while you're at it, swing by the Maxim, Linear Technologies, Allegro, and Unitrode web sites. And, if you see anything that catches your eye, drop me an E-Mail. If it seems to work well with a BASIC Stamp, I might just write an article on it (and, of course, give you credit for pointing it out to me). **NV**

## PRINTED CIRCUIT BOARDS

**QUALITY PRODUCT**  
**FAST DELIVERY**  
**COMPETITIVE PRICING**

**PROTOTYPE THROUGH PRODUCTION**

**PULSAR, INC**

9901 W. Pacific Ave.  
Franklin Park, IL 60131  
Phone 847.233.0012  
Fax 847.233.0013  
Modem 847.233.0014  
yogii@flash.net - flash.net/~yogii

- \* UL approved
- \* Single & Double sided
- \* Multilayers to 8 layer
- \* SMOBC, LPI mask
- \* Reverse Engineering
- \* Through hole or SMT
- \* Nickel & Gold Plating
- \* Routing or scoring
- \* Electrical Testing
- \* Artwork or CAD data
- \* Fast quotes

**Your shrinking options are expanding!**

**MicroCore-11™**

**NEW!**

- tiny 2" x 2" 68HC11 module
  - RS232, 5V regulator, 8MHz crystal
  - 32K SRAM plus 8K or 32K EEPROM
  - plugs into your breadboard like a DIP
- 8K Starter Package #MC11SP8K.....\$75\*  
32K Starter Package #MC11SP32K...\$89\*


\* plus shipping & handling  
Visa\*MasterCard\*Discover\*Amex

**Technological Arts**

Phone: (416) 963-8996

Fax: (416) 963-9179

**www.technologicalarts.com**

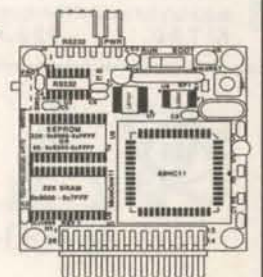



Download our latest catalog at <http://www.alltronics.com>

### WEATHERPROOF CCD COLOR BULLET CAMERA

Get crisp and clear picture quality with this sleek small bullet camera. Reliable operation in virtually any environment. 400 lines of resolution, 1 Lux minimum illumination, 8-12VDC, 120mA. 115VAC power supply included.  
2" Length x 1 1/4" Diameter.

99V004 \$229.95



### CCD COLOR ULTRA MINIATURE CAMERA

Ultra compact mini camera with 420 lines of resolution. 0.5 Lux minimum illumination, 9-12VDC, 100mA. Metal housing with mounting bracket and power cord. 115VAC power supply included.

99V005 \$219.95

### DONUT MAGNET

2 3/4" O.D., 1 1/4" I.D., 1/2" thick.

99N005 \$4.95

### "FLUKETYPE" METER PROBE KIT

Shrouded type banana plugs fit Fluke and other popular DMMs.

97Z017 \$4.95 set

### TV AUDIO DEMULATOR

Originally used in cable TV application, this subassembly takes channel 3, 4 or 5 signal and demodulates the audio. Comes with documentation and schematics, plus additional schematics to build add-on video demodulator board.

92A028 \$9.95 each

### PLANO-CONVEX LENS

21mm (5/8") dia. Focal length 25mm (approx. 1"). Glass.

97L018 \$1.50 each

### VU METER KIT

A simple, low cost stereo VU meter. Two LM3915 dot/bar display driver ICs are used to drive 2 rows of 10 LEDs (14 green, 6 red) in a moving bar display. This VU meter indicates "peak music power" when used with audio amplifiers. Ideal add-on for any of the amplifier kits.

KIT 89 \$23.45 each

### COMPUTER CASE & POWER SUPPLY

Mini tower case with 250W power supply, two 5.25" and two 3.5" external bays, plus one internal bay for hard drive. LEDs for power, turbo and HDD.

97C001 \$24.95 each

### MULTIMEDIA SPEAKERS

Amplified, with cables and power supply. Size: 10.25"H x 2.5"W x 6"D.

98V004 \$19.95 Pair

### THERMOCOUPLE WIRE

20 gauge shielded type T/S? wire. It has clear PVC outer insulation.

99W010 \$0.50/foot

### FUNCTIONALLY CHALLENGED SIGNALLING UNITS

These units don't work! What you get are three sets each consisting of one 9V, 49.9kHz crystal-controlled FM transmitter, and a matching dual conversion narrow-band FM crystal-controlled receiver/tone decoder/signal unit that runs on 6VDC. With documentation.

98Z011 3 for \$10.00

### 1999 ARRL REPEATER DIRECTORY

The authoritative source of VHF-UHF repeater listings. Y2K edition.

99X005 \$8.00

### MINIATURE C-BAND LNB

Low-noise block converter. Better than 40°K noise temperature. Spec sheet included.

94G001 \$29.95 each

### RIGHT ANGLE PRINTER CABLE

Six foot cable with DB-25M to 36-pin Centronics right-angle connector.

PC-6R \$4.95 each  
PC-6R10 10 / \$25.00  
PC-6R100 100 / \$200.00



### ECOHEAT™ HEAT GUN


An economical, lightweight, multi-use heat gun with two heat settings (500° and 1000°F). Has 3-position slide switch, built-in hand guard, 3-wire grounded cord, thermoplastic case. UL listed, 120VAC.

EC-100 \$32.95 each

### BLUE LED

T1-3/4 blue water clear.

SE5064N \$4.95 each

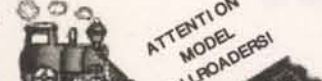

### HEXADECIMAL DISPLAY WITH LOGIC

TIL311. Red, high-brightness, 0.3" tall LED with 4x7 alphanumeric display and left and right decimals. Internal integrated TTL MSI chip with latch, decoder and drivers. Visible from a wide viewing angle. Good for direct bus connections.

93S033 \$9.95 each

### GENERAL INSTRUMENTS UNIVERSAL REMOTE CONTROL

Model XRC11D

98V011 \$9.95 each

### 1N4148 DIODE

92S024 1000 for \$9.95

### WALL WART ASSORTMENT

A random selection of wall power supplies with assorted voltages and current ratings.

94E004 10 for \$14.95

### 12/14.5 VAC POWER TRANSFORMER

110VAC input. 12VAC or 14.5VAC out @ 25A (tapped primary). Specs included.

98E005 \$29.99 each

### ATARI 1020 COLOR PRINTER

For all Atari 8-bit computers. (Not PC-compatible!) Package includes: printer, power supply, software, pens, paper and interface cable. These are new units in factory sealed boxes.

94C037 \$14.95 each

### PROTO BOARD

5 Distribution Strips - Tie Points 500  
3 Terminal Strips - Tie Points 1890  
4 Binding Posts  
Mounted on a Base Plate  
175mm W x 230mm L x 31mm H  
PB104 \$29.80

### 2 X 10W STEREO AMP KIT

The TDA2009 is a class AB dual Hi-Fi Audio power amplifier monolithic IC designed for quality stereo applications. This is the standard data book application circuit using a minimum of external components. Each channel is capable of delivering 10W into 4-ohm speakers. Recommended supply voltage 8-22V.

KIT88 \$19.95 each

### 20cc SYRINGE

Disposable syringe with luer taper tip.

99U006 \$0.95

### 30cc SYRINGE

Disposable syringe with catheter tip.

99U007 \$1.25

### DC LIGHTING / EMERGENCY LIGHTING

Concerned about Y2K? Frequent power outages? Want to conserve electricity? Want an unbreakable light source that will last a lifetime? Just need a nightlight? Use these 12VDC powered lamp assemblies. These small white LED arrays can be individually powered from 12VDC or paralleled to light a walkway, hallway, or surround large room. Parallel circuits can mix or match between the three:

### 6 LED LIGHT

This set of LEDs gives off a nice, bright, white light to shine on a gate, walkway, or to be used as a bright reading light.  
Power usage: 60 milliamps  
DIY-6 \$34.95 each

### 12 LED LIGHT

This set provides "very" bright light. Recommended for lighting up a small room, tool shed, paint locker, or front porch.  
Power usage: 120 milliamps  
DIY-12 \$64.49 each

### 18 LED LIGHT

This is a great room or deck light. It is a bright light that uses very little energy and lasts and lasts.  
Power usage: 180 milliamps  
DIY-18 \$94.95 each

### LED FLASHLIGHT

This flashlight is the newest in portable lighting technology. Three "AA" batteries will give 60 hours of light when you use the PL-W1 with one LED. There's no bulb to replace. This is a great light for cavers, backpackers, boaters and anyone who doesn't want to carry a lot of batteries and wants a dependable light. Put one into your Y2K "survival kit."

PL-W1 (1 LED) \$14.95  
PL-W2 (2 LEDs) \$19.95  
PL-W3 (3 LEDs) \$24.95

### HIGH VOLTAGE ELECTROLYTIC

470µF, 250V1-3.16" dia. by 2" high, PC mount.

92P043 4 for \$10.00

### "SEXY FETS"

IRFM250 "N" channel hexfet, rated 200 Volts, 0.100 Ohm, 27.4 Amps. These are mil-spec parts in TO-254AA packages. Ref: MIL-S-19500/592. Full documentation included.

95I003 \$14.95 each

### 2000 GAUSS SUPER MAGNET

Black rectangular magnet, 2.5" long x 1.125" wide by 0.375" deep. These will definitely hold your calendar up!

98N013 \$5.95 each

### MINI HORN TWEETER

2" diam. 4 ohm tweeter is ideal for car stereo applications. 7" wire lead. Two mounting holes are 2 3/8" on center.

99V003 \$1.95 each

### PULSE MOTOR

42mm dia., 22mm thick. Shaft: 3mm dia. x 12mm long, with 13-tooth gear approx 16.6mm dia x 5mm thick. 7.5"/step, 48s/rev., 12VDC, 50 Ohms, 6-wire. With spec sheet.

92M010 \$3.95 each

### UNI POLAR STEPPER MOTOR DRIVER IC

UCN5804. Drives a unipolar stepper in one of three operating modes: single phase, two phase or half step. Up to 1.25 Amps per phase. Step and direction input. Drive with a 555 timer, parallel port, etc. Build your own robot, anything that requires precision positioning.

93I002 \$4.50 each

### COMBO PACK!

One 93I002 IC and 92M010 motor (both shown above) with schematics.

93I003 \$7.95/ set



# ALLTRONICS

2300-D Zanker Road - San Jose, CA 95131-1114

World Wide Web: <http://www.alltronics.com>

(408) 943-9773 - Fax (408) 943-9776

Store Hours: 9-6 M-F & 10-3 Sat. - Pacific  
Visa, M/C, AmEx Accepted. All Sales Final.  
California Residents Add Sales Tax.  
Shipping Additional on All Orders  
Prices Subject to Change Without Notice.  
Prices Good 60 Days from Date of Publication



Visit our website and  
download our catalog.



# Events

## AUGUST 1999

### AUGUST 1

**IN - ANGOLA** - Hamfest. Land of Lakes ARC, Bill Brown WD9DSN, 219-475-5897.  
E-Mail: sharon.l.brown@gte.net

**OH - RANDOLPH** - Hamfest. Portage County Fairgrounds. 8am-4pm. VE Exams. Talk-in: 145.39 600 MHz. Portage ARC, Joanne Solak KJ3O, 330-274-8240. E-Mail: ljsolak@apc.net  
Web: http://parc.portage.oh.us

**VA - BERRYVILLE** - Winchester Hamfest. Clarke County Ruritan Fairgrounds. 6am. VE Exams. Talk-in: 146.82 (-) W4RKC repeater. Shenandoah Valley ARC, Guy Avey W3INT, 540-678-9970; Jane Barb KD4IET, 540-955-1745.  
E-Mail: ibarb@visuallink.com Web: http://www.vvalley.com/svarc/hamfest or http://www.visuallink.net/shenvalleyarc

### AUGUST 6-7

**TX - AUSTIN** - Texas State ARRL Convention. Austin ARC, Austin Repeater Org & Texas VHF-FM Society, Joe Makeever W5HS, 512-345-0800.  
E-Mail: jomak@ibm.net  
Web: http://www.repeater.org/summerfest/

### AUGUST 6-7-8

**SD - WATERTOWN** - Dakota Division Convention. Lake Area Radio Klub, Jerry Hegg NOJH, 605-886-7151. E-Mail: n0jh@dailypost.com

### AUGUST 7

**CA - CHICO** - Hamfest. Golden Empire ARS, Muriel Pope K6GSK, 530-342-4765.  
E-Mail: k6gsk@w6rhc.org

**CA - SANTEE** - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

**IL - CARLINVILLE** - Hamfest. Macoupin County Fairgrounds, Rt. 4, I-55 exit 60. 7am-12pm. Talk-in: 146.82- or 443.400+ 103.5PL Macoupin County ARC, Tim Jones 217-627-2355. KA9VIV E-Mail: jester25@ctnet.net. Jim Pitchford N9LQF, E-Mail: esda@ctnet.net

**IL - QUINCY** - Hamfest. Western Illinois ARC, Jim Funk N9JF, 217-336-4191. E-Mail: jfunk@adams.net Web: http://www.qsl.net/s9awe

**ME - ST. ALBANS** - Hamfest. Snow Mobile Club. Howard WA1SBI, 207-876-3702

**MI - TAWAS** - Hamfest. Isosco County AR Enthusiasts, John Hanley KA8AIP, 517-756-2845.  
E-Mail: ka8aip@centuryinter.net

**MO - CRANE** - Hamfest. City Park. 8am-3pm. Talk-in: 145.330-. VE testing. Lonnie Allen, 417-723-5671. E-Mail: n0tdw@gte.net

**MO - SPRINGFIELD** - Hamfest. Southwest Missouri ARC, Karen Thorpe N0TDW, 417-889-6775. E-Mail: n0tdw@juno.com

**NY - PLATTSBURGH** - Hamfest. Champlain Valley ARC, Bernard Jakobetz KC2ALG, 518-643-9657

**NY - WEEDSPORT** - Hamfest. Auburn ARA, Joe Kahler WA2NGX, 315-364-5135.  
E-Mail: htx@usa.net

**OH - COLUMBUS** - Hamfest. Aladdin Shrine Facility. 8am-3:30pm. VE Exams. Talk-in: 147.24 receive/147.84 transmit. Voice of Aladdin ARC, Jim Morton KB8KJP, 614-846-7790

**PA - LEWISTOWN** - Hamfest. Decatur Township Fire Co. Grounds, US 522. Talk-in: 146.91. JVARC, Richard Yingling 717-242-1882

**PA - MATAMORAS** - Hamfest. Tri-State ARA, Dave W2DRH, 914-856-2529; Ray WY2D, 914-856-1733; Rich K3BBC, 570-559-7401

### AUGUST 7-8

**WA - SPOKANE** - ARRL Eastern WA Section Convention. University High School, 10212 E. 9th Ave. Sat: 9am-5pm, Sun: 8am-12pm. VE Exams. Neil Gallup N7LVO, 509-928-7442. E-Mail: n7lvo@cet.com Betsy Ashleman N7WRQ, 509-448-5821. E-Mail: n7wrq@aol.com  
Web: http://www.leva.com/~n7utg

### AUGUST 8

**IA - AMANA** - Hamfest. Cedar Valley ARC, Wayne Kolosik K10FE, 319-393-4224.  
E-Mail: k10fe@usa.net

**IL - PEOTONE** - Hamfesters Hamfest. Will County Fairgrounds. Tom Davis KB9NUQ, 708-210-9548; David Brasel NF9N, 708-448-0580.  
E-Mail: nf9n@aol.com or tdavis@internetplus.net

**OH - LISBON** - Hamfest. Triangle ARC, Mike Mays KB8JNM, 330-386-6021. E-Mail: mike.mays@usa.net Web: http://www.qsl.net/tarc

**OH - MARTINS FERRY** - Hamfest. Triple States RAC, Ralph McDonough K8AN, 740-546-3930.  
E-Mail: k8an@aol.com

**OH - MARTINS FERRY** - Hamfest. Triple States RAC, Ralph McDonough K8AN, 740-546-3930.  
E-Mail: k8an@aol.com  
Web: http://www.qsl.net/tsrac

### AUGUST 14

# CALENDAR

The Events Calendar is a free service for publicizing electronic events such as amateur radio hamfests, flea markets, etc. If your organization is sponsoring an event and would like a free listing, contact us at least 60 days in advance. Include your flyer, estimated attendance, name of the person to contact, and phone number.

Complimentary issues are available upon request for distribution to your attendees. A street address for UPS is required.

While we strive for accuracy in our calendar, we can not be responsible for errors or cancellations. The information contained in this column is for the use of the readers of *Nuts & Volts* and may not be republished in any form without the written permission of T & L Publications, Inc.

All listing information should be sent to:

**Nuts & Volts Magazine**

**Events Calendar**

430 Princeland Court

Corona, CA 91719

Phone 909-371-8497

Fax 909-371-3052

E-mail events@nutsvolts.com

## COMPUTER SHOWS

**AGI Shows**, 317-299-8827.

E-Mail: info@agishows.com

http://www.agishows.com

**Blue Star Productions**

612-788-1901

http://www.supercomputersale.com

**Computers And You**, 734-283-1754.

www.a1-supercomputersales.com

**Computer Central Shows**

847-412-1900 & 1-888-296-6066.

E-Mail: compcent@megsnet.net

www.computercentralshows.com

**Five Star Productions**

810-890-0988 E-Mail: jeff@fivestar

www.fivestarshows.com

**Georgia Mountain Productions**

706-838-4827.

E-Mail: gamtnpro@blrg.tds.net

georgiamountain.com

**Gibraltar Trade Center, Inc.**

734-287-2000. Taylor, MI.

**Gibraltar Trade Center, Inc.**

810-465-6440. Mt. Clemens, MI.

**KGP Productions**

1-800-631-0062, 732-297-2526.

E-Mail: kgp@mail.com

**MarketPro, Inc.**, 201-825-2229

http://www.marketpro.com

**MarketPro, Inc.**, 301-984-0880.

E-Mail: md@marketpro.com

http://marketpro.com

**Narisaam Computer Show**

770-663-0983.

E-Mail: narisaam@aol.com

Web: http://www.showsale.com

**Northern Computer Shows**

978-744-8440

E-Mail: inquiries@ncshows.com

Web: ncshows.com

**Peter Trapp Computer Shows**, 603-

272-5008. Web: www.petertrapp.com

& Electronic Swapmeet. Santee Drive-in. 619-561-0052

**CANADA - MANITOBA - AUSTIN** - MARM Hamfest. Dave Snyder VE4XN, 204-728-2463.

E-Mail: dsnyder@mb.sympatico.ca Web: http://

WWW.MBNET.MB.CA/~donahue/austin.html

**GA - ELLIJAY** - Hamfest. Legion Rd., Telephone

Co. Pavilion off old Hwy 5. 8am-12:30pm. Talk-in:

146.95. Ellijay ARS, Dot Beam K4PPS, 706-276-

6660

**IN - WARSAW** - Hamfest. Kosciusko County

Fairgrounds. 8am-2pm. VE Exams. Hoosier Lakes

Radio Club, Loren Melton WB9OST, 219-858-9374

eves. E-Mail: WB9OST@WAVEONE.NET

**NJ - OAKLAND** - Flea Market. American Legion

Hall, 65 Oak St. 8am-Noon. Talk-in: 147.49 in/

146.49 out & 441.175 in/446.175 out & 146.52

simplex. Ramapo Mountain ARC, Tony Cassera

N2KDZ, 973-839-3564.

E-Mail: acassera@intac.com

**NY - ITHACA** - Hamfest. Tompkins County

Airport. Talk-in: 146.97 (-600). Tompkins County

ARC, David Flinn W2CFP, 607-533-4797.

E-Mail: dave@starflinn.com

**TX - GREENVILLE** - Hamfest. Sabine Valley ARA,

Michael Ihry N5KB, 903-883-3789. E-Mail:

mihry@argontech.net Web:

http://www.thehallco.com/SVARA

**VA - VINTON** - Hamfest. William Byrd High

School, Washington Ave. 9am-3pm. VE Exams.

Roanoke Valley ARC, Mike Marsh KF4MJB, 540-

389-3056. E-Mail: mikedf4mjb@aol.com Web:

http://ourworld.compuserve.com/homepages/fcu

pp/rvarc.htm

**WA - LONGVIEW** - Hamfest. Cowlitz County

Expo Center, Fairgrounds. 9am-1pm. Talk-in:

147.26+ K7ZVV repeater. Lower Columbia ARA,

Bob Morehouse KB7ADO, 360-425-6076 (after

6pm wkdays). E-Mail: kb7ado@aol.com

Web: http://www.qsl.net/nc7p/

### AUGUST 21-22

**AL - HUNTSVILLE** - Convention. Von Braun

Center. Sat: 9am-4:30pm, Sun: 9am-2:30pm.

Southeastern Division, Scotty Neustadter W4WW,

**CA - FONTANA** - Inland Empire ARC Amateur

Radio & Electronics Swapmeet. A B Miller High

School. Bill 909-822-4138 eves

**ME - ST ALBANS** - Hamfest. Piscataquis ARC,

George Dean WA1JMM, 207-965-8864.

E-Mail: wa1jmm@midmaine.com

Web: http://www.qsl.net/parc/

**NY - WESTMORELAND** - Hamfest. Rome RC,

Jack Roux KB2TXR, 315-336-1391

**OH - NELSONVILLE** - Hamfest. Sunday Creek

AR Federation, Russell Ellis N8MWK, 740-767-

2226. E-Mail: scarf@hocking.edu

**VT - CHARLOTTE** - Hamfest. Burlington ARC,

Ralph Stetson KD1R, 802-878-6454. Web:

http://homepages.together.net/~kd1r/fest99.htm

**WV - HUNTINGTON** - Hamfest. Tri-State ARA,

Dwight Smith WB8JPJ, 304-522-7865 eves; 304-

523-6675 days. E-Mail: wb8jpj@arri.net

E-Mail: tara.amateur.radio@juno.com

### AUGUST 15

**CA - GOLETA** - Hamfest. Santa Barbara ARC,

Chuck Steris N6CJL, 805-563-6062.

E-Mail: chuckstr@west.net

**CO - GOLDEN** - ARRL Colorado State

Convention. Jefferson County Fairgrounds, 15200

W. 6th Ave. (Indiana Exit). 8:30am-2pm. Denver

Radio Club, Bob Lindell N0YIX, 303-422-0610.

E-Mail: KB0QAB@arri.net

Web: http://users.ntr.net/~chastain/hamradio

**IN - LAFAYETTE** - Hamfest. Tippecanoe County

Fairgrounds. Talk-in: W9REG 147.135/443.775.

E-Mail: ddull@compuserve.com

**KY - LEXINGTON** - Hamfest. National Guard

Armory. 8am-4pm. VE Exams. Talk-in: 146.760.

John Barnes KS4GL, 606-253-1178.

E-Mail: KS4GL@juno.com

Web: http://www.qsl.net/k4kjq/

**MA - ADAMS** - Hamfest. Northern Berkshire ARC,

Joel Miller N1WCF, 413-442-2609. E-Mail:

n1wcf@nobarc.org

**MA - CAMBRIDGE** - Flea at MIT. Albany and

Main Sts. 9am-2pm. Talk-in: 146.52 &

449.725/444.725 W1XM/R PL 114.8 (2A). Nick

Altenbernd KA1MQX, 617-253-3776 (9-5). Web:

http://web.mit.edu/w1xm/www/swapfest.html

**MI - JACKSON** - Hamfest. Jackson Community

College. VE Exams. Talk-in: 146.88 W8JXN.

Cascades ARS, Dennis Byrne KC8JLZ, 517-522-

4058. E-Mail: byrmeda@voyager.net

Web: http://www.qsl.net/cars-jxn/

**NJ - BAYVILLE** - Hamfest. Jersey Shore ARS,

Bob Murdock WX2NJ, 732-269-6379.

E-Mail: JARSFEST@aol.com Web:

http://members.aol.com/jarsfest/jarsfest.html

**NY - DEPEW** - Hamfest. Hearstone Manor, 333

Dick Rd. Lancaster ARC, Luke Caliano N2GDU,

716-634-4667. E-Mail: lcaliano@freewweb.com

Web: http://hamgate.sunyerie.edu/~larc/Gre

aterBuffaloHamfest.ht

**OH - WARREN** - Hamfest. Trumbull County JVS

School, Educational Hwy. Warren ARA, Frank

Fitzhugh KD8KJ, 330-652-0452. E-Mail:

kd8kj@onecom.com Ray Solinger N8HRZ, 330-

652-5028. E-Mail: n8hrz@onecom.com

**PA - YORK** - Swapfest and Auction. York VO Tech

School, Pauline Dr. (1 blk S of I-83 Exit 6, Rt

74S). Talk-in: 146.865. Swap Fest, John Salony

(Ph) 717-741-1780; Greg Towson (fax) 717-741-

0874. Gene Warner E-Mail: ad3e@arri.net

**WA - NORTH SEATTLE** - Antique Radio Swap

Meet. Shoreline Museum Parking Lot, N. 175th &

Linden Ave. 9am-1pm. Puget Sound Antique

Radio Assn., 425-747-1323 or 206-546-5495. Web:

http://www.eskimo.com/~hhagen/psara.html

### AUGUST 21

**CA - SANTEE** - ARC of El Cajon Ham, Computer

256-880-8004. E-Mail: scotty@hiwaay.net.

**NM - ALBUQUERQUE** - Duke City Hamfest.

Marcus Lieberman KM5EH, 505-836-1724. Fax:

505-352-6154. E-Mail: buckml@lobo.net

Web: http://www.qsl.net/dchf



# Events CALENDAR

**IN - LA PORTE** - Hamfest. County Fairgrounds. 7am-1pm. Talk-in: 146.610 (131.8PL), 146.520 simplex. La Porte ARC, Neil Straub W29N, 219-234-7525. E-Mail: nstraub@netnetco.net  
Web: www.geocities.com/siliconvalley/byte/1653  
**KS - CHANUTE** - Hamfest. Central Park Pavilion. 9am-1pm. Talk-in: 146.745. Chanute Area ARC, Charlie Ward WD0AKU, 316-431-6402  
**MA - GARDNER** - Hamfest. Mohawk ARC, John Doud AE1B, 978-249-5905. E-Mail: ae1b@gis.net  
**TX - GAINESVILLE** - Hamfest. Civic Center. 7am-5pm. Bob Ray, 940-665-2544. E-Mail: bray@mortexinfo.net  
**WV - WESTON** - Convention. Jackson's Mill Conference Center. 8am-11pm. West Virginia State AR Council, Dick Fowler N8FMD, 304-623-9479. E-Mail: n8fmd@neumedia.net  
Web: http://qsl.net/wvsarc

## AUGUST 28-29

**CO - WOODLAND PARK** - Hamfest. Mountain ARC, Wes K0HPZ, 719-687-8758. E-Mail: w1w@prodigy.net  
**FL - SARASOTA** - Computer Show. Municipal Auditorium. Frank Cox 941-954-0202

## AUGUST 29

**IL - WOODSTOCK** - Hamfest. Tri-County Radio Group, Bob Grosse N9KXG, 708-944-0500. E-Mail: N9KXG@quality-enterprises.com  
Web: http://quality-enterprises.com/torg/  
**PA - NEW KENSINGTON** - Swap/Flea Market. Skyview Radio Society Club House. Bob 724-727-2194  
**TN - LEBANON** - Hamfest. Short Mountain Repeater Club, Patsy Pierce K3PAT, 615-395-4488.

## SEPTEMBER 1999

### SEPTEMBER 4

**CA - SANTEE** - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052  
**CANADA - ONTARIO - CARP** - Hamfest. Ottawa ARC, Jim Cummings VE3XJ, 613-446-1225. E-Mail: fleamarket@oarc.net  
Web: http://oarc.net/fleamarket  
**NM - ALAMOGORDO** - Hamfest. Otero County Fairgrounds, US 54 & Fairgrounds Rd. VEC testing. Alamogordo ARC, Larry Moore WA5UNO, 505-437-0145  
**PA - UNIONTOWN** - Hamfest. Uniontown ARC, Carl Chuprinko WA3HQK, 304-594-3779

### SEPTEMBER 4-5

**NC - SHELBY** - Hamfest. Shelby ARC. John Ledford N4GOQ, 704-482-4507. E-Mail: n4goq@shelby.net  
Web: http://www.shelby.net/n4fan

### SEPTEMBER 10-11

**AR - MENA** - Hamfest. Queen Wilhelmina Hamfest Assn., Charlotte Lee KC5DOR, E-Mail: blee@ipa.net. Ray Lively W5DLC, 903-764-5599. E-Mail: raysoft@intrastar.net

### SEPTEMBER 11

**AR - MOUNTAIN HOME** - Hamfest. Twin Lakes ARC, Miles Waldron N5QMI, 870-492-4466. E-Mail: mpwaldron@centuryinter.net  
**CA - FONTANA** - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves  
**DE - DOVER** - Hamfest. Kent County ARC, Larry Roll K3LT, 302-678-4841. E-Mail: yodoc@aol.com or k3lt@magpage.com  
**IN - SPENCER** - Hamfest. Owen County ARA, Kathryn Smith K9INQ, 812-829-2140  
**ME - WINDSOR** - Hamfest. Fairgrounds. AARA, Frank N1ITR, 207-623-9217  
**MN - RUSH CITY** - Hamfest. East Central MN ARC, Larry Jilek KA0MEN, 320-358-4205  
**MO - COLUMBIA** - Hamfest. Good Time Country, 5551 S. Hwy. 63. 8am-2pm. VE Exams. Central Missouri Radio Assn., Bruce Odle, 3315 Berrywood Dr., Ste. 101, Columbia, MO 65201  
**NY - BALLSTON SPA** - Hamfest. County Fairgrounds. 7am-3pm. VEC Exams. Talk-in: WA2UMX 146.40/147.00 & 147.84/147.24. Saratoga County RACES Assn., Darlene Lake N2XQG, 518-587-2385 E-Mail: lake@capital.net  
**PA - ERIE** - Hamfest. Franklin Twp. Firehall. VE Exams, 9am, Franklin Center Methodist Church, Rt. 98. Talk-in: 146.01/61. Radio Assn. of Erie, Dr. Tom McClain N3HPR, 814-833-1640. E-Mail: TEM@ERIE.NET  
Web: http://www.erie.net/~n3ntj/hamfest.htm  
**WA - GRAHAM** - Tacoma Electronics Fleamarket. (Pierce County Fairgrounds), Frontier Park, 21718 Meridian Ave. E. 9am-3pm. Talk-in: 147.38+ PL 103.5, simplex 146.58. RCT, Roger 253-475-4293. E-Mail: rtwig@worldnet.att.net Web: www.mashell.com/~roblee/rct.htm

### SEPTEMBER 11-12

**FL - MELBOURNE** - Hamfest. Auditorium. Platinum Coast ARC, Tim Madden K14TG. E-Mail: k14tg@msn.com  
**KY - LOUISVILLE** - ARRL KY State Convention. Bullitt County Fairgrounds, I-65 (South 25 min.). Greater Louisville Hamfest Assn., Herbert Rowe W4WQD, 812-282-7007 or 812-948-0037 (commercial), 502-935-7197 or 606-284-9090 (FleaMkt/TailGate) E-Mail: wd4ixl@juno.com Web: http://www.thepoint.net/~glha/

### SEPTEMBER 12

**DE - FELTON** - Hamfest. Kent County ARC, Larry Roll K3LT, 302-678-4841. E-Mail: W3HZW@hotmail.com  
**IL - JOLIET** - Hamfest. Bolingbrook ARS, Marti Barton KA9ZJJ, 815-436-0559. E-Mail: mkbarton@flash.net  
**MA - SOUTH DARTMOUTH** - Hamfest. At club. SE MA ARA, Bill K1IBR, 508-996-2969  
**OH - FINDLAY** - Hamfest. Hancock County Fairgrounds. Talk-in: 147.15+, 444.15. Findlay RC, Bill Kelsey N8ET, 419-423-4604. E-Mail: kanga@bright.net  
Web: http://www.bright.net/~kanga/w8ft/  
**PA - BUTLER** - Hamfest. Butler County ARA, Gerald Wetzel W3DMB, 724-282-6777 E-Mail: w3dmb@aol.com  
Web: http://www.nauticom.net/www/cliff/bcara

### SEPTEMBER 17

**NJ - PISCATAWAY** - Ham & Electronics Auction. North Stelton Firehouse, Haines Ave. E of Stelton Rd. 6pm. Piscataway ARC, Marty 732-396-1836 (before 9pm)

### SEPTEMBER 18

**AR - LITTLE ROCK** - Hamfest. CAREN, Scott Derden K5SCD, 501-834-1881 E-Mail: sderden@flash.net  
Web: http://carenclub.webjump.com  
**CA - SANTEE** - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052  
**IL - ROLLING MEADOWS** - W9DXCC Convention. Northern Illinois DX Assn., Bill Smith W9VA, 847-945-1564 E-Mail: w9va@aol.com  
Web: http://www.qth.com/w9dxcc  
**KY - CAYE CITY** - Hamfest. Convention Center. VE Exams. The Southern KY DX Assn., Larry Brumett KN4IV, 502-651-2363. E-Mail: lbrumett@glasgow-ky.com Web: http://www.geocities.com/CapitolHill/5421  
**MA - MARSHFIELD** - Hamfest. Fairgrounds, Rt. 3A. Genesis ARS, Lou N1WNT, 781-837-6651. E-Mail: n1wnt@mediaone.net  
Web: http://home.ici.net/~marsfair/marsfair.html  
**ME - LINCOLN** - Hamfest. Burr School. VE testing. Bagley ARC, Sylvia N1JNR, 207-732-5185.  
**MI - GRAND RAPIDS** - Hamfest. Grand Rapids ARA, Ed Novakowski N8UXN, 616-458-9029. E-Mail: barbv@voyager.net  
Web: http://www.w8dc.org  
**MI - MT. CLEMENS** - Hamfest. L'Anse Creuse ARC, John Slobodnik N8NXW, 810-791-4484 or 810-757-8192 Ext. 151. E-Mail: irish12@juno.com Betty McGinn N8SIH, 810-791-4484. E-Mail: boops@juno.com  
Web: http://www.flash.net/~lcarc/  
**NY - HAMBURG** - Western NY ARRL Section Convention. Harold Smith K2HC, 716-424-7184 E-Mail: info@buffalohamfest.org  
Web: http://www.buffalohamfest.org  
**NY - MARGARETVILLE** - Hamfest. Margaretville ARC, Harold Murken NQ2Y, 914-586-3893. E-Mail: bourke@catskill.net  
**PA - SCHNECKSVILLE** - Hamfest. Fire Dept. on PA Rt. 309. Talk-in: 146.70 (PL 151.4)/R, 444.90 (PL 151.4)/R. DLARC, William Goodman K3ANS, 610-258-5063. E-Mail: aa3ix@arrl.net Web: http://www.kutztown.edu/faculty/chuk/dlarc/  
**RI - FORESTDALE** - Flea Market and Auction. VFW, Rt. 146. Rhode Island Amateur FM Repeater Service, Rick Fairweather K1KYI, 401-725-7507. E-Mail: k1kyi@juno.com  
**TX - WEBSTER** - Hamfest. Clear Lake ARC, Bob Biekert KA5GLX, 281-488-2913 E-Mail: ka5glx@clear.org Web: http://www.clarc.org  
**SEPTEMBER 18-19**  
**IL - PEORIA** - Hamfest. Peoria Area ARC, Jim Williams N9HHU, 309-692-3378. Fax: 309-698-8643. E-Mail: jimeoc@worldnet.att.net or jimn9hhu@juno.com Web: http://www.w9uvi.org  
**TX - EL PASO** - International Hamfiesta. Craig Lyles KC7UXM, 915-821-7501  
**VA - VIRGINIA BEACH** - Hamfest and VA State ARRL Convention. Pavilion. Sat: 9am-5pm, Sun:

9am-4pm. Talk-in: 146.970. Manny Steiner K4DOR, 757-HAM-FEST. E-Mail: HAMFEST@EXIS.NET or Lewis B. Steingold W4BLO, 757-486-3800  
Web: WWW.VAHAMFEST.COM

### SEPTEMBER 19

**CT - NEWTOWN** - Hamfest. Edmond Town Hall, Rt. 6. 9am-2pm. Talk-in: 146.67. Candlewood ARA, Jeff Cantor WB3DLG, 203-798-6860. E-Mail: wb3dlg@earthlink.net  
Web: http://www.danbury.lib.ct.us/org/cara/  
**MA - CAMBRIDGE** - Flea at MIT. Albany and Main Sts. 9am-2pm. Talk-in: 146.52 & 449.725/444.725 W1XM/R PL 114.8 (2A). Nick Altenbernd KA1MQX, 617-253-3776 (9-5). Web: http://web.mit.edu/w1xm/www/swapfest.html  
**MI - ADRIAN** - Hamfest. Lenawee County Fairgrounds. VE Exams. Adrian ARC, Brian Sarkisian KG8CO, 517-265-1537. E-Mail: kg8co@ini.net Web: http://www.ini.net/~w8tqe  
**NJ - TRENTON** - Hamfest. Tall Cedars of Lebanon picnic grove, Sawmill Rd. Talk-in: 146.67-. Delaware Valley Radio Assn., Darryl Foyuth N2JVP, 609-882-2240. E-Mail: n2jvp@amsat.org  
Web: www.slac.com/w2zq  
**NY - BETHPAGE** - Long Island Hamfair. Briarcliffe College, 1055 Stewart Ave. 8:30am-2pm. VE Exams. Talk-in: W2VL 146.85 repeater (136.5PL). Long Island Mobile ARC, Rich N2WJL, 516-520-9311. E-Mail: hamfest@limarc.org  
Web: http://www.limarc.org  
**OH - CINCINNATI** - Hamfest. Kolping Center. 8am-4pm. Greater Cincinnati ARA, Jim Weaver K8JE, 513-825-2868. E-Mail: JimWeaver@aol.com Tom Denham K8VOE, 513-779-3951. E-Mail: tdenham@eos.net  
**PA - YORK** - Hamfest. York County Area Vocational Technical School, Queen St. (Exit 6E off I-83). 8am-3pm. York Hamfest, 717-764-8193 (ph/fax). E-Mail: W3SST@juno.com  
Web: http://www.yorkhamfest.org

### SEPTEMBER 24-25

**MI - FLINT** - State Convention. University of MI-Flint Riverfront Campus. Tuscola County ARA & Bay Area ARA, Val Rose N8EXV, 810-607-7732. E-Mail: n8exv@yahoo.com

### SEPTEMBER 24-25-26

**NH - LANCASTER** - Super Moose Festival. Lancaster Fairgrounds, Rt. 3. The United Way of Northern NH, 603-752-3343. E-Mail: unitdway@ncia.net

### SEPTEMBER 25

**AL - MOBILE** - Hamfest. Mobile ARC, Tommy Thompson KC4OLV, 334-653-9239 or 334-431-2019. E-Mail: kc4olv@zebra.net  
Web: http://www.angelfire.com/al/marc3/  
**FL - DAYTONA BEACH** - Hamfest. Embury Riddle Aeronautical University Campus, Clyde Morris Blvd. 9am-5pm. ARRL Exams. Talk-in: 147.150 +600. DBARA, E-Mail: munseyj@mindspring.com  
Web: http://www.america.com/~dbara/ or http://www.db.erau.edu/campus/student/club/erara  
**NJ - MT. HOLLY** - Hamfest. South Jersey Radio Assn. Joseph Cramer N2XYZ, 609-268-2135.

Continued on page 61

Converters ★ Remotes ★ Converters ★ Remotes ★ Converters ★ Remotes

Modern Communications • (405) 691-0594 TEL & FAX

Converters

Converters:	10	50	100
Panasonic: TZPC-175	\$49.00	\$45.00	\$39.00
Panasonic: TZPC-145	\$45.00	\$39.00	\$35.00
Centurion CF-3000 (NEW)			
True 99 Channel	\$65.00	\$60.00	\$55.00
Regal: CR-83	\$39.00	\$35.00	\$32.00
Remotes:			
Jerrold: 400, 450, 550	\$4.50	\$4.00	\$3.75
CFT: 2XXX	\$4.95	\$4.50	\$4.25
S/A: 175, 475	\$4.95	\$4.50	\$4.25
S/A: 8600 Display	\$4.95	\$4.50	\$4.25
Panasonic: 170, 175	\$4.95	\$4.50	\$4.25
Zenith (ALL)	\$4.95	\$4.50	\$4.25
Pioneer (ALL)	\$4.95	\$4.50	\$4.25
Tocom 5503-VIP	\$4.95	\$4.50	\$4.25
4-in-1 Universal	\$5.95	\$5.50	\$5.25



Parts, Parts, Parts

	10+	50+	100+
PIC16C622	\$3.15	\$2.95	\$2.75
PIC16C54RC/P	\$2.15	\$1.95	\$1.75
PIC16C56RC/P	\$2.15	\$1.95	\$1.75
Micro 68H705C8P	\$6.50	\$6.15	\$5.95
4 MHz (Resonator 2 pins)	\$0.45	\$0.40	\$0.35
4 MHz (3 pins)	\$0.45	\$0.40	\$0.35
Crystal: 117, 119	\$3.75	\$3.50	\$3.25
18 pin IC Socket	\$0.15	\$0.12	\$0.10
Toggle Switch on/on	\$0.95	\$0.85	\$0.75

Call for Larger Quantity Quotes

Remotes

Converters ★ Remotes ★ Converters ★ Remotes ★ Converters ★ Remotes



**Affordable? NOW Cheaper than Ever!** Netcom #1 in Customer Service Since 1983

**"REFEREE"**  
**CROSS REFERENCE & SPEC**  
**Transistors, ICs & Diodes**  
 A Specialist in "Hard to Cross House Numbers"  
 Easy, Powerful & Fast.  
 The Most Comprehensive Software Sold.


A selection yields Device Specifications & 75 to 250 Potential Replacements!  
 Replacement Numbers are Totally Global including Domestic, Asian, European, House  
 Branded, as well as ECG, NTE, SK & GE. Displays Case Drawings, Lead  
 Configuration & Pin-outs for many Devices. Coverage of Replacement Numbers  
 is Very Impressive. 7 Disk Set (17 Meg decompressed) For DOS, Win3.1 & 95  
 Latest Version 7.11 Includes Many Helpful Conversion Utilities, Tables & Formulas.

Includes: 4 HUGE Consumer Electronics Industry Directories  
 1- Consumer Electronics Parts Sources (Service) 2- Consumer Electronics Manufacturers  
 3- The Entire Computer Industry 4- Semiconductor Manufacturers
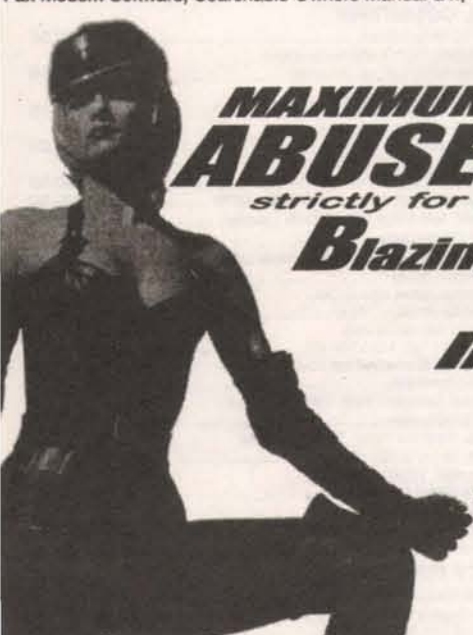
#1 Choice of Service Centers

**Racy & Web Ready**  
**IBM THINKPAD 486 DX4-100**

Huge 10.5" Active Matrix Color Display (the Best)  
 (Much Sharper & Brighter than a standard display, a \$300 value) Wow!  
 810Meg Hard Drive Standard -or- (optional 1 Gig Drive \$297 - 2Gig \$597)  
 16M Ram Standard -or- (optional 24M Ram \$247)  
 33k FAX MODEM - 2 PCMCIA Expansion Slots  
 Dual Infrared Ports (Front & Rear)  
 Track Point Mouse All Standard Ports (1S, 1P, 1VGA, 1Kbd)  
 Pop out - Hard Drive, Ram, & Battery  
 Ram & Hard Drive Expandable & Upgradable.  
 Includes Power Supply & Hydride Battery (a \$150 value)  
 Free Lifetime Tech Support  
 Web Site Creator Software  
 Internet Ready, America On Line 4.X Latest Version  
 Fax Modem Software, Searchable Owners Manual s/w, W95



**MAXIMUM ABUSE**

strictly for professionals

**Blazing Sunlight or Rain Storm**

On the **DESERT** or **SNOW**

**Instant ON - ZERO boot up time**

**Drop 3' to Concrete**

Actual Selling  
 Price From IBM  
**\$6992**

Rain: (4"/hr Rain w/ 40 MPH Winds)  
 Silicone Rubberized & Diecast Case!  
 Ultra Shock Mounted 1GIG EIDE Hard Drive!  
 ESD/EMF & RF Resistant, Works from -4 to 120 Deg F  
 & Vacuum to 15,000 ft

- > 1- PCMCIA (type 1, 2 or 3), Serial & Parallel Ports in rear
- > 16m Ram / 1m Video / 32 Bit Local Bus 486-50 Mhz & Math Co-processor, 28.8k Modem (Internet Ready)
- > Long Lasting Hydride Battery (\$150 Value)
- > Sound & Microphone, External Mini 3.5 Floppy
- > 8.25" Display-64 Shade Monochrome REFLECTIVE
- > (Optional) Touch Screen with

Handwriting Recognition

Rough Service Handle with Loops for optional Shoulder Strap  
 Roxanne's Voice Annotates all Windows 3.X Functions  
 (a real kick)

**OPTIONS**

- > W95 \$89
- > 12V Car cord \$29
- > Touch Screen \$200
- > 33k Baud PCMCIA Fax- Modem Upgrade \$35 / 56k \$89

This was a unique (one shot) purchasing opportunity  
**IT'S NOT OPEN STOCK**

**WHEN THEY'RE GONE, THEY'RE GONE FOR GOOD**  
 Sold till recently by IBM through their Local Area Network  
 Division at \$4,699 & \$6,912 as shown here. (they were never discounted)

**IBM ROAD WARRIOR**

An Extremely Serious Piece of Equipment

3 easy payments of

**\$268**

0% Financing!  
 On Credit Cards only



Sturdy Handle

Rubber Sides

2 Easy Payments  
 Over a Quarter  
 Million Devices  
**\$49!**  
**ORDER NOW & Get**  
**FREE**  
 Upgrade which  
 will include  
 Separate Asian  
 Transistor Spec  
 Data (a \$69 option  
 in the new version  
 Offer EXPIRES Sep

**Oh - My - GOD!**  
 Get an IC MASTER for  
**\$29!!**  
 Limited Time  
**ICMaster**

**Bible of the IC Industry**  
 Every Cross-reference  
 3 Volume Set with Tons of Information

ICMaster Earlier Editions Perfect for Service or Lite Design. Later Editions Perfect for Advanced Design

<b>ICM</b>	95 3Book Set \$29 !!!!!!!
<b>\$195</b>	96 3Book Set \$49 !!!!!!!
<b>Publisher</b>	97 3Book Set \$69 !! CD Rom \$99!!
	98 3Book gone CD " \$135!
	99 3Book gone CD " \$189!

EEM Contains the Complete Catalogs of Most Electronic Component Manufacturers & Distributors

<b>EEM</b>	97 4 Book Set only on CD \$35
	98 4 Book Set only on CD \$55

**The Screamer**

**IBM THINKPAD Pentium P-75**

2 Gig Hard Drive Standard  
 All other features same as the IBM DX4-100  
**INCLUDES Lifetime Tech Support**

3 easy payments of  
 Wow **\$286!**  
 0% Financing!  
 On Credit Cards only

Original **\$3,499**

**NEW STOCK**

**Auto Power Adapter '69**

Style may vary slightly

**Notebook Attache'**

**\$39**  
 with purchase

**\$59**  
 alone

**\$139**  
 in Office Max



Contents NOT included

Tons of Pockets

1 Year Warranty - Satisfaction Guaranteed - The Friendliest People - The Best Customer Service  
 3 PAYMENT PLAN with Credit Card -or- Layaway ONLY 843-650-5700 For Questions-or- email: netcomd@aol.com  
 COD's SINGLE PAYMENT ONLY ORDERS ONLY 800-733-3733 ORDERS ONLY FAX 843 650 5777 10-8 EST Mon-Fri



# WESTERN TEST SYSTEMS

WE HAVE  
MOVED!

## WE BUY AND SELL

Inquiries 307-635-2269 • Fax 307-635-2291

Orders 800-538-1493

2701 Westland Court, Unit B, Cheyenne, Wyoming 82001

### OSCILLOSCOPES & ACCESSORIES

#### OSCILLOSCOPES

TEK 2445 150 MHz 4-channel Oscilloscope	\$1,400.00
TEK 2465 300 MHz 4-channel Oscilloscope	\$2,250.00
TEK 7104 1 GHz 2-Channel Oscilloscope, w/7A29,7A29-04,7B10,7B15	\$3,000.00
TEK 7844 400 MHz Dual Beam Oscilloscope with 7A24,7A26,7B80,7B85	\$900.00
TEK 7904 500 MHz Oscilloscope, with 7A24, 7A26, 7B80, 7B85	\$900.00
TEK SC502 15 MHz Dual Trace Oscilloscope, TM500 series	\$325.00
TEK SC503 10 MHz Dual Trace Storage Oscilloscope, TM500 series	\$375.00

#### PROBES

HP 1122A Probe Power Supply	\$150.00
HP 54701A 2.5 GHz 10X FET Probe, for 54700 series oscilloscopes	\$1,000.00
TEK 1101A Accessory Power Supply, for FET probes	\$200.00
TEK P6015A 75 MHz 40 kVpk 1000X Probe	\$600.00
TEK P6046 100 MHz Differential Probe	\$500.00
TEK P6150 9 GHz 10X/3 GHz 1X 50 Ohm Probe, SMA(m) output	\$400.00
TEK P6201 900 MHz 1X/10X/100X FET Probe	\$450.00
TEK P6202A 500 MHz 10X FET Probe	\$250.00
TEK P6701-opt.02 O/E Converter, 450-1050 nm/0-1 mW: DC-700 MHz, ST conn.	\$175.00

#### CALIBRATION

TEK SG503 Level Generator, 250 kHz-250 MHz, TM500 series	\$600.00
--	----------

### WAVEFORM GENERATORS

#### FUNCTION

HP 3310B 5 MHz Function Generator, variable phase trigger	\$350.00
HP 3312A 13 MHz Function Generator	\$500.00
HP 3314A-001 20 MHz Function Generator, HPIB	\$1,500.00
HP 3325A 21 MHz Synthesized Function Generator, HPIB	\$1,000.00
HP 3325A-002 21 MHz Synthesized Function Generator, HV output option	\$1,500.00
HP 8165A-002 Prog. Signal Source, 1 mHz-50 MHz, log sweep	\$1,500.00
HP 8904A-001,002,004 Multifunction Synthesizer, DC-600 kHz	\$2,500.00
TEK AWG5102 Arb.Waveform Gen., 20 MS/s, 12 bits, 50ppm synthesis <1MHz	\$900.00
TEK AWG5105-opt.02 Arbitrary Waveform Generator, dual channel option	\$1,250.00
TEK DD501 Digital Delay & Burst Gen., for function & pulse gen's	\$275.00
TEK FG501 1 MHz Function Generator, TM500 series	\$225.00
TEK FG502 11 MHz Function Generator, TM500 series	\$300.00
TEK FG503 3 MHz Function Generator, TM500 series	\$250.00
TEK RG501 Ramp Generator, TM500 series	\$175.00
WAVETEK 288 20 MHz Synthesized Function Generator, GPIB	\$750.00

#### PULSE

BERKELEY NUCLEONICS 7085B Digital Delay Generator, 0-100 mS, 1 nS res., 5 Hz-5 MHz	\$750.00
HP 214B 10 MHz 100 Vpk Pulse Generator	\$1,200.00
HP 8007B 100 MHz Pulse Generator	\$650.00
HP 8012B 50 MHz Pulse Generator, variable transition time	\$600.00
HP 8080A/81A/83A/84A 300 MHz Word Generator	\$800.00
HP 8080A/91A/92A/93A 1 GHz Single Channel Pulse Generator	\$950.00
HP 8112A 50 MHz Programmable Pulse Generator, HPIB	\$4,000.00
HP 8115A 50 MHz Dual Channel Pulse Generator, HPIB	\$2,750.00
HP 8116A-001 50 MHz Pulse / Function Generator, burst & log sweep	\$3,900.00
TEK PG502 250 MHz Pulse Generator, Tr<1nS, TM500 series	\$600.00
TEK PG505 100 kHz Pulse Generator, 80 V peak, TM500 series	\$275.00
TEK PG506 50 MHz Pulse Generator, TM500 series	\$500.00
WAVETEK 802 50 MHz Pulse Generator	\$300.00

### VOLTAGE & CURRENT

#### VOLTMETERS

FLUKE 845AR High Impedance Voltmeter / Null Detector	\$400.00
HP 3456A 6-1/2 Digit Voltmeter, HPIB	\$500.00
HP 3457A 7-1/2 digit Voltmeter, HPIB	\$1,200.00
HP 3478A 5-1/2 digit Multimeter, HPIB	\$600.00
KEITHLEY 181 6-1/2 digit Nanovoltmeter, 10 nV sensitivity, GPIB	\$900.00
SOLARTRON 7081 8-1/2 digit Voltmeter	\$3,250.00
TEK DM5010 4-1/2 digit Multimeter, TM5000 series plug-in	\$300.00
TEK DM501A 4-1/2 digit Multimeter, TM500 series plug-in	\$225.00

#### CALIBRATION

FLUKE 510A AC Reference Standard, 10 VRMS, 0-10 mA	\$450.00
FLUKE 515A Portable Calibrator, DC/AC/Ohms, line & battery power	\$900.00
FLUKE 5220A Transconductance Amplifier, DC-5 kHz, 0-20 A	\$3,000.00
VALHALLA 2703 AC Volt.Std., 0-120V/10 Hz-100 kHz; 120-1200V/10 Hz-1 kHz	\$1,500.00

#### VOLTAGE SOURCES

HP 6114A Precision Dual Range Power Supply, 20 V 2 A / 40 V 1 A	\$850.00
HP 6115A Precision Dual Range Power Supply, 50V 0.8A / 100V 0.4A	\$850.00
KEITHLEY 228 Programmable Voltage/Current Source	\$1,900.00

### CURRENT METERS & SOURCES

HP 4140B Picoammeter / DC Voltage Source, without test fixture	\$2,000.00
HP 6177C DC Current Source, to 50 V, 500 mA	\$500.00
HP 6181C DC Current Source, to 100 V, 250 mA	\$500.00
HP 6186B DC Current Source, to 300 V, 100 mA	\$300.00
HP 6186C DC Current Source, to 300 V, 100 mA	\$750.00
KEITHLEY 225 Current Source, 0.1 uA-100 mA, 10-100 V compliance	\$500.00
KEITHLEY 227 Current Source, 1 uA-1 A, 0-50 V compliance	\$800.00
KEITHLEY 614 Electrometer	\$650.00
TEK CT-5 High Current Transformer for P6021/A6302, to 1000A	\$375.00
TEK P6022 AC Current Probe w/termination, 935 Hz-120 MHz, 6 A pk	\$275.00

### IMPEDANCE & COMPONENT TEST

#### L.C.R.

BOONTON 62AD 1 MHz Inductance Meter, 2-2000 uH	\$550.00
BOONTON 72BD 1 MHz Capacitance Meter, 3-1/2 digit display	\$650.00
HP 4262A-101 3-1/2 digit LCR Meter, 120 Hz/1 kHz/10 kHz test, HPIB	\$1,500.00
HP 4280A-001 1 MHz C Meter / C-V Plotter, 5-1/2 digit res. C	\$3,000.00

#### STANDARDS

E.S.I. SR-1 Standard Resistor, various values	\$125.00
E.S.I. SR1010 Resistance Transfer Standards, 1 Ohm-100 K/step	\$550.00
E.S.I. SR1050-1M Resistance Transfer Standard, 1 Megohm/step	\$2,000.00
GR 1404-A 1000 pF Reference Standard Capacitor	\$700.00
GR 1406 Standard Air Capacitors, GR900 connector, 0.1% acc.	\$375.00
GR 1432-U 4-Decade Resistor, 0-11,110 Ohms, 0.01 Ohm resolution	\$100.00
GR 1433-J 4-Decade Resistor, 0-11,110 Ohms, 0.1 Ohm resolution	\$150.00
GR 1433-K 4-Decade Resistor, 0-1,110 Ohms, 0.1 Ohm resolution	\$150.00
GR 1433-L 4-Decade Resistor, 0-11,100 Ohms, 10 Ohms resolution	\$150.00
GR 1433-N 5-Decade Resistor, 0-11,111 Ohms, 0.1 Ohm resolution	\$200.00
GR 1433-X 6-Decade Resistor, to 111,111.0 Ohms, 0.1 Ohm res.	\$250.00

#### HI & LO RESISTANCE

HP 4328A Milliohmeter	\$1,200.00
T.D.R.	
TEK 1502-opt.04 Time Domain Reflectometer, 0-2,000 feet, chart recorder	\$1,400.00
TEK 1503B-03.04 T.D.R., 0-50,000 ft., chart recorder & battery power	\$3,000.00
TEK 1503-opt.04 Time Domain Reflectometer, 0-50,000 feet, chart recorder	\$1,400.00

### POWER SUPPLIES

#### SINGLE OUTPUT

GLASSMAN PS/WH-03R150XE2 0-3000 V 0-150 mA CV/CC Power Supply	\$800.00
HP 6011A Autotransforming 0-20 V 0-120 A Power Supply, 1000 W max.	\$1,400.00
HP 6032A 0-60 V/0-10 A/1000 W Autotransforming System Supply, HPIB	\$2,000.00
HP 6200B Dual Range Supply, 0-20 V 0-1.5 A/0-40 V 0-750 mA CVCC	\$200.00
HP 6201B 0-20 V 0-1.5 A CV/CC Power Supply	\$175.00
HP 6207B 0-160 V 0-200 mA CV/CC Power Supply	\$200.00
HP 6256B 0-10 V 0-20 A CV/CC Power Supply	\$250.00
HP 6263B 0-20 V 0-10 A CV/CC Power Supply	\$400.00
HP 6266B 0-40 V 0-5 A CV/CC Power Supply	\$400.00
HP 6267B 0-40 V 0-10 A CV/CC Power Supply	\$550.00
HP 6269B-028 0-40 V 0-50 A CV/CC Power Supply; 230 VAC line	\$900.00
HP 6274B 0-60 V 0-15 A CV/CC Power Supply	\$650.00
HP 6281A 0-7.5 V 0-5 A CV/CC Power Supply	\$150.00
HP 6282A 0-10 V 0-10 A CV/CC Power Supply	\$200.00
HP 6289A 0-40 V 0-1.5 A CV/CC Power Supply	\$200.00
HP 6299A 0-100 V 0-750 mA CV/CC Power Supply	\$200.00
HP 6384A 4.0-5.5 V at 8 A CV/CL Power Supply	\$125.00
HP 6443B 0-120 V 0-2.5 A CV/CC Power Supply	\$450.00
HP 6672A System DC Power Supply, 0-20 V 0-100 A CV/CC, HPIB	\$2,750.00
KEPCO ATE 36-30M 0-36 V 0-30 A CV/CC Power Supply	\$900.00
KEPCO ATE 36-8M 0-36 V 0-8 A CV/CC Power Supply	\$375.00
LAMBDA LK-352-FM 0-60 V 0-15 A CV/CC Power Supply	\$600.00
SORENSEN DCR 20-25B2 0-20 V 0-25 A CV/CC Power Supply	\$550.00
SORENSEN DCR 300-1.25A 0-300 V 0-1.25 A CV/CC Power Supply	\$400.00
SORENSEN DCR 600-0.75B2 0-600 V 0-750 mA CV/CC Power Supply	\$550.00
SORENSEN DCR 600-1.5B 0-600 V 0-1.5 A CV/CC Power Supply	\$700.00
SORENSEN SRL 20-12 0-20 V 0-12 A CV/CC Power Supply	\$400.00
SORENSEN SRL 60-8 0-60 V 0-8 A CV/CC Power Supply	\$600.00
TEK PS501-1 Power Supply, 0-20 V, 2 mV res., 400 mA, TM500 series	\$175.00

#### MULTIPLE OUTPUT

HP 6205C Dual Power Supply, 0-40 V 300 mA & 0-20 V 600 mA, CV/CL	\$300.00
HP 6228B Dual 0-50 V 0-1 A CV/CC Power Supply	\$450.00
HP 6236B Triple Output Supply, to +20 V 0.5 A & 0-6 V 2.5 A	\$375.00

HP 6237B Triple Output Supply, to +20 V 0.5 A & 0-18 V 1 A	\$375.00
HP 6253A Dual 0-20 V 0-3 A CV/CC Power Supply	\$450.00
HP 6255A Dual 0-40 V 0-1.5 A CV/CC Power Supply	\$450.00
KEPCO MPS-620M Triple Output Supply, dual 0-20V 1A tracking & 0-6V 5A	\$250.00
LAMBDA LPD-422-FM Dual 0-40 V 0-1 A CV/CC Power Supply	\$300.00
LAMBDA LPT-7202-FM Triple Output Power Supply	\$450.00
TEK PS5010 Programmable Triple Power Supply, TM5000 series	\$650.00
TEK PS503A Dual Power Supply, TM500 series	\$200.00

#### MISCELLANEOUS

ACME PS2L-500 Programmable Load, 0-75 V / 0-75 A / 500 Watts max.	\$350.00
ELGAR 501C/400SD AC Power Source, 45 Hz-5 kHz, 500 VA, 0-135 VAC	\$1,150.00
HP 59501B HPIB Isolated DAC/Power Supply Programmer	\$175.00
HP 6825A Bipolar Power Supply/ Amplifier, +/- 20 V 2 A	\$800.00
KEPCO BOP 20-20M Bipolar Op Amp/Power Supply, to 20 V 20 A	\$675.00
KEPCO BOP 36-5M Bipolar Op Amp/Power Supply, to 36 V 5 A	\$400.00
KEPCO BOP 50-2M Bipolar Op Amp/Power Supply, to 50 V 2 A	\$400.00
TRANSISTOR DEVICES DAL-50-15-100 Programmable Load, 0-50 V, 0-15 A, 100 Watts max.	\$200.00

### TIME & FREQUENCY

#### UNIVERSAL COUNTERS

HP 5314A-001 100 MHz/100 nS Universal Counter; TCXO reference option	\$275.00
HP 5315A-001 100 MHz/100 nS Universal Counter, TCXO reference option	\$450.00
HP 5315A-002,003 100 MHz/100 nS Univ. Counter; batt. power & 1 GHz C-ch.	\$650.00
HP 5315A-003 100 MHz/100 nS Univ. Counter, 1 GHz C-channel option	\$550.00
HP 5315B 100 MHz/100 nS Universal Counter	\$500.00
HP 5316A 100 MHz/100 nS Universal Counter, HPIB	\$600.00
HP 5316A-001,003 100 MHz/100 nS Univ. Counter, HPIB, TCXO, 1 GHz C-ch.	\$750.00
HP 5316B 100 MHz/100 nS Universal Counter, HPIB	\$750.00
HP 5364A Microwave Mixer / Detector, for modulation domain an.	\$3,000.00
HP 5370B 100 MHz/20 pS 11 digit Universal Time Interval Counter	\$1,200.00
PHILIPS PM6672/411 120 MHz/100 nS Universal Counter, C-channel 70-1000 MHz	\$450.00
TEK DC5004 Programmable 100 MHz/100nS Counter/Timer, TM5000 series	\$250.00
TEK DC5009 Programmable 135 MHz Univ. Counter/Timer, TM5000 series	\$400.00
TEK DC5010 350 MHz / 3.125 nS Universal Counter, TM5000 series	\$950.00
TEK DC503A 125 MHz/100 nS Universal Counter, TM500 series	\$275.00
TEK DC509 135 MHz/10 nS Universal Counter, TM500 series	\$275.00

#### FREQUENCY COUNTERS

EIP 545A 18 GHz Frequency Counter	\$750.00
EIP 575 18 GHz Source Locking Counter, GPIB	\$1,250.00
FLUKE 7220A-010,131,351 1.3 GHz Counter; battery power, OCXO, and res. mult.	\$500.00
HP 5340A 18 GHz Frequency Counter	\$450.00
HP 5343A-001 26.5 GHz Frequency Counter, OCXO reference	\$3,500.00
HP 5345A/5355A/5356B 26.5 GHz CW/Pulse Frequency Counter	\$3,500.00

#### STANDARDS

HP 105B Quartz Oscillator, 0.1 / 1.0 / 5.0 MHz, battery power	\$1,500.00
HP 5087A-opt.032 Distribution Amplifier, 12 outputs at 5 MHz	\$1,750.00

### AUDIO & BASEBAND

#### SPECTRUM ANALYSIS

HP 3586C Selective Level Meter, 50 Hz-32.5 MHz, 50 & 75 ohms	\$1,200.00
TEK 7L5/L3/R7603 Spectrum Analyzer, 20 Hz-5 MHz, 10 Hz min. res., w/frame	\$1,500.00

#### DISTORTION ANALYZERS

HP 339A Distortion Analyzer, built-in low distortion osc.	\$750.00
HP 8903A-001 Audio Analyzer, 20 Hz-100 kHz; rear panel input	\$1,500.00
TEK DA4084 Programmable Distortion Analyzer	\$750.00

#### RMS VOLTMETERS

FLUKE 8922A True RMS Voltmeter, 180 uV-700 V, 2 Hz-11 MHz	\$450.00
---	----------

#### OSCILLATORS

HP 3336C Synthesizer / Level Generator, 10 Hz-21 MHz	\$1,000.00
TEK SG502 Sine/Square Osc., 5 Hz-500 kHz, 70 dB step atten., TM500	\$200.00


#### MISCELLANEOUS

HP 3575A-002 Phase-Gain Meter, 1 Hz-13 MHz, dual display	\$850.00
KROHN-HITE 3103 High/Low Pass Filter, 10 Hz-3 MHz, 24 dB/octave	\$350.00
KROHN-HITE 3202 Dual HP/LP/BP/BR Filter, 20 Hz-2 MHz, 24 dB/octave	\$450.00




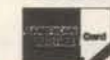
# 90 DAY WARRANTY PARTS AND LABOR • 10 DAY INSPECTION TEST EQUIPMENT WANTED CALL OR FAX LIST • OPEN ACCOUNTS



KROHN-HITE 3342R Dual HP/LP Filter, 0.001 Hz-99.9 kHz, 48 dB/octave	\$900.00
KROHN-HITE 3750 LP/HP/BP/BR Filter, 0.02 Hz-20 kHz, 6/12/18/24 dB/oct.	\$600.00
KROHN-HITE DCA-10R 10 Watt Amplifier, 20 dB gain, DC-1 MHz, 600-1000 Ohms	\$450.00
ROCKLAND 852 Dual Highpass/ Lowpass Filter, 0.1 Hz-111 kHz	\$900.00
TEK AM502 Differential Amplifier, 0.1 Hz-1 MHz, TM500 series	\$475.00

## RF & MICROWAVE

### SPECTRUM ANALYZERS

HP 11517A/18A/19A/20A Mixer Set, 12.4-40.0 GHz, for HP 8555A/8569A	\$500.00
HP 11970A WR28 Harmonic Mixer, 26.5-40 GHz	\$1,100.00
HP 11970K WR42 Harmonic Mixer, 18.0-26.5 GHz	\$1,100.00
HP 11970Q WR22 Harmonic Mixer, 33-50 GHz	\$1,400.00
HP 11970U WR19 Harmonic Mixer, 40-60 GHz	\$1,400.00
HP 3585A Spectrum Analyzer, 20 Hz-40 MHz, 3 Hz min. res. bw.	\$4,500.00
HP 8559A/853A-001 Spectrum An., 0.01-21 GHz, 1 kHz res., w/rackmount frame	\$3,750.00
HP 8565A-100 Spectrum Analyzer, 10 MHz-22 GHz, 100 Hz min. res.	\$3,500.00
HP 8568B Spectrum Analyzer, 100 Hz-1.5 GHz, 10 Hz min. res.	\$8,500.00
HP 8569B Spectrum Analyzer, 10 MHz-22 GHz, 100 Hz min. res. bw.	\$7,500.00
TEK TR502 Tracking Generator, 0.1-1800 MHz, for 7L13/7L14	\$950.00
TEK WM782V WR15 Harmonic Mixer, 50-75 GHz	\$1,500.00

### NETWORK ANALYZERS

HP 11850A Network Analyzer Accessory Kit, APC7	\$600.00
HP 35676A Reflection/Transmission Test Kit, 5 Hz-200 MHz	\$1,000.00
HP 8405A Vector Voltmeter, 1-1000 MHz	\$450.00
HP 85020A Directional Bridge, 10-4300 MHz, N(f) test port	\$650.00
HP 85027C Directional Bridge, 0.01-18 GHz, N(f) test port	\$1,750.00
HP 85044A Reflection/Transmission Test Set, 300 kHz-3 GHz	\$1,500.00
HP 85054A Type N Calibration Kit, for HP 8510 series	\$1,800.00
HP 8758A Scalar Network Analyzer	\$2,500.00
HP R85026A WR28 Detector, 26.5-40 GHz, for HP 8757 series	\$1,200.00
WILTRON 560-98KF50 SWR Autotester, 10 MHz-40 GHz, for Wiltron 560 series	\$1,800.00

### SIGNAL GENERATORS

FLUKE 6080A Synthesized Signal Gen., 0.1-1050 MHz, 10 Hz res., GPIB	\$1,900.00
FLUKE 6080A/AN Synthesized Signal Gen., 10 kHz-520 MHz, 10 Hz res., GPIB	\$1,500.00
FLUKE 6080B/AB Synthesized Signal Gen., 0.1-1050 MHz, 10 Hz res.	\$1,900.00
GIGATRONICS 1018 Synthesized Signal Gen., 50 MHz-18 GHz, 1 MHz res.	\$4,500.00
GIGATRONICS 600/6-12 Synthesized Source, 6-12 GHz, 1 kHz res., GPIB	\$2,500.00
GIGATRONICS 840-18 Freq. Multiplier, 18-26 & 26-40 GHz outputs 0 dBm	\$2,750.00
GIGATRONICS 875/50 Levelled Multiplier, x4, 50.0-75.0 GHz output, -3 dBm	\$2,500.00
GIGATRONICS 875/86 Levelled Multiplier, 26.5-40.0 & 50.0-75.0 GHz outputs	\$3,750.00
GIGATRONICS 900/2-8 Synthesized Signal/Sweep Gen., 2-8 GHz, 1 MHz res., GPIB	\$2,500.00
HP 11720A Pulse Modulator, 2-18 GHz, 80 dB on/off ratio	\$450.00
HP 3335A Synthesizer / Level Generator, 200 Hz-81 MHz	\$4,500.00
HP 85100V Frequency Mult., 10-15 GHz in / 50-75 GHz out >0 dBm	\$3,750.00
HP 8540B Signal Generator, 0.5-512 MHz, AM, FM, pulse modulation	\$950.00
HP 8556B-001 Synth. Signal Gen., 0.1-990 MHz, 10 Hz res., OCXO ref.	\$2,500.00
HP 8557A-002 Signal Generator, 0.1-1040 MHz, 10 Hz res., HP1B	\$3,250.00
HP 8660C/86602B-002 Synth. Sig. Gen., 1-1300 MHz, FM / Phase mod. w/86635A	\$2,750.00
HP 8660C/86603A Synthesizer, 1-2600 MHz, AM / FM, w/86633B	\$3,250.00
HP 8672A Synthesized Signal Generator, 2-18 GHz, +3 dBm output	\$6,000.00
HP 8673D Synth. Signal Generator, 50 MHz-26 GHz, AM/FM/Pulse	\$18,500.00
HP 8673E Synthesized Signal Generator, 2-18 GHz, +8 dBm output	\$9,500.00
HP 8673G-004, 008 Synth. CW Signal Generator, 2-26 GHz, +8 dBm output	\$12,500.00
HP 8684B Signal Generator, 5.4-12.5 GHz, AM/ WBFM/ Pulse	\$3,500.00
P.T.S. 250 Frequency Synthesizer, 1-250 MHz, 1 Hz res., +13 dBm	\$750.00

### SWEEP GENERATORS

HP 8350A/83545A-002 Sweep Oscillator, 5.9-12.4 GHz, 70 dB step attenuator	\$4,000.00
HP 8601A Generator/Sweeper, 0.1-110 MHz, +20 dBm levelled	\$400.00
HP 8620C Sweep Oscillator Frame	\$550.00
HP 86222B-002 RF Plug-in, 10-2400 MHz, +13 dBm levelled, 70 dB atten.	\$1,250.00
HP 86230B RF Plug-in, 1.8-4.2 GHz, +10 dBm unlevelled	\$375.00
HP 86240C RF Plug-in, 3.6-6.6 GHz, +18 dBm levelled	\$700.00
HP 86241A-001 RF Plug-in, 3.2-6.5 GHz, +8 dBm levelled	\$300.00
HP 86242D-004, 008 RF Plug-in, 5.9-9.0 GHz, +10 dBm levelled	\$300.00
HP 86245A-001 RF Plug-in, 5.9-12.4 GHz, +17 dBm levelled	\$600.00
HP 86250D RF Plug-in, 8.0-12.4 GHz, +10 dBm levelled	\$500.00
HP 86260A RF Plug-in, 12.0-18.0 GHz, +10 dBm unlevelled	\$500.00
HP 86260A-H04 RF Plug-in, 10.0-15.0 GHz, +10 dBm unlevelled	\$500.00
HP 86290A-004 RF Plug-in, 2.0-18.0 GHz, +7 dBm levelled, rear output	\$1,750.00
HP 86290B-004 RF Plug-in, 2.0-18.6 GHz, +10 dBm levelled, rear output	\$1,850.00

WAVETEK 962 Sweep Generator, 1.0-4.0 GHz, markers, +12 dBm unlvld.	\$1,250.00
WILTRON 6647M Sweep Generator, 10 MHz-20 GHz, +10 dBm levelled	\$4,500.00

### POWER METERS

ANRITSU MP-81B/ML-83A Power Meter, 75-110 GHz (WR10), -20 to +20 dBm	\$2,500.00
BOONTON 4200-01A, 03/8-4A x2 Dual Channel Microwattmeter, w/(2) 1 MHz-7 GHz sensors	\$950.00
BOONTON 42B/41-4E Analog Power Meter, with 1 MHz-18 GHz sensor	\$450.00
HP 435B/8481A Power Meter, -30 to +20 dBm, 10 MHz-18 GHz	\$900.00
HP 435B/8482H Power Meter, -10 to +34 dBm, 100 kHz-4.2 GHz	\$900.00
HP 436A/8481A Power Meter, -30 to +20 dBm, 10 MHz-18 GHz	\$1,400.00
HP 8477A Power Meter Calibrator, for HP 432 series	\$500.00
HP K486A WR42 Thermistor Mount, 18.0-26.5 GHz, for 432 series	\$350.00
HP Q8486A Power Sensor, 33.0-50.0 GHz, WR22, for 435/6/7/8	\$1,500.00
HP R486A WR28 Thermistor Mount, 26.5-40 GHz, for 432 series	\$350.00
HP R8486A WR28 Power Sensor, 26.5-40 GHz, for HP 435/6/7/8	\$1,500.00

### RF MILLIVOLTMETERS

BOONTON 92B-opt.05 RF Millivoltmeter, 10 kHz-1.2 GHz, 75 Ohms scale	\$500.00
RACAL 9303 TRMS Level Meter, 10 kHz-2 GHz, -77 to +23 dBm, GPIB	\$875.00

### AMPLIFIERS, MISCELLANEOUS

AMPLIFIER RES. 1W1000 Amplifier, 30 dB gain, 1-1000 MHz, 1 Watt output	\$500.00
BOONTON 82AD-opt.01A Modulation Meter, AM, FM, 10-1200 MHz, GPIB	\$750.00
ENI 1040L Amplifier, 55 dB gain, 10-500 kHz, 400 Watts	\$2,750.00
HP 11729C-130, 140 Carrier Noise Test Set, AM Noise & Rear Panel Inputs	\$9,500.00
HP 415E SWR Meter	\$200.00
HP 465A Amplifier, 20/40 dB, 5 Hz-1 MHz, 1/2 Watt/50 Ohms	\$125.00
HP 8406A Comb Generator, 1/ 10/ 100 MHz increments, to 5 GHz	\$500.00
HP 8447A Amplifier, 20 dB, 0.1-400 MHz, 5 dB NF, +6 dBm output	\$375.00
HP 8447E Amplifier, 22 dB, 0.1-1300 MHz, +13 dBm output	\$750.00
HP 8901A Modulation Analyzer, 150 kHz-1300 MHz	\$2,500.00
HP 8901B-1.2.3 Modulation An., 0.15-1300 MHz, rear input, OCXO, ext. LO	\$3,000.00
HP 8970A Noise Figure Meter	\$4,000.00
HUGHES 1077H12F000 TWT Amplifier, 30 dB gain, 26.5-40 GHz, 1 Watt output	\$5,000.00
ROHDE & SCHWARTZ ESH2 Test Receiver, 9 kHz-30 MHz	\$5,000.00

## COAXIAL & WAVEGUIDE

AMERICAN NUCLEONICS AM-432 Cavity Backed Spiral Antenna, LHC, 2-18 GHz, TNC(f) "NEW"	\$95.00
AVANTEK AMT-400X2 WR28 Active Doubler, 13-20 GHz +10 dBm in, +10 dBm out	\$450.00
BAYTRON 3-28-300/10 WR28 Directional Coupler, 10 dB, 26.5-40 GHz	\$300.00
BIRD 4410A/4410-3 Wattmeter, 2-30 MHz, 10 W - 1 kW f.s., N(f)	\$400.00
BIRD 6735-300 1 kW Load, 25-1000 MHz, LC(f), with wattmeter	\$650.00
BIRD 8201 500 Watt Oil Cooled Load, DC-2.5 GHz, N(f)	\$350.00
CONTINENTAL MW. RAE28-K-M WR28 x K(m) Endfire Adapter	\$225.00
FXR/MICROLAB S3-02N Triple Stub Tuner, 200-1000 MHz, 100 Watts max., N(m/f)	\$125.00
FXR/MICROLAB SL-03N Stub Tuner, 0.3-6.0 GHz, 100 Watts max., N(m/f)	\$75.00
GR 874-LTL Constant Impedance Trombone Line, 0-44 cm, DC-2 GHz	\$400.00
HP 11590A-001 Bias Network, 1.0-18.0 GHz, APC7	\$450.00
HP 11636A 2-Way Power Divider, DC-18 GHz, N(m/f)	\$300.00
HP 11692D Dual Directional Coupler, 22 dB, 2-18 GHz	\$800.00
HP 33321K Programmable Step Atten., 0-70 dB, DC-26.5 GHz, 3.5mm	\$475.00
HP 33327L-006 Programmable Step Attenuator, 0-70 dB, DC-40 GHz, 2.9mm	\$1,000.00
HP 774D Dual Directional Coupler, 20 dB, 215-450 MHz	\$275.00
HP 777D Dual Directional Coupler, 20 dB, 1.9-4.1 GHz	\$275.00
HP 778D-011 Dual Dir. Coupler, 20 dB, 100-2000 MHz, APC7 test port	\$450.00
HP 8431A 2-4 GHz Band Pass Filter, N(m/f)	\$150.00
HP 8493C-003 3 dB Attenuator, 2 Watts, DC-26.5 GHz, APC3.5	\$150.00
HP 8493C-020 20 dB Attenuator, 2 Watts, DC-26.5 GHz, APC3.5	\$150.00
HP 8494G-002 Programmable Step Attenuator, 0-11 dB, DC-4 GHz, SMA	\$350.00
HP 8495H-002 Programmable Step Attenuator, 0-70 dB, DC-18 GHz, SMA	\$400.00
HP 8497K-004 Programmable Step 2 Attenuator, 0-90 dB, DC-26.5 GHz	\$750.00
HP K382A WR42 Direct Reading Attenuator, 0-50 dB, 18-26.5 GHz	\$2,900.00
HP K422A WR42 Flat Broadband Detector, 18.0-26.5 GHz	\$350.00
HP K532A WR42 Frequency Meter, 18.0-26.5 GHz	\$450.00
HP K870A WR42 Slide Screw Tuner, 18.0-26.5 GHz	\$275.00
HP K914B WR42 Moving Load, 18.0-26.5 GHz	\$300.00
HP Q752D WR22 Directional Coupler, 20 dB, 33-50 GHz	\$650.00
HP R382A WR28 Direct Reading Attenuator, 0-50 dB, 26.5-40 GHz	\$2,000.00
HP R422A WR28 Crystal Detector, 26.5-40 GHz	\$400.00
HP R532A WR28 Frequency Meter, 26.5-40 GHz	\$500.00
HP R752C WR28 Directional Coupler, 10 dB, 26.5-40 GHz	\$450.00
HP R752D WR28 Directional Coupler, 20 dB, 26.5-40 GHz	\$450.00
HP R914B WR28 Moving Load, 26.5-40 GHz	\$250.00
HP V365A WR15 Isolator, 25 dB, 50-75 GHz	\$750.00

HP V752D WR15 Directional Coupler, 20 dB, 50-75 GHz	\$650.00
HP X870A WR90 Slide Screw Tuner	\$150.00
HUGHES 45712H-1000 WR22 Frequency Meter, 33-50 GHz	\$900.00
HUGHES 45714H-1000 WR15 Frequency Meter, 50-75 GHz	\$900.00
HUGHES 45716H-1000 WR10 Frequency Meter, 75-110 GHz	\$900.00
HUGHES 45721H-1000 WR28 Direct Reading Attenuator, 0-50 dB, 26.5-40 GHz	\$900.00
HUGHES 45724H-1000 WR15 Direct Reading Attenuator, 0-50 dB, 50-75 GHz	\$1,000.00
HUGHES 45732H-1200 WR22 Level Set Attenuator, 0-25 dB, 33-50 GHz	\$250.00
HUGHES 45772H-1100 WR22 Thermistor Mount, -20 to +10 dBm, 33-50 GHz	\$400.00
HUGHES 45775H-1100 WR12 Thermistor Mount, -20 to +10 dBm, 60-90 GHz	\$800.00
HUGHES 47316H-1111 WR10 Tuneable Detector, 75-110 GHz, positive polarity	\$600.00
HUGHES 47741H-2310 WR28 Phase Locked Gunn Osc., 32.00 GHz, +18 dBm	\$2,000.00
HUGHES 47742H-1210 WR22 Phase Locked Gunn Osc., 42.00 GHz, +18 dBm	\$2,750.00
HUGHES 47974H-1000 WR15 SPST PIN Switch, 250 MHz speed, 60-62 GHz response	\$375.00
KRYTAR 2616S Directional Detector, 1.7-26.5 GHz, K(t/m)/SMC	\$200.00
M/A-COM 3-19-300/10 WR19 Directional Coupler, 10 dB, 40-60 GHz	\$450.00
MICA C-121S06 Circulator, 17.5-24.5 GHz, SMA(f/m/m)	\$75.00
MIDWEST MICROWAVE 3537 DC Block, 0.1-12.4 GHz, SMA(m/f) "NEW"	\$40.00
MINI-CIRCUITS ZFDC-20-4 Directional Coupler, 19.5 dB, 1-1000 MHz, SMA(f)	\$25.00
NARDA 3000-SERIES Directional Couplers	\$150.00
NARDA 3024 Bi-Directional Coupler, 20 dB, 4-8 GHz	\$300.00
NARDA 3090-SERIES Precision High Directivity Couplers	\$225.00
NARDA 368BNM Coaxial High Power Load, 500 Watts, 2.0-18 GHz, N(m)	\$500.00
NARDA 3752 Coaxial Phase Shifter, 0-180 deg./GHz, 1-5 GHz	\$1,000.00
NARDA 3753B Coaxial Phase Shifter, 0-55 deg./GHz, 3.5-12.4 GHz	\$1,000.00
NARDA 4000-SERIES SMA Miniature Directional Couplers	\$75.00
NARDA 4226-10 Directional Coupler, 10 dB, 0.5-18.0 GHz, SMA(f)	\$275.00
NARDA 4227-16 Directional Coupler, 16 dB, 1.7-26.5 GHz, 3.5mm(f)	\$325.00
NARDA 4242-20 Directional Coupler, 20 dB, 0.5-2.0 GHz, SMA(f)	\$100.00
NARDA 4247-20 Directional Coupler, 20 dB, 6.0-26.5 GHz, 3.5mm(f)	\$200.00
NARDA 4247B-10 Directional Coupler, 10 dB, 6.0-26.5 GHz, 3.5mm(f)	\$200.00
NARDA 5070-SERIES Precision Reflectometer Couplers	\$300.00
NARDA 582 DC Block, 10 MHz-12.4 GHz, 100 V max., N(m/f)	\$65.00
NARDA 765-10 10 dB Attenuator, 50 Watts, DC-5 GHz, N(m/f)	\$165.00
NARDA 768-10, 20 10 dB or 20 dB Attenuator, 20 Watts, DC-11 GHz, N(m/f)	\$120.00
NARDA 792FF Variable Attenuator, 0-20 dB, 2.0-12.4 GHz	\$375.00
NARDA 794FM Direct Reading Variable Attenuator, 0-40 dB, 4-8 GHz	\$375.00
OMNI-SPECTRA 2085-8010-00 Crystal Detector, 1-18 GHz, negative polarity, SMA(m/f)	\$50.00
PAMTECH KYG1014 WR42 Junction Circulator, 18.0-26.5 GHz	\$250.00
SONOMA SCIENTIFIC 21A3 WR42 Circulator, 20 dB, 20.6-24.8 GHz	\$75.00
TRG B510 WR22 Direct Reading Attenuator, 0-50 dB, 33-50 GHz	\$1,000.00
TRG B528 WR22 Direct Reading Phase Shifter, 0-360 deg., 33-50 GHz	\$1,250.00
TRG V551 WR15 Frequency Meter, 50-75 GHz	\$600.00
TRG W551 WR10 Frequency Meter, 75-110 GHz	\$750.00
WAVELINE 100080 WR28 Terminated Crossguide Coupler, 30 dB	\$200.00
WEINSCHEL DS109 Double Stub Tuner, 1-13 GHz, N(m/f)	\$150.00
WEINSCHEL DS109LL Double Stub Tuner, 0.2-2.0 GHz, N(m/f)	\$150.00

## COMMUNICATIONS

HP 3780A Pattern Generator / Error Detector, 1 kb/s - 50 Mb/s	\$1,000.00
HP 4935A-001 Transmission Test Set, 20 Hz-110 kHz, battery option	\$700.00
HP 59401A HPIB Bus Analyzer	\$400.00
TEK 1410R NTSC Gen., w/SPG2 sync. generator, TSG7 color bars	\$800.00
TEK 1411R PAL Gen., w/SPG12 sync; TSG11 color bars; TSG13 linearity	\$750.00
TEK 1411R PAL Test Gen., w/SPG12, TSG11, TSG13, TSG15, TSG16	\$1,000.00
TEK 1411R PAL Test Gen., w/SPG12, TSG11, TSG12, TSG13, TSG15, TSG16	\$1,100.00
TEK 1411R-opt.04 PAL Test Gen., w/SPG12, TSG11, TSG13, TSG15, TSG16	\$1,400.00
TEK 147A NTSC Test Signal Generator, with noise test signal	\$800.00
TEK 148 PAL Insertion Test Signal Generator	\$700.00
TEK 520A NTSC Vectorscope	\$750.00
TEK 521A PAL Vectorscope	\$750.00

## MISCELLANEOUS

FLUKE 2180A RTD Digital Thermometer	\$500.00
HP 7090A Measurement Plotting System	\$1,500.00
P.A.R. 5206-95, 98 Two-Phase Lock-in Amp., 2 Hz-100 kHz, GPIB	\$1,500.00
TEK TM5006 5000-series 6-slot Programmable Power Module	\$600.00
TEK TM5014 500-series 4-slot Power Module	\$175.00
TEK TM506 500-series 6-slot Power Module	\$250.00
TEK TM515 500-series 5-slot Traveller Power Module	\$275.00



# TECH FORUM

This is a READER TO READER Column. All questions AND answers will be provided by *Nuts & Volts* readers and are intended to promote the exchange of ideas and provide assistance for solving problems of a technical nature. All questions submitted are subject to editing and will be published on a space available basis if deemed suitable to the publisher. All answers are submitted by readers and **NO GUARANTEES WHATSOEVER** are made by the publisher. The implementation of any answer printed in this column may require varying degrees of technical experience and should only be attempted by qualified individuals. Always use common sense and good judgement!

## QUESTIONS

Send all material to **Nuts & Volts Magazine**, 430 Princeland Court, Corona, CA 91719, OR fax to (909) 371-3052, OR E-Mail to [forum@nutsvolts.com](mailto:forum@nutsvolts.com)

I have a dead Motorola model 19032WNSSD bag phone. It indicates "No Service." Does anybody service these, or have data that might allow me to repair it?

The local cell phone company just sold me a new one, calling it unrepairable.

**8991** **David Schoepf**  
**Marianna, FL**

I have an IBM Thinkpad computer. The hard drive is missing and I cannot get into CMOS. Any suggestions how I can tell it that it has no hard drive and boot on a floppy?

Also, where can I find a hard drive?

**8992** **Cliff**  
**Salem, OR**

I have several used Commodore 64 floppy drives, the 1541. I would like to use them for data logging in a standard RS-232 port. Has anyone done this?

**8993** **Gary Depietro**  
**Deltona, FL**

I need a circuit that will operate on 120 VAC and will control up to a 1 hp 120 VAC motor?

Objective: To cycle this motor at any off/on (continuous) interval (selectable in 5 minute increments) up to 60 minutes. (Same time off as on.)

**8994** **Dean Freeland**  
**Stoneville, NC**

I have the LabTec CS-150 stereo computer speakers. I need the headphone plug for one wire to play the tape cassette or portable radio.

I also need another small headphone, this one connected to the right speaker from the left amp speaker. I need three in all.

**8995** **Fran Armijo Jr.**  
**San Antonio, NM**

I have a custom wound 9 VDC motor/generator that when in generation mode, will output up to 5 amps DC.

The purpose of the motor/generator is two-fold: 1) To electric start a small gas engine; 2) after engine kicks over and runs, the motor is now a generator.

While generating power

restores the battery and/or capacitor, and also powers the "running" lights, and/or accessories, the lamps are to be ELs, approximately six-eight panels of various dimension.

Can someone help me with the little data I provided; design a VERY compact, lightweight DC-AC inverter, as flat as possible, and no bigger than a cigarette pack? This is to be worn.

**8996** **William Donald McNeal Jr.**  
**Philadelphia, PA**

I have scrapped out several loads of computer boards and sent them to Denver, CO for the gold in them.

I was told that there is a place somewhere in the US that buys the programmable chips, cleans them up and reuses them.

Do you have any knowledge of a place like this?

**8997** **L. M. Laird**  
**Ogallala, NE**

I have a Pioneer PDR-05 CD recorder which uses only consumer audio blanks. I have seen what appears to be the same machine sold as a Fostex pro-model that uses any (consumer or computer) blanks.

Is there something I can do to the PDR-05 to use it as a pro audio machine?

**8998** **Anonymous**

I need information on how to hook up a "Rustrak" model 288 strip chart recorder. It seems to be operational, but I don't know how to input a signal to it.

A current address for this company (a division of Gulton Industries) would be helpful, too.

**8999** **Richard Flaws**  
**Oswego, IL**

I know it may be a difficult product to locate, but I am in search of a dual socket7 motherboard, as I have two matched P-100 processors, and four matched 32 MB EDO SIMMs.

I would like to locate a motherboard for these items so I can build a small Linux box.

**89910** **David Draper**  
**via Internet**

I have a two-axis accelerometer

that has an output of 2.5 VDC in the level state. In the pitched up state, the output will go to 2.812 VDC. In the pitched down state, the output will go to 2.188 VDC.

This is too small of a voltage swing for me to work with. What I have is a board that takes 0-5 VDC to drive a model air plane servo; 0 VDC full left, 5 VDC full right, and 2.5 VDC at center.

What can I do to increase the voltage swing without changing the 2.5 VDC center? Example: pitch up 3.5 VDC, pitch down 1.5 VDC?

**89911** **David F. Jones**  
**via Internet**

Recently, the 1.35-volt KX-625 battery failed in my Olympus OM-1 camera.

Since mercury batteries are no longer commonly available, I am wondering if anyone knows of an adaptive circuit I could use, perhaps with an externally mounted six- or nine-volt battery?

I am not so worried about appearance as function. (I understand some expensive commercial replacements use short-lived 1.5-volt silver oxide batteries which snap into some sort of voltage reducing circuit.) Any ideas?

**89912** **Allan Souigny**  
**via Internet**

Is there a way to connect a phone hand-set to a computer as to take the place of the microphone and speakers when making an Internet call? Something simple that could be built using RadioShack parts.

**89913** **J. Kato**  
**Naples, FL**

I am interested in experimenting with bio feedback on my computer. I need to monitor blood pressure and heartbeat.

I have seen probes that attach to the finger in hospitals. Would it be possible to create something along that line and interface it to my "O" scope on my computer? How? Where to start looking?

**89914** **Dave Bell**  
**via Internet**

Does anyone have information on some type of very small (size of a

## ANSWER INFO

- Include the question number that appears directly below the question you are responding to.
- Payment of \$25.00 will be sent if your answer is printed.
- In most cases, only one answer per question will be printed.
- Your name, city, state, and E-Mail address, (if submitted by E-Mail), will be printed in the magazine, unless you notify us otherwise with your submission.
- Due to space limitations, we can not reprint the original questions with the answer. The question number and the issue it appeared in are printed above the answer.
- Unanswered questions from a past issue may still be responded to.
- Comments regarding answers printed in this column may be printed in the Reader Feedback section if space allows.

## QUESTION INFO

### TO BE CONSIDERED FOR PUBLICATION

All questions should relate to one or more of the following:

- 1) Circuit Design
- 2) Electronic Theory
- 3) Problem Solving
- 4) Other Similar Topics

### INFORMATION/RESTRICTIONS

- No questions will be accepted that offer equipment for sale or equipment wanted to buy.
- Selected questions will be printed one time on a space available basis.
- Questions may be subject to editing.

### HELPFUL HINTS

- Be brief but include all pertinent information. If no one knows what you're asking, you won't get any response (and we probably won't print it either).
- Write legibly (or type). If we can't read it, we'll throw it away.
- Include your Name, Address and Phone Number. Only your name will be published with the question, but we may need to contact you.

quarter) tracking transmitter that I can build or purchase to track my cat at night?

It should be on all the time and transmit some type of tone or beep that I can track with a small handheld directional radio. The range needs to be only 500 to 1,000 feet.

**89915** **Vernon Miller**  
**via Internet**

I have Caller ID, and there are a few callers that display Private or Out of Area. Most of those blocked calls are people trying to sell me



# TECH FORUM

## ANSWERS TO #59912 - MAY 1999

*I need help to find a distributor for a stepper motor driver IC and other ICs for stepper motors.*

**#1** The SAA1027 by Signetics is an alternative stepper motor driver IC. I obtained mine through **Quality Kits**, Kingston Ontario, Canada [www.qkits.com](http://www.qkits.com).

As an alternative, you might consider purchasing a kit, such as the Velleman K8005 stepper motor driver board. Information and purchasing can be obtained through Quality Kits, or through any Velleman distributor in the U.S.

**Eric North**  
Kingston, Ontario, Canada

**#2** There are not many distributors or manufacturers of stepper motor ICs, because unfortunately, many of these parts are rapidly becoming obsolete. This is due in part to the introduction of specialized motion ICs and the ability of low-cost micro-controllers to emulate the functions of these chips.

I have needed to use these parts myself to control both Unipolar and Bipolar stepper motors for robotic's projects. I appreciated the convenience of having only three control lines: STEP, DIRECTION, and BRAKE, to use a micro-controller to drive a stepper motor, thus saving many lines of code in the micro-controller software.

In your question to *Nuts & Volts*, the stepper motor power requirement, the type of stepper motor (Unipolar or Bipolar), and the precision and resolution was not specified for your application. This information is critical to determine the correct IC or PLD to use.

For example, if your application requires simple single-axis positioning or low-speed rotation of a gear or platform, then a Unipolar stepper motor chip such as the UCN5804 would be most appropriate for your application. For applications that require more torque or high speed, then a Bipolar stepper motor IC or "H-Bridge" should be used.

To control a stepper motor with increased resolution, the IC must be able to support half-step, as well as full-step control modes.

Finally, if your application requires high speed, precision positioning for robotics, multi-axis control, factory automation, and CNC applications, or all of the above, then you may need a more expensive motion IC or PLD with an encoder or tachometer feedback attached to your stepper motor.

These extra features are needed to perform closed-loop control of the stepper motor using velocity or acceleration profiles.

For driving high-current stepper motors, a power high-voltage high-current Darlington array, such as the ULN2803, can be added to the outputs of a stepper motor controller IC, to handle the large currents.

The use of clamping diodes or opto-isolation between the micro-controller and the stepper motor controller IC driver lines is required if the IC does not provide this protection; otherwise the micro-controller might sustain damage from "back" EMF caused by the collapse of stepper motor coil magnetic fields.

A new stepper motor controller IC which I find particularly interesting is the EDE1200 from E-Lab Digital Engineering, Inc. In addition to the stepper motor controller IC functions, this chip supports a self-clocking "RUN" mode.

E-Lab also sells a Power

Transistor Kit (for use with motors which draw up to 10A (75W) per phase). I have not tried using this IC, since I only just discovered it during my latest survey, but its specs and price are similar to the UCN5804.

My latest research using the Web and reading data books on various types of stepper motor ICs, reveal the following sources, including part number, company name, and URL (if any). These are listed below for your convenience:

List of stepper motor controller IC sources:

### UNIPOLAR ICs:

**MicroSystems** UCN5804, Allegro [www.allegromicro.com/control/partnum1.htm](http://www.allegromicro.com/control/partnum1.htm)  
**Motorola** SAA1042 [www.newark.com](http://www.newark.com)  
**E-Lab Digital Engineering, Inc.**, PDB3517/1 [www.elabinc.com/ede1200.htm](http://www.elabinc.com/ede1200.htm)  
**ERICSSON** [www.ericsson.se/microe/pdf/Industri/3517.pdf](http://www.ericsson.se/microe/pdf/Industri/3517.pdf)

### BIPOLAR ICs:

**L297 ST Microelectronics** [sbtm.yonsei.ac.kr/data/1334.pdf](http://sbtm.yonsei.ac.kr/data/1334.pdf)  
**L297D ST Microelectronics** [sbtm.yonsei.ac.kr/data/1334.pdf](http://sbtm.yonsei.ac.kr/data/1334.pdf)  
**L298 ST Microelectronics** [sbtm.yonsei.ac.kr/data/1334.pdf](http://sbtm.yonsei.ac.kr/data/1334.pdf)  
**LMD18200 National Semiconductor** [wirz.com/motor/lmd18200.html](http://wirz.com/motor/lmd18200.html)  
**PBL3717/2 ERICSSON** [www.ericsson.se/microe/pdf/Industri/3717\\_2.pdf](http://www.ericsson.se/microe/pdf/Industri/3717_2.pdf)

### MOTION CONTROL ICs:

**MCX305 (single-axis) Auretek** [www.robot.com.tw/mcx305.htm](http://www.robot.com.tw/mcx305.htm)  
**MCX314 (multi-axis) Auretek** [www.robot.com.tw/mcx314.htm](http://www.robot.com.tw/mcx314.htm)

**Daniel F. Ramirez**  
Amherst, NH

**#3** There are two stepper motor controller ICs manufactured by E-Lab and available from **All Electronics Corp.** <http://www.allcorp.com> for \$8.30 each.

The EDE1200 is for six-wire unipolar stepper motors and the EDE1204 is for four-wire bipolar

stepper motors.

These are 5 VDC, 18-pin ICs designed to interface a logic-level signal to a stepper motor and can be self-clocked in the RUN mode or external-clocked in the STEP mode. Capable of half-stepping, directional control, continuous run and stepping rate changes while the motor is stepping.

The inputs are TTL/CMOS with TTL level outputs. Specifications and hook-up diagrams are included with the ICs.

You can contact All Electronics Corp. at the above listed Web URL, or via E-Mail at: [allcorp@allcorp.com](mailto:allcorp@allcorp.com). Mailing address: **All Electronics Corp., P.O. Box 567, Van Nuys, CA 91408-0567.**

I have done business with this company in the past and recommend them.

**Robert Turner**  
Via Internet

**#4** The Hewlett Packard HCTL-1100 is a decent general-purpose controller, available through Newark Electronics and a host of other distributors that carry HP stuff. HP also makes some other related items, including incremental encoders and quadrature decoder/counter chips.

National Semiconductor and Allegro both make some nice chips for power applications, like motor control.

The following web sites are for distributors that carry motor control chips of some sort or another:

**Mouser Electronics:** [www.mouser.com](http://www.mouser.com)  
**Digi-Key:** [www.digikey.com](http://www.digikey.com)  
**Newark Electronics:** [www.newark.com](http://www.newark.com)  
**Allied Electronics:** [www.allied.avnet.com](http://www.allied.avnet.com)

**Mark Dobrosielski**  
Bradford, MA

**#5** Unitrode Corp. makes three stepper motor control ICs, which are the UC1517, UC1717, and the UC3717 (10V-45V).


They might have other types available since I discovered these in the 1994 IC master.

The contact information for Unitrode Corp. is: **Unitrode Integrated Circuits Corp., 7 Continental Blvd., Merimack, NH 03054-0399. Phone: 603-424-2410 fax: 603-424-3460.**

**Dennis Gifford**  
Henagar, AL
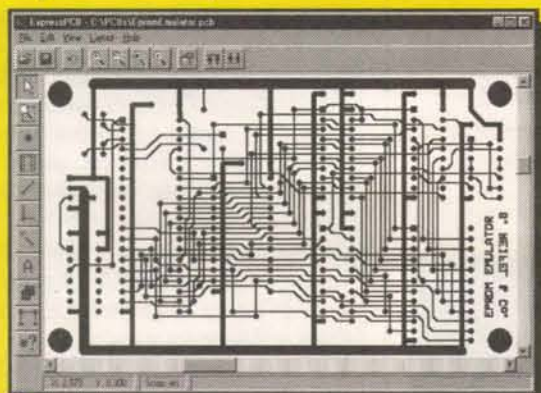
## PCB LAYOUT Software For Win95 - FREE

- 1 Download our board layout software
- 2 Design your 2 sided plated-through PCB
- 3 Send us your layout over the Internet
- 4 In 2-3 business days, UPS delivers your boards, often under \$100



[www.expresspcb.com](http://www.expresspcb.com)

## PIC'n Books

### LEARN ABOUT PIC MICROCONTROLLERS

**EASY PIC'n - Beginner** \$29.95  
**PIC'n Up The Pace - Intermediate** \$34.95

## NEW!

**PIC'n Techniques - Intermediate** \$34.95  
• 8-pin PICs  
• Timer 1, timer 2 and the capture/compare/PWM (CCP) module  
• Talking to a PIC with a PC using a terminal program  
• Test equipment and data logger experiments

See Table Of Contents: <http://www.sq-1.com>  
Secure Online Ordering is Available

+ \$4 s/h in US for 1 book, \$5 for 2 books, \$6 for 3 books  
VISA, MC, AMEX, MO, Check  
CA residents please add 7.25% CA sales tax  
PIC and MPLAB are trademarks of Microchip Technology Inc.

**SQUARE 1 ELECTRONICS**

P.O. Box 501, Kelseyville, CA 95451  
Voice (707) 279-8881 FAX (707) 279-8883  
<http://www.sq-1.com>  
E-Mail [sqone@pacific.net](mailto:sqone@pacific.net)



# SUPERCIRCUITS

America's #1 Microvideo Source

**AMAZING!**  
**MICRO VIDEO TOP 10**  
**OVER 120 NEW VIDEO PRODUCTS!**

1. World's Smallest Video Camera\* ..... 1 lux, .3oz. \$59.95
2. Pinhole Video Camera..... 410 lines, 0.5 lux, Sharp chip \$39.95
3. Color Video Camera ..... 350 lines, 2 lux, Remote head \$69.95
4. Live Aerial Video R/C Videotape..... How to & more \$24.95
5. Wireless Covert Tape Cam ..... 300' range, FCC OK \$349.95
6. Super Tiny Color Pinhole.... 350 lines, less than 1" sq. \$99.95
7. Micro Video Transmitter..... 1000' range, ATV band \$159.95
8. Complete Wireless ATV Video Set ... 3 Miles Range \$419.95
9. World's Smallest Wireless Video Cam..... Please Call
10. Video Goggles ..... Dual hi-res LCD's, 3D capable \$599.95



Buy your microvideo equipment where NASA, The Air Force, JPL, Lawrence Livermore Labs and the FBI does. Call us today.

For the best in high performance microvideo equipment, call the experts at Supercircuits. We've grown to be America's microvideo leader by consistently offering the best equipment at the lowest prices, with unbeatable service...compare our plug 'n play ease of use, warranties and return policies. Of course, Supercircuits microvideo is used by some of the biggest names in science, industry and national defense. But with prices starting at under \$40 for tiny high resolution video cameras, it is technology that is as affordable as it is amazing. Call us today, and get our free 72 page Microvideo Catalog, loaded with photos, specs and more.

Listed In Guinness Book of Records\*

1-800-335-9777 ext NV

Or fax us at 512-260-0444

One Supercircuits Plaza Leander, TX 78641

www.supercircuits.com

\*Supercircuits PC-21XP and PC-51XS are listed as world's smallest pinhole and spy video cameras

Write in 81 on Reader Service Card.

**Metric**  
Equipment Sales, Inc.

800-432-3424

Fax: 510-264-0886

www.metricsales.com

**RENT • BUY • SELL**  
Yes, we will buy your surplus equipment!

Scopes, Meters, Analyzers, Power Supplies, Signal Generators, Counters, Recorders and more

Hewlett-Packard, Tektronix, Fluke, Dranetz, TTC, Anritsu, Wavetek, Keithley, and more

**Test & Measurement Instruments**

Over 7000 Models • 6-Month Warranty

Save 30-90% • 5-Day Free Trial

## TECH FORUM

something.

There are times that my work, or family living outside my area are trying to call me. That's when it would be nice to know it's them and not listen to those telemarketers.

Now I know that it is possible to get the caller info even though it's blocked or out of the area. I was told the 911 operator and Police can see it along with many government agencies.

How can I see it? Can I modify an existing unit to show all call information? Is it possible to build a device to be used with the Caller ID unit? Where can I find more information on the Caller ID system?

89916

Joe Reed  
Charlotte, NC

I have an Apollo inkjet printer. I keep getting an error message that says "out of paper." I have tried quite a few different things, but I can't get this thing to print on a 486 running Windows 95.

89917

Lou Baugh  
via Internet

I have a Dentron linear amplifier that is no longer in production. I fixed the problem that caused arcing between the plates of the variable capacitor, but they keep arcing. I tried to file them smooth, but they still arc, so I tried looking for another variable capacitor, to no avail.

Can you please lead me to a supplier of this Dentron variable capacitor #D-232-45?

It measures about 15-250 pF and is approximately 3" long (not including the shaft), about 2-1/2" wide, and 2- 3/4" high. I must assume that this was a stock item that Dentron used, but I can't find a source for this size and capacity.

89918

Ken Weger  
Colfax, CA

## ANSWERS

### ANSWERS TO #6995 - JUNE 1999

I need a computer program that enables me to make a polar map (a great circle map) with any GTH being the center.

#1 I wrote a BASIC program in 1978 for the TRS-80 Model I that calculates direction and distance along a Great Circle between any two points on earth, using the spherical trigonometry I learned as a Navy fighter pilot. It has been published in several magazines, and has been updated to run in IBM BASIC, QuickBASIC, or QBASIC. I even have an EXE file to run from DOS. I do not have a Windows version.

Contact me at 818-346-7024 9am-5pm pacific time, or at fblechman@juno.com to receive a copy of the program, variously called "DX Beam Aimer," "Long-Distance

### ANS. TO #W69914 - JUNE 1999

I have a CGA monitor that I would like to turn into a parts tester. There are several testers that tie to an oscilloscope and do this job, using horizontal and vertical deflection. Has anyone ever designed one of these circuits?

It is not very practical to turn a CGA monitor into an "oscilloscope" with X-Y deflection. A CGA monitor — like a television — is a raster scanning device. The electron beam covers the screen by scanning at a high rate (15750 Hz) left to right, and at a slower rate (60 Hz) top to bottom.

It is practically impossible to drive the deflection with another signal because of the way the CRT is powered.

The CRT requires a high voltage to light the screen. The high voltage is generated by the inductive energy from the horizontal deflection. Basically, the energy that is used to deflect the electron beam across the screen is "recycled" during the retrace.

A flyback transformer takes the magnetic energy in the deflection yoke (that is released as the beam "flies back"), and converts it to tens of thousands of volts of electrical energy.

If you disable the horizontal scanning in order to drive the X-Y deflection yoke directly, you lose the high voltage, and the tube goes black. There are ways around this, but they usually end up costing a lot more than the results you get are worth. And, of course, if you don't know exactly what you are doing, you could contact some of that high voltage and really hurt yourself.

I would recommend that you find a used oscilloscope for a parts tester. Really old models with very low bandwidth will work fine for a curve tracer.

Tim Godfrey  
Via Internet

Navigator," or "Great Circle Program."

Fred Blechman  
West Hills, CA

#2 Byte Magazine, June '79, has an article and BASIC programs for generating several varieties of maps, and it includes an azimuthal equidistant projection.

Unfortunately, I have lost the rest of the citation, and cannot tell you the author or the title. I found the article when looking for information about satellite tracking.

The article's code computes projections, but it does not include a map database (although it does give some pointers about where to obtain some).

Gerald Roylance  
Mountain View, CA



# TECH FORUM

## ANSWER TO #7994 - JULY 1999

I need to set up a remote, wireless, video cam surveillance system. Where can I find instructions on doing so? Including the set up, specific parts that would be needed, and an explanation of the various terms and jargon i.e., "410 lines CCD, 0.3 lux, AGC, 4mm 78 FOV lens."

The jargon that you seek on CCD cameras is as follows; 410 lines refers to the scan lines of the camera.

The standard TV set in the US has 480 lines of scan from top to bottom, 60 times per second, which makes up the picture that you see.

The way to think of this would be analogous to a page in a book that starts at the top right, and letter after letter is typed on that line until one line is full. Then the next line is started and filled until the entire page is full.

In the camera that you mention, there are 410 lines that make up a single page instead of the 480 that make up a standard TV picture.

What they are saying about the camera, is that its page is smaller and contains less information per page than on a standard TV set. Less information means lower quality in the picture, commonly referred to as resolution.

## ANSWER TO #6993 - JUNE 1999

Recently, I committed to creating a buzzer and contestant identification light set-up for my high school debate club to use during competitions. I need help with the circuit design for this purpose.

This circuit operates as follows: Closing the reset switch sets the Q outputs of all the flip flops high, which causes the '08 output to go low. When a contestant closes a switch, the '32 output goes low making the '08 output high, which inhibits any other contestant's switch from having an effect.


The inverted Q output drives an LED through a NPN emitter follower.

If you want a brighter light, put a relay in place of the resistor and LED, and light an AC lamp.

The 555 timer energizes the relay for two seconds to operate the buzzer. The timer output could drive a small buzzer — like 273-054 — but the relay will drive a really loud one.

The logic VCC is five volts, but the 555 requires seven volts minimum to drive the five-volt relay. If the 555 supply voltage is too high, it may not trigger. I used a '00 gate to invert the trigger signal, but any inverting gate will do.

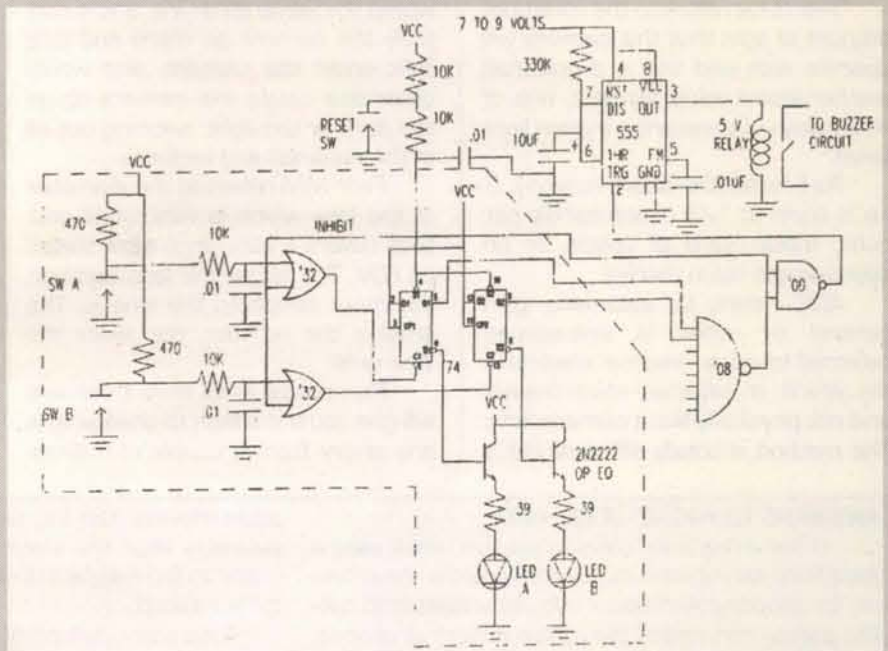I have shown only two contestant's switch inputs to save space. Repeat the circuit in the dashed lines four times to fill the '08 inputs and



complete the circuit.

The 10K resistor and .01uF capacitor at the '32 input is to prevent noise from causing false triggers and protects from static damage. The circuit will not work with TTL logic, but the type specified is CMOS.

PART	RADIO Shack
470 ohms	271-1317
10K ohms	271-1335
33 ohms	271-1104
330K ohms	RSU-11345352

.01 uF	272-131
10 uF	272-1025
LED	276-086
Switch	275-1566
5V relay	275-243
LM555	276-1723
74HC00	276-2801
76HCT08	276-2805
74HCT32	276-2813
74HCT74	276-2816
2N-NPN	276-2058

Russell Kincaid  
Milford, NH

## MICRO VIDEO CAMERAS



**MB-650PA** - \$139.95  
2.8mm Pinhole Lens.



**MB-650UA** - \$129.95  
4.3mm Micro. Lens




**MB-750P** - \$129.95  
2.8mm Pinhole Lens.




**MB-750U** - \$119.95  
4.3mm Micro. Lens

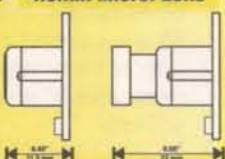**MB-650a Series**  
• Built-In Audio  
• 1.18" sq.  
• 380 TV Line



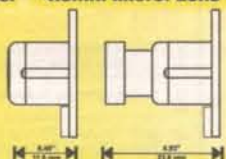**MB-750 Series**  
• 1.25" sq.  
• 420 TV Line



The Best, Smallest, Micro Cameras on the Market Today!  
Call and Compare! We Match or Beat All Prices!

## Panasonic Color Camera Sale



**MB-45cB** - \$99.95

Size: 1.25 x 1.25 sq. w/ Footprint

### Micro Color MB-45cB: \$99.95

- Wide Voltage Range, 5-14 Volts!
- Small Footprint!
- Self contained ultra small package design for various applications.
- MCM PCB design for minimizing the size and improve durability.

### Specifications: MB-45cB Color Camera

Pick-up device	1/4" Interline transfer
Effective Pixels	512 (H) x 496 (V)
Scanning System	2:1 Interlace
	525 lines - 60 fields
Frame per second	30 frames
Synchronization	Internal
Video output	VBS, 1vpp 75 Ohms
Horizontal Res.	More than 330 lines
AGC	On fixed
White Balance	ATW fixed
Operating Temperature	32°F to 104°F
Ambient conditions	Indoors
Lens	F2.8 Hor. Angle 45° - Ver. Angle 34°

## WIRELESS VIDEO

Compatible with  
AC or Battery

Wireless 4-Channel B/W &  
COLOR Cameras Available!



**GFT-1001** \$189.95  
Gives any camera the  
ability to be Wireless.

Wireless Observation System's  
GFS-1001 (900MHz) - \$499.95  
GFS-1001c (900MHz) - \$599.95  
(900, 1.2 & 2.4 Ghz  
systems available.)



Visit Polaris Ind. Web Site at:  
<http://www.polarisusa.com>

**1-800-752-3571**

**Polaris Industries** 470 Armour Drive NE • Atlanta GA 30324 • Tech Info: 404-872-0722 • FAX 404-872-1038

Write in 79 on Reader Service Card.

## Our Smallest Video Camera



**CMOS Camera**  
**CM-550u** - \$69.95

**Pin Hole Camera:**  
**CM-550p** - \$69.95



## LIPSTICK CAMERAS

These cameras are supplied with a PCM-1 Video/Power cable. The BNC connection is for standard video connection to a Monitor or VCR.



**LP-850p**  
\$139.95

Length: 1.37"  
Diameter: .87"

**LP-850i**  
\$129.95

Length: 1.9"  
Diameter: .91"



Prices, availability and specifications are subject to change without notice. Shipping and Handling are not included with price.



# TECH FORUM

The .3 lux refers to the minimum amount of light that this camera will operate with and this is a universal mathematical value for light, one of many ways of measuring a given light value.

As I recall (the short version), .3 lux is equal to 1/3 of one candle per cubic meter/yard of space, or an approximate value thereof.

AGC refers to automatic gain control or what is sometimes referred to as an internal electronic iris which is adjusted electronically and not physically like a camera lens. The method is totally different but it

works the same as an iris, and it controls the camera as more and less light enter the camera, and would otherwise cause the camera to go too dark or too light, washing out all of the contrast and features.

Four MM refers to the diameter of the lens which is very small and, thus covers a very large view, stated as FOV. The larger the lens number, the more telephoto the lens is. The smaller the number, the wider the view gets.

Purchasing a "C" mount camera will give you the option to change lens any where from a couple of millime-

ters to several thousands millimeters, which means that you can use the camera for astronomy, as well as house surveillance.

Seventy eight FOV refers to 78 degrees, field of view, which simply means that the camera can see from left to right and top to bottom, a view that is 78 degrees wide. This is generally referred to as a "wide angle lens."

As to the wireless transmission, the best way is to purchase a microwave transmitter which sends the signal down a 900 MHz or 2.4 GHz signal and gives you up to 1,000'

of distance. They come in several versions that can handle one or more cameras at a time. They are reasonably priced and are available through advertiser's in *Nuts & Volts*.

The alternative is to build one, but working with microwave isn't recommended for the beginner.

Chris  
Bieber, CA

## ANSWERS TO #6996 - JUNE 1999

I need an inexpensive device to register the frequency of a PTO driven generator, so I can adjust the

Continued on page 92

## ANSWERS TO #6992 - JUNE 1999

I have a "big dish" satellite system which uses a feed horn polarization motor that rotates the antenna for proper polarization. I do not understand how the pulses can rotate the motor in both directions, and also how the receiver determines just what the angle is. There doesn't seem to be any feedback from the motor shaft location to the receiver.

#1 The "polarity motor" is, in fact, a "servo motor" that many RC enthusiasts use to control their airplanes, cars, and what not ...

In general, a squarewave signal is applied with a specific duty cycle to place the motor between the extremes of  $\pm 90^\circ$ .

The duty cycle range is approximately 10% to 90% (varies slightly per manufacturer).

Oddly, there is no feedback given to the source of the pulses. Not exactly a "servo loop," right?

The servo-loop is internal to the motor assembly. The source of the control signal (your receiver) simply applies pulses over enough time to assure the motor positions itself where it's supposed to be (despite where it is currently).

The duty cycle when filtered, represents a DC voltage that is compared to a feedback potentiometer. When the two signals are equal, the motor

stops moving. The DC motor inside drives a gear assembly that translates so many turns of the motor to the number of degrees, the antenna "pick-up" is rotated.

A common failure of a servo motor is "wear-out" where "backlash" from the potentiometer, the gears, even the housing contribute to the inability of the servo to settle into position. An oscillation results.

This can be tested by attaching the servo to the satellite receiver where it can be watched: Single-step the polarity adjustment slowly. Every third or fourth time, reverse direction for only one step, then resume until the end is reached. Repeat in the opposite direction. If, at any time, the servo appears to be "shaking its head NO!" the servo is bad.

Note that the feedback potentiometer is a very small Japanese or Korean model that is not easily found. I have no idea where you can obtain the gears or housings. If it is mechanically sloppy, just get a new one.

Don't confuse random movement with oscillation. Sometimes, strong RFI from a nearby radio station causes random "drift" from where the servo is supposed to be positioned. The reason it does this is because no pulse train is present.

Manufacturers of satellite receivers depended

on the fact that the servo-motor had plenty of gears (with friction) that would tend to hold the polarity pick-up in position. Unfortunately, because the servo motors are made as cheaply as possible, they are not shielded. Some manufacturers wised up.

To compensate, they supply either a constant stream of pulses or pulses every 10 to 20 seconds to keep the servo "refreshed." You can check this by replacing the servo with an LED and a 200- to 300-ohm resistor in series across the polarity signal and GND.

If you determine that your receiver is not sending pulses as described above, obtain a Chaparral "Polarotor" from the Electronic Goldmine surplus house in Arizona. This device doesn't depend on a CPU to update the polarity. It's a simple multivibrator circuit that operates at the correct frequency. (You'll have to adjust the polarity of every station manually, however.) Make sure you are getting the "servo controller," NOT the "ferrite controller!"

If the servo doesn't move at all, check your connections. Chances are that a fragment of wire trapped in the receiver's "polarity" connector is obstructing a good connection. Then, there's the possibility that the DC motor inside the unit is fried because of an electrical storm or spikes on the AC power source ... [The "Polarotor" would make a good test signal source without having to construct the whole thing!]

Before you try to test the device on a bench, you must really be sure you're matching the device to its environment. If your receiver doesn't send pulses regularly, the bench test is meaningless. And, all grommets should seal out moisture and spiders!

Matthew T. Allen  
Santa Clara, CA

#2 The motor sounds like a typical servo motor such as used in RC planes. The motor angle is controlled by pulse width modulation setting the angle.

The motor has its own internal feedback loop to keep it in position. So, the main receiver only needs to send the correct pulse width and be assured of its angle without a feedback loop to it.

To build a test rig, I don't remember where I saw the schematic, but you can build a pulse width generator by using a 555 timer and some parts. Look under RC servos for info, other circuits should exist.

Tony Gonzalez  
Gardena, CA

## AMAZING PRODUCTS!

BOX 716 AMHERST, N.H. 03031

## INFORMATION

UNLIMITED adn6990

VISIT OUR "ACTION" WEB SITE@  
<http://www.amazing1.com>

### Laser Window Listener

Access Internal Sounds Via A Beam Of Light!!

Remarkably simple concept uses a beam of laser light to illuminate a window acting as a microphone vibrating to the sounds and reflecting back to a sensitive filtered optical receiver that now reproduces this modulated light back into the actual sounds as heard thru a set of headphones.

LWB9 Plans for Three Complete Systems.....\$20.00

Complete System for Demonstration of Concept

LWB60 Demo System with 5mw VisRed Laser..\$159.95

Below Electronics for Two High Performance Infra Red Systems Shown Built From Above LWB9 Assembly Plans

LLR40 Optical Receiver/Processor.....\$199.95

CWL10 10 mw Infra Red Class IIIB Laser.....\$149.95

### PLASMA FIRE SABERS

All New Duplicate the Effect Used in the SCI-FI Motion Picture Epic of the Century!!

Visit our web site at [amazing1.com](http://amazing1.com) and see many Plasma Fire Saber Devices Ready to Use Sabers Parts and Accessories

\*Patented effect by Robert Iannini

Visual plasma field is controlled by grip pressure and adjusts saber length. No switches are used.

Active energy field produces weird and bizarre effects.

Specify available colors of Photon Blue, Neon Red, Starfire Purple, and Phaser Green.

PFS36K Kit of 36" Active Length....\$79.95

Please add \$20.00 for special handling of above

PFS26K Kit of 26" Active Length....\$59.95

Please add \$10.00 for special handling of above

PFS16K Kit of 15" Active Length....\$29.95

### FM Transmitter Kits

- 1 Super Sensitive Ultra Clear 1 Mile+ Voice Transmitter
- 2 1 Mile+ Phone Transmitter
- 3 Line Powered Phone Transmitter Never Needs Batteries!
- 4 Tracking/Homing Beacon "Beeping Transmitter"
- 5 Video/Audio Rebroadcaster+1 Mile
- 6 TV/FM Radio Disrupter Neat Prank!!! Discretion Required

Includes Tricks Using Wireless Devices

COMBOX Above 6 Kits/Plans...\$59.95

COMBOP Above 6 Plans Only..\$10.00

### Kinetic Electric Gun

Pioneer a Futuristic Weapon

500 Joules Energy Storage Constant Current Charging Triggered Spark Switch Ballistic Velocities Handheld, Battery Operated Labeled "Dangerous Product"

EGUN1 Plans.....\$20.00

All Parts are Individually Available

### 250 KV Tesla Coil

10-14" Explosive Bolts of Lightning! Transmits Energy, Ion Motors Anti Gravity, Size - 20"H x 8" Square Weight - 25 Pounds Input - 115 VAC/2Amps See in "Action" on web [www.amazing1.com](http://www.amazing1.com)

BTC3 Plans.....\$15.00

BTC3K Kit/Plans.....\$349.95

BTC30 Ready to Use.....\$449.95

BTC4 Plans 30" Sparks.....\$20.00

### Ion Ray Gun

Projects Energy

Star Wars Technology Demonstrates Weapons Potential, Force Fields, IonMotors, Antigravity etc. Projects electric shocks without contact! Conduct many weird and bizarre experiments

IOG7/9 Plans.....\$10.00

IOG7K Kit/Plans.....\$99.95

IOG70 Assembled/Testing.....\$149.95

Higher Powered Device

IOG9K Kit/Plans.....\$129.95

IOG90 Assembled/Testing.....\$199.95

### Gravity Generator

Demonstrates a unique phenomena of electrical reactions that produce the effect of "anti-gravity". You build a small mock space ship from simple materials and use our power supply for energizing. Excellent demonstration of a fascinating method of levitation.

GRA3 Plans with Book.....\$20.00

GRA3K Pwr Sup Kit/Plans/Book.....\$99.95

GRA30 Assembled with Book.....\$149.95

### Shock Force Field Vehicle Object Electrifier

Hand shock balls, wands. Mini circuit is easily hidden Great payback for those wise guys.

SHK1K Kit/Plans.....\$19.95

### Attention

High Voltage Experimenters Battery Powered Mini Sized Modules For Research In: Hovercraft, Ion Guns, Force Fields, Shockers Etc.

MINIMAX4 4KV@10ma.....\$19.95

### 500,000 VOLTS!

SIZZLER Produces Explosive Stunning and Stopping Power Intimidatingly Effective to 20'

SIZZ500 Complete..\$79.95


1 800 221 1705 Orders Only! Fax 1 603 672 5406 Information 1 603 673 6493 Free Catalog on Request

Pay by MC,VISA,Cash, Check, MO, COD. Please Add \$5.00 S&H plus \$5.00 if COD. Overseas Please Contact for Proforma


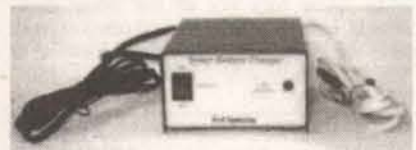
## HAM GEAR FOR SALE

**WANTED: ROCKWELL**-Collins HF-80 equipment, 851S-1, 237B-3 log periodic, Collins literature. Jim Stitzinger 805-259-2011, 805-259-3830 (fax), bfl-jfs@smartlink.net



**THE SMART BATTERY CHARGER** for lead acid or gel cell batteries. Can be left connected to the battery **INDEFINITELY**, will not overcharge! Standard kit is 12V @ 1 amp. This kit is 100% complete. For the kit order #150-KIT at \$59.95. For an assembled and tested unit, order #150-ASY at \$79.95. CA residents add 7.75% sales tax. Add \$6.50 per unit shipping. MC/VISA accepted. A&A Engineering, 2521 W. La Palma #K, Anaheim, CA 92801. 714-952-2114, FAX 714-952-3280.

**NEW PRODUCTS FROM S & S: UPGRADE YOUR OLD RIGS!** Digital dial (counter) has 10Hz resolution HF, 100Hz VHF and frequency range 50KHz to 230MHz; kit \$99.95; assembled \$149.95. **NEW Digital VFO** with 1Hz resolution to 54MHz; kit \$169.95; assembled \$219.95. S&H \$7 (Continental US). **GUARANTEED TO WORK.** For info send **SASE.** Call/write to order: S & S Engineering, 14102 Brown Rd., Smithsburg, MD 21783. 301-416-0661, E-Mail: N3SAD@aol.com or see <http://www.xmetric.com/sseng>

**FOR SALE: ORBIT 360** antenna rotator. Full instructions. Never used, \$40 obo. 949-494-0072.

**GENERAL COVERAGE** HF receivers. G133F (Collins 51S1 with LTV aircraft panel), overhauled and calibrated, \$1,100. Like new LOWE HF-235, \$700. Also nice Drake R4A, \$250. U ship, 10 DRP. Call Art @ 814-861-6904 or E-Mail: ahogrefe@statecollege.com

**GRAND OPENING special:** FREE Internet auctions! Buy and sell around the world in an on-line auction dedicated to amateur radio and related electronic equipment. Commercial businesses are welcome to participate as well as inquire about banner ads. [www.HamRadioAuction.com](http://www.HamRadioAuction.com) GearHead Electronics, 716-636-4370 fax: 716-636-4808 administrator@HamRadioAuction.com

## HAM GEAR WANTED

## CB - SCANNERS

**SALES & SERVICE:** CB equipment, modification kits, meters, antennas, mics, radios, transistors, repairs & hard-to-find items. Complete list \$4. D&R Electronics, 10 Park St., Thomaston, CT 06787. 860-283-9492 or RTed821836@aol.com

**CB MODIFICATIONS!** Frequencies, books, kits, high-performance accessories, plans, repairs, amplifiers, 10-meter conversions. The best since 1976! Catalog \$3. CBCI, Box 1898NV, Monterey, CA 93942. [www.cbciintl.com](http://www.cbciintl.com)

**KONNEX DISTRIBUTING.** Call 1-888-777-7874. PO Box 451372, Los Angeles, CA 90045. CBs, antennas, meters, transistors. Best prices. Credit card acceptable.

**240+ CHANNEL CB/HAM/COMMERCIAL** radios: AM/FM/SSB/CW export/domestic: RCI, Motorola, Uniden, Cobra, Alinco, Kenwood. Mics, antennas, linears, meters, books, night scopes, and tons more stuff! Catalog \$3. MAXTECH, Box 8086, New York, NY 10150. 718-547-8244.

**SCANNING USA:** monthly magazine 100% scanning. All the news and product reviews from the writers you trust. Get more from your scanner. Subscriptions \$24.95, samples \$3. Call 1-800-651-0922 your Visa or MasterCard, or write 2054 Hawthorne, Joliet, IL 60435

**MESSANGER, RED** Devil, Shooting Star, Palomar, Superstar, Uniden, CB radios, microphones, exports, Galaxy, etc., more! 5 page picture price sheets \$1 (refundable) scanners too! Galaxy, Box 1202, Akron, OH 44309. Over 15 yrs. in business!

**HALCON COMMUNICATIONS** Wholesale only: Cobra, Uniden, Midland, Galaxy, CTE, Super Star, Kenwood, Yaesu, Icom. Free catalog, Free call 1-800-683-6999.

## MUSIC & ACCESSORIES


## COMPUTER HARDWARE

**COLORADO BACKUP** tape drives, \$35; notebook floppies, \$45; bar code scanners, \$45; thermal wire strippers, \$25; microscopes, \$135. <http://downtown.ala.net/~myoung/flyer.htm> 334-889-4637.

**CANNON INNOVA** book 360 CD laptop computer, bubblejet printer, carry case, like new, \$900, trade ham/test equipment, transistor radios. 904-362-1521, leave message. rmorison@suwanneevalley.net
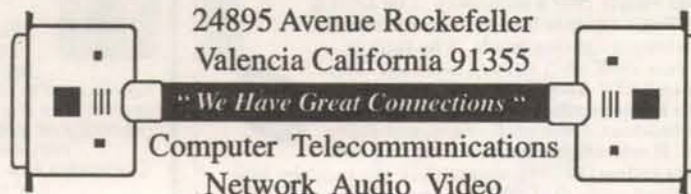
# Roger's Systems Specialist

24895 Avenue Rockefeller  
Valencia California 91355



Computer Telecommunications  
Network Audio Video

[www.rogerssystems.com](http://www.rogerssystems.com)

### Category 5 Patch Cables



TE-068-L5X	7 ft. Crossover	\$2 <sup>00</sup>
TE-068-L5	7 ft. Straight Patch	\$2 <sup>00</sup>
TE-508-L5	50 ft. Straight Patch	\$10 <sup>00</sup>
TE-108-L5	100 ft. Straight Patch	\$20 <sup>00</sup>

### USB Cables

CC-USB-6	6ft. USB "A" to "A" M/M	\$5 <sup>00</sup>
CC-USB-AB6	6ft. USB "A" to "B" M/M	\$5 <sup>00</sup>
CC-USB-PP	6ft. USB to IEEE Printer Cable	\$36 <sup>00</sup>
CC-USB-AB10	10ft. USB "A" to "B" M/M	\$6 <sup>00</sup>
CC-USB-AB15	15ft. USB "A" to "B" M/M	\$8 <sup>00</sup>
CC-USB-X10	10ft. USB Extension	\$6 <sup>00</sup>



### USB Accessories

CC-USB-8	USB (2) to 2x8 pin w/ Bracket	\$5 <sup>00</sup>
CC-USB-9	USB (2) to 2x5 pin w/ Bracket	\$5 <sup>00</sup>
USB-PCI	USB x2 PCI Add on Card	\$27 <sup>00</sup>
USB-KB-104	USB 104-Key Kybrd Win98/PS2	\$24 <sup>00</sup>
USB-MOUSE	3-Button USB Mouse 4200dpi	\$12 <sup>00</sup>
USB-CAM	C-IT USB Cam w/ Software	\$69 <sup>00</sup>



### Clip/Stick-on Lapel Microphone



3.5 MM PLUG  
6 FT. CORD


TM-MIC-2

\$1<sup>00</sup>

### Network Cards



NT-TBT-10	10-Base 16Bit ISA Slot Card	\$12 <sup>00</sup>
NT-TBT-100	10/100 32-Bit PCI Slot	\$19 <sup>00</sup>
NT-TBT-200	10-Base 32-Bit PCI Slot	\$12 <sup>00</sup>
NT-TBT-3C905B	3COM 3C905B-TX 10/100 PCI	\$62 <sup>50</sup>

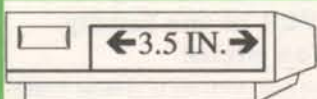

### External SCSI Case

TM-CASE-HDS \$15<sup>00</sup>

Limited to stock on hand


50 Pin centronics pass through connector  
Push button I.D. setting, On/Off switch  
Internal Fan, 50P Ribbon, 30watt Power Supply

## Mice

TM-290	3-Button Serial DB9	\$6 <sup>00</sup>
TM-290-2	2-Button Serial DB9	\$6 <sup>00</sup>
TM-290-Mic	Microsoft Mouse OEM	\$25 <sup>50</sup>
TM-290-Net	Designer Netmouse PS/2	\$12 <sup>00</sup>
TM-290-PS	PS/2 2-Button 6-pin Din	\$6 <sup>00</sup>



### Major Brand!!

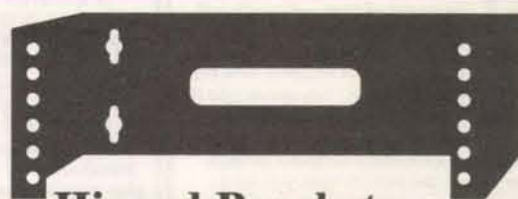


### Hinged Brackets

HB3	19" wide/ 5.25" tall	\$10 <sup>00</sup>
HB4	19" wide/ 7.00" tall	\$11 <sup>00</sup>
HB6	19" wide/ 10.5" tall	\$14 <sup>00</sup>
HB8	19" wide/ 14" tall	\$17 <sup>00</sup>

We'll Beat anyone's price on these Brackets!

For Hubs, Patch Panels, Wire Minders

## Patch Panels

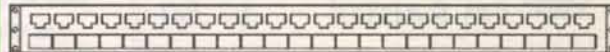

PP-24P-5	24 Port Cat5 Patch Panel	\$59 <sup>00</sup>
PP-48P-5	48 Port Cat5 Patch Panel	\$79 <sup>00</sup> SPECIAL
PP-12P-5	12 Port Cat5 Patch Panel	\$42 <sup>00</sup>
PP-64P-5	64 Port Cat5 Patch Panel	\$255 <sup>00</sup>

All Category 5 568B Wiring

- \$20.00 min. order required
- Add \$4.50 shipping for prepaid orders
- Prices subject to change without notice
- All major credit cards accepted
- Special offers only valid on items in stock
- California residents add tax
- Call for quantity discounts
- No out of state checks accepted

800-366-0579 661-295-5577 Fax 661-295-8777



**WE CARRY** a variety of cables, switch boxes, accessories, and adapters to connect PCs, printers, Mac's, networks, telecommunications, and audio/video equipment. We offer: custom cables, free catalogs, and same day shipping on most orders. Visit our website at [www.rogerssystems.com](http://www.rogerssystems.com) or call 1-800-366-0579.

**COMPAQ PENTIUM** Deskpro \$250. Hard drive liquidation. 420 megabytes \$35. 2.5 gigabyte \$75. 3.2 gigabyte \$89. 8.4 gigabyte \$155. Mouse \$1.95, SVGA monitors \$95, flatbed scanners \$45, 56K modems \$35, 1.2 floppy \$10, Adaptec SCSI controllers \$45, memory 1.00/megabyte. 714-778-0450.

**DEC EQUIPMENT WANTED!!!** We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dialog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

**NewComputer.com!** OVER 50,000 hardware and software products. Orders over \$500 shipped free. Our unique product categories and search features let you quickly locate the item you're looking for. The next time you need computer equipment, try NewComputer.com


**EVERYTHING NEW** w/warranty! MII 333MHz \$165, 15"/17" SVGA monitors \$135/215. Pentium systems from \$250. Also multimedia kits, hard drives, scanners, printers, SCSI adapters \$45. Memory, cases, etc. Call for monthly specials. CCI 714-778-0450. E-Mail: [cci@net999.com](mailto:cci@net999.com)

**NEW EXTERNAL SCSI CD-recorder kit** with Adaptec card and software \$135, includes 11 pcs. of medial New 4meg PCI video card (ATI clone) \$25. There are other deals too! For all the latest dealsheets E-Mail: [dealsheets@utwe.com](mailto:dealsheets@utwe.com) or call 626-930-1121 (10am-5pm Pacific) or fax 626-930-1123. E-Mail: [sales@utwe.com](mailto:sales@utwe.com)

**LOOKING FOR cheap clone PC parts that actually work?** Call UTWE for CD-ROMs, hard drives, disk controllers, video cards, mainboards CPUs, etc. For example, NEW Clone-o-matic mainboard with 4 PCI, 3 ISA, 256K cache, I/O built on board with 200MHz AMD \$75. 486 "all-in-one" mainboard (video and IDE I/O) \$35 ea. Remember, today we have it, tomorrow we don't! Used 56K ISA PnP WinModem by Multitech \$20. There are other deals too! For all the latest dealsheets E-Mail: [dealsheets@utwe.com](mailto:dealsheets@utwe.com) or call 626-930-1121 (10am-5pm Pacific) or fax 626-930-1123. E-Mail: [sales@utwe.com](mailto:sales@utwe.com)

**CRTs CHEAP.** Buy direct from the manufacturer. Save money. Mfg. all CRT types since 1950. 3 year warranty. Reg-Res 19" tubes \$75; 25" \$100; hi-res 13" tubes from \$80. We specialize in hi-resolution video/computer CRTs. T.M.C. 215-226-0749/215-223-0388.

**INTELLIGENT INSTRUMENTATION!** Burr Brown model TM-8700/8701 industrial stand-alone microterminal. Heavy-duty watertight case with IR bar-code wand scanner. Can interface printers, CRTs, and scales to host computer. RS 232/422. Specs at [www.instrument.com](http://www.instrument.com) 28 units, \$250 per. Pedestal floor mounts also available. 1-888-651-1932 [atrgroup@home.com](mailto:atrgroup@home.com)

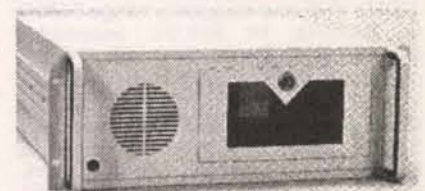

**19" RACKMOUNT PC chassis:** Heavy duty, 4U, for standard 7 slots ATX motherboard. Four (three hidden) 3.5"/two 5.25" drive bays, power supply not included, \$169 with this ad! Add \$6 for 7 slots AT conversion kits. Monitor chassis \$229, keyboard chassis \$129. 8255-8253 I/O card with prototyping area \$69, 12-bit ADDA card \$89. **Computronics Technology**, 972-242-8087, [www.cti-texas.com](http://www.cti-texas.com)

**BUILD YOUR own Pentium I, II, or III computer** from available parts with an easy to view 60+ minute highly acclaimed VHS video tape that shows you how. Gain knowledge and save money or start a business. Limited supplies, order today, only \$29 (reg. \$59.95) plus \$2.95 P&H. Call 1-800-754-5096, or send check to **EVP, PO Box 2201, Northlake, IL 60164-0201, now!**

**PC CABLES:** <http://www.cablesusa.com> 100s of hard-to-find new cables and parts, pictures, free technical information. Low prices, RS232, SCSI, keyboard, network, VGA, Cat-5, USB, Firewire, fast secure online ordering & browsing. 954-418-0817.

## COMPUTER SOFTWARE

**FREE IBM DISK CATALOG** of quality Shareware and CD-ROMs. **MOM 'N' POP'S SOFTWARE <ASP>**, PO Box 15003-N, Springhill, FL 34609-0111. 352-688-9108. [momnpop@gate.net](mailto:momnpop@gate.net)

**CAM & MOTION SW/HW:** Z-trace, PCB toolpath. Plotcam motion control, step drivers. [www.megabits.net/ddt](http://www.megabits.net/ddt) MSG/FAX 407-452-7197, 407-459-2729. [Heater@megabits.net](mailto:Heater@megabits.net)

**GCODE95 FOR Windows 95/98/NT.** Reads AutoCad DXF files and converts data to GcodeMcode RS274. Writes DXF files or ASCII. RS 232 serial connection to machine tool. Full function editor and 3D graphing. For milling, turning, flame-cutting, etc., easy to customize for almost any machine. Download a free trial copy. <http://members.aol.com/andrewc119/index.htm> E-Mail: [andrewc119@aol.com](mailto:andrewc119@aol.com)

### PHOTON II MICROLIGHT

The popular photon microlight has been improved. These super-bright (better than 8 candellas!) LED lights are visible over a mile away. The LED is secured in a tough ABS case and offers a squeeze button for quick use, and a constant on slide switch for prolonged lighting needs. The lithium batteries last a very long time (10 year shelf life!) and are included. The light won't burn out because it is an LED! Specify your choice of five incredible bright colors. Great for home or office use, popular with fire and rescue professionals, pyrotechnicians, stage performers, and dimly lit restaurant patrons. PHOTON II microlights include a keyring and come in ruby red (\$13.50), amber yellow (\$13.50), orange (\$13.50), sapphire blue (\$17.50), turquoise (\$17.50), diamond white (\$17.50), and emerald green (\$17.50). Includes two replaceable 2016 lithium batteries.



### Itty Bitty Phone \$29.95

Did you ever wish for an Incredibly small hands-free telephone that keeps your computer desk clear. Gateway's Got It! This little touch-tone phone can sit on your desk, counter top, or even be stuck to your computer monitor! Measuring only about 61mm x 48mm, it is even small enough to fit in your pocket! The detachable earset features a single earbud and a mini boom mic for lightweight hands-free operation. Handy redial and flash buttons too! Mini phone includes detachable ear piece/boom mic, modular phone cord, plastic hang tab, and instructions.



### Passive Infra-red Talking Motion Detector III \$27.50

"Stay out of that refrigerator!", "Watch your step!", "Do your homework", "Don't touch that remote!" ... The possibilities are mind-boggling with this talking motion detector. You speak into it to record your message (up to 12 seconds long), turn the unit on, and instantly your voice (or your mother-in-law's) reminds anyone in the vicinity that you were expecting them. Message can be changed with the flip of a switch. Uses 4 AA batteries (not included), or an external power source (built-in jack). May be used independently (80 db output) or with an amplified speaker to blast your message throughout the house. Approx 4"x3-1/2"x1-1/2".



### BE A FLY ON THE WALL!!!

Well, actually, those little wings would look pretty stupid on you, but you can build a miniature "bug". Surface mount technology is the latest techno-buzz word, and a challenging new frontier for kit builders. The manufacturer understood that the first try might be a bit rough, so they included enough components to assemble two units. (so it is o.k. to lose or damage a SMT component!) With the entire FM broadcast band (from 88 - 108 MHz) for your receiver, and a transmit range of 300 feet, even James Bond would like this kit! This unit is powered by a 1.5 volt watch battery (included) and features an electret type high gain microphone for superior audio quality and extended pick up range - hear a whisper at 10 feet. A lot of fun in less than a square inch!!! Micro Size FM Wireless Transmitter Kit \$19.95

### Geophone vibration sensing kit Detect a fly stomping across the desk!

Well maybe not that sensitive, but almost. These vibration sensors made by Geosource® were used in oil exploration to determine geological statistics. They are made with a magnet suspended in a coil and are very sensitive to vibration. Compact size, the unit measures approx. 1.6" high and 1.2" dia. The kit includes a geophone vibration sensor along with parts to build a basic detector that will light an LED. In addition we include a schematic that will show you how to operate a relay. The sensitivity is adjustable, so you can set it to detect elephants and other small creatures. Similar units were used by our armed forces to detect enemy troop movements...the perfect device to alert you to the pitter patter of little Leroy's feet! Unit sensitivity can be set high enough to detect a business card dropped on a table, and we've made it work with vibrations up to 40 feet away! Earthquake or Aunt Agatha...you decide! It's a fun gadget with many uses.

COMPLETE GEOSENSOR KIT...\$9.95  
GEOSENSOR UNIT ONLY...\$7.95

### Need A Catalog?

[www.gatewayelex.com](http://www.gatewayelex.com)

You can find many of our fun gadgets and interesting items online! Check out our kits (over 300 of 'em!), project supplies, tools, and much more on the ever expanding Gateway Electronics web site. Things at Gateway change so often we can't publish a paper catalog, so check us out online...you'll be glad you did!

### NO TAN LINES!!!

**AMAZING MINI MICRO FM RADIO! \$7.50**

Much lighter than a heavy jam box with really good sound! This tiny radio (1.5"x1.06"x0.38") has a seek button, reset control, and an on/off switch. Personal listening has never sounded better! Ideal for ballgames, studyhall, and workouts. Battery and nugget style earphones included. Perfect for listening on the beach...compact to fit easily on even the skimpiest swimsuit, and no bulky headset means no tan lines around your ears!



### 4 inch color video monitor \$195.00


**Mini LCD monitor is great for RV use (add a camera and you can watch the rear of your vehicle as you back-up - nifty reversing switch adjusts the image on the display for exactly this use!) Requires 12 VDC, and includes a power cable with an auto cigarette lighter plug for car use. Mounting stand also included! Measures approx. 5.7" x 4.1"x1.6", with a 4" color display. Inputs for both video and audio - great for camcorder playback viewing, and the kids will love it when you include your VCR in the family vacation plans!**



[www.gatewayelex.com](http://www.gatewayelex.com)

8123 PAGE BLVD \* ST. LOUIS, MO 63130 \* (314)427-6116  
9222 CHESAPEAKE DR. \* SAN DIEGO, CA 92123 \* (619)279-6802  
2525 FEDERAL BLVD. \* DENVER, CO 80211 \* (303)458-5444  
MAIL ORDERS CALL TOLL-FREE 1-800-669-5810  
FAX ORDERS (314)427-3147

THE FINE PRINT: PRICES SUBJECT TO CHANGE WITHOUT NOTICE \* GATEWAY IS NOT RESPONSIBLE FOR PRINTING ERRORS \* MASTERCARD, VISA AND DISCOVER ACCEPTED \* YES, WE'LL TAKE YOUR CHECK - SORRY, NO C.O.D.'s \* \$10 MERCHANDISE MINIMUM ON MAIL ORDERS \* SUPPLY OF SOME ITEMS IS LIMITED \* PRICES DO NOT INCLUDE SHIPPING \* UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. \* YOU'RE JUST JEALOUS BECAUSE THE VOICES ARE TALKING TO ME AND NOT YOU!

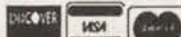



# C and H SALES COMPANY

2176 E. Colorado Blvd. • Pasadena, CA 91107

**TOLL FREE:**  
**1-800-325-9465**

.....  
**FREE**  
**148 PAGE**  
**CATALOG!**  
.....

C & H SALES COMPANY HAS BEEN IN BUSINESS FOR OVER FIFTY YEARS.  
WE'RE THE BEST SOURCE FOR GREAT BUYS ON ITEMS LIKE THESE - AND MORE!

## ELECTRONIC COUNTER

HEWLETT PACKARD,  
Model 5328A. Universal  
counter. Usable to 100  
MHz, 100 ns single shot resolu-  
tion. Has frequency, period, period average, ratio, total-  
ize, scale functions. A built-in digital voltmeter allows  
measurements of input voltage. Two input channels  
provide individual slope, polarity and level settings. Has  
9 digit LED readout. Input power 100-240 VAC 48-66  
Hz 100 VA max. Dimensions: 17" wide x 17-1/4" deep x  
3-1/2" high.

Stock #TE9808

\$250.00



## MILLIOMETER

HEWLETT PACKARD,  
Model 4328A.  
Designed to measure  
very low resistances.  
Measurement range  
1m ohm to 100 ohms.  
Resolution 20 u ohms.  
Analog meter readout. Ideal for  
measuring contact resistance of switches or relays. This  
unit is also useful for measuring the resistivity of semi-  
conductor devices. (Requires special 4 terminal probes  
which are not supplied, but probably are available from  
Hewlett Packard.) Power input: 115-230 VAC 48-66 Hz,  
5 VA max. Dimensions: 5-1/8" wide x 11-1/2" deep x  
6-1/2" high.

Stock #TE9812

\$200.00



## ALTIMETER/BAROMETER

KOLLMAN, #MC-2  
MS28074-2.  
Scale type altimeter  
with barometric  
setting scale  
window. Altimeter  
scale range  
-1000 to 80,000  
feet. Barometric  
range 28.1 to  
31.0 inch of mercury. An adjustment knob is provided for  
scale setting to local altitude or barometric pressure. Has  
white numerals on a black background. Illumination is  
provided. Electrical input is rated 115 VAC 400 cycles.  
Pressure input port is female 7/16"X20 thread. Standard  
aircraft panel 3-1/8" mount. Dimensions: 2-17/64" sq. x  
7-1/2" deep.

Stock #STOCK #IN9900

\$79.50



## SOLA CONSTANT VOLTAGE TRANSFORMER

SOLA ELECTRIC, #93-13-150. Harmonically neutralized  
constant voltage transformer. Rated at 500 watts. Input  
voltage 95 to 130 VAC 60 Hz. Output voltage 120 VAC.  
This unit is designed for rack or bench mounting. The  
meters on the front panel indicate output current and  
input/output voltage. A toggle switch is provided for  
selection of input or output voltage. The input voltage is  
connected at the rear of the unit via a covered electrical  
panel. Two standard 3-wire grounded electrical outputs  
are supplied on the front and rear panels. Dimensions:  
19" wide x 14-1/4" high x 10-1/4" deep. Weight 59 lbs.

Stock #STR9900

\$225.00

☒ Master Charge ☒ Visa ☒ American Express ☒ Discover

Call us first if you have surplus inventories of electronic, optical, or mechanical items for disposal

**WE BUY & SELL!**

Write in 97 on Reader Service Card.

**GAME WIZARD** cartridge for  
PlayStation. Works like a mod chip and  
the best cheat cartridge all in one. It will  
use all the same cheat codes the others  
use. Only \$29.95 free shipping. Toll Free  
1-888-467-6150 all credit cards accept-  
ed. [www.computerconnectionusa.com](http://www.computerconnectionusa.com)

**LIQUIDATION WIN** 95/98, Office97,  
Win95 Companion \$9, WindowsNT call,  
10 PACK CDs 1,000 games \$25, Lotus  
SmartSuite \$10, Wordperfect Suite \$35,  
Printmaster \$9, Antivirus \$5. 714-778-  
0450.

**STEALTH MOD** chips for Sony  
PlayStation. Now even your anti-mod  
games will work. Only \$9.95 ea. + \$3.35  
shipping. Call Toll Free 1-888-467-6150.  
All credit cards accepted. [www.computerconnectionusa.com](http://www.computerconnectionusa.com)

**MAKE MONEY ON THE INTERNET!**  
Illustrated manual and IBM 3.5" disk  
shows how to build your own web site.  
Step-by-step guide with sample pages,  
source code, HTML tags list, and page  
layout templates get you started FAST!  
Complete system, \$15. BP Cunningham,  
12506 NW 234th St., Alachua, FL 32615.  
E-Mail: [b.cunningham@cwix.com](mailto:b.cunningham@cwix.com)

**MICROSOFT OFFICE97** Professional  
Edition. New factory sealed, unopened.  
CD only. **WORD, EXCEL, POWER-  
POINT, OUTLOOK, and ACCESS**  
included. CD only. **ONLY \$49.95! FREE  
SHIPPING!** Quantity discounts available.  
[brucesullivan@msn.com](mailto:brucesullivan@msn.com)

## COMPUTER EQUIPMENT WANTED

**WANTED: FOR** historical museum, pre-  
1980 microcomputers, magazines, and  
sales literature. Floyd, VA 24091-0341  
(540-763-3311/540-382-2935).

**WANTED: HPI5C** calculators. Will pay.  
Call Hugh Adams 850-864-2414.

**WANTED: TERMINALS + PRINTERS:**  
DEC, Wyse, IBM, ADDS, Okidata, Data  
South, Epson, C.I.TOH, etc. Call for quote  
on any surplus computer equipment. Call  
Jeremy, 603-673-8077.

**DEC EQUIPMENT WANTED!!!** We are  
buying DEC systems, boards, terminals,  
drives and peripherals. Also Scientific  
Micro Systems (SMS), DSD, Datability,  
Dilog, other DEC compatibles, and  
Computer Output Microfilm (COM) units.  
Please call for a quote or fax us your  
equipment list. We buy, sell, and trade.  
**KEYWAYS, INC.,** 937-847-2300 OR fax  
937-847-2350.

**HP CALCULATORS** wanted: models 10,  
70, calculator watch, others for private  
collection. Cash paid. Bob Morrow, 765-  
855-2348, [rkmorrow@aol.com](mailto:rkmorrow@aol.com)

**SEEKING MITS/Altair, IMSAI** original S-  
100 boards for hobby restoration project.  
CPU, RAM, I/O. Also graphics, speech,  
music boards. Call Shawn, 650-846-  
8208, [maxweb@pacbell.net](mailto:maxweb@pacbell.net)


Write in 47 on Reader Service Card.

# LOWEST COST LCD'S ON EARTH


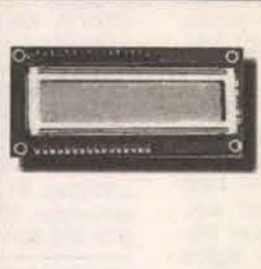
## VIDEO LCD

4 Inch Video NTSC \$150  
Sharp P/N 4LU4E  
Composite NTSC & RGB Input  
12:00 OR 6:00 Viewing Angle  
Integrated Backlight & Inverter  
Extended Temp: -10 to + 60 C  
Brightness: 260 nits  
Power Consumption: 4.3 Watts  
Contrast: 50 to 1



## CHARACTER LCD

OPTREX DMF-5005SN-EW  
240 x 64 Graphic EL Backlit STN \$30  
OPTREX DMF-5005N  
240 x 64 Graphic Reflective STN \$30  
SANYO DM2023-7G1  
2 x 20 Character Reflective STN \$8  
SHARP LM20A21  
2 x 20 Character Reflective STN \$8  
VIKAY 2035TNLD NOTW-D  
2 X 16 Character LED Backlit STN \$8



## LCD MONITOR

10.4" DSTN or 12.1" TFT  
Analog SVGA Input  
Autosync  
Auto Sizing  
Automatic Expansion of VGA  
images to SVGA (On 12.1")  
Very Aggressive Pricing  
Starting under \$500!



## TOUCH MONITOR

EarthVue 10.4  
10.4" VGA TFT  
Analog VGA Input  
105 Nit Brightness  
RS-232 Touch Screen Option  
Only 9.9"W x 7.7"H x 1.5"D  
Ideal For Factory Automation  
Fully Articulating Ball Mount  
Only \$1095 With Touch



## LCD DISPLAYS

6.3" Mono STN \$60  
9.4" Mono Reflective \$60  
8.4" TFT \$250  
9.4" DSTN \$150  
10.4" TFT \$350  
10.4" DSTN \$240

**NoteBook Screens**  
340 Models in Stock  
Obsolete Screens Stocked  
Hard To Find LCD? Call!



## CONTROLLERS

ISA  
PCI  
PC/104  
NTSC  
Analog VGA  
Complete LCD Kits with LCD,  
Controller & Cable Starting  
under \$200



**EARTH**

Computer Technologies

"The World Leader In LCD Recycling"

Ph: (949) 361-2333 Fax: (949) 361-2121

<http://www.flat-panel.com>

Write in 98 on Reader Service Card.

## TEST EQUIPMENT


**FEITEK PROVIDES** repair, calibration  
and traceable certifications of test equip-  
ment. Free estimates. We buy, sell and  
trade all makes of test equipment. Visa  
and MasterCard accepted. Check out our  
inventory and specials at [WWW.FEIT-  
EK.COM](http://WWW.FEIT-<br/>EK.COM) 2752 Walton Road, St. Louis,  
MO 63114, 314-423-1770.

**KENTRONIX TEST EQUIPMENT SPE-  
CIALS.** Check our WEB site at  
<http://www.kentronix.com> for monthly  
specials. We are also looking to buy test  
equipment, coaxial and waveguide com-  
ponents, manuals, etc. Contact Brian at  
732-681-3229 or FAX 732-681-3312. E-  
Mail: [brian@kentronix.com](mailto:brian@kentronix.com)

**AFFORDABLE HP** power sensor repair!  
Most 8481As repaired for \$255 or less.  
We also handle 478As and many others.  
Call or fax for more information.  
Willamette RF, Inc., 541-754-7226, FAX  
541-753-4629.

**EQUIPMENT SALE:** HP 8565A 21GHz  
spectrum analyzer \$3,250; Wavetek  
3001 signal generator \$300; Hewlett  
Packard 8015A opt 03, \$350; 8015A  
\$250. HP 3403C opt 03 TRMS voltmeter  
\$300; 3403C \$200. HP 3763A error  
detector \$400. ROD L 100AVS5 HYPOT  
tester excellent \$50. Psitech Plus 707-  
745-4804, [www.psitech-plus.com](http://www.psitech-plus.com)

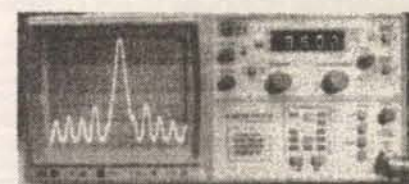**POOR MAN'S** Spectrum  
Analyzer/Monitor Receiver Kit. 2 to 1,700  
MHz. Basic kit only \$78. Now available  
with switched resolution filters, tracking  
generator and direct digital frequency  
readout. Works with ANY scope or IBM  
compatible computer. Send stamped  
envelope for details. Science Workshop,  
Box 310B, Bethpage, NY 11714.  
<http://www.science-workshop.com>



**ENGINEER TESTED:** Spectrum analyz-  
ers, frequency counters, frequency stan-  
dards, meters, scopes, generators, curve  
tracers, and more. **VISA, MASTER-  
CARD, AMEX.** "Performance tested."  
**NIST calibrated. Warranted. New &  
used.** Gary N6ZD. [HTTP://TECH-SER-  
VICES.COM](http://TECH-SER-<br/>VICES.COM) 831-385-7519.

**TEST EQUIPMENT** for sale/wanted  
(NEW/USED): RF, Microwave, video and  
fiber optic. Cable TV, Broadcast TV, satel-  
lite and related industries. Wavetek,  
Tektronix, Hewlett Packard and other  
manufacturers. Spectrum analyzers, sig-  
nal level meters, sweep systems, TDRs,  
OTDRs, and much more. **PTL Test  
Equipment, Inc.** Phone 561-747-3647  
FAX 561-575-4635. E-Mail: [PTLTE@aol.com](mailto:PTLTE@aol.com)  
<http://www.PTLTEST.com>



**AS NEW OSCILLOSCOPES: FLUKE PM 3394A** autoranging, combiscope, 200MHz analog and digital with service manual, as new \$3,250. All with money back warranty. **Psitech Plus** 707-745-4804, [www.psitech-plus.com](http://www.psitech-plus.com)

**DESOLDERING EQUIPMENT:** Pace MBT250 base, \$350; MBT220, \$700; hot air reflow, \$600; hot plate, \$100; hot tweezer, \$50; Ungar 6966C heat gun, \$55; Plato digital solder pot, \$200; hot air pencil, \$200; solder stations: OK SA-G-75, \$55; Weller digital readouts, \$100-\$225 used, new; Weller WTCN base w/new Ungar-Weller pencil, \$55. Trade, repair, buy, 310-515-2058.

**BRUEL & KJAER BUY, SELL, BEST PRICES. EXCALIBUR ENGINEERING, 1398-C AIRPORT LOOP DRIVE, COSTA MESA, CA 92626. 714-540-0169, FAX 714-540-5417.**

**TEK 2246** mod A 4 ch 100MHz scopes w/pouch, front cover and copy of service manual, \$725; HP 8901B/001/030/032/037 modulation analyzer, \$1,995; HP 8640B/003 signal generator, \$750. All plus shipping. John, 912-922-8244.

**TEKTRONIX TM503** 3 slot mainframe with SC503 10MHz storage scope and DC505A universal timer/counter, \$295. Circuit Tek, 208-528-7869.

**DEC EQUIPMENT WANTED!!!** We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dialog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

**HEWLETT PACKARD** spectrum analyzer 141T, 8552B, 8554A 1.4GHz RF section \$875; with 18GHz 8555A \$1,400. 5517B laser head accepting offers; HP 8350A, sweep mainframe as new with new battery \$650. Psitech Plus 707-745-4804, [www.psitech-plus.com](http://www.psitech-plus.com)

**INSTRUMENT REPAIR** Labs. Excess equipment for sale. Tektronix 2225 50MHz 2 ch analog scope, see CON0200, \$500; Tektronix 2445 150MHz 4 ch analog scope w/cursors, \$2,100; Tektronix 2465 analog scope w/cursors 300MHz 4 ch, \$3,100; Tektronix 2465 analog scope 4 ch 300MHz, \$3,118.75; Tektronix 2465A analog scope 4 ch 350MHz, \$3,743.75; Tektronix 2465ACT analog scope 4 ch 350MHz, \$4,119.94; Tektronix 2465BCT analog scope 4 ch 400MHz, \$5,993.75; Tektronix 2465DVS analog scope w/measurements, \$3,250; Tektronix 2467 analog scope 350MHz, \$6,900; Tektronix 314 10MHz portable analog scope, 2 ch, \$1,195; Tektronix 465B analog scope 100MHz 2 ch, \$700; Tektronix 475 200MHz 2 ch analog scope, \$850; Tektronix 5B42 delay time base, \$125; Tektronix 7603 analog scope display sect., \$150; Tektronix 7704A analog scope display scrap parts, \$250; Tektronix 7704A analog scope MF as-is older unit, \$250. [sales@calibration.com](mailto:sales@calibration.com) <http://www.calibration.com> phone: 303-469-5335. Fax: 303-469-5336. Used listings web page: <http://www.calibration.com/sale/index.html>

**QUALITY EQUIPMENT SALE: HP 3488A** switch control unit \$500 (cards available); **HP 4140B** pA meter, DC voltage source with **HP 16055A** \$2,000; **HP 436A/022** RF power meter with cable \$925; **HP 5343A/1,6,11** 26.5GHz microwave frequency counter \$2,995; **HP 6033A** autoranging power supply (20V, 30A) \$900; **HP 8112A** 50MHz pulse generator \$3,600; **HP 8161A/020** 100MHz dual channel pulse generator \$2,300; **HP 83522A** .01-2.4GHz 8350B plug-in \$2,500; **HP 83570A** 18-26.5GHz 8350B plug-in \$3,400; **HP 8410C**, 8410B network analyzer mainframes \$575, 400; **HP 8411A/018**, 8411A harmonic frequency converters \$350, 175; **HP 8743B/018**, test set \$425; **Audio Precision SWR-122F** switcher \$600. All with warranty, excellent condition. Pepper Systems (<http://home.earthlink.net/~peppersys>) 214-353-0257 (Fax 214-902-9511). E-Mail: [peppersys@earthlink.net](mailto:peppersys@earthlink.net)

**PICMASTER EMULATOR** system, new, complete, all parts, documentation, boxes, w/16C63 probe, MPLAB software, registered w/Microchip, \$900 obo. 818-349-7920.

**AC POWER SUPPLIES:** Elgar 2 phase (9.1 amp), 3 phase (5.75 amp) output power supply 0-130 VAC, variable frequency 45Hz to 1KHz oscillator 9023PIP with digital readout and keypad entry, HPIB input 120 single phase, in factory boxes, \$2,500. 305-948-4796 in a hurry? Fax 305-717-9947 or E-Mail at [atlasaer@bellsouth.net](mailto:atlasaer@bellsouth.net)

**INEXPENSIVE NEW ARRIVALS (MOST UNITS LOOK NEW AND WERE RECENTLY CALIBRATED).** HP 8901B, \$1,000; HP 8903B, \$1,500; HP 8901A, \$750; HP 8903A \$750; HP 8590D, \$4,500; HP 8657A, \$2,000; HP 8657D WITH HI STAB & DQPSK IQ MODULATOR, \$3,000; HP 3852A, \$750; HP 44705A, \$300; HP 44725A, \$300; FLUKE 6071A, \$1,250; HP 6034L, \$500; HP 6002A, \$500; HP 4191A, \$9,000; ENI 603L, \$1,200; MARCONI 2955A, \$2,500; MARCONI 2955, \$1,500; HP 8175A, \$2,500; HP 3562A, \$4,900; HP 8496H, \$350; HP 8590B, \$3,900, ETC., ETC., ETC. SHOP AND COMPARE! MANY MODELS PRICED MORE THAN 50% OFF COMPETITOR'S PRICES. TRU CAL INT'L, ISO 9002 & A2LA ACCREDITED CALIBRATION LABORATORY. [tru-cal@aol.com](mailto:tru-cal@aol.com) Toll free 1-800-681-5540, phone# 630-238-8100, fax# 630-238-8101. ASK ABOUT OUR BRAND NEW HANDHELD 3-1/2 DIGIT KEITHLEY DMMs FOR \$50.

**ELECTRONIC TESTING & ESCROW SERVICE.** Don't get burned on an "AS-IS" deal! Use our trusted 3rd party testing & escrow service. **VISA, MASTERCARD, AMEX, Gary, N62D.** [HTTP://TECH-SERVICES.COM](http://TECH-SERVICES.COM) 831-385-7519.

## World's Smallest TV Transmitters

We call them the 'Cubes'.... Perfect video transmission from a transmitter you can hide under a quarter and only as thick as a stack of four pennies - that's a nickel in the picture! Transmits color or B&W with fantastic quality - almost like a direct wired connection to any TV tuned to cable channel 59. Crystal controlled for no frequency drift with performance that equals law enforcement models that cost hundreds more! Basic 20 mW model transmits up to 300' while the high power 100 mW unit goes up to 1 1/4 mile. Audio units include sound using a sensitive built-in mike that will hear a whisper 15 feet away! Units run on 9 volts and hook-up to most any CCD camera. Any of our cameras have been tested to mate perfectly with our Cubes and work great. Fully assembled - just hook-up power and you're on the air!

C-2000, Basic Video Transmitter Cube.....\$89.95  
C-3000, Basic Video & Audio Transmitter Cube.....\$149.95  
C-2001, High Power Video Transmitter Cube.....\$179.95  
C-3001, High Power Video & Audio Transmitter Cube.....\$229.95

## CCD Video Cameras

Top quality Japanese Class 'A' CCD array, over 440 line line resolution, not the off-spec arrays that are found on many other cameras. Don't be fooled by the cheap CMOS single chip cameras which have 1/2 the resolution, 1/4 the light sensitivity and draw over twice the current! The black & white models are also super IR (Infra-Red) sensitive. Add our invisible to the eye, IR-1 illuminator kit to see in the dark! Color camera has Auto gain, white balance, Back Light Compensation and DSP! Available with Wide-angle (80°) or super slim Pin-hole style lens. Run on 9 VDC, standard 1 volt p-p video. Use our transmitters for wireless transmission to TV set, or add our IB-1 Interface board kit for audio sound pick-up and super easy direct wire hook-up to any Video monitor, VCR or TV with A/V input. Fully assembled, with pre-wired connector.

CCDWA-2, B&W CCD Camera, wide-angle lens.....\$69.95  
CCDPH-2, B&W CCD Camera, slim fit pin-hole lens.....\$69.95  
CCDC-1, Color CCD Camera, wide-angle lens.....\$129.95  
IR-1, IR Illuminator Kit for B&W cameras.....\$24.95  
IB-1, Interface Board Kit.....\$14.95

## Mini Radio Receivers

Imagine the fun of tuning into aircraft a hundred miles away, the local police/fire department, ham operators, or how about Radio Moscow or the BBC in London? Now imagine doing this on a little radio you built yourself - in just an evening! These popular little receivers are the nuts for catching all the action on the local ham, aircraft, standard FM broadcast radio, shortwave or WWV National Time Standard radio bands. Pick the receiver of your choice, each easy to build, sensitive receiver has plenty of crystal clear audio to drive any speaker or earphone. Easy one evening assembly, run on 9 volt battery, all have squelch except for short-wave and FM broadcast which has handy SCA output. Add our snazzy matching case and knob set for that smart finished look.

AR-1, Airband 108-136 MHz Kit.....\$29.95  
HFRC-1, WWV 10 MHz (crystal controlled) Kit.....\$34.95  
FR-1, FM Broadcast Band 88-108 MHz Kit.....\$24.95  
FR-6, 6 Meter FM Ham Band Kit.....\$34.95  
FR-10, 10 Meter FM Ham Band Kit.....\$34.95  
FR-146, 2 Meter FM Ham Band Kit.....\$34.95  
FR-220, 220 MHz FM Ham Band Kit.....\$34.95  
SR-1, Shortwave 4-11 MHz Band Kit.....\$29.95  
Matching Case Set (specify for which kit).....\$14.95

## Tiny FM Transmitters

Gosh, these babies are tiny - that's a quarter in the picture! Choose the unit that's best for you. FM-5 is the smallest tunable FM transmitter in the world, picks up a whisper 10' away and transmits up to 300'. Runs on tiny included watch battery, uses SMT parts. FM-4 is larger, more powerful, runs on 5-12 volts, goes up to a mile. FM4.5 operate in standard FM band 88-108 MHz. FM-6 is crystal controlled in 2 meter ham band, 146.535 MHz, easily picked up on scanner or 2 meter rig, runs on 2 included watch batteries. SMT (surface mount) kits include extra parts in case you sneeze & lose a part!

FM-4MC, High Power FM Transmitter Kit.....\$17.95  
FM-5, World's Smallest FM Transmitter Kit.....\$19.95  
FM-6, Crystal Controlled 2M FM Transmitter Kit.....\$39.95  
FM-6, Fully Wired & Tested 2M FM Transmitter.....\$69.95

## Super Pro FM Stereo Transmitter

Professional synthesized FM Stereo station in easy to use, handsome cabinet. Most radio stations require a whole equipment rack to hold all the features we've packed into the FM-100. Set freq with Up/Down buttons, big LED display. Input low pass filter gives great sound (no more squeals or swishing from cheap CD inputs!) Limiters for max 'punch' in audio - without over mod, LED meters to easily set audio levels, built-in mixer with mike, line level inputs. Churches, drive-ins, schools, colleges find the FM-100 the answer to their transmitting needs, you will too. Great features, great price! Kit includes cabinet, whip antenna, 120 VAC supply. We also offer a high power export version of the FM-100 that's fully assembled with one watt of RF power, for miles of program coverage. The export version can only be shipped outside the USA, or within the US if accompanied by a signed statement that the unit will be exported.

FM-100, Pro FM Stereo Transmitter Kit.....\$249.95  
FM-100WT, Fully Wired High Power FM-100.....\$399.95

## FM Stereo Radio Transmitters

No drift, microprocessor synthesized! Excellent audio quality, connect to CD player, tape deck or mike mixer and you're on-the-air. Strapable for high or low power! Runs on 12 VDC or 120 VAC. Kit includes case, whip antenna, 120 VAC power adapter - easy one evening assembly.

FM-25, Synthesized FM Stereo Transmitter Kit.....\$129.95

Lower cost alternative to our high performance transmitters. Great value, tunable over FM band, plenty of power and manual goes into great detail about antennas, range and FCC rules. Handy kit for sending music thru house and yard, ideal for school projects too - you'll be amazed at the exceptional audio quality! Runs on 9V battery or power from 5 to 15 VDC. Add our matching case and whip antenna set for a nice 'pro' look.

FM-10A, Tunable FM Stereo Transmitter Kit.....\$34.95  
CFM, Matching Case and Antenna Set.....\$14.95  
FMAC, 12 Volt DC Wall Plug Adapter.....\$9.95

## RF Power Booster

Add muscle to your signal, boost power up to 1 watt over a frequency of 100 KHz to over 1000 MHz! Use as a lab amp for signal generators, plus many foreign users employ the LPA-1 to boost the power of their FM transmitters, providing radio service through an entire town. Runs on 12 VDC. For a neat finished look, add the nice matching case set.

LPA-1, Power Booster Amplifier Kit.....\$39.95  
CLPA, Matching Case Set for LPA-1 Kit.....\$14.95  
LPA-1WT, Fully Wired LPA-1 with Case.....\$99.95

## FM Station Broadcast Antenna

For maximum performance, a good antenna is needed. Properly tuned and matched antenna is fully PVC enclosed for weather protection and rugged use. Vertical or horizontal mounting, 'F' style connector, 5' long.

TM-100, Tru-Match FM Station Antenna Kit.....\$39.95

## AM Radio Transmitter

Operates in standard AM broadcast band, set to clear channel in your area. AM-25 'pro' version is synthesized for stable, no-drift frequency and is settable for high power output where regulations allow, typical range of 1-2 miles. Entry-level AM-1 has tunable transmit oscillator, runs FCC maximum 100 mw power, expected range 1/4 mile. Both accept line-level inputs from tape decks, CD players or mike mixers, run on 12 volts DC. Pro AM-25 includes AC power adapter, matching case and bottom loaded wire antenna. Entry-level AM-1 has an available matching case and knob set for a finished, professional look. High level modulation for low distortion.

AM-25, Professional AM Transmitter Kit.....\$129.95  
AM-1, Entry level AM Radio Transmitter Kit.....\$29.95  
CAM, Matching Case Set for AM-1.....\$14.95

## RAMSEY Binocular Special

Wow, did we nab a deal on these first rate binoculars! Absolutely identical to a famous big name brand here in Rochester, NY - but without their name. Well made with fully coated optics, super nice rubber armored housing over hi-alloy aluminum, includes lens cleaner cloth, neck lanyard and carry case. 4 styles: roof prism 10x25 (10 power, 25 mm), 10x25 high performance roof prism ruby coated objective lens model for demanding use in bright sun, 10x25 high-end BAK-4 lens porro prism ruby coat with Tac-Grip housing, and Ultra-View 10x50 porro prism ruby coats. First quality, yet at a close-out price on the exact same units as the 'Trademarked' units - but at half price!

BNO-M, 8x21 Mini Monocular.....\$14.95  
BNO-1, 10x25 Roof Prism Binoculars.....\$24.95  
BNO-1EX, 10x25 Ruby Coated Porro Prism.....\$29.95  
BNO-2, 10x25 TacGrip Ruby Coat Porro Prism.....\$59.95  
BNO-6, 10x50 Ultra-View Ruby Coat Porro Prism.....\$69.95

## World's Smallest FM Radios

Everyone who sees one of these babies says they just gotta have one! Super cute tiny FM radios have automatic scan/search tuning, comfortable ear bud earphones and we even include the battery. The pager style unit looks like a shrunken pager and even has an LCD clock built-in. You will be amazed at the crystal clear amazing sound! That's a quarter in the picture for size comparison - pretty tiny, huh?

MFMT-1, World's Smallest FM Radio.....\$11.95  
PFMR-1, Pager Style LCD Clock & FM Radio.....\$12.95

## Speech Descrambler

Decode all that gibberish! This is the popular descrambler / scrambler that you've read about in all the Scanner and Electronic magazines. Speech inversion technology is used, which is compatible with most cordless phones and many police department systems, hook it up to your scanner speaker terminals and you're in business. Easily configured for any use: mike, line level and speaker output/inputs are provided. Also communicate in total privacy over telephone or radio, full duplex operation - scramble and unscramble at the same time. Easy to build, all complex circuitry contained in new custom ASIC chip for clear, clean audio. Runs on 9 to 15VDC. Our matching case set adds a professional look to your kit.

SS-70A, Speech Descrambler/Scrambler Kit.....\$39.95  
CSS, Custom Matching Case and Knob Set.....\$14.95  
SS-70AWT, Fully Wired SS-70A with Case.....\$79.95  
AC12-5, 12 Volt DC Wall Plug Adapter.....\$9.95

## Call for our Free Catalog!

See our complete catalog and order on-line with our secure server at:

[www.ramseyelectronics.com](http://www.ramseyelectronics.com)

**RAMSEY ELECTRONICS, INC.**

793 Canning Parkway Victor, NY 14564

**Order Toll-free: 800-446-2295**

Sorry, no tech info. or order status at this number

**For Technical Info, Order Status**

**Call Factory direct: 716-924-4560**



**ORDERING INFO:** Satisfaction Guaranteed. Examine for 10 days, if not pleased, return in original form for refund. Add \$6.95 for shipping, handling and insurance. Orders under \$20, add \$3.00. NY residents add 7% sales tax. Sorry, no CODs. Foreign orders, add 20% for surface mail or use credit card and specify shipping method.



**USED TEKTRONIX 475 scope**, dual trace, 200 megahertz, for sale. Hardly used since repaired and calibrated, manual included, \$425 plus shipping. Also for sale, Electronic Troubleshooting & Repair Handbook by Homer Davidson, 1,008 pages, \$35 plus shipping. 717-272-1415

## SECURITY


**QUAD MULTIPLEXER BLOW-OUT.** JUST IN big load of color + B/W quads from American Dynamic+ Robot. AD-1473 real-time B/W quad reg. \$400, NOW \$100. AD-1474 4 cam B/W multiplexer \$150. AD-1480SL16 16 cam B/W multiplexer reg. \$600, NOW \$250. AD-1584SL16 16 cam COLOR multiplexer call for price. Robot video telephone transmitters 50-80% OFF. Robot quads + multiplexers 50-75% OFF. Burle waterproof metal camera housings reg. \$85, NOW \$25. Burle steel high security inside corner housings reg. \$250, NOW \$50. Burle auto-iris lenses TC-9908 8mm 1.2 reg \$70, NOW \$40. Burle 12 mm 1.4 auto-iris reg \$75, NOW \$40. TONS of Panasonic auto-iris lenses NEW=USED. Pan + tilts, receiver drivers, fiber optic equipment. WE'LL BEAT ANY PRICE! "I must be outta my mind." **PRO-VID SYSTEMS Co., Woburn, MA, 781-933-0827.** E-Mail: RicksVideo@Medial.NET



**CONVERTS PC MONITOR to SECURITY MONITOR.** The VGA-801 accepts standard NTSC or PAL inputs for display on any existing VGA/SVGA computer monitor. Small compact size, 4-1/2" x 2-1/2" x 3/4". Over 600 lines of resolution, twice that of standard TV monitor! High quality audio output feeds speakers directly. Excellent grey-scale conversion; works well with B/W inputs. Power supply included; \$69 each. Dealers welcome. **MATCO, Inc., 1-800-719-9605; Fax 847-619-0852; E-Mail: sales@mat-co.com** Website: [www.mat-co.com](http://www.mat-co.com)




**B/W 430 LINE CCD CAMERA** with optional black low-profile swivel adjustable enclosure. Pin hole or Std. lens type. 6, 8, and 12mm lens are available. 1/3" CCD, 3.6mm/F2.0 lens included; 9-14 VDC, 0.08 lux, IR sensitive; 1.27" x 1.27" x 0.5"D pinhole or 1" deep standard. Price @ 10 pcs., \$44 each. Enclosure: \$8; optional lens: \$18. Dealers welcome. **MATCO, Inc., 1-800-719-9605. Fax 847-619-0852. E-Mail: sales@mat-co.com** Website: [www.mat-co.com](http://www.mat-co.com)

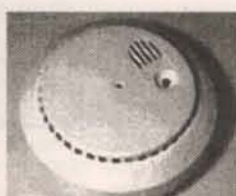

**SALE! PS 102:** Built-in pin hole CCD, lens size: 3.6mm. 5-1/2" (D) x 1.7" (H). \$79 @ 5 pcs., \$72 @ 10 pcs. Distributors welcome. **Matco, Inc., 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@mat-co.com** Web site [www.mat-co.com](http://www.mat-co.com)
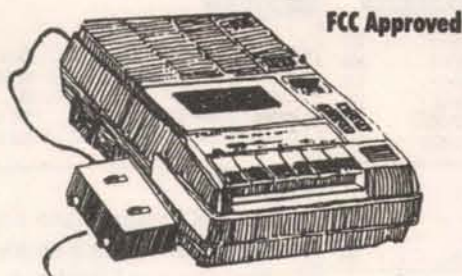
## TELEPHONE LISTENING DEVICE WITH 12 HR. RECORDER



Record telephone conversations in your office or home. Starts automatically when phone is answered, records both sides of phone conversation. Recorder stops when phone is hung up. \$99.95 + \$7 shipping. For telephone listening device separately \$19.95 + \$2 ship.

For comprehensive 50 page catalog of Micro Video, VHF transmitters, Surveillance, and Counter-surveillance and much more! Send \$3.00

Call 407-725-1000

**USI CORP**

P.O. Box N2052 Melbourne, FL 32902  
COD'S OK

Write in 100 on Reader Service Card.

## World Passing You By?

Are you interested in Microprocessors & Embedded Control Systems? If not you should be! Look around, just about everything these days has an embedded microprocessor in it. TVs, cars, radios, traffic lights & even toys have embedded computers controlling their actions. The Primer Trainer is the tool that can not only teach you how these devices operate but give you the opportunity to program these types of systems yourself. Examples & exercises in the Self Instruction manual take you from writing simple programs to controlling motors. Start out in Machine language, then move on to Assembler, & then continue on with optional C, Basic, or Forth Compilers. So don't be left behind; this is information you need to know!

### Examples Include:

- Measuring Temperature
- Using a Photocell to Detect Light Levels
- Making a Waveform Generator
- Constructing a Capacitance Meter
- Motor Speed Control Using Back EMF
- Interfacing and Controlling Stepper Motors
- Scanning Keypads and Writing to LCD/LED Displays
- Bus Interfacing an 8255 PPI
- Using the Primer as an EPROM Programmer
- DTMF Autodialer & Remote Controller (New!)

The PRIMER is only \$119.95 in kit form. The PRIMER Assembled & Tested is \$169.95. This trainer can be used stand alone via the keypad and display or connected to a PC with the optional upgrade (\$49.95). The Upgrade includes: an RS232 serial port & cable, 32K of battery backed RAM, & Assembler/Terminal software. Please add \$5.00 for shipping within the U.S. Picture shown with upgrade option and optional heavy-duty keypad (\$29.95) installed. Satisfaction guaranteed.


**EMAC, inc.**  
11 EMAC WAY, CARBONDALE, IL 62901  
618-529-4525 Fax 457-0110 BBS 529-5708  
World Wide Web: <http://www.emacinc.com>

1985 - 1998  
OVER  
12  
YEARS  
OF SERVICE

Write in 101 on Reader Service Card.



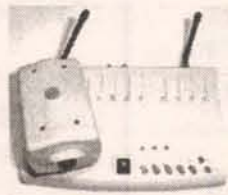**SPECIAL! IC 113:** PIR motion detector with audio! W/ NO/NC alarm output. CCD camera with audio can be turned on by detector. 5-1/4" (L) x 2-3/4" (W) x 2" (D). \$89 @ 5 pcs., \$82 @ 10 pcs. **Matco, Inc., 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@mat-co.com** Web site [www.mat-co.com](http://www.mat-co.com)



**AS-1004,** FCC approved. 2.4GHz transmitter & receiver with audio! Capable handling total of 4 wireless cameras, range: >300'. Built-in camera, 400 TV line. \$189 a pair @ 5 pcs., \$179 @ 10 pcs. Additional camera \$119 @ 10 pcs. **Matco, Inc., 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@mat-co.com** Web site [www.mat-co.com](http://www.mat-co.com)

## FOR THE BEST PRICES ON PROFESSIONAL TOOLS, CALL ELECTRO-TOOL



**platt** - Case - Deluxe Polypropylene. Chemical Resistant. Tools by CooperTools and others. 800T Case, complete with tools ... \$419.95  
800T Case Only ... \$121.80




**platt** - Case - Cordura Exterior. Two exterior pockets & one literature pocket. 660ZT Case, complete with tools ... \$223.00  
660ZT Case Only ... \$59.45  
Optional Sperry meter #DM6510 as shown ... \$65.00



**Weller WCC100-** Electronically controlled station, temperature adjustable from 350°F-850°F, Zero voltage circuit-safe for sensitive components, 40 Watt pencil ... \$97.90

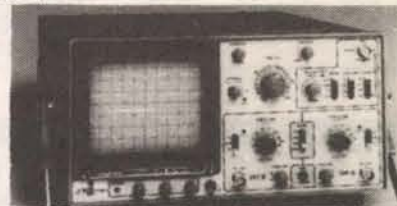**OptiVISOR** - Superior magnification, Optical Glass Prismatic lenses (not plastic). Select any one of (6) magnifications ... \$24.00



**GoldStar** - 20 MHz Dual Trace Oscilloscope OS-9020A-Large 6" rectangular, high sensitivity: 1mV/div, high accuracy: ±3%, stable, low-drift design, 8 divisions of displayed dynamic range and accurate, distortion-free waveform measurements ... \$372.00

## Electro Tool, Inc.



9103 Gillman, Livonia, MI 48150  
Customer Service: (734) 422-1221  
ORDERS ONLY: 1 (800) 772-3455  
FAX: (734) 422-3432



"Tools American Made."


**CONSUMERTRONICS 120+** exciting manuals: Electronics, computers, Internet, phones, energy, radionics, financial (including stocks), crime-fighting, security, survival, phenomena, **SPECIAL PROJECTS.** Catalog \$3. PO Box 23097, Albuquerque, NM 87192. [www.tsc-global.com](http://www.tsc-global.com)

**SEEKING DISTRIBUTORS FOR SECURITY PRODUCTS.** **Matco, Inc., Schaumburg, IL 630-350-0299.** [www.mat-co.com](http://www.mat-co.com)

**STOP THEM** from listening in or recording your telephone conversations with the **TELEPRIVACY-PLUS.** Send \$49 to Vakis, 1402 Pine Ave., Niagara Falls, NY 14301.



## The Pocket Programmer

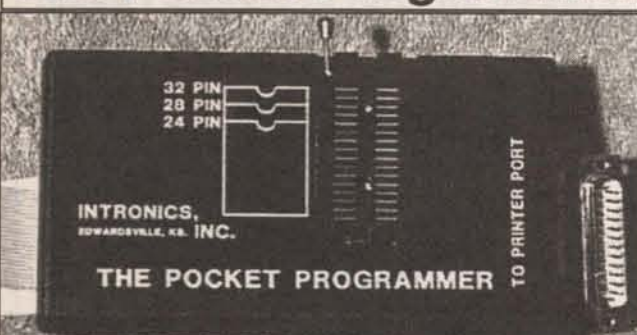

The portable programmer that uses the printer port of your PC instead of an internal card. Easy to use software that programs E(P)rom, Flash & Dallas Ram. 27(C)/28(C)/28F/29F/29CXXXX & 25XX series from 16K to 8 Megabit with a 32 pin socket. Adapters available for Pic, MCU's 874X, 875X, 40-Pin X 16 & Serial Eprom's, PLCC, 5-Gang, 82/74 Prom's and Eprom Emulator to 32K X 8.

Only \$129.95

Same Name, Address & Phone Number for 16 Years....  
Now isn't that Amazing?

### Intronics, Inc.

Box 13723 / 612 Newton St.  
Edwardsville, KS 66113 Add \$5.00 COD  
Tel. (913) 422-2094 Add \$4.00 Shipping  
Fax (913) 441-1623 Visa / Master Charge / Amex

**ALL NEW: THE COVERT CATALOG 2000.** The MASTER LIST of information suppliers, specialized newsletters, OEM lock picks, reverse engineers, spy shops, alternate IDs, program crackers, and more. Locate impossible equipment, shop where the smart guys shop. Provides hundreds of addresses, sample pages, catalog prices and recommendations that will save you money on everything from break-in books to undetectable bugs. Catalog #COVCAT-2, price \$34.95 + S&H \$6 US, \$7 CAN. NY state add \$3.38 tax. Visa, MC, Discover, money orders. Mail: CRB, PO Box 56-NV, Commack, NY 11725. Phone: 516-543-9169.

**SURVEILLANCE-COUNTERSURVEILLANCE:** I buy and sell used equipment. Steve 410-879-4035.



**COUNTER-SURVEILLANCE=\$250 HRI**  
Electronic eavesdropping is unbelievably widespread! Are you sure you're safe? Learn how others (without prior experience) earn \$250 HR in the fascinating field of COUNTER-SURVEILLANCE! For FREE catalog call: 1-800-732-5000.

## COMPUTER PARTS

### Attention Dealers and Consultants

Scrambled data while flashing upgrade BIOS? Our BIOS repair service will correct any virus or flashing errors. Save the cost of a new BIOS chip, or worse yet, a new motherboard. BIOS RECOVERY SERVICE \$25.00

#### MEMORY UPGRADES

2Mx32 72-pin SIMM F/P	\$20
4Mx32 72-pin SIMM F/P	\$29
8Mx32 72-pin SIMM F/P	\$59
64MB SDRAM (PC100)	\$59
128MB SDRAM (PC100)	\$99
256MB SDRAM (PC-100)	\$245

#### CACHE

64Kx1-15ns 22-DIP.....	\$5.50
32Kx8-25/20/15ns 28-DIP.....	\$3/2/2.50
64Kx8-15ns 32-DIP.....	\$6
128Kx8-15/20ns 32-DIP narrow.....	\$12 & up
128Kx8-15/20/25ns 32-DIP wide.....	\$12 & up

#### CPU

Pentium II 400.....	\$199
Pentium II 333.....	\$189
Celeron 333 PGA.....	\$95

#### VIDEO

1MB KIT(2-256x16)2CAS SOJ/ZIP.....	\$18/35
1MB KIT(2-256x16) 2WE SOJ/ZIP.....	\$19/36

#### MISC.

**IDEAL BIOS Enhancer Card.** Break the 8.46GB barrier. Supports any IDE hard drive over 528MB up to 128MB. Works with any X86, Pentium, or PII System. **\$29.95**

## PACKARD BELL UPGRADES

PRICES SUBJECT TO CHANGE WITHOUT NOTICE  
TERMS: VISA/MC - MIN. ORDER \$20 - SHIPPING & HANDLING: \$7 MIN.  
ORDER LINE: (800) 586-4199

### LA PAZ ELECTRONICS INT'L

www.lapazusa.com  
P.O. BOX 261095, San Diego CA 92196  
TEL (858) 586-7610 FAX (858) 586-1482  
e-mail: lapazusa@pobox.com

Write in 102 on Reader Service Card.

**8 CAMERA DUO-QUAD DISPLAY BLOW-OUT.** 8 camera B+W 2 page hires. real-time quad w/2 video outputs. Selectable display quad/sequencer or both. These units are brand new discontinued American Dynamics AD1475A. Similar units in this magazine are twice the price. Not a China imitation. Industrial unit. Our reg. price \$350, **NOW \$175 EA.** While they last! Pro-Vid Sys. 781-933-0827. E-Mail: RicksVideo@MSN.COM

**Don't miss a single issue!**  
Have Nuts & Volts delivered right to your door every month for only \$19 per year. Call 1-800-783-4624

## SATELLITE EQUIPMENT



**FREE BIG dish catalog.** Low prices! Systems, upgrades, parts, and "4DTV." Skyvision, 1010 Frontier Dr., Fergus Falls, MN 56537. www.skyvision.com  
Call 1-800-543-3025.



**BEST PRICING** on 18" satellite TV systems for home and RV. DSS, DISH Network programming, multi-room viewing options, accessories. www.skyvision.com  
Call 1-800-543-3025.

**1999 DSS SOFTWARE COOKBOOK 700+ CD-ROM COLLECTION:** CLONING, REVERSE-ENGINEERING, PPV, ADULT, EMULATORS, DIAGRAMS, SCHEMATICS, PATCHES, PLANS, MUCH MORE. (SPECIAL: 1ST 700 ORDERS GET 700+ ADDITIONAL PROGRAMS!) **WHOLESALE ONLY \$22 (BUY 2, GET 1 FREE!!!).** DSS TEST-CARD INFO SOURCE MANUAL \$10. VISA/MC/AMEX/COD/CHECKS/MO. BRINKER ENGINEERING LABS, USA. **CALL NOW 407-654-9677.**

**THE BEST** is back to stay. Master code recovery. 16c5x, 16c62x, PALS, GALS, other microcontrollers, etc. Check out our web page at www.acdinc.com for details or call 703-764-5361 or write Advanced Circuit Designs, Inc., 5765-F Burke Centre Parkway, Suite 317, Burke, VA 22015.

**DSS TEST CARD information.** Call toll free, 1-888-416-7296.

**FREE FLYER** on DBS files, hacking, hardware info. Smart card socket \$5 ea. New Atmel 89C52 \$10 ea. Bill 1-800-879-9657.

**SATELLITE RADIO BOOK AND GUIDE.** New book covers all Audio Services, SCPC, Subcarriers, FM Squared, Facsimile, Press Services, Weather Services. Simple how-to-receive instructions. \$16.95 plus \$3 Priority Mail. UNIVERSAL ELECTRONICS, 4555 GROVES ROAD, #12, COLUMBUS, OH 43232. 614-866-4605.

**\$25 SAT-TV 18" DISH** systems. 40 channels \$19.99/mo. **FREE** dual system, rebate and programming package required. JTI 408-988-0963.

## MILITARY SURPLUS ELECTRONICS

**WANTED: ARC-5 & SCR-274N** receivers and manuals. John Broussard, 312 Guilbeau, Breaux Bridge, LA 70517.

## AUDIO - VIDEO - LASERS

**FREE LASER CATALOG.** Helium-Neon, Argon, ruby, visible laser diode modules, lightshows, holography, laser pointers. Lowest prices. Midwest Laser Products, PO Box 262, Frankfort, IL 60423. 815-464-0085 [www.midwest-laser.com](http://www.midwest-laser.com)

**WANTED: PRO** video equipment, VCRs, switchers, cameras, etc. Advanced Media 702-874-1911.

## ACP's 93rd GIANT COMPUTER SWAP★MEET

Orange County's Original! All Day Sunday 8am-2pm  
**Sept 26th**  
**FREE** Admission & Parking  
Shop 100's of Sellers  
in ACP's Giant Parking Lot !!!

Advanced Computer Products, Inc.

**ACP SUPER★STORE**  
Since 1976

1310 E. Edinger  
Santa Ana, CA  
714-558-8813



## CABLE TV(MMDS) CONVERTER

Our converters are designed for your specific need

**85 Ch Plain Converter, Ch-3, AFT/MFT**  
PG Lock, HRC/STD and Sleep Timer  
Price: between \$29 - \$49

**99 Ch Plain Converter, Ch-3, AFT/MFT**  
PG Lock, HRC/STD and Sleep Timer  
Price: between \$49 - \$69

**125 Ch Volume Converter, Ch-3/4 out**  
ACW/MFT, PG Lock, HRC/STD and Sleep Timer  
Price: between \$59 - \$89

**FREE BROCHURE**  
CALL (310)515-5085 or  
FAX 1-800-579-5000

PCW Company



**ATV 2.2GHz to 2.7GHz** wireless video data link module tuner & transmitter 100mW. Picotronic, web: <http://members.aol.com/picotronic/atv.htm>

**SONY PLAYSTATION MODCHIPS.** Allows playing of CDR backups & imports. \$10 + \$3 shipping. 619-590-9320.

**BROADCAST VIDEO** equipment wanted: all types, new or old. Please call, Jon with info. 1-800-539-2859.

**STEALTH MOD** chips for Sony PlayStation. Now even your anti-mod games will work. Only \$9.95 ea. + \$3.35 shipping. Call Toll Free 1-888-467-6150. All credit cards accepted. [www.computerconnectionusa.com](http://www.computerconnectionusa.com)

**GAME WIZARD** cartridge for PlayStation. Works like a mod chip and the best cheat cartridge all in one. It will use all the same cheat codes the others use. Only \$29.95 free shipping. Toll Free 1-888-467-6150 all credit cards accepted. [www.computerconnectionusa.com](http://www.computerconnectionusa.com)

**LASER SHOW SYSTEMS AND COMPONENTS.** Hobby and professional projectors. [www.redline-lasers.com](http://www.redline-lasers.com)



**SYNC-A-LINKS's 3-D Scopers™** digital color CCD cameras for stereoscopic imagery. At a reasonable cost. Phone or Fax 918-479-6451 or write to Sync-A-Link, PO Box 4, Locust Grove, OK 74352.



**ANTIQUE VIDEO TRANSFER SERVICE:** transfer any 2" QUADRUPLX tape. Affordable fast! Phone/fax 415-821-7500 or 415-821-3359. 5001 Diamond Heights Blvd., San Francisco, CA 94131-1621.

**SYNC-A-LINK UNIVERSAL video sync generators.** For more details phone or fax 918-749-6451 or write to Sync-A-Link, PO Box 4, Locust Grove, OK 74352.



**CONVERTS PC MONITOR to SECURITY MONITOR.** The VGA-801 accepts standard NTSC or PAL inputs for display on any existing VGA/SVGA computer monitor. Small compact size, 4-1/2" x 2-1/2" x 3/4". Over 600 lines of resolution, twice that of standard TV monitor! High quality audio output feeds speakers directly. Excellent grey-scale conversion; works well with B/W inputs. Power supply included; \$69 each. Dealers welcome. MATCO, Inc., 1-800-719-9605; Fax 847-619-0852; E-Mail: [sales@mat-co.com](mailto:sales@mat-co.com) Website: [www.mat-co.com](http://www.mat-co.com)

**FACTORY VIDEOS:** \$5-\$10, new Sony color circuit board camera, \$50. 310-515-2058.

**LASER, OPTICS** equipment suitable for Schlieren system or holography, 619-223-4983.

## CABLE TV

**CABLE PARTS & EVERYTHING.** Best prices & quantity discounts. WE DON'T SELL BOXES. 1-800-MODULE-0.

**SONY PLAYSTATION MODCHIPS.** Allows playing of CDR backups & imports. \$10 + \$3 shipping. 619-590-9320.

**GENUINE UNMODIFIED JERROLD DPBB 7312.** 410-485-7772. E-MAIL: [CLEWIS7298@AOL.COM](mailto:CLEWIS7298@AOL.COM)

**CABLE BOX** repairs and upgrade. Most models, warranty lowest prices. Call 214-695-5982.

**DTV & DISH NETWORK INFORMATION (36 pages)** only \$15. Mainline Electronics, Inc. Call toll-free 1-877-856-0923. **Cable television supplies DIRT CHEAP!** Plus descrambling plans for all systems, call 1-877-880-0197. [WWW.MELECTRONICS.COM](http://WWW.MELECTRONICS.COM)

**NEW! CABLE** converter electronic service equipment and supplies for most cable converter boxes. Highest service, lowest prices. Call Ken Erny Electronics. 24 hr. order and information hot line 516-389-3536.

**CABLE CONVERTERS.** Original equipment with remote. Like new, ready to go. Lowest prices guaranteed. Limited models. Novicor Electronics, 412-833-0773.



**NOTCH FILTERS** 110, 108.5, 106.5, 97.5 75dB deep notch. \$19.95 ea., 1-5 qty. \$15.95 ea., 6-10 qty. \$11.95 ea., 11-20 qty. \$9.95 ea., 21 or more qty. Call 24 hr. order and information hot line 516-389-3536.



## RAINBOW KITS

### TV NOTCH FILTERS FOR CHANNELS 2 thru 22 ONLY



Our TV filters eliminate unwanted TV channels or interference that alters both sound and video with a BEEP BEEP BEEP. Works on cable channels (2 thru 22) only.

NOTE: All TV Filter Kits are sold for educational purposes only. You must obtain permission from your local cable company before using these filters on your cable system.

DF-222 KIT \$14.95

### FLASHING SAFETY LIGHT

- Push ON / Push OFF switch.
- Flashes 3 weeks on 2 AAA batteries.
- Great for kids, bike riders and joggers.
- Keep in car for emergencies.
- Tough ABS case with belt clip
- Size: 1 3/8" x 2 1/4" x 1 1/8"

BFL-3 BUILT \$6.95  
2 for \$9.95




### FAN CONTROLLER

Use this kit to control cooling fans, or any device that is temperature activated. Output is 100mA. For a 3 Amp application use the Relay kit RP-1 or the new Micro-controlled Relay PRC-1 kit. Temperature probe included. Operating voltage: 7.5 to 18v DC. Size: 1.5" x 1.2" (Temperature Range 32°-200°F)

FC-1 KIT \$14.95
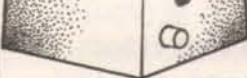
### FM STEREO TRANSMITTER

Have your own FM radio station. Any stereo signal you plug into the FMST-100 transmitter kit will be transmitted to any FM radio tuneable from 76 to 108MHz FM. Plug in your CD player, tape deck and have a wireless link to any FM radio, within 200 ft. Listen to your CD while mowing the lawn. Transmit from your car to your camper, or through an auditorium. Transmit music on one channel sing on the other. Compatible with any audio system. Clarity is excellent, approx. 40dB stereo separation. Length of antenna determines distance of transmission. Comes complete with left & right input level control as well as a crystal for left & right stereo separation. ANTENNA NOT INCLUDED 9v Battery operation.



FMST-100 Cabinet SIZE: 1.5" x 1.6" KIT \$29.95  
SIZE: 1.5" x 2.5" x 3" \$8.95

### RAINBOW MINI-LIGHT Super Bright Flashlight

- LED's don't burn out!
- Battery lasts for years!
- If you have your keys, you'll have a flashlight.
- Replaceable battery!
- Better buy 2, your wife is going to take yours!

Lights up a complete bedroom at night

Red MLR \$9.95 each  
Yellow MLY  
Blue MLB \$12.95 each  
White MLW  
Infrared MLI



### LIE DETECTOR

This kit can be great fun at parties. When you lie, generally your hands will sweat and the more you sweat the louder the tone. This kit allows you to measure these changes, only a slight amount of change will cause the tone to increase in frequency. Power requirement 6 to 12v DC. SIZE: 8" x 1.2"

LD-1 KIT \$9.95



### BUSY PHONE LIGHT


Add this little kit to any or all of your telephones. When one phone is used a red LED will light on the other extension. This lets everyone know when your computer modem is in use. Power requirement 9v DC. SIZE: 1.1" x .8"

TEL-LITE KIT \$9.95



This Manual contains schematics, parts lists & P.C. board layouts for many of the Rainbow Kits. Use your own parts to construct our kits.

KIT BOOK \$14.95

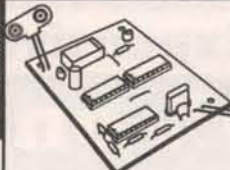

### Sweet 16 TONE DECODER

Sweet 16 tone decoder operates great over phone lines, radios or scanners.

- 16 TTL Level Outputs
- DTMF Decoder Decodes 16 different touch tones using the phone, radios, or scanners.
- One relay & driver circuit on board.
- 9v battery powered. Size: 2 3/4" x 2 1/8"

TT-16 KIT \$34.95

# SUMMER SALE

EVERYTHING IN OUR AD IS

# 20% OFF

Sale Ends September 15, 1999



### SUPER SNOOPER BIG EAR

Listen through walls, hear conversations across the room. Add a parabolic reflector and hear blocks away. The BIG EAR can be hidden about anywhere. Makes an ultra sensitive intercom. Can be used as a 1.5W AMP. We supply a mini-electret mike in the kit. Power requirement 6 to 12v DC. SIZE: 1.75" x 1"


AA-1 BUILT \$29.95 KIT \$10.95



### AUDIO PREAMP

Boost your microphones output up to line level! Plug your mic into our AP-1 and drive your amp. to full capacity. Connect an AP-1 to a pair of amplified speakers, plug your mic in and you have an instant PA system. Requires 6 to 12v DC. Size: 1.75" x 1"


AP-1 KIT \$9.95

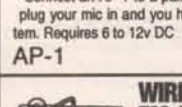

### WIRELESS FM MICROPHONE

Small but mighty this little jewel will out perform most units many times its price. It really stomps out a signal. The WM-2 kit is a buffered wireless mike that operates from 80MHz to 120MHz FM, the frequency of any broadcast FM radio. Includes a mini-electret mike, 6 to 12v DC. SIZE: 1.25" x 1"


WM-2 KIT \$14.95

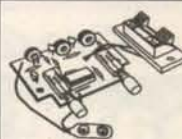

### INDUCTANCE METER

This is the kit everyone has been asking for. Turn your digital volt ohm meter into an inductance meter. It will read inductors 3uH to 7mH. Power requirement 9v DC. SIZE: 1.75" x 2.5"


IA-1 KIT \$14.95  
IA-1CABINET \$8.95

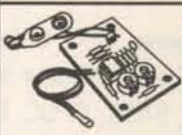

### DIGITAL THERMOMETER

The DT-3 kit will turn your digital volt ohm meter into an accurate digital thermometer with .1 degree resolution. Measure temperatures from -40° to 250°F. The remote sensor is .25" sq. and can be mounted many feet from the meter. Power requirement 9V DC. SIZE: 2" x 1.35"

DT-3 KIT \$8.95

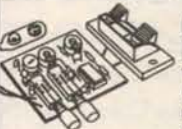

### CAPACITANCE METER

This kit will turn your digital volt meter into a capacitance meter. Turn that junk box of unmarked capacitors into a fortune of usable parts. Measure capacitors from <2.2pF to 2.2uF. Power requirement 9v DC. SIZE: 1.80" x 2"

CA-1 KIT \$12.95



### VOICE ACTIVATED SWITCH

This VOX circuit can be used to operate a tape recorder, ham radio, CB radio, or turn on an alarm. The VOX-1 kit has 100mA of output that operates a relay, light, motor, ? What could you do with a sound activated switch? Power requirement 7.5 to 18v DC. SIZE: 1.5" x 1.3"

If you want to switch more power see our Triac (TP-1) or Relay (RP-1) Power kit.

VOX-1 KIT \$6.95



### PHONE RECORDING SWITCH

This phone line powered switch is small enough to be installed anywhere. Every time the phone is picked up the recorder will record both sides of the conversation automatically. Use it in your office to record all phone calls so you don't lose important information. SIZE: 1" x .6"

If you want to switch more power see our Triac (TP-1) or Relay (RP-1) Power kit.

TEL-SW1 KIT \$12.95



### DC VOLTAGE MONITOR

If battery status is important, you need this kit. This kit uses 7 LEDs to monitor 12v DC in 1v, 1/2v, or 1/4v steps. Monitor 8v or 5v in 1/4v steps. Great for boats, motor homes, model planes or race car rigs. All parts and instructions are included. SIZE: 1.3" x 2.7". If you want to switch more power see our Triac (TP-1).

VM-1 KIT \$7.95  
For 110 AC VM110 KIT \$10.95



Please add sufficient postage First lb \$5.50 Canada \$7.50 Additional LB. add \$1.00 US FUNDS ONLY We will accept telephone orders for Visa or Mastercard  
**Electronic Rainbow Ind., Inc.**  
6227 Coffman Rd. Indianapolis, IN 46268  
CALL 317-291-7262 FAX 317-291-7269  
INTERNET: [www.rainbowkits.com](http://www.rainbowkits.com)



**PLAYSTATION MOD** chips. Works with all models up to 750x. Color instructions. Seven wire hook up, does not come with wires. \$5 each, plus shipping charges. 10% discount for 10 or more. Call 703-764-5118 to place an order.

**GENUINE UNMODIFIED JERROLD DPBB7312 FOR SALE 10 LOT MIN. CALL 708-715-6118.**

**WANTED: GENUINE RAW UNMODIFIED CABLE TV CONVERTERS. TOP CASH PAID. CALL 708-715-6118.**

**PICS, GALS READ** if you've lost your masters. Programming service available. Call for info. Network Sales, 616-683-0500.

**CABLE TV. Panasonic TZPC 175DG2, brand new, \$80 w/volume, 1 year warranty, minimum 10 pcs. any qty., plus all major brands available. Lowest price new/field pulls. E-Mail: OCALA@BELLSOUTH.NET phone: 1-800-929-1549 fax: 305-220-9396**

**CABLE CONVERTERS, DBS, remotes, schematics, etc., free flyer. Smart card socket \$5 ea. New Atmel 89C52 \$10 ea. Jake 419-385-3100.**


**RAW CONVERTERS:** We have the best quality to your cable needs. PI-5135 \$45 ea.; Zenith ST-1600 \$75; S/A 8590 (11-B) \$85 ea.; S/A 8590 (10-B) \$75 ea. Please call for others not listed. 405-634-1535.

**PLAIN CONVERTERS:** Brand-new, the most reliable in the market today. Philips ECG-TV-3000, 181-channel only \$75 ea.; Refurbish Panasonic TZPC-145, \$35; Panasonic TZPC-175, \$39 minimum 10-lot, 1 full year warranty, same day shipping. 405-634-1535.

**UNMODIFIED CABLE CONVERTERS.** Zenith ST1600, ST1086, ST300, Panasonic 175, 145 vol. & non-vol. Regal RR-92 & RC 83, DP5, DP7, DRZ, 5503 VIP, SA 8580. Guaranteed low prices. Please call for more converters 405-631-1856.

**BRAND NEW** basic converters, 550MHz w/remote, \$19.95 ea. 10 lot min. Call 706-657-4445.

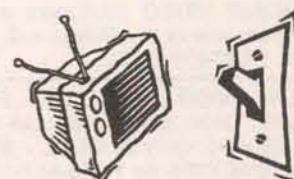**THE BEST** is back to stay. Master code recovery. 16c5x, 16c62x, PALS, GALS, other microcontrollers, etc. Check out our web page at [www.acdinc.com](http://www.acdinc.com) for details or call 703-764-5361 or write Advanced Circuit Designs, Inc., 5765-F Burke Centre Parkway, Suite 317, Burke, VA 22015.



**EXPLOSIVE CABLE TV GRAB!** BRINKER ZAPPER/SNOOPER STOPPER combo module all in one! Buy wholesale factory-direct, no middleman. Let others get fined + zapped instead. 100% COMPATIBLE. Your order shipped NATIONWIDE immediately! **LIFETIME GUARANTEE!** VISA/MC/AMEX/COD/MO/CHECKS. ONLY \$10 (SPECIAL: 3/\$20 plus FREE DESCRAMBLER PLANS!). **SUPER ZAPPER MODULES ONLY \$16! (3/\$33)!** Use **SUPER ZAPPERS** if you have COX, TCI, WARNER in: CA, TX, FL, NY, PA, MI. **DESCRAMBLER PLANS (4=\$5, 20=\$15) 130+ DESCRAMBLER SOURCES (\$5).** **FREE SHIPPING. OPEN 24 HOURS!** 407-654-9677. **BRINKER ENGINEERING LABS, USA.**

**PLANS: DESCRAMBLE CABLE FOR UNDER \$12. PLUS TWO FREE BONUSES. TOLL FREE 1-888-588-3715.**

**CABLE PARTS!** Computer parts. Call for great prices or visit us on the Web: [HTTP://WWW.CB-Electronics.com](http://WWW.CB-Electronics.com) or call 1-800-436-8630.

**CABLE DESCRAMBLER plans!!!** Plus two free bonuses: radar jammer plans & cable manual, \$14. 1-888-367-9972.

**POSITIVE NOTCH filters.** Channels available: 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15, 16, 17, 18, 19, 20, 21, 22, 23, 24, and 25, \$16 each. Channels 26, 27, 28, 29, 30, and 31, \$19 each. Channel 39 \$25 each. Order by single channel. Top quality non-tunable metal cylinder types. 75dB deep on notch. Need to block the video on a cable channel til the kids do their homework, order a negative notch filter from our company. We carry large stock on all channels. Visa, MasterCard, Discover and UPS COD. "The Filter Company" Quantity pricing on 5 or more. 100 pcs. \$7 each. Call 1-800-235-8080. On the web go to [www.gofilters.com](http://www.gofilters.com) lots to see. Open 8am to 5pm Central Standard Time, Monday-Friday. All sales must comply with FCC 1996 cable act.

**AUCTION AUCTION Auction.** Join us online to buy and sell. [www.cabletv-auctions.com](http://www.cabletv-auctions.com) We have a lot to see. Companies and individuals can put equipment up on the Internet. Cable TV equipment, computers, electronics, telephony, and anything else related. Sell surplus electronic equipment. Phones, faxes. Join us online or call for details. 1-888-451-0083. We advertise in the following publications: USA Today, Nuts & Volts, Popular Electronics, Electronics Now, Popular Science, and Popular Mechanics. Our website is taking 10,000 hits per month. Call to advertise your company. We also advertise in small newspapers in the USA and Canada. You now have pure exposure to the world. Let us help you sell your equipment.

**ATTN. DEALERS:** Are you a current dealer or just getting started? Buy factory direct & save. New 125 channel volume control converter, 800MHz tuner. Also available non-volume converters. Call for lot pricing. A & S Wholesale, 1-800-370-0801.

**TOCOM UNMODIFIED 5503 cable converters, untouched, \$6 ea. 10 lot min. Call 706-657-4445.**

## Tired of Expensive Inkjet Cartridges ? Save 90% on Inkjet Inks !

Printer	# of Refills		Cost/Refill		Kit Price	
	Black	Color	Black	Color	Black	Color
HP 500 Series, 400, Officejet 300, 350, Fax	7	14	4.71	2.85	32.95	39.95
HP 600 Series, Officejet 500, 570, 600	7	14	4.71	3.21	32.95	44.95
HP 820C, 855C, 870C, 1000C, 1150C, Copier 120, 210	6	10	6.67	4.00	39.95	39.95
HP 720C, 722C, 712C, 880C, 890C, 895C 1120C, 1170C	6	10	6.67	4.50	39.95	44.95
Canon BJ-10, 200, 210, 240, 250 Apple SWriter 1200, 1500	14	20	2.15	2.00	29.95	39.95
Canon BJC-4000 Series, C2500, C3000, C3500, C5000	60	60	0.50	0.67	29.95	39.95
Apple StyleWriter 2400, 2500						
Canon BJC-600, 610, 620 Apple SWriter Pro	20	13	1.50	3.07	29.95	39.95
Epson Stylus Color, Color Pro, Pro XL	12	12	2.50	3.33	29.95	39.95
Epson Stylus Color II, IIs, 1500 (Black)	15	15	2.00	2.66	29.95	39.95
Epson Stylus Color 500, 200	20	17	1.50	2.35	29.95	39.95
Epson Stylus Color 400, 600, 800, 850, Photo	20	17	1.50	2.65	29.95	44.95
Lexmark JP 1000, 1020, 1100, ExecJet II, IIC, Medley 4C	10	17	3.00	2.35	29.95	39.95
Lexmark JetPrinter 5700, 5000, 7000, 7200, 3200	15	17	2.67	2.35	39.95	39.95
Compaq IJ700, IJ900, Xerox XJ9C	15	17	2.67	2.35	39.95	39.95
Xerox Home Center 450C, XJ6C Inkjet	22	12	1.36	3.33	29.95	39.95

## SAVE 30 - 50% on New Compatible Cartridges!

Printer	BLACK	COLOR
	CARTRIDGE	CARTRIDGE
Canon BJC-4000 Series, C2500, C3000, C3500, C5000	\$5.50	\$12.95
Apple StyleWriter 2400, 2500	\$5.50	\$12.95
Canon BJC-600, 610, 620 Apple StyleWriter Pro	\$4.95 (9cc)	\$4.95 @ (9cc)
Hi-Capacity Canon BJC-600, 610, 620	\$5.95 (15cc)	\$5.95 @ (12cc)
Canon BJC-70, BJC-80	\$9.95 (3-pak)	\$14.95 (3-pak)
Epson Stylus Color, Color Pro, Pro XL	\$12.00	\$19.00
Epson Stylus Color II, IIs	\$14.00	\$19.00
Epson Stylus Color 500, 200	\$14.00	\$19.00
Epson Stylus Color 400, 600, 800, 850, 1520, Photo	\$14.00	\$19.00
Epson Stylus Color 440, 640, 740	\$14.00	\$19.00

- BULK Inks, Refill Accessories
- Glossy card stock & Coated Paper
- School & Government PO's Welcome
- 2 - 3 Day Shipping

**Quality Inks for:**  
HP • Epson • Lexmark  
Canon • Apple • DEC

**Call or see us online!**

Monday - Friday  
8:30 - 5:30 PST 11:30 - 8:30 EST

**Inkjet**

**Southwest**



[www.inkjetsw.com](http://www.inkjetsw.com)

(480) 668-1069 Fax

**1-800-447-3469**

(480) 668-0959



**UNMODIFIED CABLE** converters. SA 8590, \$39.95 ea. 10 lot min. Call 706-657-4445.

**ZENITH UNMODIFIED** converters. ST 1000-288, \$16 ea. 10 lot min., ST 1086, \$25 ea. 10 lot min., ST 1600, \$59.95 ea. 10 lot min. Call 706-657-4445.

**BOARD R US**, for all your cable needs or computer software, programming service available. 4 MHz resonators 3 pins as low as 34¢. For info call 909-948-3736 or visit us at our web site <http://members.aol.com/BoardRUS>

## TELEPHONE/FAX

**PHONE SYSTEMS WANTED!!!** We buy AT&T MERLIN, SYSTEM 25/75/85 and other AT&T phone systems. Please call for a quote or fax us your equipment list. **KEYWAYS, INC.**, 937-847-2300 or FAX 937-847-2350.



**CELLULAR CLONING COLLECTION.** 1999 CELLULAR CLONING INFO BIBLE \$22, 1999 CELLULAR CLONING SOFTWARE COLLECTION \$33, 1999 CELLULAR SECRETS & PROGRAMMING MANUAL \$11. ALL 3 FOR \$44, WOW!! (SAVE \$22). FOR EDUCATIONAL/TECHNICIAN TESTING USE ONLY. (VISA/MC/AMEX/COD). OPEN 24 HOURS! 407-654-9677. BRINKER ENGINEERING LABS, USA.

**12 HOUR** fully automatic heavy duty professional **TELEPHONE RECORDER**, \$79 including shipping. Send check or money order to: **VAKIS**, 1402 Pine Ave., Niagara Falls, NY 14301.


**CELLULAR PHONES & equipment.** 1-800-735-6944, 24 hrs., include area code.

**FOR SALE:** All items new in MFG box. Toshiba, computer, telephony-system, PC Strata, DK 424, Iwatsu-build Adix, vs to suit your needs. Cortel Co., Aries, digital, key-system, ADKS 144, ACB cards for many applications. Send for mfg. items list. Ohio Service Supply Co., PO Box 8802, Canton, OH 44711.

**AT&T TELEPHONE** hardware, NOS, 24 boxes, \$200. List available. 904-362-1521, leave message. [rmorison@suwanneevally.net](mailto:rmorison@suwanneevally.net)
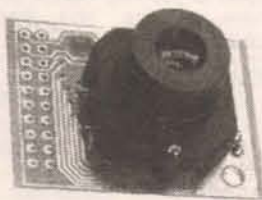
## COMPONENTS

**SEE OUR** ad on 4-channel 2.4GHz wireless system in the AdMart section on page 81. Matco, Inc.



**B/W 1/4" CMOS CAMERA** module with digital & analog 75W output, \$65.95 + \$4.95 shipping (code CM4881). 5V. Size: 35 x 29 mm, lens: f7.4mm, F2.1. non-interlace (progressive) scan. Programmable exposure setting, image size & frame rate (0.5-50fps). See [www.electronics123.com](http://www.electronics123.com) for full details. Amazon Electronics, tel: 1-888-549-3749.

When Visiting Disney World And Sea World... Come To The World Of Electronic Surplus!

## SKYCRAFT

PARTS & SURPLUS, INC.  
ORLANDO, FLORIDA



Located At The Intersection Of I-4 And Fairbanks Avenue.

Self-Service Retail Outlet Featuring Commercial And Government Electronic Surplus Including:

- |                    |                       |
|--------------------|-----------------------|
| ★ WIRE             | ★ COAX                |
| ★ SWITCHES         | ★ RELAYS              |
| ★ RESISTORS        | ★ HARDWARE            |
| ★ TRANSISTORS      | ★ CAPACITORS          |
| ★ TRANSFORMERS     | ★ PANEL METERS        |
| ★ TEST EQUIPMENT   | ★ CIRCUIT BOARDS      |
| ★ NI-CAD BATTERIES | ★ INTEGRATED CIRCUITS |


### HOURS:

Monday - Friday 8:30-6:00  
Saturday 8:30-5:00

★★★★★★★★★  
We Buy Surplus  
Electronic Parts —  
FAX your list.  
[www.skycraftsurplus.com](http://www.skycraftsurplus.com)  
FAX 407/647-4831  
PH 407/628-5634  
P.O. BOX 536186  
ORLANDO, FLA. 32853-6186



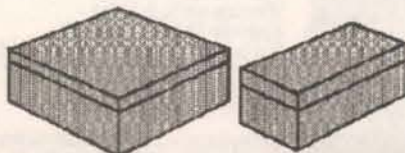**RF TRANSISTORS, TUBES, SD1446, MRF455, MRF454, 2SC2290, 2SC1969, 2SC2166, 2SB754, TA7222AP, 2SC1947, TIP42C, KIA7217, MRF422, MRF448, MRF247, MRF317, SAV7, SAV17, 3-500ZG, 4CX250B, 572B, 3CX400A7/8874, 3CX3000A7, 4CX400A, silver mica caps, resistors, electrolytics, etc. Westgate 1-800-213-4563.**



**POCKET MINI-BOXES:** Small plastic boxes. High quality, LOW COST! Low as \$0.49. Attention manufacturers! Great for products! 805-339-0702.  
[www.ElectronicsUSA.com](http://www.ElectronicsUSA.com)




**AMAZING! 35¢ ALL TOGGLE SWITCHES.** Brand new. Rated 6A/125V. Hardware included. 1/4" panel hole. SPDT or DPDT on-on, or on-off-on. Minimum 100pcs./package. Add \$6 freight. Gateway Products Corporation, PO Box 936397, Margate, FL 33093, 954-974-6864, Fax: 954-974-6818, VISA/MC, no COD.

**CASH PAID FOR ICs.** Military or commercial integrated circuits, transistors, diodes, any semiconductors. **ELECTRONIC SURPLUS, INC.**, 5363 Broadway, Cleveland, OH 44127. 216-441-8500 or fax 216-441-8503, since 1946. [www.electronicsurplus.com](http://www.electronicsurplus.com)
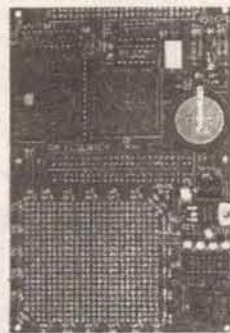
## MORE POWER!


68HC11, 80C51 & 80C166

AM Research supports over 30 of the most popular Embedded controllers with both **hardware** and **software**.



- ✓ More Microcontrollers
- ✓ Faster Hardware.
- ✓ Faster Software.
- ✓ More Productive.
- ✓ More Tools & Utilities.
- ✓ IIC Peripherals.
- ✓ Single Chip Capable.
- ✓ Outstanding Support.
- ✓ Custom designs.

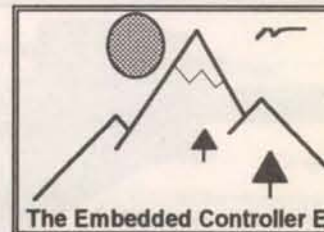Call or email for a free full line brochure



Orders (800) 949-8051  
Info (916) 652-7472  
fax (916) 652-6642  
[www.amresearch.com](http://www.amresearch.com)

**AM Research, Inc.**  
PO Box 43  
Loomis, CA 95650

The Embedded Controller Experts

Write in 105 on Reader Service Card.



**B/W 430 LINE CCD CAMERA** with optional black low-profile swivel adjustable enclosure. Pin hole or Std. lens type. 6, 8, and 12mm lens are available. 1/3" CCD, 3.6mm/F2.0 lens included; 9-14 VDC, 0.08 lux, IR sensitive; 1.27" x 1.27" x 0.5"D pinhole or 1" deep standard. Price @ 10 pcs., \$44 each. Enclosure: \$8; optional lens: \$18. Dealers welcome. MATCO, Inc. 1-800-719-9605. Fax 847-619-0852. E-Mail: [sales@mat-co.com](mailto:sales@mat-co.com) Website: [www.mat-co.com](http://www.mat-co.com)



## TZPC-175 Converters

\$39.00

20-lot



THE BEST  
DEALER  
PRICING

**Centurion: CF-3000**  
(Brand New)  
True, 99-Channel

\$49.00

20-lot

**Intek Electronic Systems**  
405-634-1535

- ✓ Call for other models
- ✓ One stop shop
- ✓ Same day shipping
- ✓ One full year warranty

Write in 106 on Reader Service Card.



**WANT TO Buy:** ICs, military & aircraft relays, diodes, transistors, Cannon, TRW, Amp, Burndy, Deutsch, Bendix connectors, electronic test equipment & most components. Hoffer Electronic Ent., 818-718-1165, FAX 818-341-5506. E-Mail: Hoffer1165@aol.com

## MICROCONTROLLERS

WIN \$500 USD cash dontronics.com

**Closing Date**  
For Next Issue - August 5th



**PIC MICROCONTROLLER PROGRAMMER KIT.** Super value at \$19.95 + \$4.95 shipping. See our web site for the complete range of PICs that can be programmed. Includes PCB, parts and instructions. P16PRO shareware must be downloaded from the web. Amazon Electronics, tel 1-888-549-3749. Lots of other products. [www.electronics123.com](http://www.electronics123.com)

## ANTIQUE ELECTRONICS

**WANTED: FOR** historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 24091-0341 (540-763-3311/540-382-2935).

**CRYSTAL SETS.** Parts, plans, books, kits. Largest source in the world. Catalog \$2. MIDCO, PO Box 222288, Hollywood, FL 33022.

**RADIO TUBES** and phono. needles. 870-347-2281.

**WESTERN ELECTRIC** wanted: 1920s-1960s. Amplifiers, mixers, pre-amps, speakers, tubes, etc. FREE OFFER 1-800-251-5454.

## AVIATION ELECTRONICS

**BUY, SELL,** trade, avionics equipment, Collins, King, Sperry: test equipment, IFR, Litton LTN series INUs. 941-625-3222 P, 941-625-0494 F, E-Mail: [avionics@afcon.net](mailto:avionics@afcon.net)

## PUBLICATIONS

**Discount electronics books.** See the NV Bookstore ad on page 91.

**Handbook of Radio and Wireless Technology,** by Stan Gibilisco \$44.95 10% discount to *Nuts & Volts* subscribers. Call 1-800-783-4624 to order using Visa or MasterCard.

**Programming and Customizing BASIC Stamp Computers.** By well known author Scott Edwards, originator of the *Nuts & Volts* Stamp Applications column. Only \$34.95. 10% discount to *Nuts & Volts* subscribers. Call 1-800-783-4624 to order using Visa or MasterCard.

**WEBBOOKS OFFERS** discount prices on technical/engineering books plus free assistance to authors. Please visit us at <http://webbooks.net>

**NEW SURVIVAL COMMUNICATIONS BOOK.** How to build complete home communications systems. Covers all needs: shortwave radio, amateur radio, citizens band, scanners, federal, weather, alternate news, satellite radio, equipment sources. How to build and use alternate emergency power sources, solar, generators, backup batteries. 200 pages. \$24 Fast delivery Priority Mail. MC or Visa. Call Universal Electronics 1-800-241-8171.

**TORMET'S ELECTRONICS BENCH REFERENCE** is now at REV03. More laser, op-amp and Tesla coil circuits. New optics and statistics pages. Check the web site at [www.ohio.net/~tormet/index.htm](http://www.ohio.net/~tormet/index.htm) or send \$19.95 + \$2.50 postage to RMT Engineering, 6863 Buffham, Seville, OH 44273.

**CONTROL SPEECH,** robotics, etc., with your brain waves and PC, provide electronic speech for canines. Book and video tape, \$9.95. Rose, PO Box 7589, Chula Vista, CA 91912.

**31 PAGE** book measuring SWR & things every CB'er should know, \$3.95 postpaid. Riley's Electronics, PO Box 142, Harrisonburg, VA 22801.

## ROBOTICS

**ROBOT BOOKS.COM** visit our web site for reviews of robotics books, plus robot kits, toys, movies, and magazines! [www.robotbooks.com](http://www.robotbooks.com)

**H-BRIDGE MOTOR** controllers, 12VDC, 35A average, 50A peak PWM out. Forward, reverse, ramp-up and ramp-down on acceleration/deceleration. Current foldback when hot, reverse polarity protected, conformal coated, regenerative braking, compact, approx. 3.75"x5.5". \$25 & S&H. 570-735-5053. <http://members.tripod.com/~divelec>

**www.futurorobots.com** ROBOTS are coming soon to our homes. Most of the technology is now here, as well as the need. Read technical papers and construction articles for active security systems.

# PROFESSIONAL DESOLDERING with the World's Best Transportable, Totally Self-Contained Desoldering Tool



**Mike Murphy - Service Center - Van Nuys CA** 818-785-7805

The single best investment of repair equipment we've made. It outperforms all other desoldering tools we've used. Easier to use and least expensive.

**Dick Manning - Dicks Electronics - Hartland WI** 414-367-8339  
The ease & speed of component removal greatly increases productive time. The SMD kit makes SMD removal a breeze, even for inexperienced Techs.

**Don Scott - LAV Electronics - Healeah-Miami Lakes FL**  
I am a constant user of the SC7000 Desoldering Tool and for quick component removal, this unit has no equal. It also comes with excellent company support. I am very satisfied and highly recommend it to anyone in the servicing field.

**George Hefner - Hefner Electronics - Coleridge NE** 402-283-4333  
Being a one-man service center, I hesitated to spend the money on a desoldering tool, however all that changed when I nearly ruined a \$400 computer logic board. It has cut my desoldering time by 50%.

**Don Cressin - Certified Electronics Service - Ellicott City MD** 301-461-8008  
We have obtained excellent results with the SC7000 including repairing high density U/V tuners. It is one of the best purchases we have made.

**Doug Pettit - LuRay Electronics - LuRay VA** 703-743-5400  
We found that the SC7000 not only saves money vs. wick, but saves valuable time in troubleshooting. It allows you to be more accurate in removing SMD's.

MSRP \$475.00  
Sale Price \$395.00

**FREE TRIAL**  
Available on Request

Price includes  
stand worth \$25.00  
one extra filter and  
two tip cleaners.

**Timothy Kraft - Monikraft, Inc.**  
Cherry Hill NJ 609-751-3252  
We replaced all our existing desoldering stations with the SC7000. Our technicians are very pleased with the improved performance, portability, and reliability over our previous higher priced equipment.

**Bill Warren CET/CSM - Warrens Audio & Video - Knoxville TN** 234-546-1128  
We have been extremely satisfied with the quality and durability of the DEN-ON SC7000 as well as with after the sale support.

**Keith Sahs - J & M Electronics**  
Omaha NE 402-291-7100  
It's a must tool for my bench. I can desolder multiple pin IC's quickly and clean. It will even take up large solder amounts on tuner and case grounds.

**For More Info**  
and 5% Savings Go To

[www.howardelectronics.com/den-on/sc7000zb.html](http://www.howardelectronics.com/den-on/sc7000zb.html)

# DEN-ON SC7000Z

**Sale Price**  
**\$395.00**

## New Features

- ◆ Totally Self Contained diaphragm vacuum pump and AC motor for high vacuum suction or reversible hot air blow for SMD removal.
- ◆ 100 Watt Ceramic heater with zero-crossover switching heater control circuit which prevents spikes and leakage currents.
- ◆ Unique patented long lasting filter cartridge design. Solder builds up on easily cleaned baffle, while air flows around the outside of baffle.
- ◆ Totally ESD Safe. The housing contains carbon and the tip is at ground potential for complete ESD Protection.

**Howard Electronic Instruments, Inc.**  
6222 N. Oliver Kechi, KS 67067

## New Specifications

- ◆ Voltage—AC 100v, 120V, 230V, 50/60 HZ
- ◆ Power Consumption—120W
- ◆ Pump—Diaphragm Type
- ◆ Motor Output—12W
- ◆ Vacuum Attained—650mm Hg
- ◆ Temperature Range—300° C—500° C (572° F—932° F)
- ◆ Air Flow Rate—15 Liter/Minute (Open)
- ◆ Heater—100W (Ceramic)
- ◆ Control System—Feed Back Zero Cross-over Type
- ◆ Net Weight—420 Grams

Visa - M/C - Discover - American Express - Terms to Qualifying Companies  
30 Day Money Back Total Satisfaction Guarantee - One Year Parts and Labor Warranty

**HOWARD ELECTRONIC INSTRUMENTS INC**  
Your Desoldering Specialists

Toll Free U.S. and Canada  
**1-800-394-1984**

[www.howardelectronics.com](http://www.howardelectronics.com)  
[sales@howardelectronics.com](mailto:sales@howardelectronics.com)  
International (316) 744-1993  
or Fax (316) 744-1994



# TOP 10 SOLAR PV POWER APPLICATIONS

by Kenton Chun

**When choosing an application for solar power, it is important to consider the practical end, as well as the fun of it.**

**S**olar-powered projects can be expensive, so the cost must be justified against the benefits. This month, we'll look at 10 applications of solar power that will show positive cost benefits to the hardware hacker for implementing them. This should keep even the bean counters happy!

Solar panels, or PV (Photo Voltaic devices), generally have a relatively high initial cost, and a long pay back period. However, for technological devices, they also have a surprisingly long depreciation period.

Well-maintained solar panels can provide constant power for well over a decade. Newer solar panels are guaranteed for 20 years! Compared to a personal computer — which is usually obsolete inside of three years or less — solar panels can be a good long-term investment — if you have an application for them.

Understanding how solar panels work is important if you are going to try to recover their initial cost. Obviously, they do not work in the absence of direct sunlight. Their efficiency is hampered by clouds, shadows, and other sun obstructions.

Sizing the panels to the specific applications you are employing them in is vital in order to minimize cost. And you may need to redesign the application to some extent, in order to accommodate the solar panel's operational requirements and limitations. In some areas of the country, it is possible to run an entire household off of a large PV array (Figure 1).

## 1. REPLACING ALKALINE BATTERIES

When you realize that the average household contains devices employing over 200 batteries, it becomes an interesting struggle to

keep all of them alive. Alkaline batteries are by far the world's most expensive energy source, per watt. The price for powering devices with alkaline batteries is somewhere between \$250.00 to \$500.00 per kilowatt hour, depending on the type of cells you are using. Remember that the next time you are conducting a fruitless search for something with a flashlight. In terms of payback and practical application, the top three candidates for solar power replacement of alkaline batteries are:

1. Radios, boom boxes, and CD players.
2. Small portable TVs.
3. Handheld LCD display games.

Most of these types of devices may be driven directly off a solar panel at a picnic, the beach, or other family outing, with virtually no notice-

able performance issues. After all, if it starts to rain, who is going to hang around on the beach listening to the radio? An average boom box may need from 6 to 12 volts at half an amp to be run at full output, considerably less at normal listening volumes. A 1' x 1' solar panel rated at 3 to 4 watts is ideal for this sort of application.

It has an open circuit voltage of about 23 volts and will supply 2 to 300 milliamps of current at 14.5 volts. Most solar panels are power rated at 14.5 volts which is charging voltage for lead-acid batteries. Sturdy 3.5-watt panels cost about \$40.00. A simple voltage regulator circuit will limit the voltage of the panel should your radio supply require less than 12 volts. A surprising number of devices appear to be very tolerant of fluctuating supply voltages as long as they are above nominal supply voltage. Small devices, such as handheld games, may be run off a few individual solar cells wired in series.

Assuming you take your radio to the beach, fishing, or picnics often,

and if it uses eight alkaline "C" cells, you will hit payback inside of four battery changes with a solar panel. This could be less than two weeks of continuous daily operation!

## 2. CHARGING UPS BATTERIES

In the Dec. '97 issue of *Nuts & Volts*, we showed you how to replace the dead battery in a UPS (Uninterruptible Power Supply) with a lead-acid deep cycle battery of higher capacity than the original one. This allows the UPS to be run for longer periods before requiring load shutdown. Because of the intermittent nature of UPS operation, it is an ideal candidate for solar panel charging.

In South Florida, we literally have hundreds of short duration power "hits" lasting under 500 milliseconds per year. These are very annoying because they are just long enough to reset VCR clocks, and crash computers. With UPSs on every mission-critical electronic device in the house, a solar panel makes a good free charg-

To give you some ideas, here are a few common devices and the panels they would require in order to operate. Obviously, some of these will overlap if you are willing to accept de-rated performance:

PANEL WATTAGE	Approximate Panel Dimension	DEVICES
3 - 4	12" x 12"	"Boom Box" @ 30-50% Volume Handheld GPS Handheld Cellphone Low Power Walkie Talkie High Volume Muffin Fan Personal CD or "Walkman"
4 - 6	12" x 18"	Pair of High Volume Muffin Fans CB Radio UPS Battery Charging Video Camcorder
6 - 8	12" x 24"	Ham Radio (With Battery for TX) Car or Boat Battery Charging Aquarium Pump/Filter
11 - 13	12" x 36"	6" Portable Color TV Laptop Computer 110 VAC Inverter Quick Charge Nicad Power Tool
50 - 60	19" x 36"	Portable Gorilla Guitar Amplifier Small Pool Pump 19" Color TV Coleman Electric Cooler





Figure 1 — Solar House

ing supply for the batteries. The average duty cycle of the battery in standby mode is only a few minutes a year, so a relatively small 5-10 watt panel is ideal for maintaining our lead-acid UPS batteries at top charge.

If you decide to charge lead-acid batteries on solar panels, it would be a wise precaution to use a charge regulator. A charge regulator will keep the voltage around the optimum 14.5 volts required for charging lead-acid batteries, and it will taper the charge off when the batteries approach full charge. This will prevent boiling off the electrolyte in the batteries which decreases their life. Batteries maintained in this fashion will always be ready for full standby operation for many years.

### 3. CHARGING BOAT/CAR BATTERIES

If you are like me, you manage to find the time to use your boat or jet ski maybe three or four times a year. This is a problem for the starting batteries because after a year of neglect, they often need to be replaced at a cost of \$50.00 or more. A small four-watt solar panel and charge regulator will keep these bat-

teries in top standby condition without requiring a 50 foot extension cord and a dedicated automatic charger on the battery. These two items at Sears would set you back about \$75.00. The payback on the solar panel here is inside of one year.

### 4. NIGHT LIGHTING

Night lighting is an interesting solar application because here you are nearing 50% duty cycle. You have all day to collect energy from the sun and you want to burn it all night. The key to this sort of operation is efficiency. If you are setting up night lighting in the home, you should use LEDs whenever possible in higher visible frequencies like green or yellow.

For outdoor yard lighting, use a nicad battery powering very low voltage lighting. A 24-volt nicad will run six or eight sidewalk lights rated at three volts and connected in series. A typical three-volt incandescent light will draw 200 milliamps at three volts, so a string of six of these will consume about four watts. A four-watt solar panel will therefore yield

about as many hours of nighttime operation as daytime charging. You can charge all day and burn all night.

The payback is very slow when you compare this to running your night lighting off of the power utility, but it may actually be a good alternative to nothing at all in remote places like vacation cabins, or RVs when the local power utility is not an option.

### 5. ATTIC VENTILATION

Attics get the hottest during the noon hour, so this is an ideal solar application. A large 12-volt DC muffin fan drawing about 400 milliamps can move 100 CFM of air. Four of these fans can exchange the air in even a large attic in under one hour. Significant secondary benefits from ventilating the attic can be lower air conditioning costs and decreased attic condensation damage.

Even a single fan moving only 100 CFM will exchange the air in a 50' x 30' attic in about 75 minutes. A five-watt panel is sufficient to power this project. An additional payback

on this project is convenience — it operates automatically and needs no attention. The fan runs directly off the solar panel so there is no battery maintenance.

### 6. AQUARIUMS AND FISH PONDS

Daylight-only operation is fine for aquariums and fish ponds. Fish sleep just like people during the nighttime hours, and having a constant flow and rush of air can be stressful to them. Although it is difficult to find small DC air pumps, it could be worth the trouble if you are trying to keep fish alive in a remote area (like a vacation home) where constant power is not always available.

### 7. HAM RADIOS

Radio hams have long known of the advantages of solar power. Most modern portable radios will run nicely in receive mode on less than 500 milliamps of current at 12 volts. A six- or seven-watt panel will keep the radio running all day without draining the battery, and will help recover from the larger current demands of transmitting. Most DX expeditions to remote places like Antarctica, Easter Island, and the tops of mountains are accomplished with the aid of solar power.

In the event of a natural disaster, ham operators depend on solar backup to provide power when the utility goes down. Solar-powered radios can save lives, speed aid, and provide tremendous flexibility of portable operation. Even for non-hams, within a week of a natural disaster, most cell phones would have dead batteries — staying on the air is assured with a solar standby charging arrangement. And solar power has the added attraction of being environmentally friendly and decidedly low-tech, as opposed to gas-powered generators or other alternative energy sources.

It is impossible to gauge the payback value of helping to save lives.

### 8. CHARGING ELECTRIC LAWN TOOLS

If you are a dedicated lawn warrior, you are probably out every weekend all summer working on the lawn. You may have a battery-

## ALFA ELECTRONICS

HIGH QUALITY TEST EQUIPMENT

Visit [www.alfaelectronics.com](http://www.alfaelectronics.com) for complete info  
Call 1-800-526-2532 for Order and Free Catalog

DMM	LCR/COUNTER	FLUKE SPECIALTY
DMM-898 (\$179.00): true rms, AC/DC (V,A), $\Omega$ , bar graph, freq, capac, dBm, logic, diode	CAP-15 (\$49.95): 3 1/2 digit, 0.1pF-20mF, 9 Ranges, 0.1pF resolution, zero adjustment	12B • \$94.95 • AC Current Probe \$34.95
DMM-23T (\$99.95): 4 1/2 digit, true rms, high resol. (10 $\mu$ V, 10mA, 10M $\Omega$ ), hFE, diode, contin.	LCR-24 (\$119.95): 0.1 $\mu$ H-200H, 0.1pF-2000 $\mu$ F, 0.01 $\Omega$ -20M $\Omega$ , diode test, New Model	70-III • \$99.00 • DC/AC Current Probe \$79.95
DMM-20 (\$74.95): AC/DC (V,A), Freq, cont., Capac, Induct, $\Omega$ , hFE, diode, duty cycle	LCR-131D (\$219.95): autorange, 0.1 $\mu$ H-10kH, 0.1pF-10mF, 1m $\Omega$ -10M $\Omega$ , Q Factor, serial/parallel, 120Hz/1kHz testing mode	73-III • \$125.00 • Mini AC Clamp \$59.95
DMM-122 (\$59.95): DC/AC (V,A), $\Omega$ , hFE, diode, capacitance, freq, logic, continuity	FC-1200 (\$129.95): 1.25GHz counter, Handheld, 8 digits display, 10ppm accuracy, sensitivity 5mV (130-350MHz), 30mV (440MHz)	75-III • \$155.00 • AC Clamp w/temp \$89.95
DMM-123 (\$44.95): DMM + capacitance, DC/AC (V,A), $\Omega$ , hFE, diode, continuity		77-III • \$173.00 • DC/AC Clamp \$109.95
DMM-10 (\$19.95): 3 1/2 digit, DC/AC V, $\Omega$ , hFE, diode, signal output (+3V, -0.5Vsq, 50% duty)		79-III • \$195.00 • IR Thermometer \$189.95

Single Output DC Power Supplies	Triple Output	AUDIO/RF/FUNCT. GEN.
• Constant current, constant voltage mode • Short Circuit and overload protected Analog Meters Display PS-303 (\$159.00) 30V/3A PS-305 (\$219.95) 30V/5A PS-8112 (\$399.95) 60V/5A PS-1610 (\$289.00) 16V/10A PS-8107 (\$399.95) 30V/10A	• Independence or Tracking operation • Parallel to double current output (PS-8102 & PS-8103 only) Triple Output (Analog displays) PS-8102 (\$399.95) 30V/3A/30V/3A PS-8103 (\$489.95) 30V/5A/30V/5A Digital Displays PS-8202 (\$499.95) 30V/3A/30V/3A PS-8203 (\$549.95) 30V/5A/30V/5A	RF Generator • SG-4160 (\$124.95) 100kHz-150MHz sinewaves in 8 ranges • SG-4162AD (\$229.95) with 6 digit counter Audio Generator • AG-2601 (\$124.95) 10Hz-1MHz, 0-8Vpp sine, 0-10Vpp squarewave • AG-2603AD (\$229.95) with 6 digit counter Function Generator • FG-2100A (\$154.95) 0.2Hz-2MHz, 5mV-20V <sub>pp</sub> • FG-2103 (\$329.95) Sweep 0.5Hz-5MHz


GW/INSTEK		DC POWER SUPPLIES		FUNCTION GENERATOR		BENCHTOP DMM	
20 MHz Scope	100MHz Cursor	Triple Output	Single Output	Programmable			
OS-620 \$304.95 • Most economical scope • Dual CH/X-Y operation • 1 mV/div sensitivity • Z-axis input, CH1 output • TV syn, ALT trigger • 2 probes (x1, x10)	OS-6103 \$1199.95 • Cursor Readout a meas • Dual CH / Delay sweep • 10 panel setting memory • Time base auto-range • Z-axis modulation input • 2 probes (x1, x10)	• 2 variable out 0-30V, 0-3A • One fixed 5V, 3A output • Auto track, serial, parallel • Const. volt, current mode • 4 analog or 2 digital display PC-3030 (\$499.95) PC-3030D (\$549.95) digital	• Const voltage, current mod • Voltage regulation <0.01% • Current regulation <0.2% PS-1830 (\$198.95) 18V/3A PS-1850 (\$214.95) 18V/5A PS-1830D (\$214.95) 18V/3A PS-1850D (\$244.95) 18V/5A	• Auto serial/parall (PPT ser) • Auto track (PPT series), IEEE-488.2 and SCPI compatible command set PPS-1860G (\$1,149.95) 18V/6A PPS-3635G (\$1,149.95) 36V/5A PPT-1830G (\$1,499.95) 18V/3A PPT-3615G (\$1,499.95) 36V/1.5A	FG-8015G (\$157.95) • 0.02Hz-2MHz • Sine/Sqr/Tri/Pulse/Ramp FG-8020G (\$209.95) • 0.02Hz-2MHz w/counter FG-8050 (\$449.95) Sweep • 0.05Hz-5MHz w/counter • INT/EXT AM/FM mod	DM-8034 (\$179.95) 3 1/2 dgt • AC/DC (V,A), $\Omega$ , diode DM-8040 (\$339.95) 3 1/2 dgt • ACV to 50kHz, true rms DM-8055G (\$889.95) 5 1/2 dgt • 0.006% accuracy, GPIB • dBm, auto, REL, min/max	

ALFA ELECTRONICS  
P.O. BOX 8089  
PRINCETON, NJ 08543-8089

TEL: (800) 526-2532 / (609) 897-1135  
FAX: 609-897-0206  
E-mail: [sales@alfaelectronics.com](mailto:sales@alfaelectronics.com)

Call / Write / Fax / Email for FREE CATALOG  
Visa, MC, AMEX, COD, PO Accepted. OEM Welcome.  
1 Year Warranty (2 Years for GW/Instek)



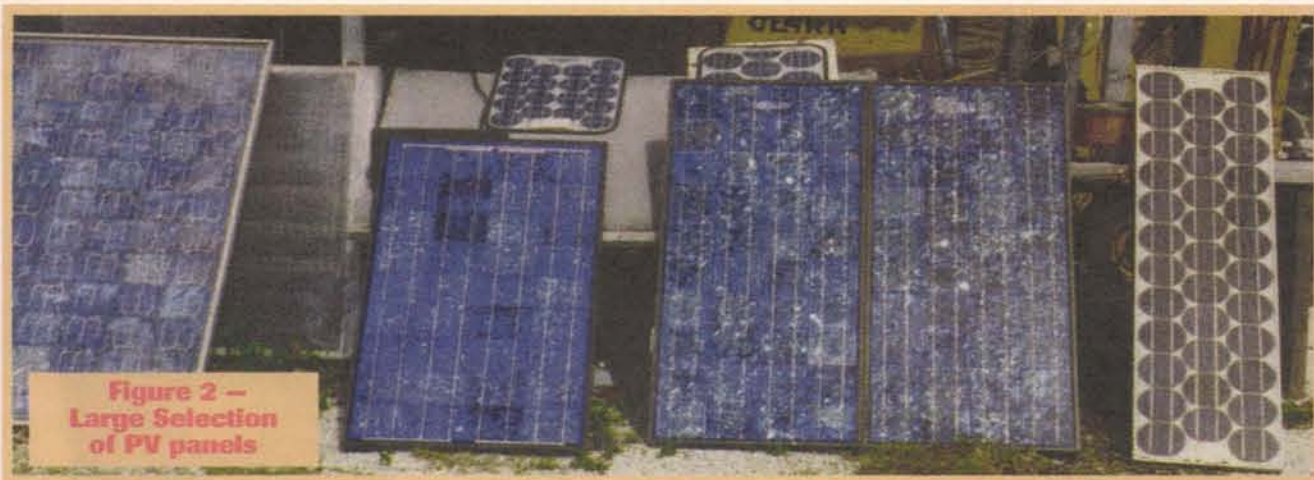

**Figure 2 —  
Large Selection  
of PV panels**



accessible, it is even possible to run a small refrigerator off of a battery-powered inverter that is being charged with a modest-size solar panel array. Two or three 80-watt panels can easily keep a small AC-powered refrigerator running (provided the door isn't open all of the time, and the compressor is cycling off periodically). PV solar panels are available in practically any power rating you may need (Figure 2).

Whether you want Mozart playing in the background or a cold one in the fridge, you can accomplish it with a solar array. With some design and consideration, you can even make it pay for itself! Remember to have fun whatever you do. **NV**

### Solar Sources:

**Tropico Solar**  
Newfound Harbor Rd.  
Big Pine Key, FL 33043  
(305) 872-3976  
E-Mail: [enewbery@inetw.net](mailto:enewbery@inetw.net)

**BP Solar**  
<http://www.bp.com>

**Photocomm, Inc.**  
<http://www.photocomm.com>

operated device like a leaf blower or edge trimmer, or even an electric lawn mower. In this scenario, the duty cycle is a couple hours of operation a week or one percent, so even low powered solar will work just fine. Slow charging nicads over the course of a week at (1/10) is easily accomplished with a 10-15 watt panel for even a large electric lawnmower. You could charge several yard tools at once with a solar panel at this rating. A 14-watt solar panel will run about \$100.00. The payback here is in convenience. If you keep your lawn tools in an outdoor shed or remote corner of the yard, the solar charging system will save on extension cords or running new utility service.

### 9. POOL PUMPS AND HEATERS

A pool is one of those awful things that costs a fortune to install, operate, and maintain, but which adds very little to the resale value of a home. Naturally, it would be nice to decrease the costs and maintenance of keeping one. A solar application works nicely for a swimming pool. Running a DC circulation pump directly off a solar panel will move water and get the job done. Sure it doesn't work when it's cloudy or raining, but who cares?

In this case, a 50-watt solar panel can move 1000 GPH of water through a pool heating and filtration system. Take 200 feet of black poly pipe and throw it in a sunny part of the yard. Run it into the intake of the filter system and connect your DC pump to the return. A 20' x 30' x 6' pool containing about 30,000 gallons will have a complete exchange of water through this system every three days or so. So what if it is only running during the daylight hours?

Conventional gas or electric pool heaters are very expensive to install and operate. Depending on how much you use your pool and how warm you want to keep it, a solar installation can easily pay back its costs in only a few summers or less. A 50-watt panel will cost from \$250.00 to \$300.00.

### 10. WATERFALLS AND FOUNTAINS

Most waterfall and fountain

pump systems run on timers because they are only intended to run during the day when people can see them. This is a perfect solar application. When the sun goes down, the fountain goes off. A small submersible DC pump makes a great water fountain or small waterfall water supply. It is especially pleasant from an environmental point of view because it "responds" to the day. Shortly after the sun rises, the fountain starts up and gets higher until the sun is directly overhead. Then as the day wanes, the fountain gets lower and finally stops as the sun drops below the horizon. How much more environmentally friendly and "in tune" with nature can a system get?

### AND EVERYTHING ELSE

All of the projects mentioned up until now have been powered with DC (direct current), and have relatively short duty cycles. There are actually quite a few AC (alternating current) devices which also have relatively short duty cycles, and which may be powered by solar panels. The differ-

ence is that they may have rather high starting power consumption requirements and require the use of a power inverter.

With the advent of efficient metal oxide field effect power transistors (MOSFETs) and excellent transformer design, power inverters have become extremely efficient. It is possible to purchase power inverters which can convert DC to AC with close to 90% efficiency. They also have excellent short-term overload capacity for starting inductive loads. In standby mode, a well-designed inverter can sit forever at no load drawing only a few milliamps of current!


With small power inverters becoming cheap and plentiful, it is now possible to run AC projects directly off solar panel power. When the solar panel begins to produce enough power to run the inverter, it begins to invert, and off you go — a conventional AC aquarium pump can easily be operated in this manner.

Larger loads will require a battery for reliable operation. For remote locations where the utility grid is not

## Use your PC as a scope and datalogger!
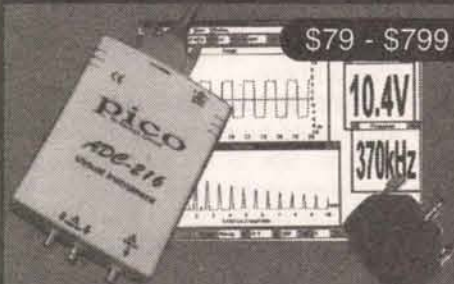
#### Parallel Port Scope

spectrum analyzer, and digital multimeter



\$79 - \$799

**ADC Virtual Instruments** turn your PC or laptop into a sophisticated storage scope AND spectrum analyzer AND multimeter. Display simultaneously on large screen! 100MS/s 8-bit or 1.2MS/s 12-bit or 333KS/s versions. Great for schools, test depts, etc. Input to Excel! LabView/NT drivers included.

#### Environmental Logging

record temperature, humidity, etc.



\$129 - \$645

**ENVIROMON** - temperature (thermistor), humidity & light sensors, door position, etc. Record for 365/24 without a PC even if power fails. Monitor 30 sensors 400 yds away. With cables and easy software. Remote audio alarm. Use **TC-08** for most thermocouples.

#### osziFOX

20MS/s handheld scope



\$129

**osziFOX** - handheld storage scope and DVM - stand-alone or plugs into your PC for display, store-to-disk, printing in color. Inputs to 100V, trigger, backlit LCD.

Download FREE demo software. Sales only: 1-888-7SAELIG

[www.saelig.com](http://www.saelig.com) 716-425-3753 • -3835 (fax) [saelig@aol.com](mailto:saelig@aol.com)

Stocked in NY by Saelig Company: Virtual Instruments, I2C and embedded controllers, BITlink 2-wire networks, RS232/422/485, frame grabbers, etc. See [www.saelig.com](http://www.saelig.com) for Product of the Month!

**pico**  
Technology Limited

PC-based Instruments!



# HIGH "TEC" REFRIGERATOR

by Kenton Chun

We have all seen them in the sports department of our local superstores – electric coolers.

It's the sort of thing that makes a hardware hacker's palms begin to sweat. The average price on one of these babies is \$80.00. But before you pull out your credit card, take a look at this month's project.

For a quarter of the price, you can build one yourself. We even decided to go a step farther and make ours solar-powered.

The heart of the electric cooler is a Thermoelectric Cooling heat pump (TEC). Also known as a Peltier device (named after its inventor), the TEC consists of semiconductor junctions that are

assembled between and bonded to two ceramic plates.

When a DC current is passed through it, heat is "pumped" from the cold side to the hot side. The cold or hot side is determined by the direction of current flow. Reversing the current flow will reverse the hot and cold sides.

In its basic form, a TEC system consists of four parts: a hot side exchanger, a cold side exchanger, the TEC device, and a power source. The hot and cold exchangers are only common aluminum heatsinks with attached fans to increase their efficiency.

All a thermoelectric heat pump requires to function is clean DC power. Batteries, automotive and marine DC systems, AC/DC con-

For a quarter of the price, you can build an electric cooler yourself. We even decided to go a step farther and make ours solar-powered.



verters, linear and switched DC power supplies are all appropriate power sources for TECs. Most applications are optimized at 75% of maximum ratings for the TEC device.

The Peltier Effect was discovered in 1834 by Jean Charles Athanase Peltier. When current passes through the junction of two different types of conductors, it results in a temperature change. However, the practical application of this concept required the development of semiconductors that are good conductors of electricity but poor conductors of heat – the perfect balance for TEC performance.

Today, bismuth telluride is primarily used as the semiconductor material, heavily doped to create either an excess (N-type) or a deficiency (P-type) of electrons. Modern TECs are capable of achieving 50-degree temperature differentials in a single stage.

When cascaded in multiple stages, TECs can achieve extremely low (near cryogenic) temperatures. The electric coolers you can buy in the sporting goods department will stabilize at just about 40 degrees in an 80-degree ambient environment.

We decided to build a cooler that would be compact and convenient to use in a car. We chose a Coleman eight-quart cooler as the basis for our project. You can use any type or size cooler for your project, but you should run some tests first to determine the efficiency of the insulation in the cooler.

The simplest test is to fill the cooler with ice and see how long it takes for the ice to melt at ambient room temperature. Our little Coleman was not bad in that, after 24 hours, it still contained about 80% of the ice. The greatest losses were through the top and bottom of the cooler where the insulation was the thinnest.

We purchased a TEC device from an advertiser in *Nuts & Volts*.

It came complete with a hot side heatsink and is rated at 4.5 amps at 12 volts. We purchased a somewhat smaller cold side heatsink at a local hamfest. We chose our cold side heatsink for its low profile, allowing us the greatest amount of room inside the cooler after installation.

Because of the lower cold side efficiency of the TECs, it is not necessary to have the same area of heatsink on the cold side as on the hot side. Our cold side sink was only about 40% of the hot side area.

The choice of the cold side heatsink has a significant effect on the final performance of the cooler. Because of variations between coolers and TECs, it may be necessary to experiment in order to determine the optimum heatsink for your cooler. One good rule of thumb to remember is to size your cold-side heatsink so that it stays a few degrees above freezing without a fan. Once the sink hits freezing, it will develop a frost coating which will decrease cooling efficiency (Figure 1). Either add a cold-side fan or increase the heatsink size to remedy this problem. We matched our hot side heatsink with a four-inch 12-volt muffin fan (Figure 2).

## GETTING STARTED

Begin by preparing the cold side heatsink. Drill holes to match the studs on the cold side of the TEC. Make sure to drill the holes in a location that falls between a pair of cooling fins, even if it is not in the exact center of your heatsink. If the fins are very close together, it may also be necessary to mill or carefully drill out an area large enough to accommodate the mounting nuts. Remember you must also tighten the nuts with a pair of needle-nose pliers or a nut driver when dimensioning this space. Check and make sure that your heatsinks and the TEC surfaces mate without rocking. Remove any metal burrs



Figure 1 — Too small of a heatsink will freeze.

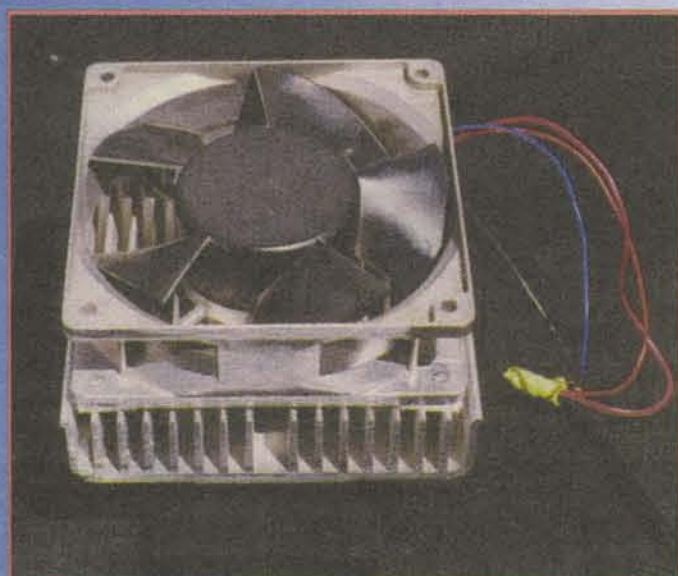


Figure 2 — Hot side muffin fan.



which may be preventing them from doing so (Figure 3).

Next, measure the cold side dimensions of the TEC. Transfer this measurement to the lid of the cooler, making sure the larger hot side heatsinks will not interfere with anything, and carefully cut a hole to fit the device with a jigsaw.

In general, it is slightly better to mount the TEC so the heatsink fins are vertical so that, in the event of fan failure, there will still be some natural air convection across all of the fins. We chose to mount the TEC in the top of the cooler to allow the greatest room for storage inside. Mounting the TEC in the lid gives you the added option of simply changing lids to turn the cooler back into a non-electronic type.

The device should fit snugly in the hole allowing the power cables to pass to the outside of the cooler without strain. If you are using a cold side fan, it is important that the power leads pass through the cooler lid leaving enough space to mount the cold side heatsink flush with the surface of the TEC.

Attach the muffin fan to the hot side heatsink, using either a dab of



When you are done, you should have something that looks similar to Figure 4. Using a good quality silicone sealant, seal the outside edges of the TEC around the hole. Clamp the device to the outside of the cooler overnight until the sealant cures.

Carefully fill any gaps between the edges of the holes and the cold side of the TEC making sure not to get any sealant on the surface of the device. If some gets on the TEC, wipe it off immediately.

Your cold side TEC surface should be flush or above the inside of the cooler lid. If you have additional space between the TEC and

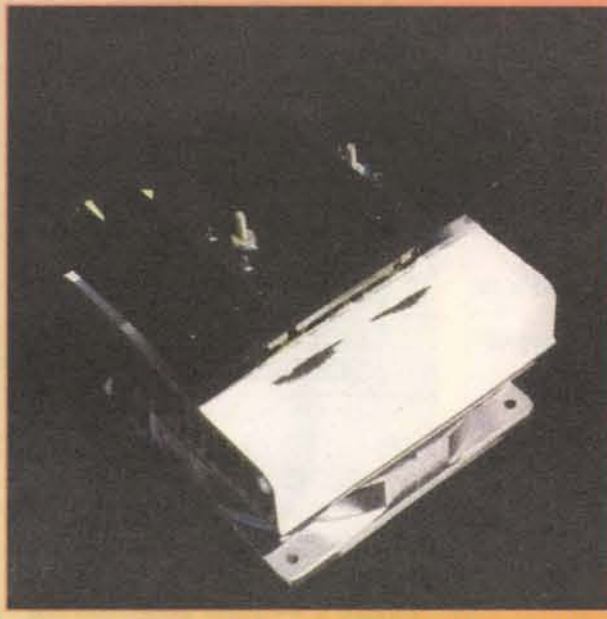


Figure 3 — Mounting the cold side heatsink.

silicone sealer on each corner, with some small angle brackets, or even with velcro. The fan should be blowing air into the center of the heatsink and the air should exit through the open ends. You can reverse the flow if you wish, but we found it runs quieter this way.

Wire the TEC and fan in parallel using a good quality stranded 18 gauge wire. Most TECs have color-coded pigtailed; the positive lead is the red one when the device is in cooling mode. You may wish to connect your TEC to a 12-volt power supply or battery to verify that this is the case with your device.

If you wish, you can terminate the power leads in either a pair of battery clamps or in a polarized power socket. Make sure it is rated for at least 5 amps at 12 volts DC.

the lid, you can use a piece of styrofoam as a spacer for a snug fit.

Next, bolt on the cold side heatsink using a tiny amount of heatsink grease between the two. You only need enough to contact both surfaces. Tighten the mounting nuts down but do not strip the bolts. Use a properly-sized pair of split lock washers under the nuts. Aluminum has a fairly high thermal expansion coefficient, so it may be necessary to recheck the nuts after the cooler has been on for a few minutes.

FINAL CHECK AND TESTING

Connect your TEC cooler to a 12-volt power supply capable of supplying 5 amps. Both fans should begin to turn, and the cold

Go Wireless With Our Modules

SILRX/TXM

SILRX — \$26.00 ea.  
TXM — \$15.50 ea.

The TXM and SILRX modules are a transmitter and receiver pair which can achieve a one-way radio data link-up to a distance of 200m over open ground.

Both units are supplied in space-saving single-in-line packages and offer SAW controlled, wide band FM transmission/reception.

The modules are particularly suited to battery-powered, portable applications where low power and small size are critical design criteria.



TX2/RX2

TX2 — \$19.50 ea.  
RX2 — \$38.50 ea.

The TX2 and RX2 radio transmitter and receiver pair enable the simple implementation of a data link at up to 40kb/s at distances up to 75m in-building and 300m open ground. Both modules combine full screening with extensive internal filtering to ensure EMC compliance by minimizing spurious radiations and susceptibilities. The TX2 and RX2 modules will suit one-to-one and multinode wireless links in applications including car and building security, EPOS and inventory tracking, remote industrial process monitoring, and computer networking.

Because of their small size and low power requirements, both modules are ideal for use in portable, battery-powered applications such as hand-held terminals.



900 MHz  
AVAILABLE NOW

RPC

RPC — \$99.00 ea.

The RPC module is an intelligent transceiver which enables a radio network link to be simply implemented between a number of digital devices. The module combines an RF circuit with processor-intensive low-level packet formatting and recovery functionality, requiring only a simple antenna and 5V supply to operate with a microcontroller or a PC.



BiM

BiM — \$69.00 ea.

The BiM module integrates a low-power UHF FM transmitter and matching superhet receiver together with data recovery and TX/RX change over circuits to provide a low-cost solution to implementing a bi-directional short-range radio data link.



Lemos International Co., Inc.

65 Southbridge Street, Auburn, MA 01501  
Phone (508) 798-5004 ♦ Fax (508) 798-4782  
www.lemosint.com ♦ sales@lemosint.com


All products available in either 418 or 433 MHz

Write in 185 on Reader Service Card.

Surveillance

You must mention ad to receive special pricing

Only Japanese Color Cameras

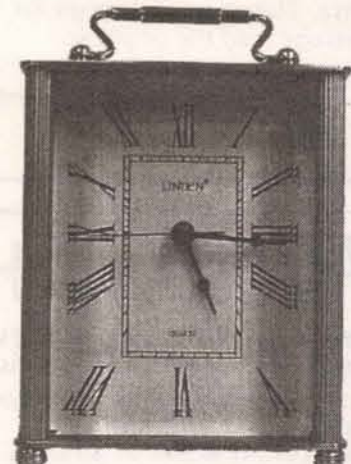

Carriage Clock Cam \$250

Sale Ends 9/15/99

BC-985 Color Board Camera	\$125
BC-985P Pinhole Lens Camera	\$145
BX-985 Black Box Camera	\$155
SD-985 Smoke Detector Cam	\$195
EX-985 Exit Sign Cam	\$195
EL-985 Emergency Light Cam	\$225
PS-985 Pencil Sharpener Cam	\$225
CL-985 Carriage Clock Cam	\$250
VB-985 Video Bag w/12 hour Battery Pack and Charger	\$295
VP-400 Video Pen w/ 2 hour Battery Pack and Charger	\$1500

Color Camera Specifications

High Resolution — Over 380 TV lines  
Low Light Sensitivity — Only 2 Lux  
Built-In Backlight Compensation  
2 Year Limited Warranty

American Innovations, Inc.  
383 West Route 59  
Spring Valley, NY 10977

M-F 11:00 - 8:00 P.M.  
Sat. 12:00 - 6:00 P.M.  
Tel (1) 914-371-3333  
Fax (1) 914-371-3885

www.spysite.com

Write in 186 on Reader Service Card.





side heatsink should immediately turn cool. If it instead begins to heat up, disconnect the power and reverse the TEC leads. The hot side heatsink will not get hot immediately because of the larger thermal area and fan cooling assistance.

If the device appears to be getting cold, wait for 5 or 10 minutes, and then recheck the tightness of the mounting nuts on the cold side heatsink. Once you have tightened it cold, you should not need to retighten it again. You can check the performance of your cooler by placing a digital thermometer sensor inside the cooler and checking it at regular intervals.

## OPERATIONAL NOTES

It is possible to reverse the direction of the heat pump by simply reversing the power leads to the cooler and thereby turn it into a heater. However, you may have to modify the fan power circuit because reversing the power polarity on many brushless DC fans will cause them to stop running. They will not reverse.

TEC devices will actually consume less power after the temperature has dropped inside the cooler. Do not be tempted to exceed the operating voltage in hopes of gaining efficiency. TECs are current devices and increasing the voltage may damage them or actually decrease your cooling efficiency. TECs will operate more quickly at

rated current, but will happily function with less. For this reason, they are ideal for use with solar power.

## SOLAR POWERED FRIDGE

We decided to take it a step farther and try a solar power experiment. Because of the good thermal insulation properties of our little cooler, we decided to try to run our TEC refrigerator off of a PV (Passive Voltaic) solar panel. From a practical standpoint, there are only a few ways one can store solar power for later use. The conventional way is to charge a battery and then discharge it later through a load after the sun has set. We decided to try and use our TEC cooler to store "cold."

With the TEC running full blast, our cooler consumes just under 50 watts. We set up the cooler to run directly off a Tropico 53-watt panel regulated with a 5-amp 12-volt voltage regulator (Figure 5). With about seven useful hours of solar energy available in February, and a starting ambient temperature of 78.8 degrees F, we were able to bring a six pack of diet cola down to a cool 42 degrees over the seven hours.

The TEC continued to operate even when a cloud passed in front of the PV panel, and the drive voltage dropped to only six volts. Our drinks stayed pleasantly cool all night. We were pleased and amazed to see that we could keep our drinks cold by using sun power alone!

Although we were unable to drop the temperature sufficiently to make ice in the cooler, we found that, by keeping the temperature low, we could easily preserve ice stored in the cooler for several days. This is good enough for the average road trip or picnic.

Remember to have fun whatever you do! **NV**



Figure 4 — Mounting the TEC assembly in the cooler lid.

## PARTS LIST:

Coleman Six-Pack Cooler or similar (see text)  
12V Thermoelectric Cooling Device (TEC)  
12V Brushless Four-inch Muffin Fan  
1 Cold Side Heatsink (see text)  
Tube Silicone Caulk  
Tropico 53W Solar Panel  
Assorted Hardware and 18GA stranded hookup wire

The author wishes to thank **Tropico Solar** for the use of the PV panel employed in this project. Tropico Solar can be reached at (305) 872-3976 and you can E-Mail them at [enewbery@inetw.net](mailto:enewbery@inetw.net).



Figure 5 — Solar powering the "fridge."



# EPROM+

A device programming system for design, repair and field service

◆ EXCEPTIONAL POWER FOR THE PRO  
◆ EASY-TO-USE FOR THE NOVICE

**Here's what you get:** A rugged, portable programming unit including the power pack and printer port cable both of which store inside the case. A real printed user and technical manual which includes schematic diagrams for the programming unit plus diagrams for all technology family adapters\*. Comprehensive, easy-to-use software which is specifically designed to run under DOS, Windows 3.1, 95 and 98 on any speed machine. The software has features which let you READ, PROGRAM, COPY and COMPARE plus much more. You have full access to your system's disk including LOADING and SAVING chip data plus automatic processing of INTEL HEX, MOTOROLA S-RECORD and BINARY files. For detailed work the system software provides a full screen buffer editor including a comprehensive bit and byte tool kit with more than 20 functions.

**Broad device support:** Including FIRST GENERATION EPROMS (2708, TMS2716\*, 25XX etc.) SECOND GENERATION EPROMS (2716-27C080)(8 MEG), 40 and 42 PIN EPROMS\* (27C1024-27C160)(16 MEG) EEPROMS (2816-28C010) PLUS ERS901, FLASH EPROMS (28F, 29C, 29EE, 29F)(32 MEG), NVRAMS (12,20,X2210/12) 8 PIN SERIAL EPROMS\* (24, 25, 85, 93, 95, 80011A) PLUS ER1400/M58657\* BIPOLAR PROMS\* (74S/82S), SERIAL FPGA CONFIGURATORS (17CXXX) MICROS\* (874X, 875X, 87C5X, 87C75X, 89C) ATMEL MICROS\* (89S, 90S)(AVR) PIC MICROS\* 8, 18, 28, 40 PIN (12CXXX, 16C5X, 6X, 7X, 8X PLUS FLASH & 17C) MOTOROLA MICROS\* (68705P/U3/R3, 68HC705C8/C9/J2/P9, 68HC711E9/D3)

**\$289**

Includes step-by-step tutorial plus explanation of EPROM fundamentals  
1 YEAR WARRANTY - 30 DAY MONEY BACK GUARANTEE  
\*REQUIRES SNAP-IN ADAPTER (ORDER FACTORY DIRECT OR BUILD YOURSELF)

\$5.00 SHIPPING • \$5.00 C.O.D.  
VISA • MASTERCARD • AMEX

ANDROMEDA RESEARCH, P.O. BOX 222, MILFORD, OHIO 45150  
(513) 831-9708 FAX (513) 831-7562  
website - [www.arlabs.com](http://www.arlabs.com) email - [arlabs@worldnet.att.net](mailto:arlabs@worldnet.att.net) MADE IN THE U.S.A.



## Moving Sale

Equipment Management Technology

Tel 650-631-1700 Fax 650-631-1200 Email [sales@emt1.com](mailto:sales@emt1.com)

SELECTED SPECIALS!			
HP 16505A	\$250	HP E1345A	Make Offer!
HP 16510A	\$100	HP E1347A	Make Offer!
HP 16515A	\$100	HP E1364A	Make Offer!
HP 16516A	\$400	HP E1400B	Make Offer!
HP 3314A	\$1400	HP E1401A	Make Offer!
HP 5335A	\$500	HP E1662A	Make Offer!
HP 59501B	\$250	HP E1671A	Make Offer!
HP 6266A	\$250	HP E1672A	Make Offer!
HP 8016A	\$500	HP E1681A	Make Offer!
HP 83545A	\$3850	HP E1682A	Make Offer!
HP 8493B	\$100	HP E1693A	Make Offer!
HP 8958A	\$5000	HP E1725A	Make Offer!

We buy, rent, and sell high quality test and measurement products. We occasionally offer great deals on computers as well.

HP OmniBook 600C color subnotebook weighs a mere 3.7lbs for ultimate portability. Special Nuts & Volts price is only \$250!

Dave is test equipment!  
[Bigdave@emt1.com](mailto:Bigdave@emt1.com)

Kerry is computers!  
[kwhite@emt1.com](mailto:kwhite@emt1.com)

956 Bransten Road San Carlos, CA 94070

**NEW ADDRESS**



# DC-TO-DAYLIGHT RADIOS: YAESU AND ICOM COMPARISONS



by Gordon West

**A**mateur radio equipment manufacturers Yaesu USA and ICOM America have simultaneously introduced a compact amateur radio transceiver that offers 100 watts output on ham bands from 160 meters to six meters, plus 50 watts output and all multi-mode capabilities on two meters, PLUS 20 watts output, full multi-mode capabilities, on the 70 centimeter bands.

ICOM calls their equipment the IC-706 MK II G, and Yaesu calls their DC-to-light amateur transceiver the FT-100. Both companies introduced this exceptional equipment within one week of each other last April, and both units have been seen selling in the \$1,375.00 price range.

What makes both of these transceivers unique to the amateur industry is their ability to combine 500 kHz to 500 MHz capabilities all in one nice, neat package. Kenwood Corporation offers the Kenwood TS-50, and Alinco offers the DX-70, and these similarly-sized transceivers are terrific high-frequency performers, but neither the Kenwood nor the Alinco combine two-meter capabilities and the incredible Yaesu and ICOM accomplishments of 440 MHz multi-mode transceive.

ICOM America was the pioneer in adding VHF to a small packaged HF transceiver back in 1995 with their IC-706. Two years later, they came out with the IC-706 MK II where they added more power on the two-meter band and enhanced wide-band receiving capabilities. Then Yaesu and ICOM simultaneously brought out their HF plus six meters, plus two meters, plus 440 MHz multi-mode transceivers with plenty of similarities between themselves, and comparable street prices that might have hams scratching

**... Two brand new HF/VHF/UHF ham transceivers from Yaesu and ICOM undergo side-by-side comparisons, along with some torture tests, too, in a review of the latest technology that goes from 500 kHz to 500 MHz, plus higher on receive ...**

their heads wondering WHICH ONE IS BEST?

Reading over the specification sheets may be a good start to figure out which one is BEST, but there is nothing better than a side-by-side, in-the-field comparison between the two, and that is exactly what I did during the month of April.

- Yaesu FT-100, serial No. 9E031474
- ICOM IC-706 MK II G, serial No. 01264

## COMPARISON PROCEDURES

Both units were obtained from the manufacturer, but neither had been opened up ahead of time for any extra "tweaking" and quality assurance. The comparison was conducted at the home station into a contest-capable, high-frequency Yagi. The equipment was also compared side-by-side in the communications van in the field near a major mountain-top relay site. This location is known for its intermod generating capabilities. The equipment was also compared side-by-side in an off-the-road dune buggy in order to maximize engine static.

Side-by-side comparisons included simultaneous receive on a common antenna with appropriate isolation networks in order to minimize

one radio loading down the receive capabilities of another. Simultaneous receive on a test antenna at a test location gave us fast and accurate comparisons of the receiver capabilities. We would also switch each set into the antenna, by itself, to further verify independent receiver performance.

## SIZE AND WEIGHT

ICOM IC-706 G weighs in at six pounds, including mike, but less the mounting bracket.

Yaesu 100 weighs in at about five pounds, including mike, but less the mounting bracket.

ICOM is about 10 inches in length, and Yaesu is about 9-1/2 inches in length. Both units are around two inches in height, with ICOM a fraction more chubby. Both units are about 6-1/2 inches wide.

Both units feature detachable head capabilities. But it will cost you another \$75.00 for the necessary head-separation kits.

The ICOM separates with a single multi-conductor cable that conveys all separated front panel information to the body. The ICOM mike plugs into the separated head, and the separated head can provide switchable headphone or speaker capabilities out the front mini phone

## DC-TO-DAYLIGHT RADIOS



## DC-TO-DAYLIGHT RADIOS

jack. The Yaesu requires three control cables: one for running the remote head, one for the external speaker, and one for the microphone. This set-up could allow the speaker and the mike to emanate from an area not necessarily directly on the head.

ICOM supplies a lightweight mike with up-and-down buttons on the top, plus a lock switch. A microphone with keypads is available as an option. On the Yaesu, they supply an elaborate mike with back-lit keys, up-and-down buttons, lock, and several additional programmable buttons. On the microphone length test, both were relatively long, but the Yaesu mike went even a foot further.

### COOLING

Both sets ran relatively cool on both receive and transmit. ICOM uses an internal big fan to blow out the hot air, and Yaesu uses two smaller fans mounted on the rear to provide plenty of fresh cool air to all of the PA transistors.

### POWER CORDS

ICOM supplies the customary six-pin power receptacle, along with twin round fuses found at the opposite end of the long cable. The fuse holders may be opened up to allow the cable to easily poke in through an extremely small fire wall rubber boot.

Yaesu offers a pigtail with heavy-duty blade connections to their long power cord. The power cord also features automotive blade fuses at the far end. If your vehicle has a large fire wall rubber boot, no problem — but if the hole in the fire wall is rather small, you may need to cut the red and black wires in order to facilitate getting through a very small fire wall hole.

### INTERNAL SPEAKERS

The ICOM internal speaker is larger with a

more full sound. The Yaesu internal speaker is smaller, with a more crisp sound. Both units offer an external speaker jack on the back of the equipment for plugging in an external speaker. When hooked up to an external speaker, both the units sounded almost identical for audio fidelity and plenty of robust audio output power. Yaesu cautions the use of headphones off of the rear

equipment, and all sounded just right at one-third volume setting. This included the Heil headset, as well as all sorts of contest headphones. But keep in mind that the ICOM also offered a second headphone/speaker jack on the left-hand corner of their front panel.


### THE LCD DISPLAYS

The Yaesu display measures a little over an inch high and about 2-1/2 inches wide. The ICOM display is the same width, but noticeably a half-inch taller. The ICOM display is an LCD light green background with black bold characters. Screen visibility at all lighting conditions and at all front panel angles was judged "the best" by several ham operators assisting with the comparison.

The Yaesu FT-100 display is an LCD light blue background with royal blue LCD characters. When back-lit at night, it was quite pleasing to drive by — but during the day, the definition of the blue-on-blue display was not as crisp as on the ICOM green and black display. The Yaesu head is best mounted up high on the dash where you can look square on it, as opposed to losing some definition when trying to view it at an angle, or looking down on it when not pointed directly at you.

### OPERATING KNOBS AND CONTROLS

We found a lot of similarities

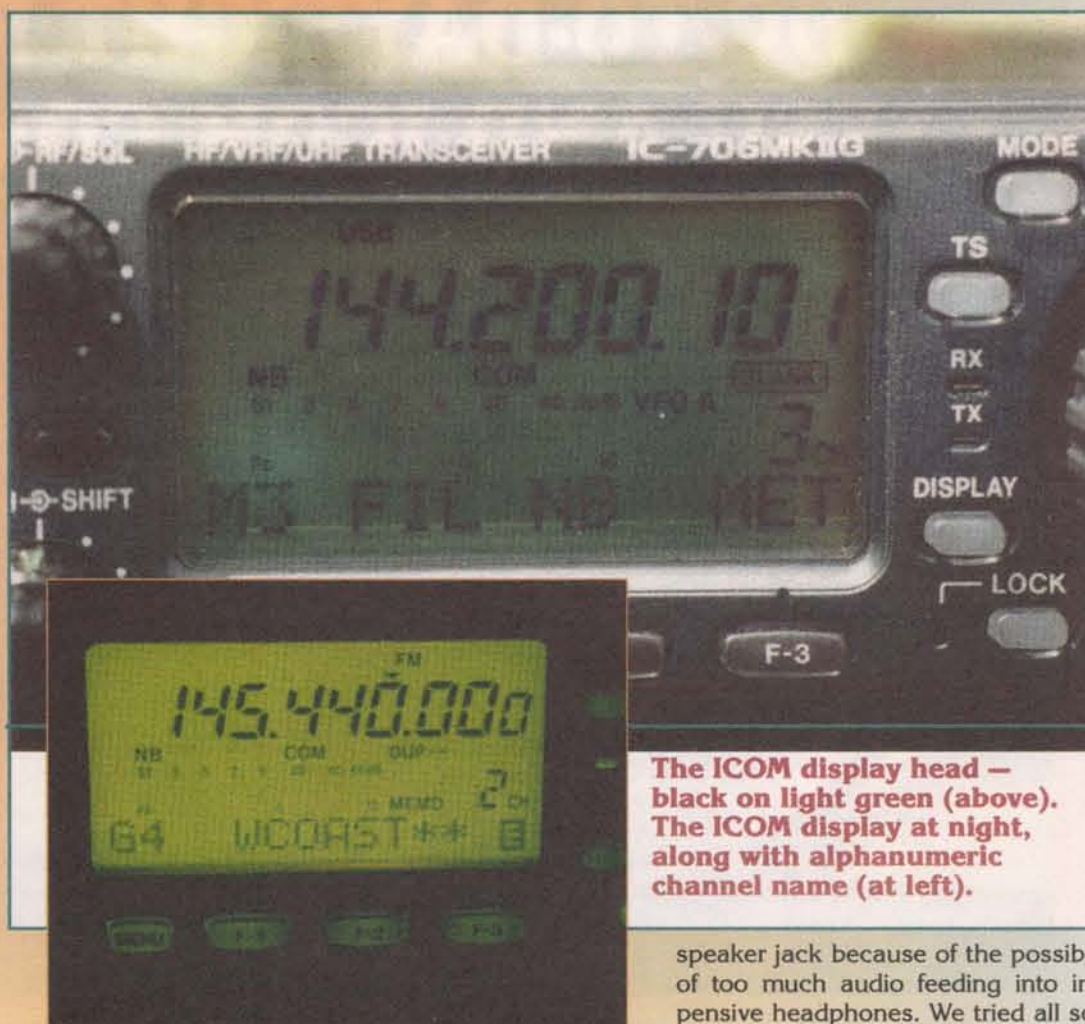

The ICOM display head — black on light green (above). The ICOM display at night, along with alphanumeric channel name (at left).

## CABLE TV CONVERTERS

The Best Prices and Service • In Business over 15 years!

Phone 218-346-6660 Fax 218-346-6664

### TIMELESS PRODUCTS

New! "TP 125 V"  
128 Channel Converter with Volume

Special Prices for  
TP1550PC  
Call for Details

Panasonic still available!

- REFURBISHED CONVERTERS ALSO AVAILABLE •
- QUALITY REPAIR DEPARTMENT FOR ALL YOUR TUNER REPAIRS •
- REMOTES AVAILABLE FOR MOST CABLE BOXES •

DEALERS ONLY • GREAT QUANTITY PRICES • NO DECODER SALES



## DC-TO-DAYLIGHT RADIOS



The Yaesu remote head, cool blue (above). The "cool blue" Yaesu display was eye-pleasing at night.



between the ICOM and Yaesu control heads. On the new ICOM "G series" of 706, ICOM now back-lights all of the keys for nighttime operation. The band up-and-down keys have little arrows on them, and the menu plus "F" keys have designators on them, too. But, in the dead of night, the mode, tuning speed, display, lock, pre-amp, and tuner keys along with RIT simply illuminate, and you will need some background light to see what their use is that has been silkscreened on the panel. Even if ICOM had put a single letter or two on the actual back-lit keys, it would have been better than trying to make out the white silkscreen letters in the dark.

Yaesu does not back-light the front panel, but they DO back-light their mobile microphone. This could allow you to make an autopatch call in the dead of dark, and see the right numbers on the keypad. But for the rest of the display in the dead of night, better go for some back-lighting.

Both Yaesu and ICOM put their most important four keys down at the bottom of the display, and the back-lit LCD display is easily seen in bright daylight or in complete darkness.

The tuning knob on the ICOM is slightly larger and has a bigger finger hole that all of our reviewers liked. The Yaesu knob is slightly smaller and, unless you use your baby finger, it is not as easy to spin the knob with your finger because the finger hole is smaller and doesn't contain the free-spinning insert that ICOM has. ICOM also has a

tension adjustment for tightening or loosening the big knob.

The band up-and-down buttons on the ICOM are on the extreme right upper and lower edge of the equipment. They are far enough away from the tuning knob that you won't accidentally bump the knob when pushing the button. On the

Yaesu, the up-and-down buttons are just to the left of the tuning knob, and they are relatively close to the tuning knob, so you must use caution when going up and down the bands that you don't accidentally slew off frequency.

Both units offer a step button that allows you to select the tuning speed. On the Yaesu FT-100, the step speed adjusts the lower left select knob but does not affect the fine-tuning speed on the big knob that is menu-adjustable. On the ICOM, the tuning speed adjustment affects both the main tuning big knob, as well as the small sub-tuning control. But on VHF and UHF weak-signal, single-sideband operation, the Yaesu step button now selects fine-tuning or coarse-tuning of the big knob, and the select knob is set at 10-kHz steps for rapidly going up and down the VHF and UHF weak-signal portions of the band.

On the ICOM 706 MK II G, tuning speed may be selected for fine-tune or coarse-tune by both the big knob, as well as the small select knob. ICOM can show tuning all the way down to one cycle, and the Yaesu FT-100 shows 10-cycle tuning, and is capable of 1.2 cycle tuning by tapping the up or down buttons on the top of the mike. I can't imagine anyone needing this type of tuning resolution, but on both units, it IS available, with each set having its own tuning speed characteristics.

Both the new ICOM and the new Yaesu "DC-to-daylight" transceivers offer a menu setting that allows you to choose RF gain or squelch control off of the inside, top-left, dual-rotating controls. Both sets give you a lock button, and both sets have a keystroke that enables menu items to be selected before you head out on the road.

### ALL THOSE MENUS

ICOM has a couple of "regions" of menus inside the equipment. By pressing the menu up to four times, you get 12 items to select. By pressing menu and display, the ICOM now gives

## Miniature Transmitters and Receivers

### 2 Button / 3 Channel Transmitter



#### RF300T

1....\$22.95  
5....\$19.95 ea  
10...\$16.95 ea

#### RF300XT

1....\$25.95  
5....\$22.95 ea  
10...\$19.95 ea

- 300' (XT), 150' (T) Range
- Frequency: 318 MHz
- 59,049 Settable Security Codes
- 12 Volt Battery and Keychain Included
- Current Draw: 4.8 ma
- Fully Assembled in Case
- Dimensions: 1.25" x 2.0" x .5"
- Push both buttons for the 3rd Channel
- Slide Button Cover Included

- Alarm Systems
- Garage / Gate Openers
- Lighting Control

- Magic Props
- Medical Alert
- Monitoring Systems

### 4 Button / 15 Channel Transmitter



#### RF304XT

1....\$27.95  
5....\$24.95 ea  
10...\$21.95 ea

- 250' Range
- Frequency: 318 MHz
- 6,561 Settable Security Codes
- 12 Volt Battery and Keychain Included
- Current Draw: 4.6 ma
- Fully Assembled in Case
- Dimensions: 1.35" x 2.25" x .5"
- Push combination of buttons to achieve up to 15 channels

- Industrial Controls
- Surveillance Control
- Motor Control

### 2-4 Data / 3-15 Channel Receivers



#### RF300RL RF300RM

1....\$27.95  
5....\$24.95 ea  
10...\$22.95 ea

#### RF304RL RF304RM

1....\$29.95  
5....\$26.95 ea  
10...\$23.95 ea

- Compatible with 300/4 Transmitters
- 11-24 volts DC Operating Voltage
- 13 ma. Current Draw
- Latching (L) or Momentary (M) Output
- Kits Available (subtract \$5.00 ea.)
- Dimensions: 1.25" x 3.75" x .5"
- 2 (300) / 4 (304) Output Data Lines
- Binary to Dec / Hex Converter can achieve up to 15 channels

- Schematics Available
- Receiver Board Layout Available
- Custom Design Consulting Available

Visitect Inc.


(510) 651-1425 Fax: (510) 651-8454  
P.O. Box 14156, Fremont, CA 94539

Email: Support@Visitect.Com  
Visa / Mastercard, COD



## DC-TO-DAYLIGHT RADIOS

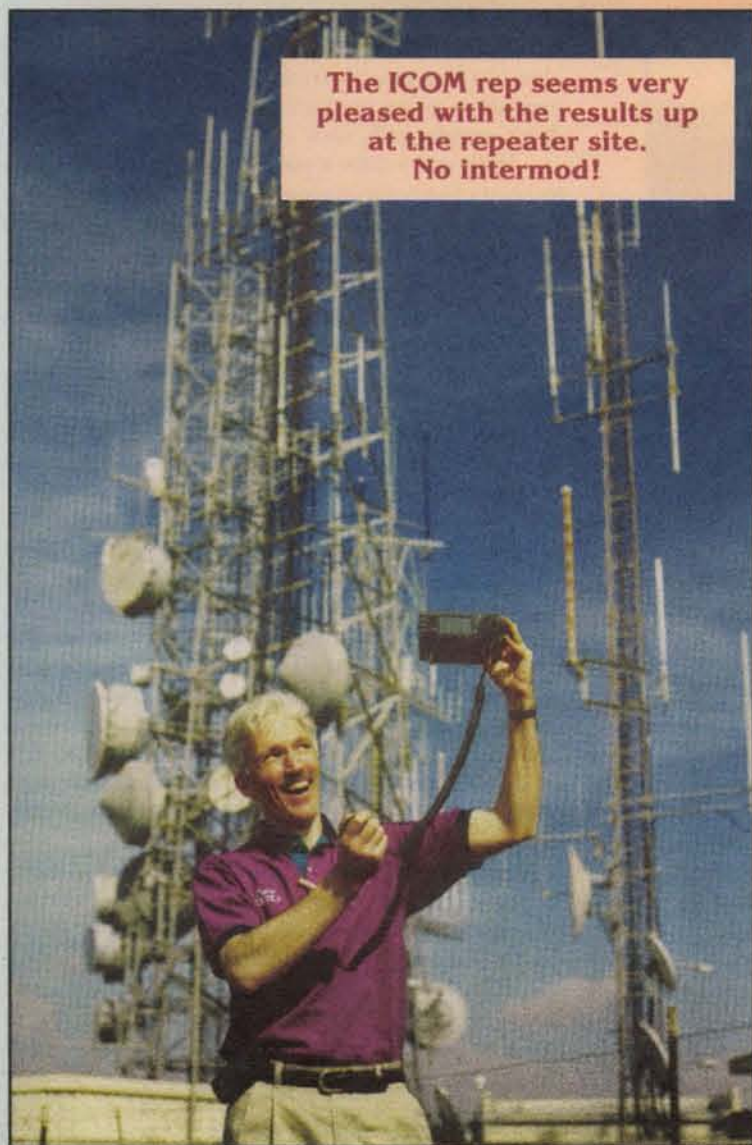**The ICOM rep seems very pleased with the results up at the repeater site. No intermod!**



for naming memorized channels.

The ICOM also gives you 37 more menu items by turning off the equipment, and then turning it on while holding the power and the lock button. These are items that you should only need to select once you have figured out how you plan to operate the equipment, and are not ones that you would normally need on the road or while operating the equipment at your shack. However, I wish they had put special menu 4 and 5 as a front-panel push button, because they are useful when driving mobile from dusk to dark and you want to adjust the back-lighting of your display. In fact, I'm amazed that neither the ICOM nor the Yaesu use a relatively inexpensive photocell circuit that automatically dims the display when the photo cell determines there isn't much light on the face of the equipment.

One of the ICOM easy-menu items is digital signal processing. The DSP electronics are now built into the 706 MK II G series, so you won't need to pay extra for it.

An often-used DSP function down on the 40-meter band is the automatic notch filter. If there is a steady carrier that is producing a tone driving you crazy, just push "ANF" and the tone disappears. And if it's just background noise that is occluding a voice or CW signal, press the noise reduction "NR" function, and then select up to 15

intelligible.

On the Yaesu FT-100, they, too, have a host of selections on the front panel via the four push buttons, as well as 66 menu items along with 59 additional secret "factory" menu pre-set adjustments. But before we go into all of the Yaesu menus, let's take a look at Yaesu's digital signal processing that has additional options over the ICOM.

The Yaesu FT-100 offers the customary DSP notch filter that worked great in canceling out a foreign broadcast carrier heterodyne tone. Now push the Yaesu DSP noise reduction feature, and hold the button in that allows you to adjust for 16 levels of noise reduction to enhance incoming weak signals laced with background hash.

And there is more that the Yaesu can do with DSP! The FT-100 has an adjustable DSP band-pass filter where high-cut and low-cut characteristics may be keyboard-changed. This allows you to select high-frequency cutoff, as well as low-frequency cutoff, and tune it to a bandwidth of your choice. And, if you're into CW, you can also adjust the center frequency of the CW DSP peaking filter so the pitch is exactly what you want to hear. The default is 240 Hz, and you can select 120 Hz, or a very narrow 60 Hz.

Both the ICOM and Yaesu DSP circuits worked amazingly well in uncovering weak signals that were buried in powerline noise, as well as hash. If you plan to play around a lot with digital signal processing with a set of headphones, you may find more adjustments with the Yaesu equipment than ICOM. But again, both units worked well in the DSP mode.

Of course, both units also have noise blanking; and if you hold the Yaesu noise-blanker button in, it allows up to 16 adjustments of noise-blanking levels. If you have a particularly noisy vehicle, go for a level that will just take out the sparkplug racket, but don't turn the level any higher because it tends to add distortion to the incoming signal, and may sometimes bring in adjacent frequency QRM. On the ICOM 706 G,

you 12 more items with additional selections among the 12. And press display again, and you get four more items including the band scope, SWR graph, transmit frequency, and capabilities

levels of noise reduction DSP to pull the signal out. And on the ICOM, it works pretty darn well. As you crank up the level, you can hear the noise disappearing and the signal becoming more

the noise-blanker level is set and it appears to be set relatively hot to take out severe sparkplug noise. Both noise blankers were able to keep up with my open-air dune buggy, and that is saying a lot on high frequency.

### Network Service Tool Set

Popular installation and service tools for networks, modems and telephones. All hand tools are professional heavy duty type.

Use the compact tester on 10BASE-T (UTP & STP), thin Ethernet (BNC), 8-position Token Ring, AT&T 258A and EIA/TIA 568A/B. Automatically scans cables for continuity, wiring sequence and polarization. Tests STP cable ground. Testing installed cables is easy with Remote Terminator and gender changers (UTP and BNC). 9V battery included.

- Coax Stripping Tool, RG-58 & RG-59
- BNC Crimping Tool, RG-58 & RG-59
- Modular Cutting/Stripping/Crimping Tool (4, 6 & 8-Position)
- Multi-Network Cable Tester
- AC Receptacle Tester
- Cable Cutter

**Order No. 55625 \$197.00**



### PC Service Tool Set

Contains all tools needed to troubleshoot & service IBM-compatible PCs. Set includes:

- AMI Diagnostic Software
- POST Card
- Logic Probe
- Digital Multi-Meter
- AC Receptacle Tester
- Serial Adapter
- Serial & Parallel Loopback Connectors
- DIP IC Puller
- PLCC IC Puller
- Grounding Wrist Strap
- Key Top Puller

**Order No. 55000 \$198.00**



**CALL TODAY!**

**800-854-7393**



### PC Diagnostic Tool Set

- AMI Diagnostic Software
- POST Card

**Order No. 55555 \$89.00**

### Network Installation Tool Set

- Network Tool Set 55625 without the Multi-Network Cable Tester.

**Order No. 55600 \$99.00**

**Call for your FREE Catalog**  
**Graymark®**

P.O. Box 2015 Tustin, CA 92781  
<http://www.labvolt.com>

### FROM FRONT TO REAR

There are so many additional menu features that we may need to study each set in detail by going to a radio store live or on the web, and looking over the instruction manuals.

Going to the rear of both the ICOM and Yaesu "DC-to-daylight" transceivers, we see that ICOM — like Yaesu — offers two antenna ports for high-frequency and 50 MHz operation, and the other port for VHF and UHF operation. Both manufacturers go with the SO-239 connector, but Yaesu puts their two connectors on eight-inch pigtails which may facilitate where you mount the equipment and have access to the jacks. Yaesu offers a data output jack, external speaker jack, accessory jack, and a miniature stereo jack for the built-in automatic keyer. ICOM offers two acces-



## DC-TO-DAYLIGHT RADIOS

sory jacks which can be used for data and other inputs and outputs, a second mike jack, an external speaker jack, a LARGE quarter-inch stereo jack for the paddles to go into the built-in keyer, plus a four-pin jack for the matching automatic antenna coupler.

As we mentioned before, the ICOM unit accepts the common six-pin power plug that almost everyone uses in the industry for an HF radio, and Yaesu goes with a pigtailed, big-blade, two-conductor power plug that is unique to this radio only.

Both the ICOM and Yaesu offer "ground-to-transmit" connections that may be used to pull in an external power amplifier, such as the SGC 500 "Power Cube." But if you're running other style high-frequency power amplifiers, such as the old and reliable Mectron and Metrons, you will need to work up an external relay to click the amplifier on. The older amps may draw as much as 250 milliamps of current on their key line, and neither set is capable of supplying this amount of current capability for a lengthy transmission. Both sets will indeed turn on an older amp, but after a few seconds, the internal circuitry will probably zap. Be aware of this!

On the two-meter band, both sets will easily run two-meter COR amplifiers, but another word of caution — you will need to reduce the power output on the two-meter band down to 30 watts, or 10 watts, depending as to what type of amplifier you have. If you try to drive a 30-watt input amp with a 50-watt output that each set has on two meters, something will give, soon. Both ICOM and Yaesu allow for independent two-meter, as well as 440, as well as high-frequency, power-down adjustments.

Incidentally, on the SGC 500-watt amplifier, even though you may have scored an export version that runs carrier-operated relay, I suggest you go inside the amp, flip the switch, and run it off of a key line which helps the equipment during key-up and key-down times without accidentally tripping out of circuit when it may detect a micro-second VSWR anomaly. The SGC amplifier is extremely touchy on SWR, and going to the hard key line will minimize amplifier cycle-out.

### OVERALL PERFORMANCE

On VHF and UHF FM, both the ICOM and Yaesu put out an identical 50 watts on two meters, and 20 watts on 440 MHz. On high frequency, both the ICOM and the Yaesu could easily whistle to 125 watts peak, and both sets averaged about the same percentage of power during voice modulation after a bit of tweaking.

Tweaking? On the ICOM 706 G, all of the sideband modes were factory-adjusted with just the right amount of ALC (automatic limiting control) to keep the equipment from over-modulating or flat-topping.

On the Yaesu FT-100, the automatic limiting control on two meters and 440 SSB was similar to the output of the ICOM 706 G, but on high frequency, the factory preset levels didn't give us quite the robust needle swing we saw with

the ICOM on our Bird wattmeter. In checking the front meter, it looked like the ALC was set a little high and was throttling back our average power output just a little too much.

A call to the Yaesu factory revealed how easy it was to change ALC settings for each band. The FT-100 SERVICE MANUAL shows how to key-stroke-in factory (only) menu items 01 through 59. Press A, B, and C in on radio turn-on, then menu. Yaesu purposely restricts this information to the technical manual that fully describes what changing some of these items could do for better or worse.

For instance, dialing down the ALC could unleash the transmitter to put out as much as 150 watts, and in no time the radio would get hot as a firecracker and probably go into meltdown. There are also menu items for upping receiver sensitivity on two meters and 440 MHz. Dialing in too much sensitivity on these two bands beyond what the factory has already preset could lead to intermodulation interference in heavy VHF and UHF radio traffic areas.


However, for the more technical amateur operators, buying the optional service manual is something routine where the amateur operator can now — with the Yaesu FT-100 — front dial-in settings to internal circuits that in years past required taking the lid off the radio, and going in with a plastic twiddle stick. This is one of the benefits of digital signal processing — many digital circuits may now be routinely adjusted without having to lift the cover.

Once I slightly readjusted ALC settings to recommendations given me by Chip Margelli K7JA, of Yaesu, I was still within factory specs (on the edge) and the set gave me plenty of output power, nice and linear without any flat-topping, and still continued to run nice and cool during prolonged transmit periods.

Yaesu also gives you a DSP microphone equalizer feature that allowed us to tailor our transmitted audio for exactly how we thought we should sound. Both Yaesu and ICOM also offer

speech processing and compression, too.

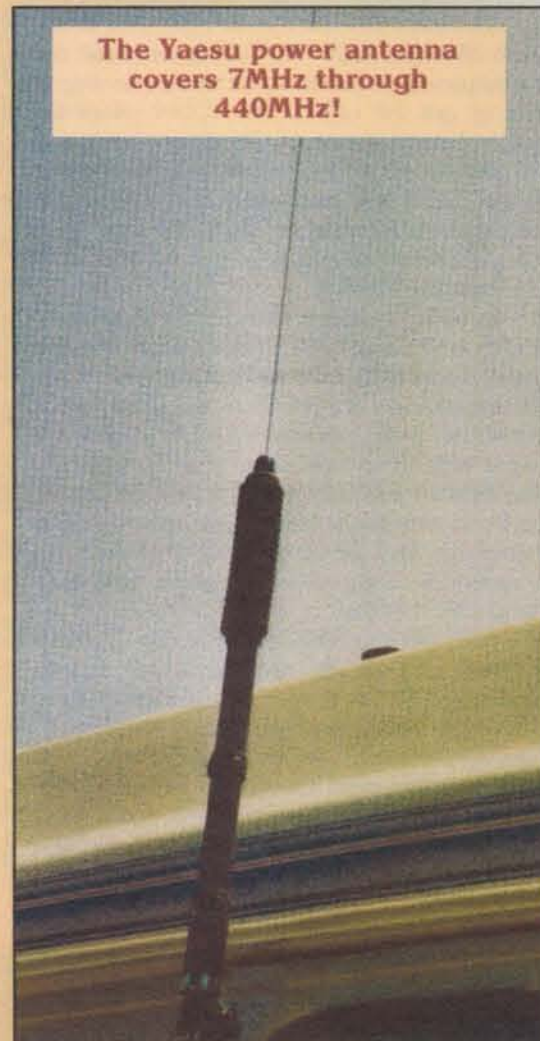Both sets included a full-featured, built-in electronic keyer. Both units allowed for setting the weight of your CW exactly as you want it, as well as CW reverse mode and transmit CW pitch. And if you do a lot of CW, you'll enjoy a unique function of the Yaesu FT-100 that has a 50-character message memory storage system to keep



The Yaesu power antenna covers 7MHz through 440MHz!

## ELECTRONIX EXPRESS

### WELLER SOLDERING STATION - MODEL WLC 100

- Variable power control (5 to 40 watts)
- Replaceable heating element
- Quality light-weight pencil iron

\$36.95



### LOWEST PRICE 20MHZ SCOPE!

Instek®  
OSCILLOSCOPE  
20MHZ  
DUAL CHANNEL  
MODEL GOS-620



\$299.00

SCOPE PROBE 60 MHZ  
SWITCHABLE X1, X10

\$12.95

DIGITAL MULTIMETER  
WITH CAP/FREQUENCY/  
TRANSISTOR TESTER  
Model DM645



\$34.95

PAD-234  
DIGITAL/ANALOG TRAINER

Complete portable workstation. Variable and fixed power supplies, function generator, digital I/O, rugged design, high impact case.

Assembled  
\$150.00

Kit  
\$110.00

### HIGH QUALITY TOOLS

With Cushion Grips and Return Spring  
Needle Nose Pliers \$2.95  
Wire Stripper \$1.50  
Diagonal Cutter \$2.95

### POWER SUPPLIES

0-30 VDC, 0-3 Amp. Built-in current limiting, overload protected, constant voltage and current operation.  
01PSGP4303A Analog Display \$165.00  
01PSGP4303D Digital Display \$189.00

### RSR TELECOMMUNICATIONS TRAINER

HANDS-ON TELEPHONY, LAN, CATV EXPERIENCE  
WITH ONE SELF-CONTAINED UNIT

T-Comm Trainer (TCM-100) \$199.95  
Lab Manual / Work Book 19.95  
Component and Supplies Kit 39.95  
Tool Kit 119.95

Only \$199.95



### SOLDERLESS BREADBOARD

830 tie points. MB102PLT model features 3 binding posts and aluminum backplate.

Part No. 1-9 10+  
MB102 5.95 5.00  
MB102PLT 8.95 8.00

### HELPING HAND WITH MAGNIFIER


#060836 \$3.50

### RESISTOR KIT

1/4W 5% film. 5 pieces each of 73 values. 365 pieces total. \$3.95

### MOTION DETECTOR

\$2 ea. - 10 For \$15

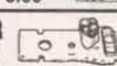

### SOLDERING IRON 3-WIRE

HIGH PERFORMANCE \$5.25  
#060501

### FREE CATALOG

MORE Low-Priced Items In Our FREE 236-Page Catalog

TERMS: Min. \$20 + shipping. School Purchase Orders, VISA/MC, Money Order, Prepaid. NO PERSONAL CHECKS, NO COD. NJ Residents: Add 6% Sales Tax.

In NJ: 732-381-8020  
FAX: 732-381-1572

365 Blair Road • Avenel, NJ 07001-2293  
800-972-2225

http://www.elexp.com  
email: electron@elexp.com



## DC-TO-DAYLIGHT RADIOS

you from wearing out your fingers during a contest when calling CQ!

The Yaesu I reviewed also had optional CW filters that were soldered in at the factory, and they really work wonders when trying to recover faint signals coming in out of the noise. ICOM optional filters plug in.

Both the ICOM and the Yaesu offer automatic repeater offsets on 10 meters, six meters, two meters, and the 440 MHz bands. I am glad to see this with the new ICOM "G" series because the older equipment required some extra pushing of buttons to get the offset. The ICOM offers full encode and decode as part of their package, and Yaesu offers encode CTCSS only with decode as an option. But Yaesu also offers built-in capabilities of digital code squelch (DCS), and the DCS encoder/decoder is built into the FT-100 as it comes from the factory.

To compare receiver sensitivity and selectivity on HF, VHF, and UHF, I built up an antenna combiner system that would provide one antenna for simultaneous reception on both radios without either radio loading down the circuit. We also went with a two-position antenna switch, but nothing beats the simultaneous reception of both radios to an extremely weak signal on one common antenna. And we tried mobile antennas, big base antennas, long wire antennas, and little VHF and UHF beams.

We tried out the receivers in relatively radio-quiet zones, and we also took both radios up to "mount intermod" that has enough RF coming off of it to just about mesmerize any receiver.

The results are in — both receivers are hot as a firecracker, and both the ICOM, as well as the Yaesu did a fabulous job of sorting out signals among the QRM and QRN. When there was

someone on high frequency operating 3 kHz away, both receivers would slightly hear the "buckshot."

Weak signals coming in just about the noise threshold could be received by both receivers, almost identically. But as you would fuss with the DSP circuits, each receiver had its own characteristic way of pulling out signals really down in the mud. And same thing for CW — when we switched to the more narrow CW filters, they did the job well with the Yaesu equipment. Had we installed the optional CW filters in the ICOM gear, it would have probably given us the same CW results.

While you'll probably hear reports about one receiver being far superior than the other, we could barely tell a difference during our operating tests — both were outrageously sensitive, selective, and AGC (automatic gain control) action was about the same. When we would set the squelch on HF SSB, and a weak signal would break through the squelch, you would hear it come over both rigs at the same time.

### THE WINNER IS ...

So who is the winner of the DC-to-daylight radios from ICOM and Yaesu? WE, as the buying public, are the winners because manufacturers have packed in so much that originally took three radios a few years ago to do. We win big time when it comes to the capabilities of both of these transceivers, and I really couldn't say which one was "better" than the other — they both were great.

Which one YOU will choose depends on how you like the sound and feel of the equipment. Try to work the two pieces of equipment, as we did,

side by side off of a common or antenna one/antenna two selector switch. Don't worry about your transmit audio — everyone will love it on either radio. But listen for yourself, try the push buttons, and then get the "feel" for how each radio operates. Learn everything you can about the equipment to discover advantages of one over the other.

We discovered that Yaesu has a matching mobile antenna that covers 40 meters through 440 MHz, and is motor-driven-adjustable by an automatic built-in tuner inside both the radio and the antenna. Just push the button and the Yaesu ATAS-100 antenna goes up and down, stopping at exactly the lowest SWR point. For VHF and UHF, it drops all the way down into the nested position to provide one-quarter wave on two meters, and three-quarter wave on 440 MHz with appropriate impedance matching. On HF, it is a loaded quarter-wave that automatically tunes within a few seconds of pushing the tune button. Sorry, no 75 meter or 160 meter automatic operation.

On the ICOM, we discovered that you could run both headphones or an external speaker off of the remote control front panel. We found a little switch that selected this option. It was probably somewhere in the instruction manual, but nothing beats working with the equipment when you have it out of the box, and right in front of you.

So do just that—find these two rigs, out of the box, turned on, right in front of you, and do as we did and give them a side-by-side comparison. Choosing which one is for you will be one tough decision — you indeed are the winners with this new technology of a transceiver that gives us DC-to-daylight coverage! NV



# You Win with Nuts & Volts

Subscribe today and be  
automatically entered in our  
new MONTHLY PRIZE  
DRAWING!!!

June Prize Winners:  
**Davis Whitaker**  
of Newport, RI  
**Bob Kennedy**  
of Parker, CO

AUGUST DRAWING HOSTED BY  
**ELECTRONIC GOLDMINE**  
(see page 83)  
**\$100.00**  
Gift Certificate  
towards purchases

SPECIAL BONUS:  
**NETCOM** (page 25)  
WILL FURNISH PRIZES  
MONTHLY!!

### Contributors ...

- Parallax (back cover) • Corporate Systems Center (pages 2, 95) • HSC (page 3) • Resources Unlimited (page 55) • Timeline, Inc. (page 81, May issue)
- Alltronics (page 22) • Electro Mavin (page 65)
- All Electronics (page 56) • Roger's Systems Specialist (page 33) • Electronic Goldmine (page 83)
- MCM Electronics (page 17) • Velleman (page 59)
- Seabird Technical (page 82)

Check us out on the web!  
<http://www.nutsvolts.com>

If you do not wish to order a subscription, but would like to be entered in our drawing, simply **send or E-Mail** your name, address, and telephone number, to NUTS & VOLTS, 430 Princeland Court, Corona, CA 91719, [drawing@nutsvolts.com](mailto:drawing@nutsvolts.com). No phone entries accepted. All orders/entries must be received by the last day of the month to be included in that particular month's drawing.

As a current, paid subscriber, you will be automatically entered each month in our drawing.

**To Subscribe** — Just fill in and mail the enclosed subscription card or call our toll free order line at (800) 783-4624 with a Visa or MasterCard.



### HP5335A, 1.3GHz, HIGH STABILITY, HPB, UNIVERSAL COUNTER

Providing true automatic measurement functionality. This system has 16 built in front panel accessible measurement functions, all available via the HPB or manually. One of the most powerful universal counters available. Math and statistics include averaging, mean, sample size, standard deviation, engineering units display offset scale and normalization. Matched dual inputs provide 200MHz on chan. A and 100MHz on chan. B. and 1.3GHz on chan. C. Nine digit resolution from 30Hz to 200MHz. Imeg. and 50 Ohm inputs. Auto trigger and much more. All the toys in one package! Excellent condition. OPTION 010 and 020. The options alone were \$1600!!

New.....\$5500 Now.....\$549

### SLEEK, 100MHz, TEK 2336, PORTABLE, FIELD SERVICE O'SCOPE with DELAY TIME

Dual trace, Delayed Sweep, 50ns/div. Sweep Rate, 5mV Vert. Sensitivity. Differential time meas. on LCD display Extra rugged, perfect for field service work. Package includes two probes and manual. Mint condition. Six month warranty.

New.....\$4850 Now.....\$695

### KIK PLZ-150W, ELECTRONIC LOAD

Industry workhorse, can handle loads up to 150Watts. The front panel controls allow selection of all voltage and current parameters. Current up to 30A and Voltage up to 60V can be accommodated. LED readout. Good condition.

KIK-EL.....\$429ea.

### HIGH RESOLUTION OPTICAL ENCODERS

2500PPR, 10,000PPR in quadrature!

DRC MODEL 25-5351-817-2500. Size: 2.5" d, 1/4" ball bearing with shaft seal. Continuous rotation, 3000 RPM max. Alum. housing. 5V powered with zero reference out, 18" cable. LTD. QTY USED.....\$49ea.

### MINI ROTARY DRIVE with on board LINEAR SLIDE, Provides 300°

rotation between removable stop. Rotates continuously with-out stop. 2 optical position sensors for start & end. Same stepper as above. Each full step = -0.25° of rotation. Made from cast & machined resin & alum. Attached slide provides 3" travel. Construction similar to slide above. Moves 0.008" per step. Dual optical end of travel sensors. Overall 7.5" x 5.25" W x 4.5" H. Special.....\$49ea or 2 for \$89

### NEW! 0.008lux, COLOR NIGHT VISION CAMERA! UNBELIEVABLE LOW LIGHT PERFORMANCE. Our GMV-2K, DOES it in COLOR TOO!



For covert, military and scientific applications that must be color, this is it. Performance is enhanced through low speed electronic shuttering and digital frame memory. With an auto iris lens, 24 hour monitoring is possible. Auto sensitivity mode starts as it becomes dark. Eight Gain/Shutter modes are user selectable. Normal, X4, X8, X16, X24, X32, X64, X128. These provide frame rates of 60, 15, 8, 4, 3, 2, 1, and 0.5 frames per second. Auto/Manual white balance. Aluminum housing with dual 1/4x20 mounts. Specs: 1/3" CCD, with 291K pixels, 320 Lines, <1 Lux std. mode sens., 12VDC @200mA, Std. video out on BNC. Size: 54mmx50mmx94mm long. With pwr. adapter. All functions can be externally controlled via an 8 pin mini DIN. Uses std. c-mount lens not included.

Special Item, GMV2K.....\$589ea.  
4mm, f1.4 A/I lens with custom cable.....\$119ea.

### MINI, PRECISE, PORTESCAP, SWISS, GEARMOTOR.

State of the art "ironless" type, mini motor type M11-210-54-0 with approx: 40:1 spur gearbox. Size: 16mm d. x 43mm L

Volt. 6V 8mA 141 TYPE B: \$15ea.  
12V 12mA 290 2 for \$27

### LAMBDA 0-120VDC @ 0.5A POWER SUPPLY

Model: LQ524, operates in constant current or constant voltage mode. LED digital readout displays Volts or Amps. (switchable) Front panel 5-way binding posts. Compact, excellent condition.

Ltd. Qty. Special.....\$159ea.

### DUAL, 20VDC @ 3A, LAB POWER SUPPLY, HP 6253A

Two independent outputs of 0-20 volts @3 amps. Extremely low ripple @ only 1mV. Each with constant current & constant voltage mode, as well as tracking & OVP, front and rear floating outputs, rack mountable.

New.....\$1350 Now.....\$249ea.

### TEKTRONIX 335, MINI SCOPE, Can be AC or DC Powered.



The 35MHz bandwidth and 1mV/Division vertical sensitivity combine to make this compact dual trace scope a true field service performer. Size: 13.6"x9.3" W x4.4" H Weight: 10.5 lbs. Can be operated from 90 to 264VAC, 48 to 440Hz or 11 to 28VDC. External jack for DC input. Package includes probe, manual, calibration and 6 month warranty.

New.....\$3000 Now.....\$395

### ANPVS-7, WEARABLE, MILITARY, NIGHT VISION GOGGLE

The NQ5001-2 is the commercial designation for the ANPVS-7. The world's most rugged and reliable, high performance night vision goggle for ground operations. Extensively used by the U.S. Army, it is the State-of-the-Art in mono-tube Night Vision Goggles. It can be used under extreme conditions, headstrap mounted or handheld. Engineered for maximum comfort and simple to use. The system contains an IR illuminator, low battery indicator & high light sensor for automatic power off to image tube. Includes soft carry case & head mount.



#### Specifications:

Generation: Two  
Photocathode: Multi Alkali  
Resolution: 28 lp/mm  
Photo Response: 450 Ma/lux  
Tube Gain: 25,000x  
System Gain: 2,200x  
Signal To Noise: 11:1  
Battery Type: 2 'AA'


Battery Life: 20 Hours  
Magnification: 1x  
Objective Lens: 25mm F/1.2  
Field Of View: 40°  
Focus Distance: 2.5m To Infinity  
Size: 14.9 x 14.9 x 9.1 cm  
Weight: 680 gm

Special.....\$2195ea.
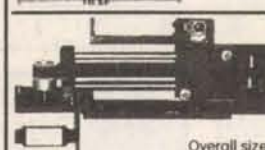
### NEW! COLEMAN DC MOTOR, w TACH

Good for general purpose applications.

Size: 1" diam. x 2.5" long. Small 5/16" diam belt drive pulley attached. 12VDC power, 200mA, No Load 6000 RPM Rugged construction. Tach output. Special, \$3ea. 10 for \$25



### MINI, LINEAR MOTORIZED MOUNT, This high quality mini slide provides

2.4" of travel for it's 1" x 1" alum. plate riding on two 0.18" diam steel rods. Motion is via a toothed belt drive from a 1.8" per step, 8 ohm stepper motor. 1 full step - about 0.008" of travel.

Overall size: 6" L x 3.5" W x 2.5" H, Dual optical end of travel sensors. Alum. construction. SPECIAL.....\$24ea. or 5/\$99

### NEWPORT TRANSLATION STAGES.


also a few other goodies too!

MODEL:	DESCRIPTION:	EACH
270	LAB JACK	\$249
RSA-2T	360 deg. Rotary Stage with Clear Aperture.	\$129
625A-4	Laser Holder	\$149
481A	Rotary Stage	\$189
M36	Translation Stage	\$249
460A-XY	X-Y Translation Stage	\$189
M37	3 Axis Trans. Stage	\$289
415	Vertical Trans. Stage	\$129
M360-90	Mnting. Plate 90deg.	\$29
M436	Translation Stage	\$199
M150	Magnetic Mtg. Base	\$129
420	Linear Trans. Stage	\$119

#### MISC. OPTICAL COMPONENTS:

HP10706A	INTERFEROMETER	\$129
HP10703A	INTERFEROMETER	\$129
HP10702A	INTERFEROMETER	\$129
HP10780A	RECEIVER	\$199
RUCKER & KOLLS 222	X-Y-Z MICRO POSIT.	\$ 50

## IS ANYBODY OUT THERE?

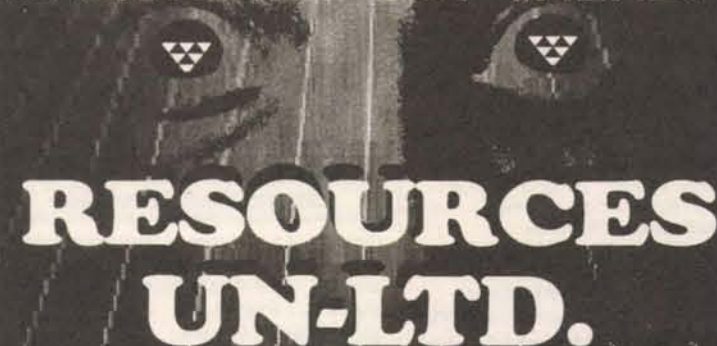

VISA, MC, AMEX, DISCOVER, COD.  
ORDER: 800-810-4070 TECH: 603-668-2499  
FAX: 603-644-7825 E-MAIL unltd4u@m20.net  
300 BEDFORD STREET, MANCHESTER, NH 03101

### NEW, "STEALTH CAM", MICRO SIZE, with AUDIO!

The sleek aluminum housing fits like a glove! Removable mounting bracket and a 1.3M cable with BNC vid., RCA aud., (internal mic) & DC barrel jack for, no sweat hook up. Why fool around with an open P.C. board? Now you can have the "STEALTH CAM". 1/3" CCD, 410 Lines, 0.3 Lux, AGC, Auto Shutter. Pwr. from 9 to 12VDC @110mA, 250k pixels, Std. model, 4mm, 78° FOV lens, Pinhole model, 90° FOV. A real glass lens. Focus from 10mm to infinity. NTSC video out. Only 1.7 ounce! SENSITIVE to IR. Size Std: 30mm sq. x 29mm d. PH is 16mm d. WARNING: Don't confuse these models with LOW RESOLUTION, HIGH LUX C-MOS CAMERAS.



GM-2000S-STD, w/aud. ....\$79.00  
GM-2000S-PH, w/aud. ....\$79.00

### 16 CHANNEL DIGITAL VIDEO MULTIPLEXER, allows real time, multi-camera recording to tape.

NEW! American Dynamics, 1484SL-16. Allows recording of up to 16 cameras on one video tape. Video loss detection and pre-loss frame memory. Manual/auto camera selection. Can be rack mounted. A commercial quality unit. Very limited quantity available.



AD1484SL-16, Special.....\$379ea.

**6V@12AH SEALED, RECHARGEABLE, BATTERY**  
New Panasonic, LCR6V12PL. Tough to get at a discount. Very compact. Two top mounted 1/4" faston connectors. Perfect for high drain projects. Size: 5.9" L x 3.7" H x 1.9" D 2 /\$20, 10/\$89

### NEW! DAYLIGHT to LOW LIGHT MINI CAM, w A/I LENS

For those applications that must work from dawn 'till dusk, this is it. Rugged aluminum housing with dual mounting sockets. Specs: 1/3" CCD, 420 lines resolution, 0.1 Lux sens., AGC, Auto shutter. 12VDC @120mA. Take full advantage of camera sensitivity with the super, 4mm, f1.4, 78° FOV Auto Iris lens included. Video out on BNC. Size: 50mm sq. X 65mm long. Power adapter included. Ready to go! GM-510A/L.....\$199 or 2/\$369

**END FIELD of VIEW GUESSWORK! 3.5 to 8mm VARI-FOCAL LENS**  
Brand New, super f1.8 lens allows you to smoothly adjust from a 97° FOV @ 3.5mm to a 44° FOV @ 8mm. Now you can frame your area of interest just the way you want it! Standard CS-Mount with adjustable focus and iris. SPECIAL.....\$99ea. or 2 for \$189

### ULTRA MINI and WEATHERPROOF, "LIPSTICK" CAMERA

Sleek black anodized, alum. housing. O-Ring sealed & RAINPROOF. Adj. tilting mount. 1/3" CCD, 380 Lines, 0.3 Lux, AGC, Auto Shutter. 9-12VDC @100mA, 4mm, f1.8, 78° FOV real glass lens, NTSC video. <1 ounce! IR SENSITIVE. 23mm d x 50mm, 36" cable with BNC video & DC barrel jack.

GM-200K-STD.....\$99  
PINHOLE Model. So tiny you can install it directly into a door. Only a 0.9" diameter hole! Specs as above. 90° FOV Pinhole lens. 1/2 ounce! Size only 23mm d. x 35mm long. Think of the places you could put this little jewel.  
GM-200K-PH lens.....\$99

### NOW YOU CAN SEE WHAT THE "FISHES ARE DOIN" (down 60 ft.)

**UNDERWATER B&W CAMERA with INTERNAL, INFRA-RED ILLUMINATOR!**  
Sleek black anodized, BRASS, housing. O-Ring sealed & WATERPROOF. Adjustable mount incl. Specs: 1/3" CCD, 400 Lines res., 0.05 Lux sensitivity, AGC, Auto Shutter. 12VDC @225mA, 4mm, 78° FOV lens. A real glass lens. NTSC video out. Superior construction. SENSITIVE to IR. Ultra small Size only: 1.25" diam. X 2" long. With 60 ft. cable. Great for general outdoor use also. GM-300KIR.....\$199

### ULTRA MINI, COLOR WEATHERPROOF "LIPSTICK" CAMERA

For those applications that must be color, this is it. Black anodized, aluminum, housing is O-Ring sealed & RAINPROOF. Adjustable tilting mount included. Specs: 1/3" CCD, 400 Lines resolution, <1 Lux sensitivity, AGC, Auto Shutter. 12VDC @180mA, 4.3mm, 78° FOV lens. A real glass lens. Std. video out. Size: 32mm diam. X 65mm long. 24" leads with RCA jack and DC jack. With power adapter. GM-400K.....\$199

**Brand New, Video Motion Sensor.** Model VM10. Attach to any standard video signal and you've got an electronic "watchman" diligently watching the entire scene. Or any adjustable sized area within the scene. Such as a doorway or even a drawer or cabinet. A state of the art security aid. The unit will close a contact when it senses a change. Use it to turn on a VCR or call the house. Auto or manual reset. Compact, ac powered. Adjustable sensitivity. Video loop through. NEW VM10.....\$189

### low cost MICRO CAMERA, w/audio 1/3"

CCD, 410 Lines Res., 0.3 Lux sens., AGC, Auto Shutter. Pwr. from 9 to 12VDC @100mA, 250k PIXELS, Std. model, 4mm, 78° FOV lens, Pinhole, 90° FOV. A real glass lens. Both focus from 10mm to infinity. Std. NTSC video out. 1/2 ounce! SENSITIVE to IR. Size Std: 1.25" sq. x 1" d. PH is 0.6" d. 1.6M long wiring harness with connectors included. WARNING: Don't confuse these models with LOW RESOLUTION, HIGH LUX C-MOS CAMERAS.

GM-1000A-STD.....\$59 GM-1000A-STD/Aud.....\$64  
GM-1000A-PH.....\$59 GM-1000A-PH/Aud.....\$64  
GM-1000A-CMNT.....\$59 GM-1000A-CMNT/Aud.....\$64

Micro Lenses for GM1000 series			
2.5mm, 150°.....	\$22	8.0mm, f2.0.....	\$22
4.3mm, 78° f1.8.....	\$22	12.0mm, f2.0.....	\$22
6.0mm, f2.0.....	\$22	5mm, 70°PH.....	\$22

#### C-MOUNT LENSES

LOW LIGHT		STANDARD	
16mm, f1.6, 15° FOV.....	\$39	4mm, 80° FOV.....	\$24
8mm, f1.3, 40° FOV.....	\$49	8mm, 40° FOV.....	\$24
4mm, f1.4, 78° FOV.....	\$49	12mm, 28° FOV.....	\$24

**NEW, 9" SECURITY MONITORS**  
We were fortunate to obtain these Hi-res 700 Line. B&W units. Original manufacturers boxes, 90 day warranty. BNC video in and loop through. Rugged steel case. Current production model. Limited qty. They will make your video look super!  
SPECIAL.....\$129.00ea. 2 for \$238.00

### NEW, 2.4GHz VIDEO + STEREO AUDIO TRANSMITTER with SONY, CCM-PC5 COLOR CAMERA.

Originally sold for \$500! Now available for a fraction of that price. Great looking styling. Camera has a very stable, adjustable tilting base, front panel LED pwr. indicator and sensitive built in electret mic, providing excellent audio and video performance from one compact package. Simply connect camera to the completely self contained 2.4GHz transmitter. All cables supplied. You can transmit up to 700 feet clear line of sight! Companion matching receiver works with any TV or VCR. Internal patch antennas. Camera has adjustable focus 6mm lens. (1" to infinity, macro capable) Auto power off when the privacy shutter is closed. Power is 7-13VDC. (all pwr. adapters and cables included) 1/3" CCD, 330Lines res. 35% better than standard VHS! Can also be used to transmit VCR output to another TV for remote viewing.

SPECIAL, 2.4GHz SONY-ASTROVIEW.....\$189ea. or 2 for \$339  
addtl. 2.4GHz TRANSMITTER/RCVR. less Camera.....\$129ea.

### MOTORIZED ZOOM LENS SPECIAL

**6X magnification, 12X on a 1/3" camera! Auto iris too!**  
New, fabulous hi-res. optics with std. C-Mount. Superior Fujinon and Vicon lenses. Normally cost from \$600 to \$1500. There is no substitute for a good lens! All drive motors will operate from 6-12VDC. Auto iris has a built in amp which works with any cameras video output for control.  
Type B-6, 12.5 to 75mm, 6X, f1.2 ..... \$179 or 2 for \$349  
ZOOM LENS CONTROLLER, NEW ..... \$169

### 10V @ 2.5 AH SEALED, LEAD ACID, PACK

Each pack consists of five, 2 Volt cells. Each cell the size of a std. 'D' battery. They are arranged as 1X5 cells. Enclosed in an ABS outer shell. (removed for photo) Mint condition. Perfect for robotics and other high drain applications. Buy several, make custom packs of any rating. Size: 7.5" L x 2.8" H x 1.5" D 5-five packs for \$20, 30 for \$99



**ROBOTS WANTED:** Dead or alive, whole or parts. Marvin (Iowa Precision), Gemini, RoPet, Hubot, RB5X, Newton SynPet, ComroTot, ELAMI, ITSABOX, HeathKit (HERO JR, 1, 2000, or Arm Trainer), Androbots (TOPO, BOB, Fred, and Androman), Rhino, Maxx Steele, Omnibots, etc. Also looking for robot prototypes, options, and literature, will pay cash. Please E-Mail [rdorr@bizserve.com](mailto:rdorr@bizserve.com) Call 810-777-1313 or write to: Robert Doerr, 26308 Cubberness, St. Clair Shores, MI 48081.

**www.nutsvolts.com**

**ARobot KIT** from Arrick Robotics uses the BASIC Stamp II. Quality metal construction. Easy to assemble and very expandable. \$235. <http://www.robotics.com/arobot>

## PLANS - KITS - SCHEMATICS

**HEATHKIT COMPANY** is selling photocopies of most Heathkit manuals. Only authorized source for copyright manuals. Phone: 616-925-5899, 8-4 ET.



**ELECTRIC POWER METER STOPPER** MAKES METER RUN SLOWER, STOP, OR EVEN REVERSE! COMPLETE PLANS \$10, SOLD FOR EDUCATIONAL PURPOSES ONLY. (VISA/MC/AMEX/COD) OPEN 24 HOURS! 407-654-9677 BRINKER ENGINEERING LABS, USA.

**HOVERBOARDS, JETPACKS, LIGHT-SABERS.** Plans, schematics, and kits for over 100 incredible devices. \$3 for catalog. Future Horizons, PO Box 125, Marquette, MI 49855. [www.futurehorizons.net](http://www.futurehorizons.net)



**CIRCUIT BOARDS.** Low-cost, precision-made PC boards from your CAD program files (no photoplots required). Single and double-sided with contour routing. Ideal for RF/analog/digital prototypes. Full details at <http://www.pcbmilling.com> E-Mail: [feedback@pcbmilling.com](mailto:feedback@pcbmilling.com) FAX: 703-818-0071.

# ALL ELECTRONICS

C O R P O R A T I O N

QUALITY PARTS

FAST SHIPPING

DISCOUNT PRICING

CALL, WRITE, FAX or E-MAIL For A Free 96 Page CATALOG. Outside the U.S.A. send \$3.00 postage.

## PM89 SERIES PANEL METERS

3.15" x 2.5" x 2" depth. 2.5% accuracy. Large clear scale, black lettering on white background. Available in a variety of ranges.



DC AMMETERS	CAT #	EACH	10+
0-100 mA DC	PMD-100MA	\$12.00	\$10.00
0-1A DC	PMD-1A	\$12.00	\$10.00
0-5A DC	PMD-5A	\$12.00	\$10.00
0-15A DC	PMD-15A	\$12.00	\$10.00

DC VOLTS	CAT #	EACH	10+
0-15V DC	PMD-15V	\$12.00	\$10.00
0-30V DC	PMD-30V	\$12.00	\$10.00

AC AMMETERS	CAT #	EACH	10+
0-5A AC	PMA-5A	\$12.00	\$10.00
0-15A AC	PMA-15A	\$12.00	\$10.00

AC VOLTMETERS	CAT #	EACH	10+
0-150V AC	PMA-150V	\$12.00	\$10.00
0-300V AC	PMA-300V	\$12.00	\$10.00

## 1.5 Volt Mini-Vibrating Motor

Tiny 1.5 Volt motor with offset-weighted shaft. Typically found in pocket pagers and cell phones for vibrating alert signal. Operates on 1.5 Volts, 80 mA. Motor body is 0.28" dia. x 0.67" long. Shaft is 0.03" (1mm) dia. x 0.16" long.

CAT# DCM-131 **\$2.50** each

10 for \$22.50 • 100 for \$200.00  
500 for \$875.00 (\$1.75 each)

## 3000 MCD ULTRA-BRIGHT RED LED

Everlight # 383URC-2/TR1-C(R) Red, "Ultra-bright" T 1 3/4 LEDs "Tape-and-reel" parts. These are 5 mm diameter water-clear LEDs that light bright red at 20 ma.

CAT# LED-50

**2 for \$1.00** 100 for \$35.00  
1000 for \$250.00

## INCREDIBLY LOW PRICE! Sony Color Video Camera with Audio


Sony# CCX-Z11/S1. Brand new color video camera with audio. Ideal for surveillance or video conferencing. Good-looking, compact design, only 3.5" X 2.33" X 1.05". Adjustable lens. On-off power switch. RCA jacks for video and audio outputs. Includes 4.5 Vdc power supply, output cables and adjustable desktop camera stand which can easily be used as a wall or ceiling mount bracket. Get one now...at this price they won't last.



CAT# VC-1100 **\$90.00** each  
3 or more \$85.00 each
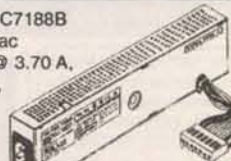
## ENCLOSED SWITCHING POWER SUPPLY

Voltek Corp # SPEC7188B Input: 100 - 240 Vac Outputs: + 5 Vdc @ 3.70 A, +12 Vdc @ 0.60 A, -5 Vdc @ 0.05 A, +5 Vdc Trickle @ 0.1 A. Metal enclosed switching supply. Standard three-prong IEC socket power input. 7 conductor, Molex-type connector output. 9" x 2.1" x 1.36". UL recognized. Removed from new equipment.



CAT # PS-27 **\$3.50** each

## "HI-8" Video Cassette

SONY Hi-8 Top quality, metal particle 120 minute video cassettes. Used for a short time, then bulk-erased. Each cassette has its own plastic storage box.



CAT # VCU-8 **\$3.00** each  
10 for \$28.00 • 100 for \$250.00

## 20 Character X 4 Line LCD

Optrex # DMC 20434-CEM (PWB 20434-CEM) 5 x 8 dot format. 3" x 1" viewing area. 3.88" x 2.38" module. Removed from new equipment. May have felt padding on metal bezel. 14 pin single row header is pre-attached. Spec/hook-up sheet included.

CAT# LCD-46 **\$7.00** each  
10 for \$60.00

## Microphone For Fish

Consists of a dart-shaped underwater transducer on a 21' wire and a small amplifier. According to the manufacturer, it enables you to hear the fish striking your bait, thus allowing you to catch more fish. We don't have the instructions, and you will need some headphones with a 3.5 mm phone plug. Also requires 4 AAA batteries (not included). Transducer is 3.3" long. Amplifier assembly is 3.5" x 2.4" x 1".

CAT # AQS-1 **\$5.00** each

## Padded Carrying Case

Good looking protective carrying case for Zip drives or Walkman players, tools, guns, photographic or electronic equipment. This well-built black canvas bag has 0.5" thick high density padding all around and nylon inner liner. 1.5" wide webbed handle and detachable shoulder strap. Heavy duty zipper. Interior pocket and adjustable velcro compartment. Interior area: 16" X 6" X 2.5". These are new bags with a company logo (Interactive Network) on a patch on one side.

CAT # CSE-10 **\$5.00** each

ORDER TOLL FREE

**1-800-826-5432**

MAIL ORDERS TO:  
**ALL ELECTRONICS CORP.**  
P.O. BOX 567  
VAN NUYS, CA 91408-0567

FAX (818) 781-2653 • INFO (818) 904-0524  
**www.allelectronics.com**  
E-MAIL [allcorp@allcorp.com](mailto:allcorp@allcorp.com)

NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail • Orders Delivered in the State of California must include California State Sales Tax • NO C.O.D. • Shipping and Handling \$5.00 for the 48 Continental United States • ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

**MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.**

**BROADCAST FARTHER!** 75-110MHz amplifier connects to stereo transmitters. Produces 2-15 watts. Requires 50-150mW drive. Complete plans with part source and antenna information only \$14 + \$2 S&H. **Progressive Concepts**, PO Box 586, Streamwood, IL 60107. 630-736-9822.

**PALM PILOT** never replace batteries again. Simple modification charges batteries in cradle. For Palm Pilots up to IIIx. \$10. Mark Lopez, 22689 Silver Dollar, Corona, CA 91719.

**ELECTRICITY — STOP BUYING IT!** Legally reduce \$150 monthly bills to as low as \$15. Make FANTASTIC money showing friends, neighbors how! FREE INFO! 1-800-668-1878.

**TRANSISTOR THEORY FOR DUMMIES.** A new, easier to understand approach. Other basic electronics theory included. Lots of useful information, 22 page text, \$6.85 ppd. Credit card orders 703-549-5325 or mail to: **THERMADYNE, INC.**, 206 Birch St., Alexandria, VA 22305. Details at: **www.THERMADYNE.COM**

**CONSUMERTRONICS** 120+ exciting manuals: Electronics, computers, Internet, phones, energy, radionics, financial (including stocks), crime-fighting, security, survival, phenomena. **SPECIAL PROJECTS.** Catalog \$3. PO Box 23097, Albuquerque, NM 87192. **www.tsc-global.com**





## REFILL INKS FOR INKJET PRINTERS

Refill your old cartridge and save. All refill kits come with instructions and needed materials for refilling inkjet cartridges. Success guaranteed. Available for the following:

**CANON BC-01, BC-02 CANON BJ10e, APPLE STYLEWRITER, BJ-200** Single Black Refill \$8.00; Triple Refill \$19.00. **CANON BJC-600 (BC-201)** Single Black or Single Colors (3 refills) \$8.00. **CANON BJ-130/300/330 & IBM Exec Jet** (Cart #BJL-481 & BJL-642) Black - 3-bottle kit \$22.00. **CANON BJC-210/240 (BC-05 Cart)** 3-color kit (3 refills each color for BC-05) \$24.00. **CANON BJC-4000** and Apple Stylewriter 2400 Black 3-bottle kit (3 refills BC-20, 9 refills BCI-21 black, 30 refills BCI-11 black, 10 refills BCI-10) \$19.00. **CANON BJC-4000/BJC70 and Apple Stylewriter 2400** Tri-color kit - 6 refills each color for BCI-21 or 15 refills each color for BCI-11 \$24.00. **CANON BJC-800/820/880** 3-bottle kit (for BJL-643B) \$19.00. **CANON BJC-800/820/880** 3-bottle tri-color kit (Cart #BJL-643CMY) \$24.00. **EPSON STYLUS COLOR PRINTER** - (Cart S020034) Single Triple black \$19.00; Tri-color kit (Cart S020036) 2 refills each color \$24.00. **EPSON STYLUS COLOR II** - (S020047) Triple Black \$19.00 (S020049). Tri-color (2 refills each color) \$24.00. **EPSON STYLUS COLOR 400, 500, & 600** (S020093) Triple black (7 refills total) \$19.00; **EPSON STYLUS COLOR 200, 500** (S020097) Tri-color 3 refills each color \$24.00. **EPSON STYLUS COLOR 400, 600, 800, 1520** Tri-color (S020089) 3 refills each color \$24.00. **EPSON STYLUS 800/1000** (S020025) 3-refill kit, black, \$19.00. **HP DESKJET 500/550/560** (51608A, 51633A, 51626A) Black single refills \$8.00. **HP DESKJET 500/550/560**, Black 3-bottle kit \$19.00. **HP DESKJET 500C/550C/560C** - Tri-color kit (5 refills each color) \$24.00. **HP DESKJET 1200C, DESIGNJET 650** (Cart #HP 51640B) Black Three pack (3 refills) \$19.00. **HP DESKJET 1200C/1600C, DESIGNJET 650** (Cart #HP 51640 C,M,Y). Tri-color kit (one refill each color) \$24.00. **HP DESKJET 600/660** (HP 51629A) Black three pack \$19.00. **HP DESKJET 600C/660C** (HP 51649A) Tri-color (5 refills each color) \$24.00. **HP DESKJET 855C/1600C** (HP 51645A) Black three pack \$19.00. **HP DESKJET 855C** (HP 51641A) Tri-color kit (2 refills each color) \$24.00. **HP DESKJET 720, 722, 890, OFFICE JET 1170 & 1175** (C1823A) Tri-color kit (2 refills each color) \$24.00. **HP PAINTJET and PAINTJET XL** (51606A) Black 3-bottle kit \$19.00. **HP PAINTJET and PAINTJET XL** (51606C) Tri-color kit \$24.00. **HP PAINTJET XL300** (C1645A & C1656A) Black 3-refill kit \$19.00. **HP PAINTJET XL300** Tri-color kit (1 refill each color) HP 51639C,M,Y \$24.00. **HP THINKJET, QUIETJET, KODAK DICONIX 150** (51604A or 92261A) black 5 refills \$9.00. **IBM/Lexmark/Execjet/4076** (1380620) black 3-refill kit \$19.00. **IBM/Lexmark Execjet IIC, WinWriter 150 C** (Cart #1380619) 4 refills each color \$24.00. **SNAP AND FILL SYSTEM** - Permits refilling HP 51626A (black for HP 500-series) and HP 51629A (black for HP 600-series) cartridges without making a hole in the cartridge. Consists of special cartridge holder, syringe, plastic tubing, and directions. **STARTER KIT** - with ink for 3 refills \$28.00. **EXTRA INK FOR SNAP & FILL SYSTEM** (black only) 4-oz. bottle \$18.00; 8-oz. bottle \$34.00. Specify whether for HP 51626A or HP 51629A.



## HARD-TO-GET PRINTER RIBBONS

Gorilla Banana, Commodore 1525 \$8.00; Adam Coleco \$12.00; TI-850/855 \$6.00; Centronics 700 Zip Pack \$5.00; C. Itosh Prowriter Jr., Riteman C+/F+ \$6.00; Riteman Informer \$8.00; Commodore MPS-801 \$5.00; MPS-803 \$7.00; Decwriter LA30/36 \$4.00; Apple Scribe \$4.00; Mannisman Tally Spirit 80, Commodore 1526 \$5.00; Epson JX-80 4-Color \$14.00. Printronix P-1013 \$11.00; Star SJ144 color 3-pack \$29.00.

ALSO HEAT & TRANSFER RIBBONS AND PAPER FOR PRINTING T-SHIRTS.

Over 300 different ribbons in stock. All ribbons new, not re-inked. Fully guaranteed. Order directly or send SASE for complete list.

Add \$4.00 per order shipping. California residents add 7.75% sales tax. On ribbon orders over \$50.00 deduct 10% discount.

## H.T. ORR Computer Supplies

249 Juanita Way, Placentia, CA 92870-2216

714-528-9822 • 800-377-2023 • FAX 714-993-6216

<http://www.extremepay.com/occomp/orr.htm>

Write in 111 on Reader Service Card.

**NEED LARGE**, precision wound coils for vehicle detectors, alarms, loop antennas, proximity detectors, metal locators, direction finders, security gates or other projects? We also sell tubes and AM radio signal boosters which improve reception. Send \$2 for details (refundable with purchase). Fala Electronics-V, POB 1376, Milwaukee, WI 53201.

**200+ ELECTRONICS PROJECTS.** Build for pleasure or make 100% (or more) profits reselling printed plans. \$1 (refundable) for catalog & dealer info. MATCO-A5, PO Box 509, ROSEVILLE, MI 48066-0509.

**BUILD THE MENDOCINO MOTOR.** This fascinating device is a solar powered, magnetically levitated motor. It will delight and amaze you and your friends. The 27 page plans book includes a list of parts suppliers. The motor uses readily available parts. Plans are \$15 plus \$2.50 S&H. Write to: St. Elmo's Fire, PO Box 141, Stow, MA 01775. E-Mail: tcv@genrad.com

**AWESOME KITS:** voice changers, levitators, lasers, solar robots, and more! Catalog \$1. LNS Technologies, PO Box 67243, Scotts Valley, CA 95067. [www.techkits.com](http://www.techkits.com)

**VOICE CHANGER:** PCB with all board mounted components plus speaker. (Watch for our N&V article.) New price \$9.95 postpaid in US. MicroMethods, PO Box 909, Warrenton, OR 97146. 503-861-1765 jdennon@seasurf.com

**THERMAL ELECTRIC** generator. Electricity from your woodstove, or any heat source. Smallest working model gives 12 amperes/day/12V. Information on how to build your own and blueprint for working model, send \$20 CC, CK or money order to: Electronic Service, Box 48, Ambler, AK 99786.

## MISCELLANEOUS ELECTRONICS FOR SALE

**CALL FOR a free electronics catalog** or visit our web site at [www.bgmicro.com](http://www.bgmicro.com) / B.G. Micro, PO Box 280298, Dallas, TX 75228. Order line 1-800-276-2206.

**HIGH QUALITY TOOLS AND STAINLESS STEEL HARDWARE.** European and American screwdrivers, nut-drivers, pliers, hex-keys, balldrivers, and more! Wiha, Bondhus, and Knipex. Stainless cap screws, machine screws, nuts, washers, U-bolts, and eyes. Free catalog. Robert Mink Import-Export, Box 6437V, Fair Haven, NJ 07704. Telephone or fax 732-758-8388. E-Mail: w2tv@csi.com

**NUCLEAR ELECTRONICS** (NIM, CAMAC), PMTs, optics, high vacuum, and high voltage components and equipment. Guaranteed quality at reasonable cost. OE Technologies, Box 703, La Madera, NM 87539. Ph: 505-583-2482, Fax: 505-583-9190, E-Mail: oetech@newmexico.com <http://www.oetech.com>

# SUMMER SPECIALS

## SUPER SAVING UPGRADE KIT

### MOBOARDS WITH CPU, 8MB AGP & SOUND:

K6-2 350 Mhz MMX	\$149
K6-2 380 Mhz MMX	\$189
K6-2 400 Mhz MMX	\$199
K6-2 450 Mhz MMX	\$229
K6-3 400 Mhz MMX	\$285
K6-3 450 Mhz MMX	\$339
Pentium II Celeron 333 w 128Kcache	\$149
Pentium II Celeron 400 w 128Kcache	\$219
Pentium II 350 MMX	\$269
Pentium II 400 450 MMX	\$295 Scall
Pentium III 450 500 MMX	\$375 call

Any other board Please Call

### CASES WITH POWER SUPPLIES

MED TOWER CASE PREMIUM.....	\$29
ATX MED TOWER CASE PREMI.....	\$49

### FLOPPY

1.44 Mitsumi.....	\$ 18.95
-------------------	----------

### MONITORS

14" 28 108 N-I, Low Radiation.....	\$119
15" 28 1024x768 N-I, Low Rad.....	\$135
17" 28 1280x1024 N-I, Low Rad.....	\$229

### KEYBOARDS

104 Keyboard.....	\$10
Keytronic.....	\$19
Focus 2000.....	Scall

### VGA CARDS

SVGA 1MB ISA.....	\$35
PCI 1MB/2MB/4MB.....	\$14/22/29
PCI OR AGP 4MB.....	\$29
PCI OR AGP VGA 8MB.....	\$39
BANSHI 16MB.....	\$119
VOODO III 12MB.....	Scall
ANY OTHER VGA CARDS.....	SCALL

### CONTROLLER SCSI

DIAMOND FIRE PORT 40.....	\$95
Adaptec 2940/2940UW/2940UZW.....	\$149/189/call

### MODEM FAX MODEM

33.6K Voice Modem/ Fax Modem.....	\$26
56K Voice Modem/ Fax Modem.....	\$29
US ROBOTIC 56K Modem.....	V90.....\$79
ISDN.....	SCALL

**BISME COMPUTERS OUTLET** 906 N Carpenter Rd. Suite A. Modesto, CA 95351



## 48X CDROM..\$49

### Orders & Price

Tel: (800) 899 6430

### 44X Bundle

**\$79**

48X Speed CD  
16 Bit Sound Card  
with Wavetable.

Amplified Speakers 80W

For ALL kinds of Drives, Sound Cards  
Speakers and CD Titles: \$Call

## HARD DRIVES SPECIALS

4.3GB..\$99	6.4GB..\$109	8.4GB..\$129	10GB..\$145
13.5GB..\$174	18GB..\$289	21GB..\$355	any other CAL

### IBM 6X86 300MMX

Motherboard  
CPU, 8MB AGP  
VGA & SOUND  
**\$129**

### Simm Memory LOW \$\$\$

Will beat any price  
Resellers  
Dealers  
Welcome

### AMD K6-2 350 MMX

Motherboard  
CPU, 8MB AGP  
VGA & SOUND  
**\$159**

All Systems carry  
3 years Parts &  
5 years Labor  
Warranty.  
Lifetime Tech  
Support

### CREDIT CARDS OK

us out  
No Minimum Charge. No Hidden Charge.  
Prices subject to change without notice.  
15% Restocking fee for Non Defective Items.  
Orders of \$950 or more, ground shipping free,  
except for Cases, Monitors, Keyboards and F.Drives.

## EVERYDAY LOW PRICES

**www.bisme.com**

Write in 112 on Reader Service Card.



**SOLAR-POWERED FAN HAT.** Baseball type hat with solar powered fan. Great for sports fans, golfers, etc. Available in red or blue. \$19 plus \$2.00 shipping. CA residents add 7.75% sales tax. Visa/MC/Disc/Amex OK. H.T. Orr Computer Supplies, 249 Juanita Way, Placentia, CA 92670. 714-528-9822, 1-800-377-2023, FAX 714-993-6216.

**ELECTRONIC PARTS: LOW, LOW PRICES!** Phone, fax, E-Mail for free flyer. Hoffman Industries, 853 Dundee Ave., Elgin, IL 60120. Ph: 847-622-8201, Fax: 847-622-8202, E-Mail: hoffind@aol.com Web site <http://hoffind.com>

**FREE FLYER** on DBS, cable TV, phones, credit cards, schematics, health items. Bill 1-800-879-9657.

**SOLDERING STATIONS:** Weller EC2002M-1 new, \$175 or \$150 for five or more. John 404-363-9602.

**FOR SALE:** Induction heater MFD by Honeywell, used to solder glass to metal such as panel meters and misc. antenna terminations, self-contained one cabinet 110V AC power supply, \$750. Antac, 310-478-3561, fax: 310-826-4058.



**ANAHEIM WIRE PRODUCTS. DISTRIBUTOR OF ELECTRICAL WIRE AND CABLE** since 1973. Items available from our stock: Hook up wire, Automotive primary wire, GXL, SXL, Plenum cable, Teflon wire, Multi-conductor cable, Irradiated PVC, SO-CORD, Mil-Spec wire, Building wire, Welding cable, Battery cable, Telephone wire, Shrink tubing, Cable ties, Connectors. Wire cut & strip to specs. If interested, please call 1-800-626-7540, FAX: 714-771-5043. Visa/MC/Amex. SEE US ON THE INTERNET: <http://www.anahemwire.com> OR E-Mail: info@anahemwire.com

**HARD-TO-find parts:** Big screen tubes, \$135; TV & VCR tuners, \$20; VCR RF modulators & trays, \$5 & \$10; ICs, \$10, radio & TV tubes. Call 912-272-6561, Scarborough TV, 1422 Old River Rd., East Dublin, GA 31027.

**PC CABLES:** <http://www.pccables.com> connectors, RS232, IDC, SVHS, ribbon cable, DB9, DB15, loopback, null modem, jumpers, SCSI, screws, rails. Secure online catalog, ordering, browsing. 954-418-0835.



# AST GLOBAL ELECTRONICS

24529 STATE HWY. 408, CAMBRIDGE SPRINGS, PA 16403  
VOICE 814-398-8080 • 1-888-216-7159 • FAX 814-398-1176

VIEW COMPLETE LISTING AT:  
<http://www.astglobal.com>

IF WE DON'T CARRY IT ... WE'LL FIND IT  
QUICKLY ... AT REASONABLE PRICES.

EIP 545, Microwave Counter 18GHz.....	\$500
EIP 931, Microwave Source, .01-18GHz, Opt. 9320.....	\$4,500
Fluke 845AB, Null Detector/Micro Voltmeter 1uV-1000VDC.....	\$375
Fluke 3330B, Constant Current/Voltage Calibrator.....	\$325
Fluke 5100B, Multifunction Calibrator, Opt. 0305.....	\$2,800
Fluke 5100B, Multifunction Calibrator.....	\$2,700
Fluke 5200A, Programmable AC Calibrator.....	\$1,000
Fluke 5215A, Precision Power Amp.....	\$800
Fluke 6070A, Synthesized RF Signal Generator.....	\$1,400
200KHz-520MHz.....	\$1,400
Fluke 8050A, DMM 4-1/2 Digit w/Battery Pack.....	\$145
Fluke 8050A, DMM 4-1/2 Digit w/Battery Pack.....	\$145
Fluke 8520A, DMM 5-1/2 Digit.....	\$275
Fluke 9010A, Micro System Troubleshooter.....	\$375
General Radio 1658, Digibridge.....	\$475
Gigatronix 6061A, Synthesized Signal Generator.....	\$2,200
10KHz-1050MHz.....	\$2,200
HP 141T, Spectrum Analyzer Mainframe.....	\$475
HP 141T, Spectrum Analyzer w/8552A/8553B, 1KHz-110MHz.....	\$1,000
HP 141T, Spectrum Analyzer w/8552B/8553B, 1KHz-110MHz.....	\$1,200
HP 141T, Spectrum Analyzer w/8552B/8556A, 20Hz-300KHz.....	\$1,100
HP 141T, Spectrum Analyzer w/8552B/8554B, 1KHz-1.2GHz.....	\$1,700
HP 141T, Spectrum Analyzer w/8552B/8555A, 10MHz-18GHz.....	\$1,900
HP 214A, Pulse Generator, 0.5V-100V.....	\$200
HP 334A, Distortion Analyzer.....	\$275
HP 339A, Distortion Analyzer w/Low Distortion Oscillator.....	\$950
HP 400EL, AC Voltmeter, 10Hz-10MHz.....	\$150
HP 400FL, RMS Voltmeter, 20Hz-4MHz, 100uV-300V.....	\$175

TURN IDLE TEST EQUIPMENT  
— INTO CASH —  
CALL OR FAX FOR QUOTATION

HP 415E, SWR Meter.....	\$100
HP 432A, Power Meter w/Cable/8478, .01-18GHz Sensor.....	\$350
HP 436A, Power Meter w/841H Sensor/Cable.....	\$1,200
HP 436A, Power Meter, Opt. 002/009/022 w/8451H Sensor/Cable.....	\$1,400
HP 651B, Test Oscillator, 10Hz-10MHz.....	\$125
HP 652B, Test Oscillator, 10Hz-10MHz.....	\$125
HP 654A, Oscillator, 10Hz-10MHz, 90dB Attenuator.....	\$195
HP 1630G, Logic Analyzer w/pdps.....	\$550
HP 1630G, Logic Analyzer w/pdps.....	\$650
HP 3312A, Function Generator, .1Hz-13MHz.....	\$490
HP 3314A, Function Generator, Opt. 001.....	\$1,500
HP 3325A, Programmable Frequency Synthesizer 1Hz-32MHz.....	\$850
HP 3330B, Automatic Synthesizer, 20Hz-13MHz.....	\$295
HP 3400A, True RMS Voltmeter, 10Hz-10MHz, 1mV-300V.....	\$125
HP 3406A, RF Voltmeter, 50uV-3V, 1.2GHz.....	\$200
HP 3455A, DMM 5-1/2 Digit.....	\$250
HP 3456A, DMM 6-1/2 Digit.....	\$525
HP 3468A, DMM 4-1/2 Digit, AC/Battery, 5 Function.....	\$175
HP 3488A, Switch Control.....	\$450
HP 3551A, Portable Transmission Test Set.....	\$550
HP 3575A, Digital Phase Gain Meter 1Hz-13MHz.....	\$500
HP 3580A, Spectrum Analyzer, 5Hz-50KHz, LED Readout.....	\$850
HP 3580A, Spectrum Analyzer, 5Hz-500KHz, Mechanical.....	\$500
HP 3582A, Spectrum Analyzer, 0.2-25.5KHz.....	\$1,800
HP 3585A, Spectrum Analyzer, 20Hz-40MHz.....	\$3,900
HP 3702B, IF/BF Receiver w/3705 DIF, Phase Detector.....	\$475
HP 3770A, Amplitude/Delay Distortion Analyzer.....	\$300
HP 3779B, Primary MPX Analyzer.....	\$500
HP 3781B, Pattern Generator.....	\$250
HP 4275A, LCZ Meter.....	\$2,400
HP 5314A, Counter, 100MHz, Opt. 002, w/Manual, Nicol.....	\$175
HP 5314A, Counter, 100MHz, Opt. 001 (icco), Nicol.....	\$175
HP 5315B, Counter, 100MHz, Opt. 001, w/Manual, Nicol.....	\$275
HP 5315B, Counter, 1GHz, Opt. 001/003, w/Manual.....	\$425
HP 5316A, Counter, 100MHz, HP1B.....	\$350
HP 5328A, Counter, 100MHz w/DVM Opt. 021.....	\$200
HP 5328A, Counter, 500MHz.....	\$250
HP 5334A, Counter, 100MHz, Opt. 010 Oven.....	\$500
HP 5340A, Counter, 18GHz (nicie).....	\$600
HP 5345A, Counter, 500MHz.....	\$450
HP 5345A, Counter, 500MHz, HP1B.....	\$650
HP 5411D, Color Scope, 500MHz, Logic Triggering.....	\$2,800
(1GIGASAMPLE/SEC) Digitizing.....	\$2,800
HP 54800A, Scope, 100MHz, Digital Storage w/54657A.....	\$1,400
HP 6101A, Power Supply, 0-20V @ 1A.....	\$125
HP 6104A, Power Supply, 0-20, 20-40V @ 2A, 1A.....	\$150
HP 6112A, Power Supply, 40V @ .5A (metered).....	\$150
HP 6116A, Power Supply, 0-100V @ 200MA.....	\$150
HP 6202B, Power Supply, 40V @ .75A (metered).....	\$150
HP 6203B, Power Supply, 7.5V @ 3A (metered).....	\$150
HP 6205B, Power Supply (dual), 0-40V @ 3A, 0-20V @ 8A (metered).....	\$175
HP 6208B, Power Supply, 0-60V @ 1A (metered).....	\$200
HP 6212A, Power Supply, CV/CCL, 0-100V @ 100MA.....	\$125
HP 6213A, Power Supply, CV/CCL, 0-10V @ 1A.....	\$75
HP 6217A, Power Supply, CV/CCL, 0-50V @ 200MA.....	\$100
HP 6218A, Power Supply, CV/CCL, 0-50V @ 200MA.....	\$125
HP 6227B, Dual Tracking PS 0-25V @ 2A.....	\$375
HP 6260B, Power Supply, 10V @ 100A (metered).....	\$300
HP 6264B, Power Supply, 0-20V @ 20A.....	\$225
HP 6265B, Power Supply, 40V @ 3A (metered).....	\$200
HP 6266A, Power Supply, 40V @ 3A (metered).....	\$200
HP 6268B, Power Supply, 0-40V @ 5A.....	\$275
HP 6289A, Power Supply, 0-40V @ 1.5A (metered).....	\$175

HP 6294A, Power Supply, 0-60V @ 1A (metered).....	\$275
New in box w/manual.....	\$275
HP 8011A, Pulse Generator, 1Hz-20MHz.....	\$175
HP 8013B, Pulse Generator, 1Hz-50MHz.....	\$275
HP 8015A, Pulse Generator, 1Hz-50MHz 30V.....	\$400
HP 8091A, Rate Generator (1GHz) w/8092A Delay Generator (1GHz) w/8093A Output Amp w/15401A & 15400A.....	\$1,000
HP 8160A, Programmable Pulse Generator, 50MHz, Opt. 001.....	\$850
HP 8160A, Programmable Pulse Generator, 50MHz, Opt. 001/020.....	\$1,000
HP 8165A, Programmable Sig Source, 1mHz-50MHz.....	\$950
HP 8443A, Tracking Generator, 1KHz-110MHz.....	\$275
HP 8445B, Auto Preset, 1.8-18GHz.....	\$275
HP 8445B, Auto Preset, 1.8-18GHz Opt. 002/003.....	\$375
HP 8601A, Sweeper Generator, 1-110MHz.....	\$400
HP 8614A, Signal Generator, 800-2400MHz, AM/FM Levelled.....	\$300
HP 8616A, Signal Generator UHF, 1.8-4.5GHz, +10-120dB, AM/FM.....	\$300
HP 8620C, Frame w/8622B Sweeper .01-2.4GHz.....	\$1,150
HP 8624D, RF Plug-in, 5.9-9.0GHz.....	\$225
HP 8640B, Signal Generator, 5-1050MHz, Opt. 002/001 or 003.....	\$1,800
HP 8640B, Signal Generator, 5-512MHz, Opt. 001 or 003.....	\$700
HP 8656A, Synthesized Signal Generator, 100KHz-990MHz.....	\$1,400
HP 8743A, Reflection Test Set, 2-12.4GHz.....	\$200
HP 8901A, Modulation Analyzer Opt. 010.....	\$875
HP 5303A, D/A Converter.....	\$125
Kepco ATE15-50M, Power Supply, 0-15V @ 50A (metered).....	\$500
Kepco JQE 36-15MVPT, Power Supply, 0-36 @ 15A (metered).....	\$275
Kepco JQE 36-3MVPT, Power Supply, 0-36 @ 3A (metered).....	\$175
Krohn-Hite 3202R, Dual Channel Tunable Filter, 20Hz-2MHz, High Pass, Low Pass Band Reject.....	\$200
National Instruments GPIB-100A, Bus Extender.....	\$175
PG506A, Calibration Generator Plug-in.....	\$500
Power Designs 2K-10 HV PS 1-2000V @ 10MA.....	\$375
Racal Dana 1991, Counter/Timer, 2 Channel.....	\$275
Racal Dana 1992, Counter/Timer, 1GHz.....	\$375
Rockland 1022F, Dual HiLo Filter.....	\$125
Rockland 5100, Synthesizer, DC-2MHz, 201 Hz Resolution.....	\$325
Sencore CM2000, Computer Analyzer.....	SPECIAL \$1,400
Sencore LC102, Capacitor/Inductor Analyzer.....	\$950
Sencore SC61, Scope (100MHz) w/New Probes, Dual Trace.....	\$750
Sencore SC61, Scope (100MHz) w/p Probes, Dual Trace.....	\$400
Sencore TVA92, TV Video Analyzer.....	\$1,100
Sencore VG91, Universal Video Generator.....	\$1,200
Sorenson DCR-60-5A, Power Supply, 80V @ 5A (metered).....	\$375
Tek 7514, Plug-in Sampling Plug-in, DC-1GHz.....	\$425
Tek AM501, Plug-in Op Amp.....	\$175
Tek AM502, Plug-in Differential Amp.....	\$225
Tek DC503, Plug-in Counter Universal, 100MHz.....	\$150
Tek DC509, Plug-in Counter, 135MHz, UNUSED.....	\$375
Tek DM502, Plug-in DMM.....	\$125
Tek DM502A, Plug-in DMM.....	\$125
Tek DM502, Plug-in DMM, 4-1/2 Digit.....	\$150
Tek FGS04, Plug-in Function Generator, .001-40MHz.....	\$375
Tek PG501, Plug-in Pulse Generator, 5Hz-50MHz.....	\$175
Tek PS501-1, Plug-in Power Supply.....	\$150
Tek PS503A, Plug-in Power Supply Triple.....	\$175
Tek OIG-502, Plug-in Optical Impulse Generator (unused).....	\$500
Tek T922, Scope (15MHz), Dual Trace, nice.....	\$175
Tek TMS03, Power Module, 3 Slot.....	\$125
Tek TMS04, Power Module, 4 Slot.....	\$150
Tek TMS06, Power Module, 6 Slot.....	\$200
Tek TR503, Plug-in Tracking Generator, 100KHz-1.8GHz.....	\$575
Tek 2213, Scope (60MHz), Dual Trace.....	\$375
Tek 2215, Scope (60MHz) Dual Trace.....	\$450
Tek 2230, Scope (100MHz) Digital Storage.....	SPECIAL \$1,600
Tek 2235, Scope (100MHz) Dual Trace.....	\$650
Tek 2236, Scope (100MHz) w/Counter/Timer/DMM.....	\$850
Tek 2246, Scope (100MHz) 4-Channel Cursor RO.....	SPECIAL \$1,200
Tek 2247A, Scope (100MHz) Dual Trace w/Counter/Timer/Volmeter.....	SPECIAL \$1,400
Tek 2336, Scope (100MHz) Dual Trace.....	SPECIAL \$525
Tek 2445, Scope (150MHz), 4-Channel Cursor Readout.....	\$1,100
Tek 2445A, Scope (150MHz), 4-Channel Cursor Readout.....	\$1,400
Tek 2465, Scope (300MHz), 4-Channel Cursor Readout.....	\$1,400
Tek 453, Scope (60MHz), Dual Trace.....	\$175
Tek 465, Scope (100MHz), Dual Trace.....	\$425
Tek 465B, Scope (100MHz), Dual Trace.....	\$475
Tek 466, Scope (100MHz storage), Dual Trace.....	\$575
Tek 475, Scope (200MHz), Dual Trace.....	\$475
Tek 475A, Scope (250MHz), Dual Trace.....	\$625
Tek 485, Scope (350MHz), Dual Trace.....	\$700
Tek 520A, NTSC Vectorscope.....	\$400
Tek 576, Curve Tracer.....	\$1,900
Tek 7104, Scope (1GHz), Dual Trace.....	\$1,200
Tek 7104, Scope (1GHz) w/7A29, 7A29, 7B10 & 7B15.....	\$2,200
Tek 7844, Scope (dual beam) w/7A24, 7A26, 7B80 & 7B87.....	\$750
Tek 7904, Scope w/7A24, 7A26, 7B80 & 7B85.....	\$750
Tek 7904A, Scope w/7A24, 7A26, 7B80 & 7B85.....	\$825
Tek 7904A, Scope (500MHz) Frame.....	\$425
Valhalla 2724A, Program. Res. Standard w/Manual.....	\$1,800
Wavelek 145, Pulse/Function Generator, .001-20MHz.....	\$300
Wavelek 157, Programmable Waveform Synthesizer.....	\$425
Wavelek 1855, CATV Sweep/Transmitter.....	\$750
Wavelek 288, Synthesized Function Generator, 20Hz-20MHz (unused).....	\$800
Wavelek 442, Dual HiLo Filter, 1Hz-10KHz.....	\$400

• 60-DAY WARRANTY  
• 10-DAY RIGHT OF RETURN  
• SATISFACTION GUARANTEED

## ELECTRONIC MILITARY SURPLUS



## FAIR RADIO SALES

WEBSITE: [fairradio.com](http://fairradio.com)

E-MAIL: [fairradio@wool.com](mailto:fairradio@wool.com)

PHONE: 419-227-6573

FAX: 419-227-1313

1016 E. Eureka - Box 1105

Lima, OH 45802

VISA, MASTERCARD, DISCOVER

Address Dept. N/V

Write in 114 on Reader Service Card.

**SOLAR ELECTRIC SUPPLIES:** All manner of solar electricity available here. 64 watt panel, \$319. 120 watt panel, \$589. Flexible 5 watt, \$89. Controllers start at \$39.95. Inverters, shunts, racks, mounts, etc., solar roofing shingles. Visit [www.planetarypower.com](http://www.planetarypower.com) 1-877-SOLAR-PA.

## MISCELLANEOUS ELECTRONICS WANTED

**WANTED: BALANCING** machines & vibration analyzing equipment manufactured by the following: Spectral Dynamics, Hofmann, Bentley Nevada, Schenck, IRD Mechanical, Gishott. Contact Mike Park at E.T. Balancing, 12823 Athens Way, Los Angeles, CA 90061. 310-538-9738, FAX: 310-538-8273.

**WANTED: AVIONICS** test equipment, IFR, 600A, 401L, others, Collins, King, Sperry, North Atlantic, Litton INUs LTN series, rate and tilt tables, air data test sets, 941-625-3222 F, 941-625-0494 F, E-Mail: [avionics@afcon.net](mailto:avionics@afcon.net)

**WANTED: GEN-RAD** 1265A DC power supply, 1266A AC power supply, 1633-PI range extension, General Radio experimenter publications, 610-932-4019.

**WANTED: X-BAND** radar equipment. Military, civilian, working or not, parts, TMs, etc. Box 10215, Pittsburgh, PA 15232.

## 30 FT MAST KIT



**AB-1244/GRC MAST KIT**, 12 aluminum alloy on steel sections form sturdy, lightweight 30 ft 1.7" dia mast. Kit includes 5 each lower and upper sections, 1 ea lower and upper adapter sections, gin pole swivel base, 4 ea 36 and 42 ft guy ropes, 4 guy stakes, 2 guy rings plus 2.5 pound sledge hammer. Part of OE-254/GRC antenna set; 30 lb sh. New, \$139.50

**ELECTRON TUBES, JAN-BOXED unused:**  
4CX300A Elmac, \$45 811A Cetron, \$25.00  
4CX5000J Elmac, \$650 1625 Nat. Union, \$4.50  
4D32 Raytheon, \$28 5908A Sylvania, \$9.95  
6B4GA Sylvania, \$17 6336B Cetron, \$30.00  
83 Sylvania, \$9 7360 ECG, \$15.00

Allow money for shipping on merchandise.

SEND FOR OUR  
NEW 1999 CATALOG

**DEC EQUIPMENT WANTED!!!** We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dialog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.



**WANTED: EXCESS ELECTRONIC COMPONENTS, BOARD-LEVEL COMPONENTS: MILITARY COMPONENTS; ICs, MEMORY, TRANSISTORS, DIODES, CAPS, RELAYS, ETC. CALL LA PALMA SEMICONDUCTOR, 714-523-8892 FAX 714-523-8898.**

**HIGHEST PRICES PAID:** I will pay the following prices for Western Electric tubes: 211A/D/E new \$300, used \$175; 212A/D/E new \$750, used \$275; 274A/B (engraved base) new \$250, used \$200; 300B (engraved base) used \$550; 422A new \$50, used \$25; 437A new \$50, used \$25; and many more. Also buying Western Electric, and other audio tube and equipment literature. Call or send us your list. Toll free tel/fax: 1-888-715-8823. Don Singerhouse/Singerhouse Sound, LLC, PO Box 321, New Richmond, WI 54017. E-Mail: [singtube@frontiernet.net](mailto:singtube@frontiernet.net)

## ABC ELECTRONICS 315 7TH AVE N. MPLS. MN. 55401

(612)332-2378 FAX (612)332-8481 E-MAIL: [SURP1@VISI.COM](mailto:SURP1@VISI.COM)

WE BUY TEST EQUIPMENT AND COMPONENTS.

VISIT US ON THE WEB AT [WWW.ABCTEST.COM](http://WWW.ABCTEST.COM)

HP 54501A 100MHZ DIGITIZING SCOPE.....	\$1300.00	HP 4935A TRANS IMPAIRMENT TEST SET.....	\$900.00
HP 54201D 300MHZ DIGITIZING SCOPE.....	\$1000.00	HP 5006A SIGNATURE ANALYZER.....	\$150.00
HP 54201A 300MHZ DIGITIZING SCOPE.....	\$1000.00	HP 86602B 1MHZ-1300MHZ RF PLUG.....	\$400.00
HP 5400A 50MHZ SCOPE/WAVEFORM ANALYZER.....	\$700.00	EIP 575 MICROWAVE COUNTER.....	\$1500.00
HP 3312A 13MHZ FUNCTION GENERATOR.....	\$250.00	FLUKE 95 50MHZ SCOPEMETER.....	\$350.00
HP 5370A 100MHZ U.T.I. COUNTER.....	\$400.00	LECROY 7200 400MHZ O-SCOPE.....	\$1000.00
HP 3386C LEVEL METER.....	\$750.00	TEK 475 200MHZ O-SCOPE.....	\$500.00
HP 4165A POWER METER W/O SENSOR&CABLE.....	\$500.00	TEK 465 100MHZ O-SCOPE.....	\$400.00
HP 8350B SWEEP OSCILLATOR MAINFRAME.....	\$2000.00	TEK 496P 1KHZ-1.8GHZ SPEC. ANALYZER.....	\$3500.00
HP 3437A 3.5DIGIT SYSTEM VOLT METER.....	\$250.00	TEK 1240 LOGIC ANALYZER.....	\$750.00
HP 3455A DIGITAL MULTIMETER.....	\$250.00	TEK TDS320 100MHZ DIGITAL O-SCOPE.....	\$1400.00
HP 3456A DIGITAL MULTIMETER.....	\$400.00	TEK 7140A 500MHZ PROG. O-SCOPE FRAME.....	\$750.00
HP 3336C SYNTHESIZER/LEVEL GENERATOR.....	\$800.00	TEK 7854 400MHZ OSCILLOSCOPE FRAME.....	\$500.00
HP 3325A SYNTHESIZER/FUNCTION GENERATOR.....	\$1000.00	TEK 7904 400MHZ OSCILLOSCOPE FRAME.....	\$250.00
HP 5335A 200MHZ COUNTER.....	\$600.00	TEK 7A26 200MHZ VERTICAL PLUG.....	\$75.00
HP 8165A PROGRAMMABLE SIGNAL SOURCE.....	\$1100.00	TEK 7A24 400MHZ VERTICAL PLUG.....	\$150.00
HP 8558B/181 100K-1.500MHZ SPECTRUM ANALYZER.....	\$1000.00	TEK 7880 400MHZ TIME BASE.....	\$75.00
HP 8559B/183 10MHZ-21GHZ SPECTRUM ANALYZER.....	\$3000.00	TEK 7892A 500MHZ DUAL TIME BASE.....	\$125.00
HP 1740A 100MHZ OSCILLOSCOPE.....	\$250.00	TEK 7512 SAMPLING PLUG.....	\$250.00
HP 6034A 60VDC-10A POWER SUPPLY.....	\$750.00	TEK 7L14 10KHZ-1.8GHZ SPEC. ANALYZER.....	\$1000.00
HP 6269B 40VDC-50A POWER SUPPLY.....	\$800.00	TEK AM503 CURRENT PROBE AMPLIFIER.....	\$250.00
HP 6553A 40VDC-12.5A POWER SUPPLY OPT.J01.....	\$1200.00	WAVETEK 145 20MHZ PULSE/FUNCTION GEN.....	\$400.00
HP 6632A 20VDC-5A POWER SUPPLY.....	\$500.00	WAVETEK 182A 4MHZ FUNCTION GEN.....	\$150.00
HP 6643A 40VDC-4.3A POWER SUPPLY OPT.J03.....	\$750.00	WAVETEK 955 7.5-12.4GHZ MICROSOURCE.....	\$1100.00





**WANTED: TUBE** HiFi/commercial amps, preamps, corner/horn speakers. Altec, Marantz, McIntosh, Western Electric, etc. 405-737-3312 fax 405-737-3355.

**WANTED: TUBES**, radios, transmitters, receivers, gyros, bearings, connectors, relays, lamps, synchros. Hyness Company, 709B Delair Road, Cranbury, NJ 08512-4212. Phone: 609-395-1116, FAX 609-395-1117.

**WANT USED** or surplus DC motor controls or adjustable frequency AC drives, 1/2 HP and up. DC motors fractional to 3 HP. C. Woodruff, 5507 55th Ave. S., Seattle, WA 98118. Voice/Fax 206-723-8487.

**CASH PAID FOR ICs**. Military or commercial integrated circuits, transistors, diodes, any semiconductors. **ELECTRONIC SURPLUS, INC.**, 5363 Broadway, Cleveland, OH 44127. 216-441-8500 or fax 216-441-8503, since 1946. [www.electronicsurplus.com](http://www.electronicsurplus.com)

**WESTERN ELECTRIC** wanted: 1920s-1960s. Amplifiers, mixers, pre-amps, speakers, tubes, etc. **FREE OFFER** 1-800-251-5454.

**WANTED: OLDER** electronics and computer magazines. Popular Electronics, Radio-Electronics, Byte, DDJ, Kilobaud, Creative Computing, Computer Hobbyist, group newsletters, etc. Call Shawn, 650-846-8208, [maxweb@pacbell.net](mailto:maxweb@pacbell.net)

## EDUCATION

**RF OSCILLATOR DESIGN**. Learn to design RF oscillators from a pro. Short course presents the knowhow of oscillator analysis, simulation and design with breadboard experiments. Requires AC/DC and some calculus. \$25 + \$6 S&H or send for free information. **RFLS**, PO Box 9185, Gaithersburg, MD 20898-9185.

## BUSINESS OPPORTUNITIES



**COUNTER-SURVEILLANCE=\$250 HR!** Electronic eavesdropping is unbelievably widespread! Are you sure you're safe? Learn how others (without prior experience) earn \$250 HR in the fascinating field of COUNTER-SURVEILLANCE! For **FREE** catalog call: 1-800-732-5000.

## REPAIRS - SERVICES

**PICS, GALS READ** if you've lost your masters. Programming service available. Call for info. Network Sales, 616-683-0500.

**PLAYSTATION MOD** chips. Works with all models up to 750x. Color instructions. Seven wire hook up, does not come with wires. \$5 each, plus shipping charges. 10% discount for 10 or more. Call 703-764-5118 to place an order.

**2-WAY RADIOS** repaired. Specializing in Motorola portables. Flat rate plus parts. All work guaranteed. FCC licensed 25 years. Fast turnaround. Call Ed at Coral Radio 954-796-9590.

**PC BOARD ASSEMBLY**. Thru hole only. Small or large quantities OK. Call Network Sales. 616-683-0500.

**ENGINEERING CONSULTING**. Product development from conceptual to manufacturing stages. Digital, analog, and RF expertise. Microcontroller designs for HC05xx, HC11xx, and PIC families. Software design for IBM PC. XILINX and Altera FPGA design. In-house schematic capture and PWB. Hicks Electronic Design, PO Box 7366, Loveland, CO 80537-0366. Toll Free 1-888-849-6792 E-Mail: [steve@hicksengineering.com](mailto:steve@hicksengineering.com) website: [www.hicksengineering.com](http://www.hicksengineering.com)

**Sell Nuts & Volts**  
in your store and earn \$\$\$!  
Contact us for details. 909-371-8497  
E-Mail [distributors@nutsvolts.com](mailto:distributors@nutsvolts.com)

**(E)EPROM PROGRAMMING** done quickly and economically. One day turn around typical. Simple copy \$3 per device. Also prototyping, design, and consulting services available. Call or send SASE to: **Luzer Electronics, 4023 North Bayberry, Wichita, KS 67226. 316-687-2127, FAX 316-687-3103.**

**PC BOARDS REPAIRED**. Prices start at \$5. Minimum 5 of one type. Network Sales, 616-683-0500.

**WELD ALUMINUM WITH PROPANE!** EZ, INEXPENSIVE, STRONG. DETAILS: WEEKS, 36 CAROLINA ST., TAYLORS, SC 29687. 1-800-547-WELD(9353) FAX 864-244-6349. <http://www.dura-fix.com>

**PRINTED CIRCUIT** design by professional with 30+ years: conventional, multilayer, downhole, fine line. Prototype and production fabrication. Reverse engineer existing 2-layer board. [www.circuit-applied-tech.com](http://www.circuit-applied-tech.com) call toll free 877-236-3223.

**CABLE CONVERTER REPAIR**: Quality repair service for all name brands. If you're tired of the runaround you're getting from the company you purchased it from, or they're out of business. Give us a call for fast and courteous service. Have model and problem ready. Sorry no box, chip, or IL repairs. **Highview Engineering 815-245-3735** or E-Mail: [HIGHENG1@AOL.COM](mailto:HIGHENG1@AOL.COM) ask for George.

47pc•kit

\$12.95

MK101  
**SWEETHEART**

Give him or her that special heartbeat. 28 leds form 2 blinking hearts. Power supply : 9V battery




14pc•kit

\$5.95

MK102  
**FLASHING LEDS**

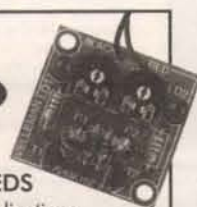For different applications (such as model construction) and educational purposes. Adjustable flashing speed. Power supply : 9V battery



30pc•kit

\$14.95

MK104  
**ELECTRONIC CRICKET**

This cricket turns on when it gets dark. Great as practical joke. The tone and repetition between two crickets is adjustable. Power supply : 9V battery



34pc•kit

\$9.95

MK103  
**LED SOUND-TO-LIGHT UNIT**

For different funny and practical applications. 4 high-intensity leds light up and react simultaneously on every sound. Power supply : 9V battery



36pc•kit

\$10.95

MK105  
**SIGNAL GENERATOR**

Several signal outputs: square wave, triangle, sine and integrator which are selectable with a jumper. The signal frequency is about 1KHz (fixed) Ideal to learn electronics. Power supply : 9V battery



26pc•kit

\$14.95

MK106  
**METRONOME**

The beats per minute are given by a built-in speaker and by a led. Adjustable volume, beats/sound. With on/off switch. Power supply : 9V battery



36pc•kit

\$12.95

MK107  
**LED RUNNING LIGHT**

8 leds running light. Different running effects are selectable (by prog push button). Adjustable effect speed. Power supply stand-by by push button. Power supply : 9V battery




8pc•kit

\$7.95

MK108  
**WATER ALARM**

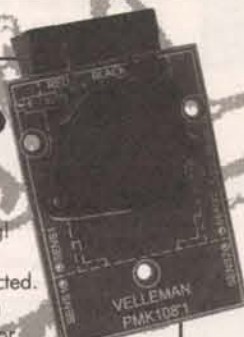Never let you surprise by flooding! Gives alarm sound when water is detected. Incorporated alarm buzzer. Water sensor can be placed at distance by cutting the board and using wires to connect the sensor. Power supply : 9V battery



35pc•kit

\$9.95

MK109  
**ELECTRONIC DIE**

No more cheating allowed! The eyes of the die are leds. Rolls out when the push button is released. Power supply : 9V battery




17pc•kit

\$12.95

MK110  
**SIMPLE ONE CHANNEL LIGHT ORGAN**

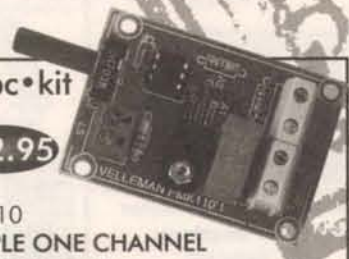With loudspeaker input. The lamp flashes on the beat of the music. Optical isolated loudspeaker input with adjustable sensitivity : 2W to 60W. Maximum load : 120W at 120Vac.



17pc•kit

\$19.95

K5300  
**STROBOSCOPE**

Adjustable flash frequency : 5-15Hz. Power supply : 120Vac. Power consumption : 13W max.



21pc•kit

\$12.49

K2637  
**SUPERMINI 2.5W AUDIO POWER AMPLIFIER**

Superb audio amplifier with incredible tiny dimensions. Integrated circuit has a pre- and power amplifier which can be used separately. Max. output power : 2.5W @ 4ohm. Frequency characteristics : 60Hz to 15KHz. Power supply : 4.5V to 15Vdc / 400mA.



Exists also as module : M2637 \$17.49

# velleman

7415 Whitehall Street Suite 119  
Fort Worth, TX 76118  
(817) 284-7785 F : (817) 284-7712  
[www.velleman.be](http://www.velleman.be) email : [velleman@earthlink.net](mailto:velleman@earthlink.net)

Questions ? Contact us for a list of US distributors or to get your **FREE** catalogue



CALL TOLL FREE

(800) 292-7711

Orders Only

Se Habla Español

# C&S SALES

Excellence in Service

CALL OR WRITE

FOR OUR

FREE

64 PAGE CATALOG!

(800) 445-3201

## Digital Multimeters

### Elenco Model M-1740



**\$39.95**

- 11 Functions:**
- Freq. to 20MHz
  - Cap. to 20µF
  - AC/DC Voltage
  - AC/DC Current
  - Beeper
  - Diode Test
  - Transistor Test
  - Meets UL-1244 safety specs.
- Model M-2760 - \$24.95 (9 functions)

### Elenco Model LCR-1810



**\$99.95**

- Capacitance .1pF to 20µF
- Inductance 1µH to 20H
- Resistance .01Ω to 2000MΩ
- Temperature -20°C to 750°C
- DC Volts 0 - 20V
- Frequency up to 15MHz
- Diode/Audible Continuity Test
- Signal Output Function
- 3 1/2 Digit Display

### Fluke 87III



**\$299**

Features high performance AC/DC voltage and current measurement, frequency, duty cycle, resistance, conductance, and capacitance measurement.

Series II (limited qty.)  
**\$289**

## Generators and Counters

### Elenco Sweep Function Generator with built-in frequency counter Model GF-8036



**\$225**

This sweep function generator with counter is an instrument capable of generating square, triangle, and sine waveforms, and TTL, CMOS pulse over a frequency range from 0.2Hz to 2MHz.

### 20MHz Sweep / Function Generator with Frequency Counter Model 4040

**\$399**



- 0.2Hz to 20MHz
- AM & FM modulation
- Burst Operation
- External Frequency counter to 30MHz
- Linear and Log sweep

**BK PRECISION**

10MHz Model 4017 **\$309**

5MHz Model 4011 **\$239**

### Elenco Handheld Universal Counter 10Hz - 2.8GHz Model F-2800



**\$99**

- Sensitivity:**
- <1.5mV @ 100MHz
  - <5mV @ 250MHz
  - <5mV @ 10Hz
  - <100mV @ 2.4GHz

Features 10 digit display, 16 segment and RF signal strength bargraph. Includes antenna, NiCad battery, and AC adapter.

### Elenco RF Generator with Counter (100kHz - 150kHz) Model SG-9500



Features internal AM mod. of 1kHz, RF output 100mV - 35MHz. Audio output 1kHz @ 1V RMS. SG-9000 (analog, w/o counter) \$119.95

### B&K Frequency Counter Model BK-1875



1Hz - 2.8GHz  
3 Channels

**\$189**

**Sensitivity:**

- <0.8mV @ 100MHz
- <8mV @ 300MHz
- <7mV @ 1GHz
- <100mV @ 3GHz

Ultra sensitive synchronous detector bargraph and RF strength.

### Elenco 10Hz - 1MHz Digital Audio Generator Model SG-9300



**\$175**

Features built-in 150MHz frequency counter, low distortion and sine/square waves. SG-9200 (w/o counter) \$119.95

## Tekk Radios

### Pro-Sport FRS Two-Way Radio Model PRO-SPORT+

- 14 Channels
- Battery Monitor
- Key Lockout
- Monitor Button
- Lightweight
- Palm Sized
- Large LCD Display
- Removable Belt Clip
- Removable Antenna
- Two Radio Call Tones
- Busy Channel Lockout
- Accessory Connector
- Highly Water Resistant

**\$79 each**  
**or**  
**\$149.95**  
Set of 2

Talk up to 2 miles!



PRO SPORT Model  
**\$109.95 set of 2**

## Miscellaneous

### Elenco Technician Tool Kit Model TK-1500

**\$49.95**

28 tools plus a DMM contained in a large flexible tool case with a handle ideal for everyone on the go.



### Elenco Quad Power Supply Model XP-551

**\$89.95**

4 Fully Regulated DC Power Supplies in One Unit  
4 DC voltages: 3 Fixed - +5V @ 3A, +12V @ 1A, -12V @ 1A  
1 Variable - 2.5 - 20V @ 2A



### Dual-Display LCR Meter w/ Stat Functions B&K Model 578


**\$219.95**



Auto/manual range  
Many features with Q factor  
High Accuracy

## Elenco Oscilloscopes

Free Dust Cover and 2 Probes

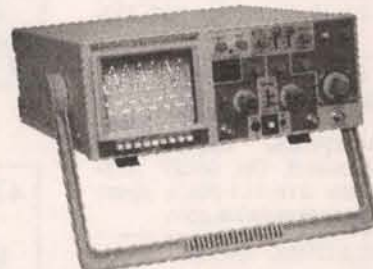


S-1325	25MHz	Dual Trace	\$325
S-1330	25MHz	Delayed Sweep	\$439
S-1340	40MHz	Dual Trace	\$475
S-1345	40MHz	Delayed Sweep	\$569
S-1360	60MHz	Delayed Sweep	\$749
S-1390	100MHz	Delayed Sweep	\$995

### DIGITAL SCOPE SUPER SPECIALS

DS-203	20MHz/10Ms/s	Analog/Digital	\$695
DS-303	40MHz/20Ms/s	Analog/Digital	\$995
DS-603	60MHz/20Ms/s	Analog/Digital	\$1295

## Four Functions in One

### Elenco Model MX-9300

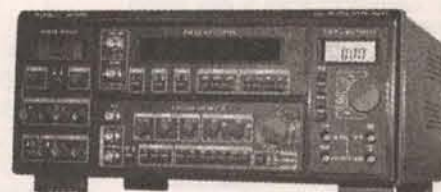

**\$459.95**

### Features:

- One instrument with four test and measuring systems:
- 1.3GHz Frequency Counter
- 2MHz Sweep Function Generator
- Digital Multimeter
- Digital Triple Power Supply - 0-30V @ 3A, 15V @ 1A, 5V @ 2A

## Elenco Educational Kits

### Model AR-2N6K



2 Motor / 6 Motor  
Amateur Radio Kit  
**\$34.95**

### Model AM/FM-108K



Transistor  
Radio Kit  
**\$29.95**



Model AK-700  
Pulse/Tone  
Telephone Kit  
**\$15.95**



Model AK-870  
Radio Control Car Kit  
• Solderless  
• 7 Functions  
• Radio Control  
Included  
**\$24.95**



Model M-1005K  
Digital Multimeter Kit  
• 18 Ranges  
• 3 1/2 Digit LCD  
• Transistor Test  
• Diode Test  
**\$19.95**



Model XP-720K  
Power Supply Kit  
• 1.8VDC - 18VDC @ 1A  
• -1.8VDC - -18VDC  
• 5VDC @ 3A  
• 6.3VAC @ 1A and  
12.6VAC center  
tapped @ 1A  
**\$54.95**



Model XK-150  
Digital / Analog  
Trainer  
**\$89.95**



Model EP-50  
Electronic  
Playground and  
Learning Center  
**\$19.95**

Guaranteed Lowest Prices

UPS SHIPPING: 48 STATES 5%  
OTHERS CALL FOR DETAILS  
IL Residents add 8.25% Sales Tax

SEE US ON THE WEB

# C&S SALES, INC.

150 W. CARPENTER AVENUE

WHEELING, IL 60090

FAX: (847) 541-9904 (847) 541-0710

http://www.cs-sales.com



15 DAY MONEY BACK GUARANTEE

2 YEAR FACTORY WARRANTY

PRICES SUBJECT TO CHANGE WITHOUT NOTICE



# Events CALENDAR

Continued from page 24

E-Mail: n2xyz@sjra.org Web: <http://www.sjra.org>  
**NY - HORSEHEADS** - Hamfest. Chemung County Fairgrounds. 6am-3pm. FCC Exams. Talk-in: 147.96/36, 444.20. ARAST, Dave Lewis, 607-589-7495. E-Mail: info@arast.org  
 hamfest@arast.org or winterfest@arast.org  
**WA - WALLA WALLA** - Hamfest. Walla Walla Valley ARC, Jack Babbitt, Sr. WA5ZAY, 509-525-7003. E-Mail: wa5zay@valint.net

## SEPTEMBER 25-26

**AK - ANCHORAGE** - Hamfest. Anchorage ARC, Rick Marvin KL7YF, 907-277-6741. E-Mail: riment@alaska.net  
**IL - GRAYSLAKE** - Radio Expo '99. Lake County Fairgrounds, Rts. 45 & 120. Sat: 8am-4pm, Sun: 8am-3pm. VEC Testing. Talk-in: 146.16/76 MHz (107.2 Hz PL). Chicago FM Club, Mike Brost WA9FTS, 708-457-0966 (Voice Mail/Fax). Web: <http://www.chicagofmclub.org>  
**NH - LANCASTER** - Hamfest. Lancaster Fairgrounds, Rt. 3 North. 9am. VE Exams. Talk-in: 145.430 & 145.150 & 147.315. Moose Swappers, Russ Boyce N1YZE, 603-922-5514. E-Mail: cusvt@together.net

## SEPTEMBER 26

**CA - SANTA ANA** - Swapmeet. ACP parking lot. Mary Russo 714-558-8813  
**CO - LONGMONT** - Hamfest. Boulder ARC, Randy Cassingham K0RCC, 303-664-5366. E-Mail: arcie@thisistruer.com Web: <http://www.thisistruer.com/barc.html>  
**FL - NEW PORT RICHEY** - Hamfest. Recreational Center. 9am-3:30pm. Talk-in: 145.35 & 147.15. SARC, Mike Whitmore WB8ONY, 727-934-0228  
**MA - FRAMINGHAM** - Hamfest. High School. FARA, Bev N1LOO, 508-626-2012  
**MD - BOWIE** - FARFEST '99. Prince George's Stadium, Rt. 301, 1/4 mi S of Rt. 50. 6am (tail-gate). VE Exams. Talk-in: 147.075 & 146.52. Foundation for Amateur Radio, Al Brown K23AB, 301-490-3188, Mary Morris N4TCI, 703-971-3905. E-Mail: Al Brown@ix.netcom.com E-Mail: amateur.radio@hotmail.com Web: <http://www.amateurradio-far.org>  
**NC - BUTNER** - Hamfest. Falls Lake ARC, Wiley Ayscue N4NCK, E-Mail: n4nck@bellsouth.net <http://www.angelfire.com/nc/n4nck/flarc.html>  
**NY - YONKERS** - Flea Market. Lincoln High School, Kneeland Ave. 9am-3pm. VE Exams. Talk-in: 440.425 PL 156.7, 223.760 PL 67.0, 146.910, 443.350 PL 156.7. Metro 70cm Network, Otto Supliski WB2SLQ, 914-969-1053  
**OH - BEREIA** - Hamfest. Cuyahoga County Fairgrounds. 8am-2pm. VE Exams. Talk-in: 146.73 PL110.9. Hamfest Assn. of Cleveland, Ron Nichols N8LZA, 1-800-CLE-FEST or 216-999-7388. E-Mail: info@hac.org Web: <http://www.hac.org>

## OCTOBER 1999

### OCTOBER 1

**WI - RACINE** - Auction. Racine Megacycle Club, Rob Madison KF9ZT, 414-552-6RMC. E-Mail: w9udu@wi.net Web: <http://www2.wi.net/~hamradio>

### OCTOBER 1-2

**AR - SPRINGDALE** - Hamfest. Northwest AR ARC, Clarence Morrow KC5UEW, 501-631-9231

### OCTOBER 1-2-3

**CA - LONG BEACH** - ARRL Southwestern Division Convention. Nate Brightman K6QSC, 562-427-5123.

### OCTOBER 2

**CA - SANTEE** - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052  
**FL - MAITLAND** - Hamfest. Bahia Shrine AR Unit, Cecil Morehouse K4KEN, 407-281-9169  
**MO - WARRENSBURG** - Hamfest. Warrensburg Area ARC, Keith Haye WE0G, 816-697-3426. E-Mail: we0g@microlink.net  
**NJ - LEONARDO** - Hamfest '99. Croydon Hall, Leonardville Rd. east of Hosford Ave. 8am. VE Exams. Talk-in: 145.485 (-). Middletown Township OEM & Garden State ARA, Mario Sellitti N2PVP, 732-787-7184. E-Mail: gsara@monmouth.com Web: <http://www.monmouth.com/~gsara>  
**NY - SYRACUSE** - Hamfest. Pompey Hills Fire Dept., off Rt. 20. 8am-2pm. Talk-in: 147.90/30. RAGS, Vivian Douglas WA2PUU, 315-469-0590. Web: [www.pagesz.net/~rags](http://www.pagesz.net/~rags)  
**PA - LEWISBURG** - Computer, Amateur Radio & Electronics Show & Flea Market. Silver Moon Antique & Flea Market Show Area. Rt. 15, 2.3 mi N of Rt. 45. 9am-4pm. Talk-in: 147.270 Repeater & 146.52 simplex. Susquehanna Valley ARC, George Machesic 570-286-2086. E-Mail: gpmac@netscape.net, Dave Welker k3si@hotmail.com Web: <http://loveland.dynip.com/svarc>  
**SC - ROCK HILL** - Hamfest & Computer Fair

## OCTOBER 3

**NY - QUEENS** - Hamfest. Hall of Science parking lot, Flushing Meadow Park Corona, 47-01 111th St. 9am-3pm. Talk-in: 444.200 repeat, PL 136.5, 146.52 simplex. Hall of Science ARC, Stephen Greenbaum WB2KDG, 718-898-5599. E-Mail: WB2KDG@Bigfoot.com  
**PA - WRIGHTSTOWN** - Hamfest. Mt. Airy VHF RC, Mark Schreiner NK8Q, 610-847-2285. E-Mail: nk8q@amsat.org Web: <http://www.ij.net/packrats/>

## OCTOBER 8-9

**FL - STARKE** - Hamfest. Bradford County Fairgrounds, US 301 N. Fri: 2pm-8pm, Sat: 8am-4pm. Talk-in: 145.150-. Bradford Area ARC, Walt Terrell 904-755-4964 or Tony Spatafore 904-964-9328. E-Mail: wb2fgl@techcomm.net Web: [www.angelfire.com/fl/arcba/index.html](http://www.angelfire.com/fl/arcba/index.html)  
**NH - ROCHESTER** - Hamfest. Fairgrounds. Hoss Traders, Joe, 207-469-3492

## OCTOBER 8-9-10

**CA - BAKERSFIELD** - Hamfest. Bakersfield ARA, Robert Gerner Jr. KB6JFL, 661-588-7065. E-Mail: w6bar@hotmail.com Web: <http://members.tripod.com/~w6bar/bara.html>

## OCTOBER 8-9-10-11

**CA - SAN DIEGO** - 17th Space Symposium & AMSAT-NA Meeting. Duane Naugle K06BT, 619-273-4088. E-Mail: k06bt@amsat.org Web: <http://www.amsat.org>

## OCTOBER 9

**CA - FONTANA** - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves  
**GA - AUGUSTA** - Hamfest. ARC of Augusta, Terry Brown KE4MHN, 706-796-1128. E-Mail: cookie4u@cheerful.com Henry Arostegui KN4AV, 706-793-1625. E-Mail: kn4av@bellsouth.net Web: <http://www.gabn.net/kd4ahqweather/arc.html>  
**WA - BREMERSTON** - Hamfest. President's Hall, Kitsap County Fairgrounds. License Exams 10am. Talk-in: WW7RA repeater 146.620, tone 103.5, simplex 146.520. North Kitsap ARC, Marcie Stilwell, 360-697-2797. E-Mail: nkarc@yahoo.com

## OCTOBER 9-10

**FL - TAMPA** - Hamfest. 4050 Dana Shore Dr. Sat & Sun 9am-3pm. Egypt Temple ARA, George Dixon 813-933-4350; Len Smith 813-684-4408; Larry Padgett 813-948-6500. E-Mail: kf4iti@ij.net  
**TN - MEMPHIS** - Memfest '99.


## OCTOBER 10

**CT - WALLINGFORD** - Connecticut State ARRL Convention. Mountaintop Special Event Facility, High Hill Rd. 9am-3pm. Nutmeg CT Conv. Nutmeg Hamfest Alliance, Gordon Barker K1BIY, 860-342-3258 E-Mail: k1biy@junio.com. E-Mail: nutmeghamfest@qsl.net Web: <http://www.qsl.net/nutmeghamfest>  
**MD - WEST FRIENDSHIP** - CARA Hamfest. Howard County Fairgrounds, S of I-70, E of Rt. 32. 8am-3:30pm. VE Exams. Talk-in: 147.135 (-) repeater, 146.52 simplex. CARA, 410-796-2587. Web: <http://www.ocbs-nl-server.umaryland.edu/cara/hamfest.htm>

## Turn Your Multimedia PC into a Powerful Real-Time Audio Spectrum Analyzer
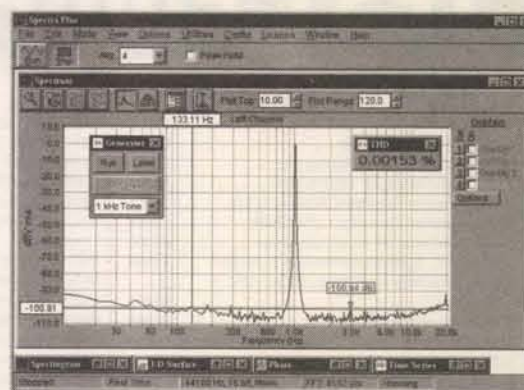
### Features

- 20 kHz real-time bandwidth
- Fast 32 bit executable
- Dual channel analysis
- High Resolution FFT
- Octave Analysis
- THD, THD+N, SNR measurements
- Signal Generation
- Triggering, Decimation
- Transfer Functions, Coherence
- Time Series, Spectrum Phase, and 3-D Surface plots
- Real-Time Recording and Post-Processing modes



### Applications

- Distortion Analysis
- Frequency Response Testing
- Vibration Measurements
- Acoustic Research

### System Requirements

- 486 CPU or greater
- 8 MB RAM minimum
- Win. 95, NT, or Win. 3.1 + Win.32s
- Mouse and Math coprocessor
- 16 bit sound card

**PHS** Pioneer Hill Software  
 24460 Mason Rd.  
 Poulsbo, WA 98370  
 a subsidiary of Sound Technology, Inc.

Sales: (360) 697-3472

Fax: (360) 697-7717

e-mail: pioneer@telebyte.com

**Priced from \$299**

(U.S. sales only - not for export/resale)

**DOWNLOAD FREE 30 DAY TRIAL!**

[www.spectraplus.com](http://www.spectraplus.com)

**Spectra Plus**  
 FFT Spectral Analysis System

Write in 88 on Reader Service Card.

**MI - MASON** - Hamfest. Central MI ARC & Lansing Civil Defense Repeater Assn., Don Tillison WB8NUS, 517-321-2004. Web: <http://www.qsl.net/cmrc/hamfair.html>  
**NC - MAYSVILLE** - Hamfest.  
**OH - LIMA** - Hamfest. Northwest OH ARC, Greg Schwark N8WBD, 419-647-6321. E-Mail: gas1950@aol.com

## OCTOBER 15-16

**MS - BILOXI** - Hamfest. MS Coast ARA, Wayne Miller KB5AAJ, 228-539-9929. E-Mail: kb5aau@worldnet.att.net Web: <http://www.ametro.net/mcara>

## OCTOBER 15-16-17

**CA - CONCORD** - Hamfest. Mt. Diablo ARC, Dick

Brown KT6X, 925-676-9048. E-Mail: paccon99@pacbell.net

## OCTOBER 16


**CA - SANTEE** - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052  
**IL - GODFREY** - Hamfest. Lewis & Clark RC, Harold Elmore N9HE, 618-466-1909. E-Mail: helmore@piasanet.com Web: <http://www.ezl.com/~lmiller/lcrrc.html>  
**MT - BOZEMAN** - Hamfest. Gallatin Ham Radio Club, Laura Marino Lubner KJ7UN, 406-586-6659. E-Mail: ghrc@bigfoot.com Web: <http://ghrc.webjump.com>  
**TN - GRAY** - Hamfest. Appalachian Fairgrounds, off I-181. Kingsport, Bristol, and Johnson City

## ADDRESSABLE STEPPER MOTOR CONTROLLER

The PARAMAX stepper motor controller is a PC parallel port based addressable controller capable of simultaneous operation of 4 uni-polar stepper motors ranging in voltages from 5 to 12 volts at up to 2 amps per phase. The PARAMAX stepper motor controller includes 8 digital inputs with a data through put rate of 500k bytes per second. Using the unique PARAMAX addressing method, up to 256 controllers can simultaneously function from a single parallel port. The programming package includes libraries that allow you to create applications both under Windows and DOS. Included libraries are: C++, Pascal, Delphi, Basic and utilities for DOS and Windows.

Also available at:  
**FORD ELECTRONICS, INC**  
 (714) 521 - 8080

Part Number: JWP1X-1A  
**\$199.95**

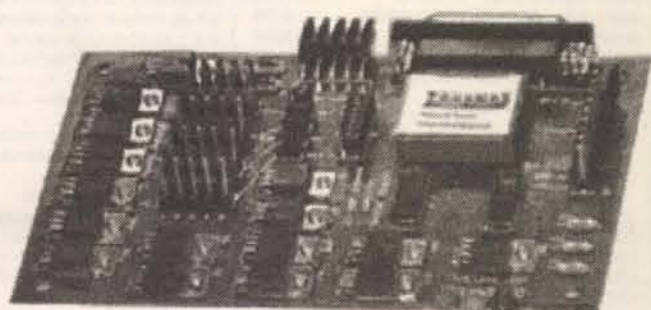

**PARAMAX INC.**  
 (800) 473 - 8080

Come and visit us on the internet at:  
[www.paramax.net](http://www.paramax.net)

Write in 89 on Reader Service Card.

Nuts & Volts Magazine/AUGUST 1999 61



# SURPLUS TEST EQUIPMENT

## HEWLETT PACKARD

11729B, Carrier Noise Test Set	\$3000
11975A, Amplifier, 2-8GHz	\$2000
16500A, Logic Analyzer Mainframe	\$750
214B, Pulse Generator, 10Hz-10MHz	\$1000
3310B, Function Generator, .0005Hz-5MHz	\$350
3312A, Function Generator, 1Hz-13MHz	\$700
3325A, Synthesizer/Function Generator	\$1000
3325A/01/02, Synthesizer/Function Generator	\$1500
3335A, Frequency Synthesizer, 200Hz-81MHz w/Opt. 01	\$4500
339A, Distortion Analyzer	\$1000
3456A, Digital Multimeter, 6.5 Digits	\$800
3478A, Digital Multimeter	\$700
3488A, Switch Control	\$600
3551A, Transmission Test Set	\$600
3575A, Phase Gain Meter 1Hz-13MHz	\$1000
3581C, Selective Voltmeter	\$800
3582A, Spectrum Analyzer, 0.02Hz-25.5KHz	\$1600
3585A, Spectrum Analyzer, 20Hz-40.1MHz	\$5500
4342A, Q-Meter	\$1800
435B, Power Meter	\$500
436A, Power Meter w/Opt. 022	\$1000
4935A, Transmission Impairment Test Set w/Opt. 003	\$1100
5087A, Distribution Amplifier	\$1000
5316B, Universal Counter	\$1000
5328B, Universal Counter	\$1000
5335A, Frequency Counter, Opt. 10/20	\$850
5340A, Frequency Counter w/Opt. 01/02/011	\$1000
5342A, Microwave Frequency Counter, 10Hz-18GHz	\$900
5355A, Frequency Converter	\$1000
5364A, Microwave Mixer Detector	\$4500
54100A, Digitizing Oscilloscope	\$1700
54100D, 1GHz Digital Oscilloscope	\$2700
54110D, 1GHz Color Digitizing Oscilloscope	\$2500
54120A, Digitizing Oscilloscope Mainframe	\$5750
54201D, Digitizing Oscilloscope	\$2650
6011A, Autorange Power Supply, 20V/120A, 1000 Watt	\$1200
6012A, DC Power Supply, 0-60V/0-50A, 1000 Watt	\$1200
6034A, DC Power Supply, 0-60V/0-10A, 200 Watt	\$1000
6274B, DC Power Supply, 0-60V, 0-15A	\$1250
6475C, DC Power Supply, 0-110V, 0-100A	\$3500
6632A, DC Power Supply, 0-20V, 0-5A, 100 Watt	\$1000
777D, Dual Directional Coupler	\$400
8013B, Pulse Generator	\$750
8082A, Dual Pulse Generator, 250MHz	\$1200
8112A, 50MHz Pulse Generator	\$4000
8116A, 50MHz Pulse/Function Generator, Opt. 001	\$4000
8165A/002, Programmable Signal Source w/AM	\$2200
8347A, RF Amplifier, 100KHz-3GHz	\$2500
8349B, Microwave Amplifier, 2-20GHz	\$4000
8350A, Sweep Oscillator Mainframe	\$1000
8350B, Sweep Oscillator Mainframe	\$1500
83522A, Sweeper Plug-in, .01-2.4GHz, w/Opt. 02	\$4000
83540A, RF Plug-in, 2.0-8.4GHz	\$2000
83540A/002, RF Plug-in, 2-8.4GHz	\$2500
83545A, Oscillator Plug-in, 5.9-12.4GHz	\$1750
83590A, Sweep Oscillator Plug-in, 2-20GHz, Rear Output	\$5500
8411A/018, Frequency Converter .11 to 18GHz	\$500
8495H, Programmable Attenuator (unused)	\$600
8501A, Storage Normalizer	\$1000
8505A, Network Analyzer w/8501A & 8503A	\$4000
8510B, Network Analyzer w/Opt. 010	\$13,000
8554B, RF Spectrum Analyzer Plug-in, 500KHz-1250MHz	\$800
8562A, Spectrum Analyzer, 1KHz-22GHz	\$15,000
8566A/B, Spectrum Analyzer, 100Hz-22GHz	\$16,000
86222B, Sweep Oscillator Plug-in, .01-2.4GHz w/Opt. 04, Rear Output and 8620C Mainframe	\$1250
8640A, Signal Generator, 0.5-512MHz	\$700
8640B, Signal Generator, Opt. 002, .5-1024MHz	\$2100
8640B, Signal Generator, Opt. 1, 2	\$2200
8654A, Signal Generator, 10-520MHz	\$450
8656A, Signal Generator, 100KHz-990MHz	\$1700
8656B, Signal Source, .01-2500MHz	\$2500
8660C, Synth. Signal Generator w/Opt. 1 & 100	\$1000
8660D, Synthesized Signal Generator	\$4000
86603A, RF Plug-in, 1-2600MHz	\$800
86603A, RF Plug-in, 1-2600MHz w/Opt. 02	\$950
8662A, Signal Generator, 10KHz-1260MHz w/Opt. 001	\$17,500
8663A, Synthesized Signal Gen., 100KHz-2560MHz w/Opt. 001 & 002	\$30,000
8672A, Synth. Signal Gen., 2.0-18.0GHz	\$4000
8672A, Synth. Signal Gen., 2GHz-18GHz, w/Opt. 08	\$5000
8748A, S-Parameter Test Set w/Opt. 026	\$1350
8756A, Scalar Network Analyzer	\$1500
8757A, Scalar Network Analyzer, 10MHz-60GHz	\$4000
8902A, Measuring Receiver, 150KHz-1300MHz, w/Opt. 02	\$13,500
8970A, Noise Figure Meter	\$4500

## TEKTRONIX

1503, TDR Cable Tester w/Opt. 04 Recorder	\$1550
2215, 60MHz Oscilloscope	\$500
2236, 100MHz Oscilloscope w/Counter/Timer/DMM	\$1000
2246, 100MHz Oscilloscope	\$1600
2247A, 100MHz Oscilloscope w/Counter/Timer/Voltmeter	\$2500
2337, 100MHz Oscilloscope w/DMM	\$1650
2430A, 150MHz Digital Oscilloscope	\$2850
2432A, 300MHz Digital Storage Oscilloscope	\$3000
2445, Four Channel 150MHz Oscilloscope	\$1500
2465, Four Channel 300MHz Oscilloscope	\$2500
2465A DV, Four Channel 350MHz Oscilloscope	\$3850
2467, Four Channel 350MHz Oscilloscope	\$3000
2467B, Four Channel 400MHz Oscilloscope	\$6000
2630, Fourier Analyzer	\$2500
466, 100MHz Storage Oscilloscope w/DM44	\$800
475, 200MHz Oscilloscope	\$850
475A, 250MHz Oscilloscope	\$800
492P, Programmable Spectrum Analyzer, 50KHz-21GHz w/Opt. 1/2/3	\$8000
576, Curve Tracer	\$2750
577/D2, Curve Tracer, Non-storage w/177 Fixture	\$1750
7D20, Programmable Digitizer	\$400
7L5/L3, Spectrum Analyzer, 20Hz-5MHz, w/Opt. 025 Tracking Generator	\$1850
7L12, Spectrum Analyzer, 100KHz-1.8GHz	\$1500

**VISIT OUR WEBPAGE AT  
WWW.RSSURPLUS.COM**

7L18, Spectrum Analyzer Plug-in, 1.5-18GHz Capable of 60GHz with Mixers	\$2500
7S12, TDR/Sampler	\$450
AFG5101, Arbitrary Function Generator	\$1500
CG5001, Programmable Calibration Generator	\$4000
PG506, Calibration Generator Plug-in	\$600
RTD710A, Digitizer w/Opt. 1R (Rackmount)	\$3750
TM5003, Three Slot Power Mainframe	\$450
TM5006, Six Slot Power Mainframe	\$550

## MISCELLANEOUS

Acme Elect. PS2L1000, Electronic Load	\$850
Datron 1061A, 6.5 Digit Autocal Multimeter, DC Only	\$700
Datron 1062, 6.5 Digit Autocal Multimeter, DC/AC/Ohms	\$900
EIP 545A, Microwave Frequency Counter	\$800
EIP 548A, Frequency Counter, 10Hz-26.5GHz	\$2000
EIP 548B, Frequency Counter, 10Hz-26.5GHz	\$3250
EIP 578, Source Locking Frequency Counter	\$2500
Electro-Metric EMC 11 MK IV, Interface Analyzer, 16Hz-50KHz	\$2000
Electro-Metric NTR-51C, Receiver	\$1250
Fuke 5101B/03, Calibrator	\$3000
Fuke 5200A, AC Voltage Calibrator w/5205A Amp	\$1850
Fuke 7261A, Universal Counter/Timer, 0Hz-125MHz	\$350
Fuke 8010A, Digital Multimeter	\$175
Fuke 8012A, Digital Multimeter	\$175
Fuke 8050A, Digital Multimeter	\$250
Fuke 8502A, Digital Multimeter, DC Only	\$225
Fuke 8520A, Digital Multimeter	\$350
Fuke 8600A, Digital Multimeter	\$65
Fuke 8810A, Digital Multimeter	\$250
Fuke 8840A, Digital Voltmeter w/Opt. 059	\$600
Keithley 195A, Digital Multimeter	\$700
LeCroy 9424, 350MHz Oscilloscope	\$3500
Marconi 2019A, Signal Gen., 80KHz-1040MHz	\$2200
Polarad 1105E-FT, Signal Generator, 0.8-2.4GHz	\$400
Sorensen DCS40-25, DC Power Supply, 40V/25A	\$750
Trans. Devices DLR400 15 3500A, Dynamic Load	\$1500
Trans. Devices DLP 50-60-1000A, Electronic Load	\$800
Trans. Devices DLVP 130-110-1000 Electronic Load	\$950
Valhalla 2703, AC Voltage Standard	\$2350
Valhalla 4150ATC, Digital Ohmmeter	\$750
W & G DA-30, Protocol Analyzer	\$3000
Wavetek 22, 11MHz Sweep Generator	\$500
Wavetek 171, 2MHz Synth. Function Generator	\$450
Wavetek 172, Programmable Signal Source w/Opt. 01/02	\$1500
Wavetek 178, Automatic Synthesizer	\$1700
Wavetek 650, Precision 2MHz Variable Phase Synthesizer	\$1550
Wavetek 852, Dual Hi/Lo Filter	\$1000
Wavetek 859, 50MHz Programmable Pulse Gen.	\$800
Wavetek 2001A, Sweep Generator, 1-1400MHz	\$450
Wavetek 3000-200, Signal Generator	\$900
Wavetek 8003, Precision Scalar Analyzer, 10MHz-40GHz	\$2000
Wavetek 8501, Peak Power Meter	\$2000
Wavetek 8502A, Power Meter, 30MHz-40GHz	\$3500
Wiltron 560-7S50, RF Detector, 10MHz-18.5GHz	\$300
Wiltron 560-7S50, RF Detector, 10MHz-26.5GHz, Opt. 2	\$400

## SOLUTIONS TO YOUR CABLING NEEDS

Cat.5 -- Enhanced Cat.5 -- USB -- IEEE1284 / 488 / 1394  
Firewire -- High-End Monitor -- Manual & Auto Switches  
Apple -- Custom Cables -- Premise Wiring -- more!  
HUGE SELECTION OF SCSI CABLES & ADAPTERS

## CUSTOM CABLE ASSEMBLIES MANUFACTURED TO YOUR SPECS

Order Online 24 hrs./day. Reseller & Qty. Discounts Available!  
No minimum order, same day shipping on most orders, A+ and CET technician available to answer your questions.



Northwest Cable & Connector Co.

www.nwcable.com

Phone: (360) 754-3606 Fax: (360) 754-0825

Write in 90 on Reader Service Card.

## Events CALENDAR

Radio Clubs, POB 3682 CRS, Johnson City, TN 37602

**TX - DENTON** - Hamfest. Denton County ARA, Don Mathis KB5YAM, 972-292-1203. E-Mail: dmthsis@lsic.net. Web: http://lsic.net/dhf

### OCTOBER 16-17

**FL - PALM BEACH GARDENS** - Hamfest. AMARA Shrine Temple, 3650 RCA Blvd. Sat: 9am-4pm, Sun: 9am-2pm. Talk-in: 147.165/147.765. Palm Beach Repeater Assn., Ken Summerell KD4CTG, 561-640-9447. E-Mail: sum@flinet.com

### OCTOBER 17

**MA - CAMBRIDGE** - Flea at MIT. Albany and Main Sts. 9am-2pm. Talk-in: 146.52 & 449.725/444.725 W1XMR PL 114.8 (2A). Nick Altenbernd KA1MQX, 617-253-3776 (9-5). Web: http://web.mit.edu/w1mx/www/swapfest.html  
**MI - KALAMAZOO** - Hamfest. County Fairgrounds. Talk-in: 147.040 K8KZO. Kalamazoo ARC & SW MI AR Team, E-Mail: ka8blo@net-link.net  
Web: http://www.qsl.net/ka8blo/hamfest.html  
**OH - ASHLAND** - Hamfest. County Fairgrounds, Claremont Ave. 8am-2pm. Talk-in: 147.105+ 71.9PL. Ashland Area ARC, David Fike N8UCA, 419-289-1082, daytime. Mike Stroub KC8LCH, 419-945-2777, nighttime. E-Mail: aaarc@hotmail.com

**PA - SELLERSVILLE** - Hamfest. NEW Sellersville Fire House, Main St. Bethlehem Pike. 7am-1pm. VE Exams. Talk-in: 145.31 (144.71 input) W3AJ repeater. R. F. Hill ARC, Linda Erdman KA3TJZ, 215-679-5764. Web: http://www.rhill.ampr.org  
**WA - CHEHALIS** - Hamfest. The Southwest Washington Fairgrounds. Talk-in: 147.06+ 110.9 pl, simplex 146.46. Chehalis Valley ARS, Jim Kruger KK7AB, 360-748-1930; KK7AB@ARRL.net or Bill Harwell KC7QHJ, 360-748-8086. E-Mail: bharwell@localaccess.com  
Web: http://www2.localaccess.com/teaser/cvars/

### OCTOBER 23

**LA - LAKE CHARLES** - Hamfest. Southwest LA ARC, Dick Rogers WB5TUG, 318-474-7947. E-Mail: hotred@linknet.net  
**NH - NASHUA** - Hamfest. Res Ctr Church, Antique RC, 617-923-2665

**OR - RICKREALL** - Swap-Toberfest. Polk County Fairgrounds. 9am-3:30pm. Talk-in: 146.86-. Mid-Valley ARES, Bob Boswell, W7LOU 503-623-2513. E-Mail: w7lou@goldcom.com Web: http://www.teleport.com/~n7ljf/swaptober.htm  
**TN - CHATTANOOGA** - Hamfest. C. Jordan in E. Ridge. Chattanooga ARC, David Hoffman KE4FGW, 423-877-7398. E-Mail: w4am@qsl.net Web: http://www.qsl.net/w4am

### OCTOBER 24

**IN - LEBANON** - Hamfest. Boone & Clinton County ARC, Sara Lecklitter KB9OEZ, 765-482-9152.  
**MD - WESTMINSTER** - Mason-Dixon Computer & Hamfest. Carroll County Ag Center. 8am. VE Exams. Talk-in: 145.410 CCAR Repeater. Carroll County ARC, Wayne Wilson N3UN, 410-795-2556 (ph/fax). E-Mail: k3pzn@qis.net. Web: http://www.qis.net/~k3pzn  
**MI - WARREN** - Hamfest. Utica Shelby Emergency Comm. Assn. Debbi Cokewell KB8YYB, 810-263-0227. E-Mail: cuer@juno.com Web: http://www.useca.org  
**NY - LINDENHURST** - Hamfest. Great South Bay ARC, Tom Carrubba KA2D, 516-422-9594. E-Mail: info@gsbarc.org Web: http://www.gsbarc.org  
**PA - GREENSBURG** - Hamfest. 8am-2pm. Talk-in: 147.180+. Foothills ARC, Jim Yex WB3CQA, 724-864-6228. Web: http://www.geocities.com/Heartland/Acres/7896/

### OCTOBER 29-30

**FL - JACKSONVILLE** - Greater Jacksonville Amateur Radio & Computer Show. Morocco Shrine Auditorium, 3800 South St., Johns Bluff Rd. Fri: 1-8pm, Sat: 9am-5pm. VE Exams. Greater Jacksonville Hamfest, Woody Parker KF4GSK, 904-743-3121. E-Mail: sbarber@mediaone.net. Web: http://www.ccse.net/~trich/hamfest98.htm  
**OK - KINGSTON** - Hamfest. Texoma Hamarama, Herb Sleeper WB5PHM, 940-855-5820. E-Mail: retmarine@cst.net  
Web: http://www.qsl.net/kc5sig/hamarama

### OCTOBER 30

**MN - ST. PAUL** - Hamfest. The New RiverCentre. 8am-4pm. VE Exams. Twin City FM Club, Dale Reak KB0VCV, 612-687-9535. Web: http://www.hamfestmn.org

## Lowest Dealer Price Available

	5+	10+	20+
Refurb. Panasonic 145	\$45	\$40	\$35
Regal w/Remote	\$38	\$35	\$30
BC4535 86 Channel	\$30	\$28	\$25
Oak Sigma 99 Channel	\$45	\$40	\$35
75 Channel Converter	\$18	\$18	\$18
Zenith ST1600 w/Remote	\$75	\$70	\$65
Panasonic Converters Model-175 (550MHz)	\$65	\$55	\$45

Six month's warranty on this model only

Call us today to satisfy all your cable equipment needs!


**SAM'S ELECTRONICS**  
**1-405-631-1856**

All Cable Equipment is unmodified.



**R & S Surplus**

1050 E. CYPRESS STREET, COVINA, CA 91724

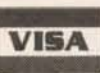

(626) 967-0846 • FAX (626) 967-1999



**MASTER<sup>®</sup> EC-100**  
**ECHOHEAT HEAT GUN**  
 2 Heat Settings:  
 500°F & 1000°F  
 Economical & Lightweight  
 UL Listed  
 120 Volts AC - 1200 Watts  
 Made in China for Master




List Price Your Price  
 \$39.90 \$24.95

Check our LOW prices on all Master  
 Heat Guns & Torches.


Sales tax and shipping charges will be added to all orders. Prices subject to change without notice.  
**1A Sales-560 N. Moorpark Road, Suite 311-Thousand Oaks-CA-91361**  
**888-651-9502, Fax 888-651-9503, www.1asales.com, 1asales@earthlink.net**

Write in 86 on Reader Service Card.

## HEAT SHRINK TUBING

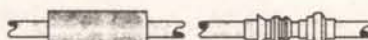

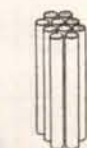Polyolefin 4' Sticks  
 2 to 1 Shrink Ratio  
 @ 250°F  
 Black or Clear  
 Size Per 4' Stick  
 1/16" \$0.55  
 1/8" \$0.62  
 1/4" \$1.02  
 1/2" \$1.39  
 3/4" \$1.79  
 1" \$2.50




# Digital Storage Oscilloscopes
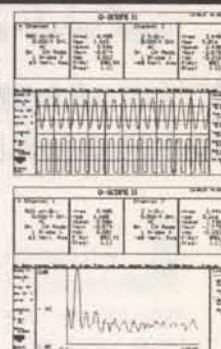
## From \$99.00

ATC modules turn your PC into a full-function DSC, spectrum analyzer, logger, & DVM. Units DC to 50MHz. O-Scope II now in Windows 3.1, 95/98, NT and DOS.

O-Scope Ip \$189.  
 O-Scope II \$349.  
 Specialty probes call.



ATC is a stocking distributor for Pico Technology LTD which offers scope modules to 100MSPS, resolutions from 8 to 16 bit. Pico offers PC based data loggers from 1 to 22 channels, 8 to 16 bit and the Enviromon environmental monitoring system.

Pico products - call

The DFA-5, low cost differential amplifier, cuts through common mode noise problems to reveal low voltage signals. With gains from 1X to 1000X and band widths from 20KHz to 1.2MHz, DFA-5 is the test accessory to help you work with signals from 5 Volts to 5 microVolts. Only \$129.00.

Serial Port Problems???  
 Check out Serial!! Our lowcost serial channel analyzer only \$99.00.

**Allison Technology Corporation**  
 2006 Finney Vallet Rd., TX. 77471 U.S.A.  
**800-980-9806 or 281-239-8500**  
<http://www.atcweb.com> atc@accesscomm.net

### OCTOBER 31

**MO - ST. LOUIS** - Hamfest. St. Louis ARC & Gateway to Ham Radio Club, Steve Welton W80JUN, 314-638-4959. E-Mail: slw@partyline.net  
**OH - MARION** - Hamfest. Marion ARC, Karen Eckard N8KE, 740-499-3565. E-Mail: meeker@gte.net  
**OH - MASSILLON** - Hamfest. Stark County Fairgrounds. Talk-in: 147.18+ & 442.85. Massillon ARC, Don Wade W8DEA, 330-497-7232. E-Mail: marc.hamclub@juno.com

### NOVEMBER 1999

#### NOVEMBER 6

**CA - SANTEE** - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052  
**FL - SORRENTO** - Hamfest. East Lake Chamber of Commerce Bldg. VE Exams. Talk-in: 147.255. Lake ARA, John Wentz W8HFK, 352-728-2615. E-Mail: capias@gate.com Chuck Crittenden KE4EXM, 352-669-2075  
**IN - FORT WAYNE** - Hamfest & State Conv. Allen County War Memorial Coliseum Expo Center. Sat: 9am-4pm, Sun: 9am-3pm. Talk-in: 146.88. ACARTS, 219-484-1314.  
 Web: <http://www.pipeline.com/~dagagnon/>  
**NH - MANCHESTER** - Hamfest. St. John Church. IRS, Paul K1LLX 603-432-1538. E-Mail: K1LLX@juno.com  
**SC - MYRTLE BEACH** - Beachfest '99. Old Myrtle Beach Air Force Base. 7am-2pm. Talk-in: 147.120 +600. Grand Strand ARC, Jim Wood KF4CJE, 843-238-0800. E-Mail: kf4cje@juno.com Web: <http://www.w4gs.org>

#### NOVEMBER 6-7

**GA - LAWRENCEVILLE** - Hamfest. Gwinnett County Fairgrounds. Talk-in: 145.45 (PL 107.2), 444.25+ (PL131.8), 146.76 (PL 107.2). Alford Memorial RC, Hotline: 770-410-3989. E-Mail: hamfest@totrbbs.radio.org  
**TX - ODESSA** - Hamfest. West Texas ARC, Robert Jordan N5RKN, 915-335-7980. E-Mail: n5rkn@apex2000.net Web: <http://nonprofit.apex2000.net/hamfest/>

#### NOVEMBER 7

**KY - HAZARD** - Swapfest. Hazard High School  
**MI - ST. JOSEPH** - Hamfest. Blossomland ARA, Duane Durlinger KX8D, 616-982-0404. E-Mail: comdac@comdac.com Web: <http://www.comdac.com/bara>  
**WI - KAUKAUNA** - Hamfest. Starlight Club. VE testing. Talk-in: 146.52 simplex. Fox Cities ARC, Chad Pennings N9PRC, 920-993-0485. E-Mail: n9prc@kb9byq.ampr.org Web: <http://www.w9zl.ampr.org>

#### NOVEMBER 13

**AL - MONTGOMERY** - Hamfest. Montgomery ARC, Arthur Price KF4ILP, 334-272-2681. E-Mail: kf4ilp.arthur@worldnet.att.net Web: <http://jschool.troyast.edu/~w4ap/>  
**CA - FONTANA** - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves  
**NM - SOCORRO** - Hamfest. Socorro ARA, Al Braun AC5BX, 720 California St., Socorro NM 87801

#### NOVEMBER 13-14

**IN - FORT WAYNE** - IN State ARRL Convention & Hamfest. Allen County AR Technical Society, Doug Jones N9NNT & Jim Boyer KB9IH, 219-484-3317. E-Mail: djoness2233@aol.com Web: <http://www.pipeline.com/~dagagnon/>

**CA - SANTEE** - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in.

619-561-0052

**MA - NEWTONVILLE** - Auction. Masonic Hall, second floor, 460 Newtonville Ave. 11am-4pm. WARA/1200 RC, Eliot Mayer W1MJ, 617-484-1089. E-Mail: W1MJ@amsat.org

#### NOVEMBER 20-21

**FL - TAMPA** - Suncoast Hamfest, FL State ARRL Convention. State Fairgrounds, Expo Hall. Florida Gulf Coast Amateur Radio Council, Jean Endicott KC4KZU, 727-525-5178. E-Mail: swaps@fgarc.org Web: <http://www.fgarc.org>

#### NOVEMBER 27

**NC - GREENSBORO** - Hamfest. Greensboro Coliseum Special Events Center. GGH, 336-851-1676. Web: <http://www.sabwc.com/gsohamfest>

#### NOVEMBER 28

**CA - SANTA ANA** - Swapmeet. ACP parking lot. Mary Russo 714-558-8813  
**NY - PATCHOGUE** - Hamfest. Mid-Island ARC, Mike Grant N2OX, 516-736-9126. E-Mail: global-cm@erols.com Web: <http://www.qsl.net/mid-islandarc/hamfest.html>

### DECEMBER 1999

#### DECEMBER 4

**CA - SANTEE** - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

#### DECEMBER 11

**CA - FONTANA** - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves  
**SC - UNION** - Hamfest. Armory. Union County ARC

#### DECEMBER 18

**CA - SANTEE** - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-005

### JANUARY 2000

#### JANUARY 8

**WI - WAUKESHA** - Hamfest. West Allis RAC, Phil Gural W9NAW, 414-425-3649.

#### JANUARY 9

**IN - SOUTH BEND** - Hamfest. Michiana Valley Hamfest Assn., Bob Dennison KA9WNR, 219-291-0252

#### JANUARY 15-16

**FL - SARASOTA** - Hamfest. Sarasota ARA, William Eddie Martin K14ZJ, 1870 Bahia Vista St., Sarasota FL 34239-2201

#### JANUARY 16

**NY - YONKERS** - Flea Market. Lincoln High School, Kneeland Ave. 9am-3pm. VE Exams. Talk-in: 440.425 PL 156.7, 223.760 PL 67.0, 146.910, 443.350 PL 156.7. Metro 70cm Network, Otto Supliski WB2SLQ, 914-969-1053

#### JANUARY 22

**NH - NASHUA** - Hamfest. Res Ctr Church. NE Antique RC 617-923-2665

### FEBRUARY 2000

#### FEBRUARY 26

**VT - MILTON** - NVT Winter Hamfest. High School, Rt. 7. Mitch W1SJ, 802-879-6589

#### FEBRUARY 27

**FL - ZEPHYRHILLS** - Hamfest. Zephyrhills ARC, Ernie Vanselow KD4VRV, 813-783-8389 E-Mail: kd4vr@gte.net

## Celebrating our 17th Year Of Service !!

### COLLIMATING LENS

This economical collimating lens assembly consists of a black anodized aluminum barrel that acts as a heat sink, and a glass lens with a focal point of 7.5mm. Designed to fit standard 9mm laser diodes. Simply place diode in the lens assembly, adjust beam to desired focus, then set with adhesive.

ITEM	1-14	15-24	25+
LSLENS Lens Assembly	24.99	23.74	21.37

### DIODE/TRANSISTOR TESTER KIT

This dynamic tester allows checking of transistors & diodes in circuit. Identifies NPN or PNP transistors. Checks all types, small or large power. Identifies anode or cathode of diodes.

ITEM	1-14	15-24	25+
DT100K	24.99	23.74	21.37

### ANTI-STATIC FOAM CLEANER

A thick, foaming cleaner for use in static sensitive applications. Safe for plastics and fiberglass. Use on computer cases and all office equipment. Also cleans soft fabrics. 5 oz. aerosol can.

ITEM	1-14	15-24	25+
SB1102	1.99	1.89	1.70

### EPROMS

ITEM	1-14	15-24	25+
2716	2.99	2.84	2.56
2732	4.49	4.27	3.84
2732A-20	5.49	5.22	4.70
2764-20	5.39	5.12	4.61
2764-25	4.49	4.27	3.84
2764A-20	3.49	3.32	2.99
2764A-25	2.99	2.84	2.56
27C64-15	2.99	2.84	2.56
27256-15	4.79	4.55	4.10
27C256-15	2.99	2.84	2.56
27512-25	3.09	2.94	2.65
27C512-25	2.99	2.84	2.56
27C010-15	2.79	2.65	2.39
27C020-15	3.49	3.32	2.99
27C040-12	5.49	5.22	4.70
27C080-12	10.99	10.44	9.40

### Popular I.C.'s

ITEM	1-14	15-24	25+
7400	.39	.37	.33
74LS00	.19	.18	.16
4017	.29	.28	.25
7805T	.33	.31	.28
7812T	.33	.31	.28
LM317T	.49	.47	.42
LM384N-1	.33	.31	.28
NE555N	.24	.23	.21
LM741N	.24	.23	.21
NE5532N	.55	.52	.47
68HC705C8P	8.99	8.54	7.69
8749	17.99	17.09	15.38
62256LP-10	2.79	2.65	2.39
2816	2.79	2.65	2.39

### FM MICROPHONE KIT

Transmit your voice on any FM radio. Range up to 1000'. Case included.

ITEM	1-14	15-24	25+
K30	15.99	15.19	13.67

### What Do We Have?

- I.C.'s
- Oscillators
- Crystals
- Diodes
- Tools
- Laser Diodes
- Vices
- Resistors
- Capacitors
- Connectors
- Trim pots
- Kits
- Vices
- Transistors
- And more!

### GADGETEER'S GOLDmine

This exciting collection of electronic projects features experiments ranging from magnetic levitation and lasers to high-tech surveillance and digital communications.

• By Gordon McComb

ITEM	1-14	15-24	25+
TB3360	24.99	23.74	21.37

• Order Line — (800) 824-3432 • International — (724) 495-1230 • Fax Orders — (724) 495-7882  
 • Technical Support — (724) 495-1231 • No Minimum Order — (Orders under \$20 subject to \$5 charge) • UPS 3 day, Blue, Red, & Fed. Ex. Shipping Available (Call for charges) • PA Res. Add 7% Sales Tax • Open Mon-Fri 9:00 AM - 5:00 PM (EST) • Corporate Accounts / Quantity Discounts Available • We accept M/C, VISA, Discover & American Express with no surcharge • Call For FREE Catalog (\$2.00 Outside U.S.)  
 • We Carry A Complete Line Of Electronic Components • Email - [unielec@aol.com](mailto:unielec@aol.com)  
 Visit us on the web! [www.unicornelectronics.com](http://www.unicornelectronics.com)

**Unicorn Electronics**  
**1142 State Route 18**  
**Aliquippa, PA 15001**

**FREE SHIPPING!!** on pre-paid orders



# Open Channel

by Joseph J. Carr


## Notes on Vibration Detectors and Seismographs — Part 2

This month, we will look at a clever sensor that can be used for earthquake detection.

Last month, we looked at various vibration sensors. Most of those instruments are intended to measure large vibrations, so they are not really too useful for making an amateur seismograph project (although a couple of them could be used for that purpose). This month, we will look at a clever sensor that can be used for earthquake detection.
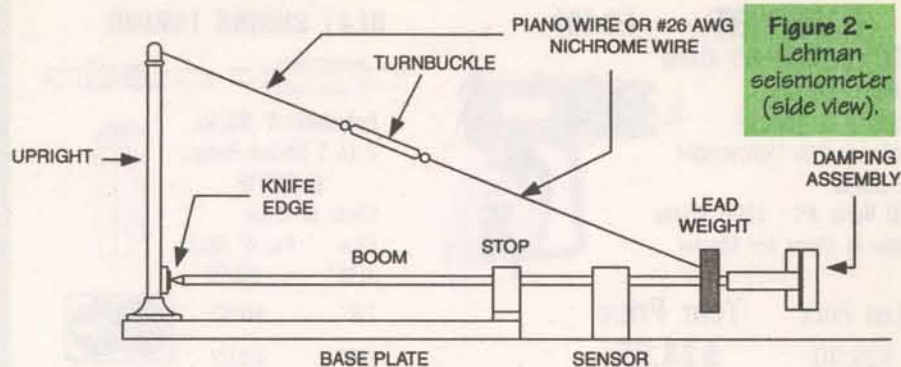
### Lehman-Type Seismometer Project



The Lehman Seismometer was designed by Dr. James D. Lehman of the Department of Physics at James Madison University in Harrisonburg, VA. It was the subject of the "Amateur Scientist" column written by Jearl Walker in *Scientific American* (July 1979, p. 152ff). This seismometer is said to be capable of detecting earthquakes of 4.8 or more on the Richter scale in the United States, and 6.0 or more in other areas of the world.



The plan (top) view is shown in Figure 1, while a side view is shown in Figure 2. A long (75-cm or more) pendulum boom made of 5/16-inch (8-mm) stock is suspended from an upright section (Figure 3) such that its "knife edge" butt end rests against a strike plate on the upright section. The last 20-cm or so of the boom is threaded to accept a 5/16-20 or finer hex nut. When side-to-side vibrations characteristic of an earthquake are present, the pendulum arm will swing back and forth in the horizontal plane. A pair of stops (Figure 4) are used to prevent over-travel of the pendulum boom arm. The components of the seismometer are mounted on a flat base plate. This plate can be made of aluminum, wood, or plastic, but it must be level and stable. Do not use thin material (less than 1.5 cm) for the base.

The upright segment is made from copper plumbing pipe, right angle joints, and a pair of universal flanges for mounting to the base plate. The overall height is about 46 cm. A lower cross piece holds the strike plate, while the upper cross piece holds a special wire attachment point fixture (more on this shortly).

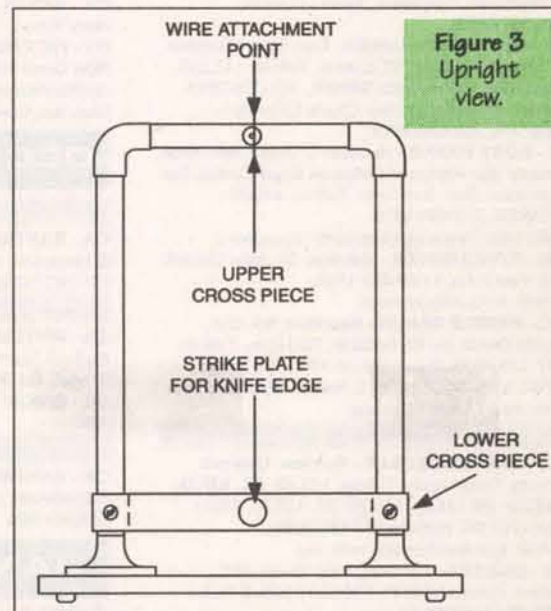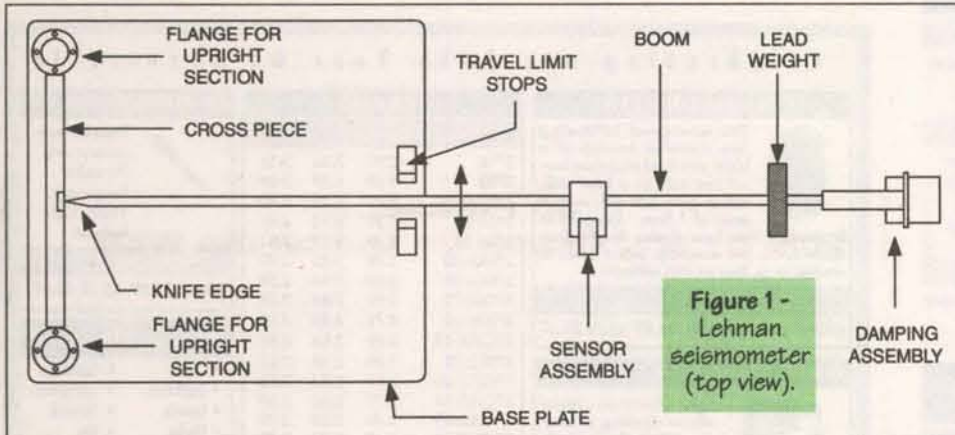In Figure 2, you saw the side view. The wire suspending the boom is either piano wire or #26 AWG nichrome wire. A small turnbuckle is used to make the wire taut and level the boom. The upper end of the suspension wire is tied off to the upper cross piece (Figure 5). The Walker article used an oil burner furnace nozzle to precisely position the suspension wire.



## 5 Axis Robotic Arm Kit \$195.00 Plus S&H



### You can build this Robotic Arm!

Impressive, fast, accurate and repeatable motion. Any computer capable of sending 2400 or 9600 baud serial data can control the arm, even a Basic Stamp! This arm makes a great foundation for AI and motion control experiments. Position the arm in an X, Y, Z, grid with a joystick or keyboard using the new RoboMotion for Windows. The kit includes all of the hardware and structural components, six quality Hitec HS-300 servos, pre-assembled SSC servo controller, DOS and Windows software, and an illustrated assembly manual.

We have many more cool robots, check out our web page or ask for our free catalog!  
3 Axis Version \$155.00 • Mobile Version \$250.00 • Mobile Robots Book \$32.00

Lynxmotion, Inc.  
104 Partridge Road  
Pekin, IL 61554-1403 USA  
<http://www.lynxmotion.com>



Tel: 309-382-1816  
Fax: 309-382-1254  
[sales@lynxmotion.com](mailto:sales@lynxmotion.com)  
[tech@lynxmotion.com](mailto:tech@lynxmotion.com)



## WHOLESALE CABLE

### COMPLETE LINE OF CABLE PRODUCTS

- ✓ Quality merchandise by brand name manufacturers
- ✓ Satisfaction guaranteed
- ✓ Free gift on first order
- ✓ Technical support
- ✓ 2 year warranty on new converters
- ✓ COD shipping & overnight shipping by request
- ✓ Experience where it counts
- ✓ Volume pricing

PLAIN CONVERTERS: ZENITH, OAK, PANASONIC, PIONEER, EAGLE, HAMLIN, STARGATE, PLUS MORE.

REMOTE CONTROLS: ALL MAJOR BRANDS, INCLUDING 2-4 FUNCTION UNIVERSAL REMOTES


WHOLESALE CABLE M-F 11am-6pm EST (718) 206-0879  
(718) 262-0900 • FAX (718) 657-4015 • (718) 297-9221

No NY sales. Federal and local laws provide criminal and civil penalties for unauthorized use. Check with your cable providers for permission to use equipment. Must be paying for all services you receive. Order by model number only. Some equipment refurbished as new.


Tell us the best price you were offered, where you got it from, and let us try to beat it.





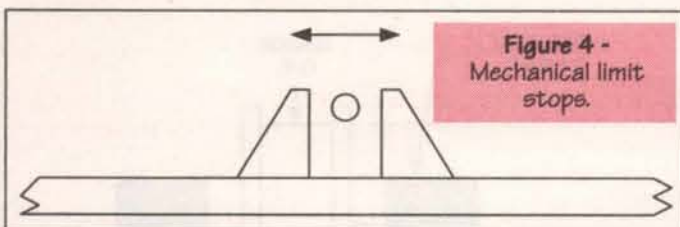

**Figure 4 -**  
Mechanical limit stops.

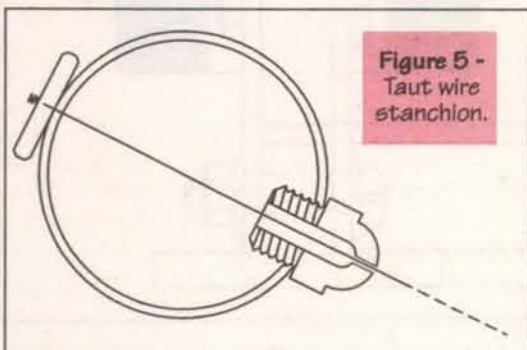

**Figure 5 -**  
Taut wire stanchion.

machine bolt is used to make the strike plate. It is cut off from the threaded segment, leaving only the head and the unthreaded portion of the shank. The head is machined flat and polished. This makes a nice, low friction surface for the knife edge end of the pendulum boom.

A hole is drilled through the cross piece just slightly larger than the strike plate. A 1/4-20 (or finer) hex nut is soldered or glued to the backside of the cross piece such that its hole is centered over the hole drilled in the cross piece. A matching hex head bolt is threaded into the


nut, so that it sits against the back of the strike plate. When this bolt is adjusted, it will adjust the

position of the strike plate.

A sensor assembly is mounted on the boom arm (refer again to Figures 1 and 2). It is used to detect motion of the boom and translate it into an electrical signal that can be recorded on paper or stored in a computer. Also on the boom arm is a lead weight to make the boom act like a pendulum, and a damping assembly. The

dampener is needed to damp out oscillations of the pendulum in order to spread out the frequency response. Without the damping assembly, the vibrations closest to the pendulum's natural period will cause the greatest response. The frequency response is thus peaked at a specific frequency, rather than being broader.

Detail for the sensor assembly is shown in Figure 7. A plan view is shown in Figure 7A, and a side view is shown in Figure 7B. The sensor's "transducible event" results from the fact that a magnetic field moving relative to a coil of wire will induce a

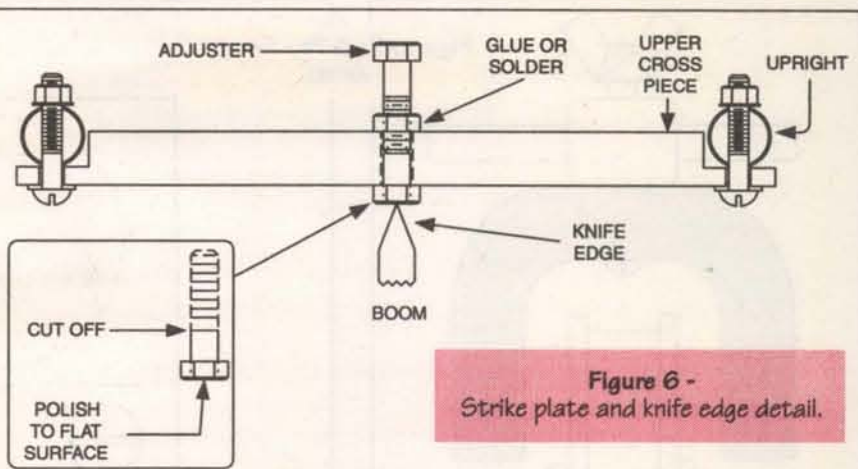

**Figure 6 -**  
Strike plate and knife edge detail.

current in that wire. In Figure 7A, you will see a strong horseshoe magnet mounted on the boom arm of the pendulum. The magnet is fixed with a wing nut connector of the sort used to fasten chemistry and optical apparatus.

Inside the curve of the horseshoe magnet is a coil of wire. The coil should be several centimeters in diameter, and consist of about 8,000 to 12,000 turns of #36 AWG (or so) enameled wire. The former for the coil can be constructed of wood or plastic. A slow speed drill is used to scramble wind the wire onto the form.


Winding the coil can be a dangerous operation, and you take your own responsibility if you attempt it.

Make sure the drill has a very slow speed (most variable speed drills will do this). Fix the drill and the form in a vise, or other fixture. The wire should be on a dowel mounted off-set from the drill and form, but positioned so that it can be unwound without kinking. **WEAR PROTECTIVE SAFETY GOGGLES WHEN WINDING THE COIL.** Injury to your eyes could occur if the wire breaks, or if you do something wrong.

The mounting of the coil and magnet are shown in side view in Figure 7B. The mounting assembly can be made from either wood or plastic, or any convenient material.

The damping assembly is shown in both plan and side views in Figure 8. The lead weight is made of

## RF Data Modules

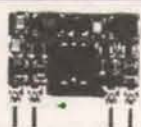

### AM TRANSMITTER

- Small size: 17.78 x 11.43mm
- CMOS/TTL input
- No adjustable components
- Low Current: 4mA typical
- 418MHz or 433.92MHz OOK
- Simple to integrate - simply add antenna, data and power
- Range up to 250ft.
- Wide supply range, 2-14Vdc
- SAW controlled - stability
- Also available in DIL package

AM-RT5 ..... \$12.10



### AM RECEIVER

- Compact size: 38.1 x 13.7mm
- On-board data recovery, CMOS
- Low current: 2.4mA typical
- 2kHz data rate, CMOS/TTL output
- 5Vdc operation
- On 418MHz or 433.92MHz (4xx)
- No adjustable components
- Patented Laser Trimmed component
- High stability
- Sensitivity: -105dBm
- Available also in 0.8mA version

AM-HRR3-4xx ..... \$10.95




### FM TRANSCEIVER

- Only 23 x 33 x 11mm
- Up to 40k bps data rate
- 19200 baud with ASCII
- Up to 500ft. range
- 5v operation
- 0.25mW into 50
- 418 or 433MHz FM
- Fast 1ms enable
- Direct interface to 5V CMOS
- Auto TX/RX changeover

BIM-4xx-F ..... \$87.36

### RS232 TRANSCEIVER MODULES

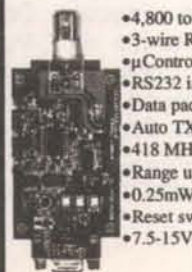

- 4,800 to 38,400 bps half duplex
- 3-wire RS232 interface
- $\mu$ Controller with user EEPROM
- RS232 interface protected to  $\pm 15kV$
- Data packetizing performed by user
- Auto TX/RX changeover
- 418 MHz and 433MHz versions
- Range up to 500ft. (0.25mW ver.)
- 0.25mW & 10mW versions
- Reset switch and status LED's
- 7.5-15V dc via DB9 connector, 20mA

BIM-4xx-RS232 .... \$139.30



70 x 65 x 15mm

- Up to 19,200 bps half duplex
- 3 wire RS232 interface
- Range up to 500ft
- Transparent data packetizing
- Supports 8 or 9 bit protocols
- Self test function
- Reset Switch & Status LED's
- 1/4 wave wire antenna on board
- Available in a Simplex Tx/Rx pair (RTcomTX & RTcomRx)
- 7.5V-15Vdc operation

Transceiver..... RTcom-4xx..... \$247.90  
Transmitter..... RTcomTx-4xx..... \$ 87.15  
Receiver..... RTcomRx-4xx..... \$105.52



**ABACOM**  
TECHNOLOGIES



Tel: (416)236-3858  
Fax: (416)236-8866  
www.abacom-tech.com  
abacomtech@compuserve.com

## Electro Mavin

**Has To Much for the AD !!!!  
We are Busting at the Seams!!!  
So Please....**

**Stop by and Check Us Out on the WEB**

**<http://mavin.com>**

**This is all you'll need to get to the  
fabulous world of Mavin Specials**

**Like....**

**Soyo Super Stable Socket 7  
Mother Boards #SY5EMA**

**Bus Over Clocks to 124 MHz -  
Uses Pentium class CPU up to 500 MHz  
Check out our low price.....**

**Other Items Include....**

**SCSI Hard Drives 3 cents a meg  
GPS Engines w/Antenna  
Microwave Goodies and Stuff  
56K V.90 Modems, 40X CDROM Drives  
Dealers Special on Designer Mice**

**We Also Buy Connectors, Contacts, Raychem**

**Electro Mavin**

**800-421-2442 or FAX 310-632-9867**



**E-Mail [john@mavin.com](mailto:john@mavin.com)**

**or**

**E-Mail [mark@mavin.com](mailto:mark@mavin.com)**



Figures 7a & 7b - Sensor detail.

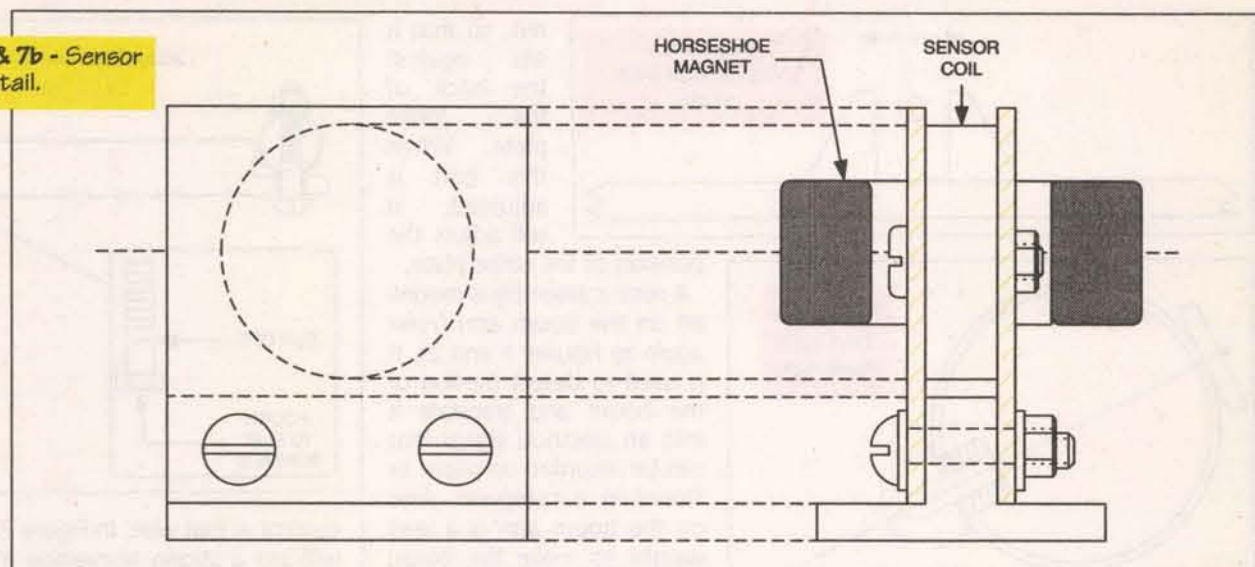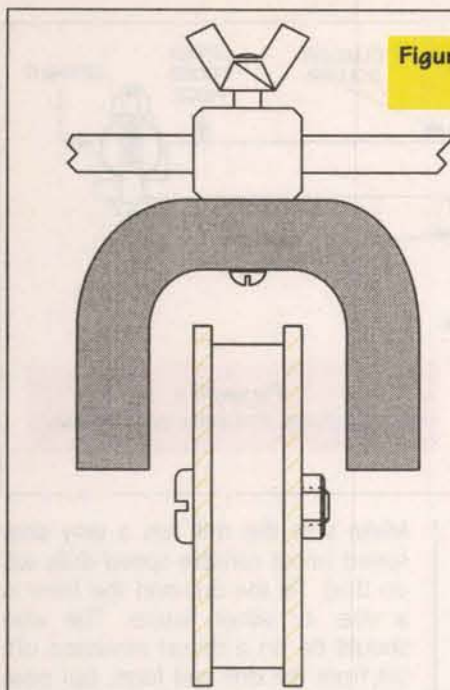

Radio Astronomy Supplies (190 Jade Cove Drive, Roswell, GA 30075; E-Mail [jmlras@juno.com](mailto:jmlras@juno.com) and website

<http://nitehawk.com/rasmit/jml0.html>). Jeff offers a book that he wrote on earthquake instruments. The Lehman-style seismometer that Jeff designed uses an oil bath to provide the damping function.

Seismometers are usually buried below grade. Some people place them in a simple box on a flat rock outcropping, but that is not terribly good practice. Others build a concrete pedestal and box to house the seismometer. Thermal insulation surrounding the inner chamber where the seismometer is located is used to keep the temperature stable. It is essential that the seismometer be perfectly level, and not tilted. It may take several days to get the seismometer adjusted properly.

### More on Lightning ...

My column on the lightning detector raised a lot of interest, but it seems that I forgot a detail. The differential amplifier is any ordinary

operational amplifier with a high input impedance. Because two are needed, a dual unit such as the CA-3240 devices are usable. Set the resistors such that the gain is about 100 to 500, depending on the sensitivity desired and the size and number of turns in the coils. The amplifiers as shown are differential, but if one side of each coil is grounded, then a single-ended amplifier can be used.

The best performance occurs when the coils are inter-twined as shown in that article. However, two coils set at right angles and close together will also serve the purpose.

The output voltage of the coil is not high tension. I had a couple people ask about high voltage amplifiers for this purpose. What you are picking up is not the HV electrical field produced by the lightning, but rather the electromagnetic wave (i.e., a radio signal!) emitted by the lightning when it strikes.

The signal sensed by the coils is the same as the static crash you hear on an AM radio when a thunderstorm approaches. In fact, an old farmer's trick for monitoring the

approach of storms (including those that produce tornadoes) is to tune an AM radio to the low end of the band, between stations, and monitor for static crashes.

The shielding is used for two purposes, as on any loop antenna. First, the frequency range is very sensitive to harmonics of the 60-Hz power line (they are audible well into the medium wave portion of the HF spectrum!). But those tend to be primarily electrical fields, not magnetic. As a result, using a shielded coil will reduce the coil's sensitivity to electrical fields, while retaining its magnetic field. Make sure that a small gap is left in the shield to prevent the shield from acting as a one-turn loop in its own right.

The second reason for the shielding is that capacitive coupling to nearby conductive objects (including the ground) tends to distort the pattern of the coils. The shielding helps reduce that effect. Indeed, most professional VLF-MW receiving loops used for radio direction finding (RDF) are shielded for exactly this reason.


### WWV Clocks

One of the problems faced by amateur scientists when collecting data is automatic recording of the time of day. If a computer is being used, then the internal time-of-day clock can be used. However, those clocks have a way of drifting into error over time. Recently, a number of clocks have been offered that have an internal WWV/WWVH shortwave receiver to provide correction. One clever soul wrote to me via E-Mail (see "Connections..." below) and told me that he had found one model that had the Binary Coded Decimal (BCD) data line easily available ... and used it for time recording. Clever dude! NV

### Connections ...

I can be reached by snail mail at P.O. Box 1099, Falls Church, VA 22041, or via E-Mail at [CARRJJ@AOL.COM](mailto:CARRJJ@AOL.COM).

Figure 8 - Damper detail.

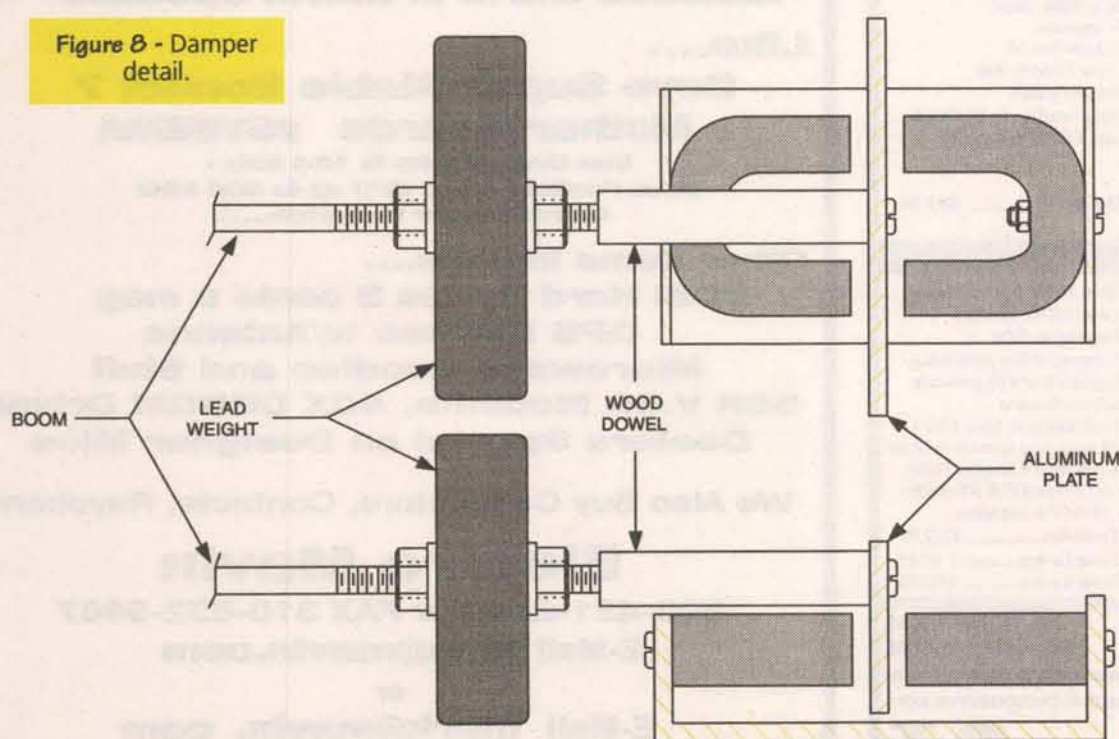



# DEALER DIRECTORY

The dealers listed below carry the latest issue of Nuts & Volts, for your convenience.

## ALABAMA

**Little Professor Book Center**  
2717 S. 18th St.  
Birmingham 35209  
**RT Systems**  
**Amateur Radio Supply**  
8207 Stephanie Dr.  
Huntsville 35802

## ARIZONA

**Batteries Plus #330**  
3014 N. Dobson  
Chandler 85224  
**Batteries Plus #334**  
1155 S. Power Rd. #108  
Mesa 85206  
**Batteries Plus #331**  
2404 E. Bell Rd.  
Phoenix 85032  
**Batteries Plus #332**  
3415 W. Glendale Ave. Ste. 4  
Phoenix 85051  
**Batteries Plus #333**  
1829 E. Southern Ave.  
Tempe 85282  
**Elliott Electronic Supply**  
1251 S. Tyndall Ave.  
Tucson 85713  
**Tower Records**  
3 E. 9th St.  
Tempe 85281

## AUSTRALIA

**DonTronics**  
P.O. Box 595  
29 Ellesmere Cres.  
Tullamarine 3043  
www.dontronics.com

## CALIFORNIA

**Abletronics**  
9155 Archibald Ave. Unit E  
Cucamonga 91730  
**Advanced Computer Products, Inc.**  
1310 "B" E. Edinger Ave.  
Santa Ana 92705  
**All Electronics**  
905 S. Vermont Ave.  
Los Angeles 90006  
14928 Oxnard St.  
Van Nuys 91411  
**Allen's To Go**  
13461 Hwy. 88  
Lockeford 95237  
**Alltronics**  
2300-D Zanker Rd.  
San Jose 95131  
**Centerfold International**  
716 N. Fairfax Ave.  
Los Angeles 90046  
**Del Amo Books & News**  
3758 Sepulveda Blvd.  
Torrance 90505  
**DSS Satellite Comm.**  
411-E 18th St. #C  
Oakland 94606  
**Electro Mavin**  
2985 E. Harcourt St.  
Rancho Dominguez 90221  
**Ford Electronics**  
8431 Commonwealth Ave.  
Buena Park 90621  
**Harding Way News**  
113 W. Harding Way  
Stockton 95204  
**Harold's Newsstand**  
524 Geary St.  
San Francisco 94102  
**Hi-Fi Doctor**  
1814 E. Ball Rd.  
Anaheim 92806  
**HSC Electronic Supply**  
4837 Amber Ln.  
Sacramento 95841

3500 Ryder St.  
Santa Clara 95051  
5681 Redwood Dr.  
Rohnert Park 94928  
**Hyatt Electronic Surplus**  
371 N. Johnson Ave.  
El Cajon 92020  
**JK Electronics**  
6395 Westminster Ave.  
Westminster 92683  
**Laurel Park News**  
4346 Laurel Canyon Blvd.  
Studio City 91604  
**Lion Electronic Labs**  
4948 E. Townsend Ave.  
Fresno 93727  
**Netseller**  
7207 Arlington Ave. Ste. G  
Riverside 92503  
**Op Amp Technical Books**  
1033 N. Sycamore Ave.  
Los Angeles 90038  
**Panorama Electronics**  
8737 Van Nuys Blvd.  
Panorama City 91402  
**Sandy's Electronics Supply, Inc.**  
20655 Soledad Cyn. Rd. #15  
Santa Clarita 91351  
**Sav-On Electronics**  
13225 Harbor Blvd.  
Garden Grove 92643  
**SIERRA MADRE NEWSSTAND**  
55 N. Baldwin Ave.  
Sierra Madre 91024  
**The Red Barn**  
Hwy. 299  
Bieber 96009  
**Tower Books**  
211 Main St.  
Chico 95928  
7840 Macy Plaza Dr.  
Citrus Heights 95610  
1280 E. Willow Pass Rd.  
Concord 94520  
630 San Antonio Rd.  
Mountain View 94040  
1600 Broadway  
Sacramento 95818  
5950 Florin Rd.  
Sacramento 95823  
2538 Watt Ave.  
Sacramento 95821  
**Tower Records/Video**  
220 N. Beach Blvd.  
Anaheim 92801  
2520 Durant  
Berkeley 94704  
212 F St.  
Davis 95616  
5703 Christie Ave.  
Emeryville 94608  
6310 E. Pacific Coast Hwy.  
Long Beach 90803  
2280 Market St.  
San Francisco 94114  
3205 20th Ave.  
San Francisco 94132  
2525 Jones St.  
San Francisco 94133  
871 Blossom Hill Rd.  
San Jose 95123  
**Video Electronics**  
3829 University Ave.  
San Diego 92105  
**CANADA**  
**Com-West Radio Systems Ltd.**

8206 Ontario St. #100  
Vancouver, BC V5X 3E3  
**Muir Communications Ltd.**  
3214 Douglas St.  
Victoria, BC V8Z 3K6

## COLORADO

**TH Electronics**  
216 Commerce Dr., Unit 2  
Ft. Collins 80524  
**Tower Records/Video**  
2500 E. 1st Ave.  
Denver 80206

## CONNECTICUT

**Archway News**  
64 Bank St.  
New Milford 06776  
**Electronic Service Products**  
437 Washington Ave.  
North Haven 06473

## DELAWARE

**Newark Newsstand**  
70 E. Main St.  
Newark 19711

## DISTRICT OF COLUMBIA

**Tower Records**  
2000 Pennsylvania Ave.  
Washington 20006

## FLORIDA

**Alfa Electronic Supply**  
1502 S. St. Rd. #7  
Hollywood 33023  
**AI's News**  
8219 S.W. 124th St.  
Miami 33156  
**Astro Too**  
2854 Sarno Rd.  
Melbourne 32935  
**Bob's News & Books**  
1515 S. Andrew Ave.  
Fort Lauderdale 33316  
**Clarks Out of Town News**  
303 S. Andrews Ave.  
Fort Lauderdale 33301  
**Mike's Electronic Distributing Co.**  
1001 N.W. 52nd St.  
Fort Lauderdale 33309  
**Skycraft Parts & Surplus, Inc.**  
2245 W. Fairbanks  
Winter Park 32789  
**Sunny's At Sunset, Inc.**  
8260 Sunset Strip  
Sunrise 33322

## GEORGIA

**Tower Records**  
3400 Around Lenox Dr. N.E.  
Atlanta 30326

## HAWAII

**SolarWorks!**  
525 Lotus Blossom Ln.  
Ocean View 96737  
**Tower Records**  
4211 Wai'alae Ave.  
Honolulu 96816  
611 Keeaumoku  
Honolulu 96814

## IDAHO

**The Current Source**  
5159 Glenwood  
Boise 83714

## ILLINOIS

**Tower Records/Video/Books**  
383 W. Army Trail Rd.  
Bloomington 60108  
2301 N. Clark St. #200  
Chicago 60614  
1209 E. Golf Rd.  
Schaumburg 60173

## INDIANA

**Harbourtown Sales**  
108 Park 32 W. Dr.  
Noblesville 46060

## KANSAS

**Hollywood At Home**  
9063 Metcalf Ave.  
Overland Park 66212  
**Lloyd's Radio & Electronic, Inc.**  
220 W. Harry St.  
Wichita 67213

## LOUISIANA

**Lakeside News**  
3323 Severn Ave.  
Metairie 70002

## MARYLAND

**Silicon Valley Electronics**  
2014-A Industrial Dr.  
Annapolis 21401  
**Tower Records/Video**  
2566 Solomons Island Rd.  
Annapolis 21401  
1601 Rockville Pike #210  
Rockville 20852

## MASSACHUSETTS

**Newsbreak, Inc.**  
579 G.A.R. Hwy. Rt. 6  
Swansea 02777

## MICHIGAN

**Little Professors Book Center**  
22174 Michigan Ave.  
Dearborn 48124  
**Purchase Radio Supply, Inc.**  
327 E. Hoover Ave.  
Ann Arbor 48104

## MINNESOTA

**Radio City, Inc.**  
2633 County Road 1  
Mounds View 55112

## MISSOURI

**Accurate Instruments**  
11201 E. 24 Hwy.  
Independence 64054  
**Electronics Exchange**  
8644 St. Charles Rock Rd.  
St. Louis 63114

## NEVADA

**Amateur Electronic Supply**  
1072 N. Rancho Dr.  
Las Vegas 89106  
**Less Buster's Electronics**  
2930 N. Las Vegas Blvd.  
VSTG-22  
North Las Vegas 89030  
**Radio World**  
1656 Nevada Hwy.  
Boulder City 89005  
**Tower Records/Video**  
4580 W. Sahara Ave.  
Las Vegas 89102  
6450 S. Virginia  
Reno 89511

## NEW JERSEY

**Tech-Systems Electronics, Inc.**  
1309 Hwy. 71  
Belmar 07719

## NEW YORK

**All Phase Video Security, Inc.**  
70 Cain Dr.  
Brentwood 11717  
**Genosha Minicade**  
3413 Ave J  
Brooklyn 11210  
**Ham Central**  
3 Neptune Rd.  
Poughkeepsie 12601

## Hirsch Sales Corporation

219 California Dr.  
Williamsport 14221  
**Tower Records/Video**  
105 Old Country Rd.  
Carle Place 11514  
350-370 Route 110  
Huntington 11746  
1961 Broadway  
New York 10023  
383 Lafayette St.  
New York 10003

## OHIO

**Compustuff**  
241 Great Oaks Trl.  
Wadsworth 44281  
**Digital One**  
7603 Mentor Ave.  
Mentor 44060  
**Footsteps**  
4925 Jackman Rd. Store #58  
Toledo 43613  
**Hosfelt Electronics, Inc.**  
2700 Sunset Blvd.  
Steubenville 43952  
**Keyways, Inc.**  
204 S. 3rd St.  
Miamisburg 45342  
**Leo's Book Shop**  
333 N. Superior St.  
Toledo 43604  
**Powermaxx, Inc.**  
1587 U.S. Route 68 N.  
Xenia 45385

## OKLAHOMA

**Steve's Books & Magazines**  
2612 S. Harvard  
Tulsa 74114  
**Taylor News & Books**  
133 W. Main, Ste. 102  
Oklahoma City 73102

## OREGON

**News & Smokes**  
2295 W. Main St.  
Medford 97501  
**News & Smokes #8**  
259-C Barnett Rd.  
Medford 97501  
**Norvac Electronics**  
7940 S.W. Nimbus Ave. Bldg. 8  
Beaverton 97005  
960 Conger  
Eugene 97402  
1545 N. Commercial N.E.  
Salem 97303  
**Powell's Technical Bookstore**  
33 N.W. Park  
Portland 97209  
**Tower Books**  
1307 N.E. 102nd Ave.  
Portland 97220

## PENNSYLVANIA

**Bedford St. News**  
308 Bedford St.  
Johnstown 15901  
**Genes Books, Inc.**  
King of Prussia Plaza  
King of Prussia 19406  
**Lehman Scientific**  
85 Surrey Dr.  
Wrightsville 17368  
**Tower Books**  
425 South St.  
Philadelphia 19147  
**Tower Records**  
340 W. Dekalb Pike  
King of Prussia 19406  
**SOUTH CAROLINA**  
**555 Electronics**  
5646 Farrow Rd.  
Columbia 29203

## TENNESSEE

**Tower Books**  
2404 W. End Ave.  
Nashville 37203

## TEXAS

**BDL News, Inc.**  
809 Pierce  
Houston 77002  
**Electronic Parts Outlet**  
3753-B Fondren Rd.  
Houston 77063  
**Mouser Electronics**  
958 N. Main St.  
Mansfield 76063  
**Tanner Electronics**  
1301 W. Beltline #105  
Carrollton 75006  
**Tower Records**  
2403 Guadalupe St.  
Austin 78705

## VIRGINIA

**American Computer Clearance**  
1609 Rhoadmiller St.  
Richmond 23220  
**Tower Records/Video/Books**  
4110 W. Ox Rd. #12124  
Fairfax 22033  
1601 Willow Lawn Dr.  
Richmond 23230  
8389 E. Leesburg Pike  
Vienna 22182

## WASHINGTON

**A-B-C Communications, Inc.**  
17541 15th Ave. N.E.  
Seattle 98155  
**Bohica Concepts**  
214 2nd St.  
Morton 98356  
**Cody Books Ltd.**  
1125 Fir Ave.  
Blaine 98230  
**Service Request**  
3304 W. Rowan Ave.  
Spokane 99205  
**Supertronix**  
16550 W. Valley Hwy.  
Seattle 98188  
**Tower Books**  
10635 N.E. 8th St.  
Bellevue 98004  
20 Mercer St.  
Seattle 98109

## WISCONSIN

**Amateur Electronic Supply, Inc.**  
5710 W. Good Hope Rd.  
Milwaukee 53223  
**Greenfield News & Hobby**  
6815 W. Layton Ave.  
Greenfield 53220  
**Cudahy News & Hobby Ctr.**  
4758 Packard Ave.  
Cudahy 53110  
**WYOMING**  
**Western Test Systems**  
2701 Westland Ct. #B  
Cheyenne 82001



# HOW TO PLACE A CLASSIFIED AD

TYPE or PRINT your **ELECTRONICALLY RELATED** ad copy **CLEARLY (not all caps)** on a separate piece of paper. Spell out words when submitting handwritten copy. Calculate the number of words and multiply it by the appropriate rate (see RATE PER WORD section). Include any charges for **bold** and/or **CAPPED** words, any artwork costs that would be applicable, and/or costs for boxing your ad (explained below). Choose the appropriate classification for your ad(s) to appear in (see below). If no classification is indicated, it will be placed in Misc. Electronics or wherever we deem most suitable. **Enclose your name, address, phone number, and Nuts & Volts account number from your mailing label** (if available) for identification purposes. Include full payment — **CLASSIFIEDS RUN ON A PRE-PAID BASIS ONLY** — and mail your completed order to:

**NUTS & VOLTS MAGAZINE**, 430 Princeland Ct., Corona, CA 91719.

## RATE PER WORD

The ad rate for **current PAID subscribers** is **60¢** per word. All others pay **\$1.20** per word. There is a **\$9.00 minimum** charge per ad per insertion.

## WORDS IN BOLD AND/OR ALL CAPS

Words to be set in **bold** or **CAPS** are each **10¢** extra PER WORD. **BOLD CAPS** are **20¢** extra per word. The first two words of each ad are bold capped at no charge. Indicate bold words by underlining. Words normally written in caps (e.g., IBM) and accepted abbreviations such as VAC or MHz are NOT charged as all cap words. Use a two-letter abbreviation for states.

## PHOTOS, DRAWINGS, AND BOXES

A photo or drawing may be run at the top of your classified ad for an additional **\$10.00** (1" depth max.) for camera-ready art. No wording is allowed in this area. Add a one-time charge of **\$5.00** to enlarge, reduce, or duplicate line

art, or **\$8.00** for halftone of photographs. To **BOX** your ad, include an additional **\$50.00** for copy-only ads, or **\$75.00** for ads with art or photos.

## FAXING IN AD COPY

You may fax in ad copy or changes before the closing date (5:00pm on the **5th**) at 909-371-3052 using MasterCard or Visa. Include credit card expiration date, the name that appears on the card, a daytime phone number, and your *Nuts & Volts* account number. Ads without credit card information will not be listed as received until payment is received in full. **WE DO NOT CALL OR FAX BACK VERIFICATION OR QUOTES OF FAXED-IN ADS.** For verification of faxed-in ads, please call 909-371-8497.

## DEADLINE

Prepaid ads received by 5:00pm on the **closing date (5th of the month)** will appear in the following month's issue. Ads postmarked through the **5th**, but received after the closing date, will be placed in the next available issue. No cancellations or changes after the 5th. Cancellations and changes must be submitted in writing.

## IMPORTANT INFORMATION

All classified ads are running copy only. No special positioning, centering, dot leaders, extra space, etc. is allowed. All advertising in *Nuts & Volts* is limited to **electronically related items ONLY**. All ads are subject to approval by the publisher. We reserve the right to reject or edit any ad submitted. We do not take ad copy or changes over the phone. We do not bill for classified ads. Repeat ads or ads run in multiple classifications within the same issue are allowed. Paid subscribers may run ads at the 60¢ rate only through their subscription expiration date. **NO REFUNDS.** Credit only. No credit for typesetting errors will be issued unless you *clearly* print or type your ad copy.

*Choose a category for your ad from the classifications listed below.*

10. Ham Gear For Sale	80. Test Equipment	120. Components	155. Manuals/Schematics Wanted
20. Ham Gear Wanted	85. Security	125. Microcontrollers	160. Misc. Electronics For Sale
30. CB/Scanners	90. Satellite Equipment	130. Antique Electronics	170. Misc. Electronics Wanted
40. Music & Accessories	95. Military Surplus Electronics	135. Aviation Electronics	175. BBS & Online Services
50. Computer Hardware	100. Audio/Video/Lasers	140. Publications	180. Education
60. Computer Software	110. Cable TV	145. Robotics	190. Business Opportunities
70. Computer Equipment Wanted	115. Telephone/Fax	150. Plans/Kits/Schematics	200. Repairs/Service

## ADVERTISER'S INDEX

1A Sales .....	63	Digital Products Company .....	81	Lemon-Pladd, Inc. ....	20	Resources Un-Ltd. ....	55
Abacom Technologies .....	65	DMD Systems Recovery, Inc. ....	82	Lemos International Co., Inc. ....	47	Roger's Systems Specialist .....	33
ABC Electronics .....	58	Earth Computer Technologies .....	35	Linear Systems .....	19	Saelig Company .....	45
ACP Super Store .....	38	EDS .....	8	LLH Technology Publishing .....	88	SAM Electronics .....	16
ActiveWire, Inc. ....	81	E.H. Yost & Co. ....	20	Lynxmotion, Inc. ....	64	Sam's Electronics .....	62
Advanced Educational Systems .....	15	Electro Mavin .....	65	M2L Electronics .....	76	Scott Edwards Electronics, Inc. ....	90
Alfa Electronics .....	44	Electro Science Applications, Inc. ....	78	Matco, Inc. ....	81, 82	Seabird Technical .....	82
All Electronics Corporation .....	56	Electro Tool, Inc. ....	37	MCM Electronics .....	17	Sescom, Inc. ....	81
Allison Technology Corporation .....	63, 80	Electronic Goldmine .....	83	Meredith Instruments .....	76	Shreve Systems .....	12
Alltech Electronics .....	73	Electronic Products .....	81	Metric Equipment Sales, Inc. ....	30	SiGEM .....	81
Alltronics .....	22	Electronic Rainbow Ind., Inc. ....	39	microEngineering Labs .....	16	Skycraft Parts & Surplus, Inc. ....	41
American Innovations, Inc. ....	47	Electronix Express .....	53	Micromint .....	77	softwarecloseouts.com .....	82
AM Research, Inc. ....	41	EMAC, Inc. ....	37	Midland Technologies .....	81	Square 1 Electronics .....	29
Andromeda Research .....	48	EPS .....	82	Miller Engineering .....	75	SuperCircuits .....	30
Antique Radio Classified .....	82	Equipment Management Technology .....	48	Modern Communications .....	24	Surplus Traders .....	80
AST Global Electronics .....	58	ExpressPCB .....	29	Mr. NiCd .....	20	Techniks, Inc. ....	80
Astro Too .....	82	Fair Radio Sales Co. ....	58	MSC Electronics .....	82	Technological Arts .....	21
Aventrade .....	80	Foss Warehouse Distributors .....	80	Netcom .....	25	Telulex, Inc. ....	79
Aviation Components Corp. ....	81	Gateway Electronics, Inc. ....	34	Norcomm .....	71	The RF Connection .....	19
BasiConcepts, Inc. ....	18	General Device Instruments .....	80	Northwest Cable & Connector Co. ....	62	Timeless Products .....	50
Baylin Publications .....	13	Glentech, Inc. ....	80	Optoelectronics .....	4	TNR Technical, Inc. ....	81
Bilocon Corp. ....	82	Graymark .....	52	Parallax, Inc. ....	Back Cover	Unicorn Electronics .....	63
Bisme Computers Outlet .....	57	Halted Specialties Co. ....	3	PARAMAX, INC. ....	60	Upstate Games .....	82
Black Feather Electronics .....	13	Howard Electronic Instruments, Inc. ....	42	PCW, Inc. ....	38	USI Corp. ....	37
Bytech Services .....	90	H.T. Orr Computer Supplies .....	57	Phelps Instruments .....	91	V&V Mach. & Equipment, Inc. ....	80-82
C & S Sales, Inc. ....	60	Information Unlimited .....	32	Pioneer Hill Software .....	61	Velleman .....	59
C and H Sales Company .....	35	Inkjet Southwest .....	40	Plans-Kits Unlimited .....	81	Vesta Technology, Inc. ....	81
Circuit Specialists, Inc. ....	94	Intek Electronic Systems .....	41	Polaris Industries .....	31	Viking International .....	18
Communications Surplus .....	81	intelligence .....	82	Prairie Digital, Inc. ....	82	Visitect, Inc. ....	51
Convergent, Inc. ....	89	Intronics, Inc. ....	38	Pulsar, Inc. ....	21	Weeder Technologies .....	78
Corporate Systems Center .....	2, 95	Jade Products, Inc. ....	80	P.V. Power Corp. ....	82	Western Test Systems .....	26-27
Cunard Associates .....	77	JK microsystems .....	82	Quality Kits .....	81	Wholesale Cable .....	64
Cyber-Test Incorporated .....	73	Junkware.com .....	81	R & S Surplus .....	62	Worldwyde .....	80
Davilyn Corp. ....	7	J-Works, Inc. ....	75	Ramsey Electronics, Inc. ....	36		
DeMar Electronics .....	82	La Paz Electronics Int'l. ....	38	R.E. Smith .....	80		



## AMATEUR RADIO & TV

Alltronics	22
Astro Too	82
Communications Surplus	81
Convergent, Inc.	89
Gateway Electronics, Inc.	34
Jade Products, Inc.	80
Lemos International Co., Inc.	47
Matco, Inc.	81, 82
Norcomm	71
Ramsey Electronics, Inc.	36
The RF Connection	19

## ASSEMBLY SERVICES

Bilocon Corp.	82
---------------	----

## BATTERIES/CHARGERS

1A Sales	63
Aventrade	80
Cunard Associates	77
E.H. Yost & Co.	20
Jade Products, Inc.	80
Mr. NiCd	20
TNR Technical, Inc.	81

## BUSINESS OPPORTUNITIES

Intek Electronic Systems	41
--------------------------	----

## BUYING ELECTRONIC SURPLUS

ABC Electronics	58
Alltech Electronics	73
Aviation Components Corp.	81
Black Feather Electronics	13
C and H Sales Company	35
Earth Computer Technologies	35
EPS	82
Equipment Management Technology	48
Intek Electronic Systems	41
Metric Equipment Sales, Inc.	30
Roger's Systems Specialist	33
Skycraft Parts & Surplus, Inc.	41

## CABLE TV

Foss Warehouse Distributors	80
Modern Communications	24
PCW, Inc.	38
Sam's Electronics	62
Timeless Products	50
Wholesale Cable	64
Worldwide	80

## CB/SCANNERS

USI Corp.	37
-----------	----

## CCD CAMERAS/VIDEO

Black Feather Electronics	13
Circuit Specialists, Inc.	94
Matco, Inc.	81, 82
MSC Electronics	82
Polaris Industries	31
Ramsey Electronics, Inc.	36
Resources Un-Ltd.	55
Seabird Technical	82
SuperCircuits	30
USI Corp.	37

## COMPONENTS

1A Sales	63
Aviation Components Corp.	81
BasiConcepts, Inc.	18
Communications Surplus	81
Convergent, Inc.	89
Electronic Goldmine	83
Electronic Products	81
Electronix Express	53
EPS	82
La Paz Electronics Int'l.	38
Linear Systems	19
Pulsar, Inc.	21
SiGEM	81
Skycraft Parts & Surplus, Inc.	41
Unicom Electronics	63
Visitect, Inc.	51

## COMPUTER

Hardware	
ACP Super Store	38
ActiveWire, Inc.	81
Allison Technology Corp.	63, 80
Alltech Electronics	73
AM Research, Inc.	41
Bismite Computers Outlet	57
Bytech Services	90
Corporate Systems Center	2, 95

DMD Systems Recovery, Inc.	82
Earth Computer Technologies	35
Electro Mavin	65
General Device Instruments	80
Halted Specialties Co.	3
La Paz Electronics Int'l.	38
MCM Electronics	17
Northwest Cable & Connector Co.	62
Roger's Systems Specialist	33
Shreve Systems	12
Techniks, Inc.	80
Upstate Games	82

## Software

AM Research, Inc.	41
Bismite Computers Outlet	57
Bytech Services	90
Electro Science Applications, Inc.	78
Pioneer Hill Software	61
softwarecloseouts.com	82

## Microcontrollers / I/O Boards

Advanced Educational Systems	15
AM Research, Inc.	41
BasiConcepts, Inc.	18
Bismite Computer Outlet	57
Bytech Services	90
Convergent, Inc.	89
EMAC, Inc.	37
JK microsystems	82
Junkware.com	81
La Paz Electronics Int'l.	38
Lemon-Pladd, Inc.	20
Micromint	77
Parallax, Inc.	Back Cover
PARAMAX, INC.	60
Prairie Digital, Inc.	82
R.E. Smith	80
Scott Edwards Electronics, Inc.	90
Square 1 Electronics	29
Technological Arts	21
Vesta Technology, Inc.	81

## Printers/Printer Supplies

H.T. Orr Computer Supplies	57
Inkjet Southwest	40

## DESIGN/ENGINEERING SERVICES

Electro Science Applications, Inc.	78
ExpressPCB	29
Midland Technologies	81
Plans-Kits Unlimited	81
Prairie Digital, Inc.	82
Pulsar, Inc.	21
V&V Mach. & Equipment, Inc.	80-82

## EDUCATION

Advanced Educational Systems	15
BasiConcepts, Inc.	18
Electro Science Applications, Inc.	78
EMAC, Inc.	37

## EVENTS/SHOWS

ACP Super Store	38
SAM Electronics	16

## KITS

Alltronics	22
C & S Sales, Inc.	60
Digital Products Company	81
Earth Computer Technologies	35
Electronic Goldmine	83
Electronic Products	81
Electronic Rainbow Ind., Inc.	39
EMAC, Inc.	37
Gateway Electronics, Inc.	34
Information Unlimited	32
Inkjet Southwest	40
Jade Products, Inc.	80
Lemon-Pladd, Inc.	20
Miller Engineering	75
Plans-Kits Unlimited	81
Quality Kits	81
Ramsey Electronics, Inc.	36
Scott Edwards Electronics, Inc.	90
SiGEM	81
USI Corp.	37
Velleman	59
Weeder Technologies	78

## LASERS

Information Unlimited	32
Meredith Instruments	76
Resources Un-Ltd.	55
Unicom Electronics	63

## MISC./SURPLUS

1A Sales	63
All Electronics Corporation	56
Alltech Electronics	73
Aviation Components Corp.	81
Black Feather Electronics	13
C and H Sales Company	35
Communications Surplus	81

**FIND**  
what you need ...

**FAST**

BY PRODUCT  
OR  
CATEGORY

Cyber-Test Incorporated	73
DeMar Electronics	82
Electronic Goldmine	83
Electronic Rainbow Ind., Inc.	39
EPS	82
Equipment Management Technology	48
Fair Radio Sales Co.	58
Halted Specialties Co.	3
Linear Systems	19
Resources Un-Ltd.	55
Shreve Systems	12
Skycraft Parts & Surplus, Inc.	41
Surplus Traders	80
Unicom Electronics	63
Viking International	18
Visitect, Inc.	51
Weeder Technologies	78

## PROGRAMMERS

Andromeda Research	48
Electronic Products	81
General Device Instruments	80
Intronics, Inc.	38
M2L Electronics	76
microEngineering Labs	16
Upstate Games	82

## PUBLICATIONS

Antique Radio Classified	82
intelligence	82
LLH Technology Publishing	88
Netcom	25
Plans-Kits Unlimited	81
Square 1 Electronics	29

## RF TRANSMITTERS/RECEIVERS

Abacom Technologies	65
---------------------	----

## ROBOTICS

Astro Too	82
Lemos International Co., Inc.	47
Lynxmotion, Inc.	64
PARAMAX, INC.	60
SuperCircuits	30

## SATELLITE

Baylin Publications	13
SiGEM	81
Worldwide	80

## SECURITY

American Innovations, Inc.	47
Information Unlimited	32
intelligence	82
Lemos International Co., Inc.	47
Matco, Inc.	81, 82
MSC Electronics	82
Norcomm	71
Polaris Industries	31
SuperCircuits	30
Visitect, Inc.	51

## SOLAR EQUIPMENT

P.V. Power Corp.	82
------------------	----

## STEPPER MOTORS

Alltronics	22
PARAMAX, INC.	60

## TELEPHONE

Digital Products Company	81
Telulex, Inc.	79
Weeder Technologies	78

## TEST EQUIPMENT

ABC Electronics	58
Alfa Electronics	44
Allison Technology Corp.	63, 80
AST Global Electronics	58
Astro Too	82
C & S Sales, Inc.	60
C and H Sales Company	35
Circuit Specialists, Inc.	94
Davilyn Corp.	7
Digital Products Company	81
DMD Systems Recovery, Inc.	82
EDS	8
Electro Tool, Inc.	37
Equipment Management Technology	48
Glentech, Inc.	80
Howard Electronic Instruments, Inc.	42
Intronics, Inc.	38
J-Works, Inc.	75
MCM Electronics	17
Metric Equipment Sales, Inc.	30
Optoelectronics	4
Phelps Instruments	91
Pioneer Hill Software	61
Prairie Digital, Inc.	82
R & S Surplus	62
Saelig Company	45
Seabird Technical	82
Sescom, Inc.	81
Telulex, Inc.	79
Western Test Systems	26-27

## TOOLS

C & S Sales, Inc.	60
Electro Tool, Inc.	37
Graymark	52
Howard Electronic Instruments, Inc.	42
Lemon-Pladd, Inc.	20
The RF Connection	19

## WIRE/CABLE & CONNECTORS

Northwest Cable & Connector Co.	62
Roger's Systems Specialist	33
The RF Connection	19



# ELECTRONICS Q & A

With TJ Byers

In this column, I answer questions about all aspects of electronics, including computer hardware, software, circuits, electronic theory, troubleshooting, and anything else of interest to the hobbyist.

Feel free to participate with your questions, as well as comments and suggestions.

You can reach me at:

**TJBYERS@aol.com**

**TJBYERS@juno.com**

or by snail mail at  
Nuts & Volts Magazine,  
430 Princeland Ct.,  
Corona, CA 91719.

## What's Up:

Servos, steppers, and flying ships (blimps). An exciting web site for monitor specs and pinouts. Some robotics stuff, and how to interface Motorola's GSPD receiver to the 'bot.

Finally, a free cure for the I-Worm. ExploreZip virus, PC RAM explained and good feedback from our readers.

## Lighter Than Air

**Q** - I'm trying to build a twin-engine electric motor R/C blimp. The biggest problem I'm having is that I'm not familiar with the way radio receivers and servos work. I need a way to control the speed of both motors using one channel for total throttle and another channel to slow one or the other down so that it will turn and, if possible, reverse as well. Do you have any thoughts or comments?

**Michael Black**  
via Internet

**A** - I'm not all that involved with RC myself (my last RC plane mysteriously flew off to the wild blue yonder, never to be seen again; out of radio range, I'm sure, or jammed by another), but I can give you some pointers. For instance, there are two schools of thought on how to control a blimp. The first uses a rudder and elevators (horizontal fins) to control the airship's movement. There are two widely-separated stepper motors that are synchronized like the motors of a twin-engine propeller plane. To steer the blimp, you use a servo motor to move the rudder left or right, and another servo to move the elevators up or down. Three channels are needed: one for the throttle, one for the rudder, and one for the elevators. The other school of thought is to throttle the motors to steer the ship. This, too, uses three channels to steer the ship: two for the motor throttles (maybe it can be done using one channel to throttle a single engine, but then you'd only have one speed — full ahead) and one for a servo that sets the angle of the prop to move the blimp up or down. According to the experts, either is easily accomplished using off-the-shelf RC equipment that you can find at most hobby shops. You can also buy blimp kits, assembled blimps, and specialty parts from the larger hobby outlets. For more information on blimps, check out the following web sites.

**West Coast Blimps & Electronics**  
760-375-2108

<http://www1.ridgecrest.ca.us/~jpirl/>

**Fil's RC Page**  
[http://www.repairfaq.org/filipg/RC/Fils\\_RC.html](http://www.repairfaq.org/filipg/RC/Fils_RC.html)

**Remote Controlled Flying Saucer/Blimp**  
<http://www.link.ca/saucer>

## High-Torque Servos For Robotics

**Q** - I met the creator of the "Ninja Turtles" at the show biz expo several years ago. He said the turtle's heads were all "D" type servos. I've always wanted a real torque-producing servo at a decent price for larger robotics. If you have some info on this, I'd be interested. In fact, I'm sure a lot of robotics folks would like to do more than move a small device via servo!

**Walt Noon**  
via Internet

**A** - The largest pulse-actuated servo (the RC variety) I can find is the **FMA Direct** (1-800-343-2934; <http://fmadirect.com/pages/servo.htm>) \$500. It has a torque of 298 oz./in., which translates to a whopping 18 pounds/in., with a fast response time of


0.20 seconds. Best of all, it sells for a low \$44.95. Hitec has a 224 oz./in. servo (model HS-805BB) which sells for about \$48.49. Airtronics also makes servos in this torque range, but they sell for a lot more unless you can find them surplus from outlets like **Alltronics** (408-943-9773; <http://www.alltronics.com>). To get more torque than this, you need a stepper motor with a gearhead and optical encoder. Check out the companion feature article "Servos, Steppers, and Optical Encoders" on page 84 for more information.

## Initializing Motorola's Encore VP GPS Receiver

**Q** - I recently read an article that described a system using a GPS satellite to obtain a very accurate reference frequency that can be used to calibrate quartz frequency standards and plot a forecast of their aging. The article was written by some very smart guys who are familiar with the theory and construction of the various equipment needed. I, on the other hand, got lost when trying to control the Motorola GPS receiver, which is programmed via the RS-232 port of a computer. I don't get it. How can I use this port for both input and output the GPS and the interface card require? I'm not even clear as to whether one or two ports are needed. I thought reading up on this serial port might shed light on the subject, but I cannot find your previous comments on the RS-232. What can you tell me?

**W.R. Risk**  
via Internet

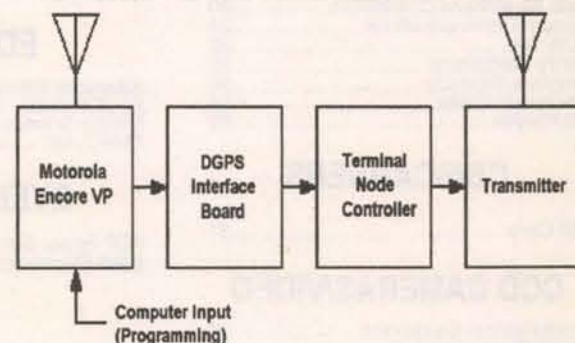**A** - The system you describe is what's called DGPS, Differential Global Positioning System. The system was originally devised to correct for the dithering of the onboard atomic clock (to prevent enemy forces from using it to guide their weapons), and it's often used by ham radio operators for a variety of applications — including a frequency reference. Here's a block diagram of the system.



The Motorola Encore VP receives the signal from the satellite and sends it to an interface board, where the various data bytes are decoded and presented in a format that is recognized by other equipment. Often the processed signal is rebroadcast over the ham bands, typically two meters (144.39 MHz). However, the Encore VP won't do anything until commanded. Here's where the PC comes in. The PC sends setup commands (you can find the setup software on the Internet at <http://www.tapr.org/tapr/html/Ftac32.html>) to the Encore VP through its RS-232 serial port. The PC supports four serial ports, COM1 through COM4, any of which can be used to setup the receiver. If all your serial ports are in use, temporarily disconnect one of the devices while you setup the receiver. Once setup, the receiver can be removed from the PC — unless power is lost, in which case, you may have to initialize the receiver again. (Motorola sells a back-up battery option that saves the setup if power is lost.) Read the next question for more details on this receiver.

## It's Telex, Not TV

**Q** - I know you have a good source of pinout information, so I'm hoping you can help me with a real dinosaur. The pinout I need is for an old Telex 10-inch monitor which was manufactured way



back in Feb. 1985 according to the label. The model number is 207243-002. When it's turned on, the screen glows amber, but that's it. There's a rotary control behind the front lip, which doesn't seem to do anything. It has a nine-pin female D connector on the bottom only marked as "20."

I was also wondering if there's a fairly simple way to convert an old IBM CGA monitor for use as a color monitor for a VCR using the RCA output jack? I have several on hand and would hate to see them go to waste.

**Gary DePietro**  
gary.depietro@dlbbs.com

**A** - It's a Telex display screen, not a computer monitor. Prior to the Internet, International business was conducted almost exclusively over dedicated Telex lines (and still is, to a large extent) because it's a secure link with a hard copy at both ends that's totally in sync — character by character. That way each party sees what the other sees as it happens, making it virtually impossible to alter the document. There are two types of telex terminal equipment that can be used for international telex service. One is KDD subscriber terminals, and the other is NTT subscriber terminals. For KDD subscribers, a direct tie-line contract is made between the customer and KDD. The NTT subscribers can also utilize international telex service by making a switched access contract with KDD. International telex service is also available using public telex terminals at KDD offices, and through telephone lines by using personal computers and other terminal equipment.

As for using a CGA monitor with your VCR, it's not practical. The VCR signal is analog with composite sync and the CGA monitor is digital with separate horizontal and vertical syncs. Such a converter would require a sync separator and three A/D 8-bit converters. It's easier to go from CGA to VCR video using an RGB-to-video converter, rather than the other way 'round.

## All About Conductivity Probes

**Q** - I'm an avid electronics hobbyist who can't get enough of my hobby, which is why it's my career as well. I do a lot of control and instrumentation work at my job, and one of the instruments is a simple conductivity cell. It measures the conductivity of regular tap-water, and provides a reading in microsiemens (uS).

Anyway, my probe and meter are currently out of commission, and in the fix-it shop. What I'd like to know is the standard setup for measuring water conductivity (meaning probe construction or arrangement), as well as the electrical parameters involved. Clearly, merely sticking the probes of a DMM into a sample bottle does NOT work — I tried it.

I've also tried a regulated 12-volt DC power supply across a pair of electrodes in series with an ammeter. I got a result that's in the neighborhood of 500 uS/cm, but the readings change too much from sample to sample to be reliable. Also, the probes have a tendency to form an electrolytic cell, which doesn't happen in a regular conductivity probe. Any information you could provide would be greatly appreciated.


**Michael J. Gordon**  
Operations Engineer  
NHMFL Long Pulse Magnet Facility

**A** - A solubridge, or conductivity meter, measures the conductivity of a liquid. Conductivity is the reciprocal of resistance — that is it expresses the liquid's ability to pass current as opposed to limiting it, as resistance does. Conductivity is expressed in millisiemens (mS) or microsiemens (uS) per centimeter. If a liquid cylinder with length 'L' and cross section 'A' has a conductance of 'G' Siemens, the conductivity 'S' is equal to

$$S = G \times L/A \text{ (S-cm/cm}^2\text{)} = G \times C \text{ (S/cm}^2\text{)}$$

It's extremely difficult to accurately measure conductivity using conventional amperometric probes because of the polarization effect you noted. The most common solution (no pun intended) is to use an AC voltage to measure the conductivity of the water, but it doesn't completely eliminate it. To try to get around the problem of polarization, different probes are sold, each with a different cell constant. Conductivity sensors are available in a variety of cell constants, typically 0.01, 0.1, 1.0, and 10. Cell constants are matched to the meter or controller for the expected range of operation. The different cell constants act like mechanical multipliers for the solution's resistance. By using different cell constants, the same meter or controller can operate over the same resistance range for both very low conductivity solutions (like ultra-pure water) and high conductivity solutions (like sea water). Unfortunately, this requires frequent probe changes coupled with a time consuming calibration for each probe change. Moreover, the results depend on factors that can't be completely controlled. Temperature, for example, is of great importance; conductivity increases with temperature at the rate of approximately 2% per degree C. That's why most conductivity probes are temperature compensated, which increases their cost.

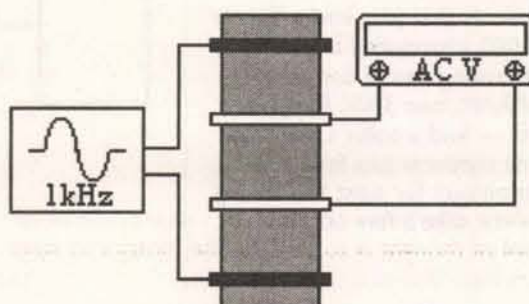Recently, I ran across a unique conductivity cell from Hanna (<http://www.hannainst.co.uk/conductivity.html>) that's every bit reminiscent of a low-resistance milliohm meter using a four-wire Kelvin circuit.



POTENTIOMETRIC  
SOLUBRIDGE

Like a Kelvin bridge, the four-ring Hanna sensor probe is a potentiometric system which overcomes the problems encountered with amperometric probes. The meter applies an alternating voltage across the top and bottom rings. When the probe is immersed in a liquid, the current flow from ring 1 to ring 4 produces a voltage across inner rings 2 and 3. This current is amplified and a calculation is performed to give the conductivity of the liquid.

## Don't Zap That Short

**Q** - I have a number of circuit boards of various types that all have shorted components. In the old days, we'd just clip off the 0.1uF caps until the short was cleared, but you can't do that with chip caps. Is there a way to "blast" these with a low-voltage, high current without damaging the ICs and other parts? I was thinking that a high-current, 5-volt power supply would do the trick.

**Jeff Kerner**  
via Internet

**A** - Sure, I can give you a circuit that will blast these shorts. The problem is that it will blast the PC board traces, too. Many years ago, I bought a boxcar lot of defective AM/FM clock radios which had mostly shorted AGC electrolytic capacitors. Once I found the defective part, it was easy to rip out and replace ONE capacitor, and make a tidy profit for myself by selling the fixed units back to the manufacturer. Your problem is more complicated in that the 0.1uF capacitor is plentiful on the boards — and more than one is likely to be bad. This is just a suggestion, but I think you could apply

## D.T.M.F. DECODER

For interconnect and  
remote control applications

**Model  
NC401**

The Model NC401 is a micro-miniature DTMF decoder, designed for selective control of local or remote applications. Measuring .80"Wx1.37"Lx.23"H, the NC401 combines three distinct, multi-addressing decoders offering multiple user-configurable functions. All programmed features are stored in non-volatile E2PROM memory and are easily programmed by means of a conventional DTMF encoder or the Model NC500 Universal/P.C. programmer. This highly engineered decoder is ideal for portable radio applications having limited space for accessories. The NC401 comes complete with micro-miniature 14 pin header and 12" color coded cable assembly.

Nor-fax Doc. #5545

## VOICE SECURITY ENCRYPTION

**Model  
NC802**

The Model NC802 is a miniature inversion scrambler designed to provide intermediate level security for two-way radio voice communication systems and is a perfect, cost-effective solution to entry-level voice scrambling as a defense against unauthorized or casual listeners. The NC802 provides eight user selectable carrier codes commonly used by other manufacturers and interfaces easily to most radios with near transparency to the user.

Nor-fax Doc. #5759

For Detailed Specifications or  
Product Catalog  
call our 24-Hour NorFax retrieval  
system at 800-874-8663 or  
on our Web Site at  
[www.norcommcorp.com](http://www.norcommcorp.com)



**800-874-8663**

15385 Carrie Drive  
Grass Valley, CA 95949 USA



a lower voltage, something along the lines of 3 volts as opposed to the 5 volts that normally power the circuit, and let your fingers do the walking — walking across the bypass capacitors, that is, looking for one that's too hot to handle. That'll be a shorted one. Rather than cut it out, I'd replace it using the SMD method I described in the Apr. '99 issue (page 9). The cap is really needed. Unfortunately, this method isn't foolproof, because a dead short will be ice cold. Do like I did and check out the markings on the defective parts you do find. Chances are they came from the same lot, and all are likely to be bad. Good luck!

### A Monitor It's Not ... But The Web Site Is Hot

**Q.** I have noticed that you get quite a few requests for information on specific monitor types and their connector pinouts. I found a wonderful resource for information of this type. It is: <http://www.monitorworld.com>. Although I have used this web site to find the pinouts for many different monitors, they have no information on a Sperry Model Number 3617-00 display, which I'm now the proud owner of two. There's a six-pin DIN connector on the back labeled simply Signal In. At first, I thought that these were some sort of data terminal — however, they are classified as an FCC type B device, which leads me to think they were manufactured for household use. I believe they are monochrome units and pretty much useless — but I'd like to connect them to my even more ancient RadioShack TS-1000, if possible. I know this is stretching it, but I hate to throw things away unless absolutely necessary.

**Robert Turner**  
via Internet

**A.** Hey, thanks a lot for the <http://www.monitorworld.com> web site. I'm sure it'll help our readers a lot. Now about your "monitors," you can toss them because you guessed right. They are terminals that plug into a Sperry (now Univac) mainframe. The Tandy (RadioShack) 1000, introduced in 1984, is a nearly 100% IBM compatible, which became its best selling line of computers ever. It came with an Intel 8088 processor, 640K of RAM, two 360K floppies, plus a good assortment of serial/parallel/game ports — and a color CGA output. CGA you ask? It's IBM's first stab at color which supports just four colors and 200 by 400 resolution. You can still find CGA monitors for next to nothing by shopping hamfests and computer flea markets — or take a few off the hands of our next reader.

### All About PC RAM

**Q.** I upgraded the memory in my laptop and would like to reuse the old modules in my desktop. I've been trying to get one of those memory converter cards that change one pin type to another, but so far, the only cards I've found are for the 30-pin and 72-pin variety. The old memory modules from my laptop are smaller and have 144 pins. Would you please help me in locating a 144-pin to 72-pin version?

**Luis Garcia**  
via Internet

**A.** Bad news, they don't make them. I recently upgraded from a Pentium 200 to a Pentium II, and now have a drawer-full of 72-pin SIMMs I can't use. Must be planned obsolescence. Anyway, you're fortunate that your left-over memory is 144-pin, which can be used in any number of notebook PCs — but never in your desktop. In other words, don't throw them away. You can always sell them. Curious about the types of PC memory out there, and where it fits? Here it is.

Memory Type	Number of Pins	Bus Width	Application
SIMM	30	8 bits	286/386
SIMM	72	32 bits	486/Pentium I
SO DIMM	144	32 bits	Pentium II laptop
DIMM	168	64 bits	Pentium II desktop


SIMM stands for single in-line memory module, which means the pins on both sides of the plug-in module are duplicated. Whether you connect to the left or right side, it's the same pin. DIMM stands for dual in-line memory module, where the fingers on opposite sides of the PC board have a different contact. SO DIMM is a small outline DIMM primarily used for notebooks. Now I suppose you want to know about memory speed. Memory modules have speeds that range from 70 nS to 10 nS. Check your PC's manual to see which speed your PC needs. As a rule, the faster the CPU clock, the faster the memory module. And there's no such thing as having too much speed, but too little speed can hang up the system. The tradeoff is that the faster the memory, the more the cost — so it's smart to match the CPU speed to the memory speed, as your manual points out.

### Stepper Motor Driver Needed

**Q.** I want to drive an AIRPAX bipolar stepper motor (rated 5 volt, 1.0 amp) from a PIC 16F84. I have seen chips for stepper control, but they only have 300 mA to 500 mA of current capability. Do you know of a stepper controller chip capable of driving the AIRPAX directly? I'd love to get this going so I can make a computer-controlled milling machine using my Shopsmith or my cross-slide and a Dremel tool.

**Jerry Rutherford**  
via Internet

**A.** There are several choices, as you'll discover from the companion article "Servos, Steppers, and Optical Encoders" on page 84, but for this particular application I'd use an L297 controller coupled with an L298 driver — both made by ST Semiconductors. Both chips are available from **Mouser Electronics** (1-800-346-6873; <http://www.mouser.com/>). About \$10.00 with shipping (Mouser Electronics doesn't have a minimum). Here's how to wire them together.

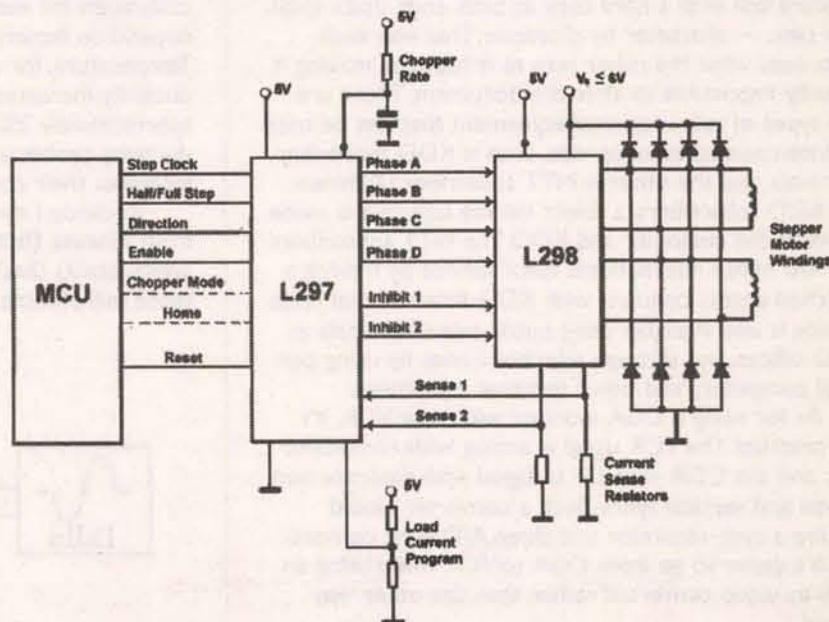


### GPS-Guided Robot

**Q.** I would like to build a mobile robot which utilizes GPS for navigation. Can you point me in the direction of a low-cost GPS receiver which I can use? I will be using a commercially available single-board computer (SBC) as the "brains" for the vehicle. Therefore, I must have detailed protocol specs for the receiver which describe how to initialize and communicate with the device via the SBC.

**K.A. Delahoussaye**  
via Internet

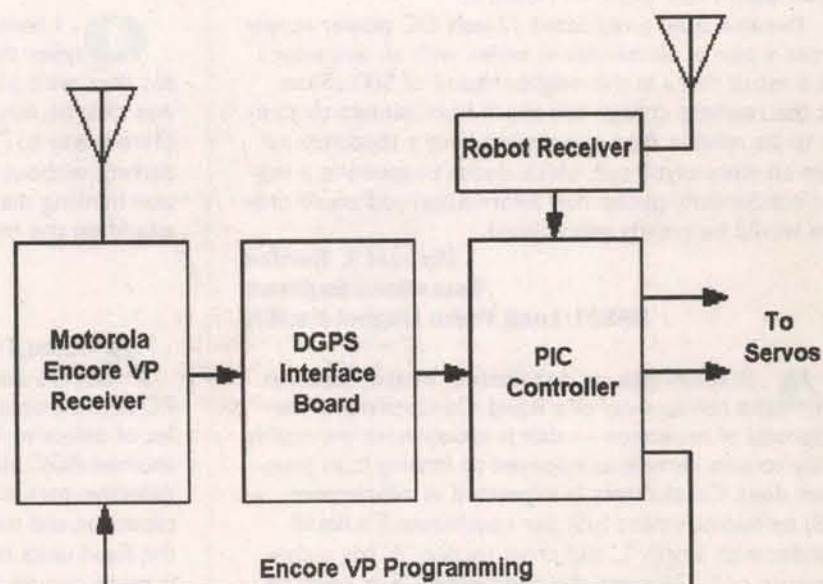**A.** I'd use the DGPS system outlined in the previous question. Here's a block diagram of what you want.



The receiver is a Motorola Encore VP (\$290.00), a PC board that measures




2 by 3 1/2 by 1/2 inches, and the decoder is the TAPR Digital GPS Reference Satation Interface Board (\$199.00); both are available from **Tucson Amateur Packet Radio** (940-383-0000; <http://www.tapr.org/gps/>). The output from the interface board is in the widely recognized RTCM SC-104 Type I Version 2.1 message format. The output is at RS-232 levels and can be processed by any device capable of receiving RS-232 serial data, like your SBC or, better yet, a PIC or Stamp chip. As before, the GPS receiver has to be programmed before use via an external PC. If you don't provide the optional battery backup, the programming will be lost when the power to the 'bot is turned off — well, kind of. Actually, the only thing lost is the almanac, which is a history of the satellites and their position. The receiver itself will re-acquire this information when power is reapplied, but it can take hours and not to the same degree of accuracy as the PC's initializing routine. So opt for the battery backup. For more details on putting this package together, check out the TAPR web site listed above.

### Auto Tune-Up


**Q** On automotive engine analyzers, there's a display that shows spark plug voltage on the y axis and time on the x axis. As the engine speed varies, so does the sweep rate of the x axis so that all eight spark plugs appear in a fixed position on the screen regardless of the engine RPM. If the sweep rate were fixed, the spark line would expand and contract as the engine speed changed. I need help designing a sweep circuit that keeps pace with the engine speed. I'll be using an inductive pickup to sense the ignition voltage.

Mike  
via Internet

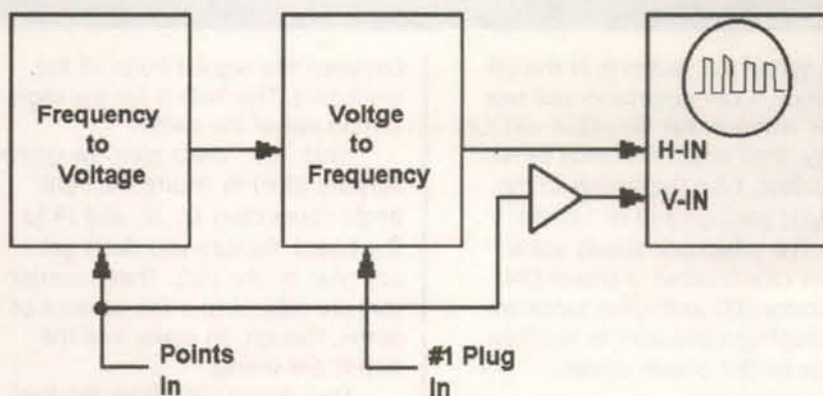**A** What you need is a tachometer to monitor the engine RPM and a circuit that converts this value into a tracking sawtooth waveform. For the tach, I'd use a frequency-to-voltage converter, then use its output to drive a voltage-controlled oscillator. Here's a block diagram.



Notice that the output of the new sweep generator replaces the internal sweep circuit of the oscilloscope, and plugs into the external horizontal input. This oscillator is triggered off the #1 spark plug sensor. The tach output voltage is generated from the signal derived from the wire that goes from the high-voltage coil to the top of the distributor cap, which is also fed to the vertical (y axis) input. Neither circuit is critical, and can be made using 555 chips.

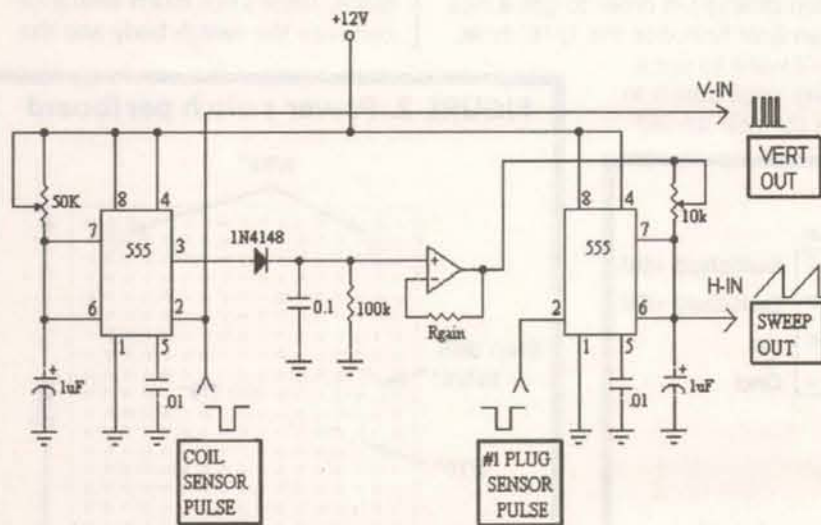

Both 555 chips are configured as monostable multivibrators. The first (left) is the tach F/V converter. Its output (pin 3) is rectified and filtered (1N4148, etc.), then buffered by an op amp. The gain of the op amp is set by  $R_{gain}$ , which changes according to the op amp you select (check out the National Semiconductor CLC series). The resultant output voltage charges the timing

Continued on page 83

## JUST ABOUT EVERYTHING YOU NEED FOR FAXES & PRINTERS IS AT ONE CONVENIENT ADDRESS:

# www.faxrepair.com

**For service, parts & sales, Cyber-Test is  
America's Largest Fax Support Center.**

- **CIRCUIT BOARD REPAIR** Component level repair on boards and power supplies for all brands & all models.
- **ENTIRE MACHINE REPAIR** We fix any thermal, ink jet or laser fax. Low flat rates available!
- **PARTS** We have a huge inventory of new & refurbished fax and printer parts ready to ship. Easy ordering with no part number necessary. H-P laser parts available!
- **SALES** Great deals on commercial grade plain paper faxes.
- **SUPPLIES** Drums, toner & developer for laser faxes or printers. Lowest prices anywhere for Okidata, AT&T, DEX and Samsung!
- **SUPPORT** Why go anywhere else? Check our Web Site or call today!



## 800-881-3344

press "6" for repair & sales

448 Commerce Way - Bldg. 100 - Longwood, FL 32750

Write in 56 on Reader Service Card.

ALLTECH ELECTRONICS		WE CHOP
WWW.COMPUTERCHOPPER.COM		PRICE\$!
<b>4X SCSI CD ROM</b> Matsushita CR504-L Apple CD 600i PC or Mac SCSI <b>\$19</b>	<b>486 Mini System</b> 486SX25 • Great for Linux DX266 Upgradable • 2 ISA Slots • VGA, LPT, 2COMs • FD <b>\$29</b>	<b>250VA Isolation Transformer</b> 115V Pri - 115V 250VA Sec Magnetek Triad 6" x 4" x 5" <b>\$39</b>
<b>10" Open Frame SVGA</b> Metal Enclosed - Displays Up to 1024 x 768 • 110V AC Also Available in a standard case. <b>\$119</b>	<b>6 SCSI CD's in a Tower</b> 6 CR-504-L Drives in a SCSI Tower <b>\$149</b>	<b>Ball Bearing Slide</b> Drawer Sliders • Extends 2' Three piece telescopic extension. See the web for more detail 6 Pair for <b>\$29</b>
<b>10" SVGA</b> The same 1024x768 .26dp monitor but with a slight burn in spot in the center. Our Pain is Your Gain! <b>\$59</b>	<b>Cellular Data Adapter</b> For Motorola Flip Phone and compatible. Use ANY landline device, modem, fax, etc. <b>\$39</b>	<b>9" Mono VGA</b> Small footprint monitor Great for servers, test benches, etc. 640 x 480 only. Refurbished. <b>\$49</b>
<b>9.75" Mono VGA LCD w/Controller</b> Great for Servers: Powered from the card Great for a headless system. Windows NT Server Console, Linux Server, etc. 16 Bit (ISA) Interface with Cirrus Logic GD6235 512K RAM. Non Upgradable Win95/98 Compatible 10" x 6.75" x 3/8" <b>\$89</b>		<b>Cheaper Ethernet Stuff</b> Industrial Surplus PC Parts • Mac Parts For more information on these products and hundreds of other products check out: <b>www.ComputerChopper.Com</b>
<b>760/724-2404</b> <b>Fax 760/724-8808</b> Computer Circulation Center, Inc. 2618 Temple Heights Drive Oceanside, CA 92056		Mon-Fri 9AM -5:30PM - Or see us on the internet. <b>VISA • Mastercard • Discover • American Express</b> Prices & Availability subject to change without notice • Government & Educational PO's Accepted. • Not Responsible for Typographical Errors

Write in 51 on Reader Service Card.

Nuts & Volts Magazine/AUGUST 1999 73



by Robert Nansel

## Chaos rules the Robot Ranch during the dog days of summer.

As I write, it is 95 degrees and muggy as all get out in Pittsburgh. We have one room that's air-conditioned (barely), so my brain hasn't boiled away, at least not yet. I've been working on the code for Breadbot's quadrature encoders, as well as the substantially more complicated I2C code for interprocessor communications for last month's multiprocessor DT111.

My hope is to get all this working on plain old 10MHz PIC16F84s, but I am finding the project to be very challenging, even without the heat to muddle my thought processes. Then, too, I'm in the middle of a major changeover in computer and OS (more on that later), and my six-month old son is teething. Did I mention that it's hot?

Anyway, when I get frustrated with slow progress on software — especially when it's 95 degrees — I retire to my basement workshop where it's cool, and I drill holes in things for a while. Though the code I promised last month isn't ready yet, the hole drilling did do some good: Breadbot now has a power switch board.

### Civilizing Breadbot

For more than a year, I've been directly plugging the +6V wire from the battery pack into Breadbot's breadboard. To turn Breadbot off, I've had to either remove the AA cells or yank the power wire. The

wire is stranded wire and tinned, so all this plugging and unplugging takes its toll, both on the breadboard and on the wire. Thoroughly uncivilized.

When I first built Breadbot, I looked around for a power switch I could plug into the breadboard, but I never found anything satisfactory. For Breadbot's latest brain transplant, I decided I should figure a way to add the switch, perhaps using the prototyping section of the DT111 where there would be plenty of room.

Not long after I installed the DT111, though, I discovered that it tended to be a bit wobbly plugged into the breadboard because it's twice the height of previous SIMMSticks I've used. The idea of adding still more mass to an already wobbly board no longer appealed to me, so I searched for another way.

While I was at it, I wanted to separate the servo power supply from the logic supply. Adding a 9V battery to power the logic is the way Parallax's GrowBot works, but where to put the battery on Breadbot?

The solution is shown in the photos and Figures 1 through 3. The board provides a place to mount the power switch and the 9V battery holder, and a mounting hole and spacer connect it rigidly to the DT111 so that neither board wobbles.

It's an easy circuit to build on perfboard. In Figure 1, SW1 is a three-position DPDT toggle switch, center position OFF. I wired SW1 so unregulated logic power from the 9V battery is applied in both of the ON positions, but the 6V servo motor supply is on only in the DOWN position.

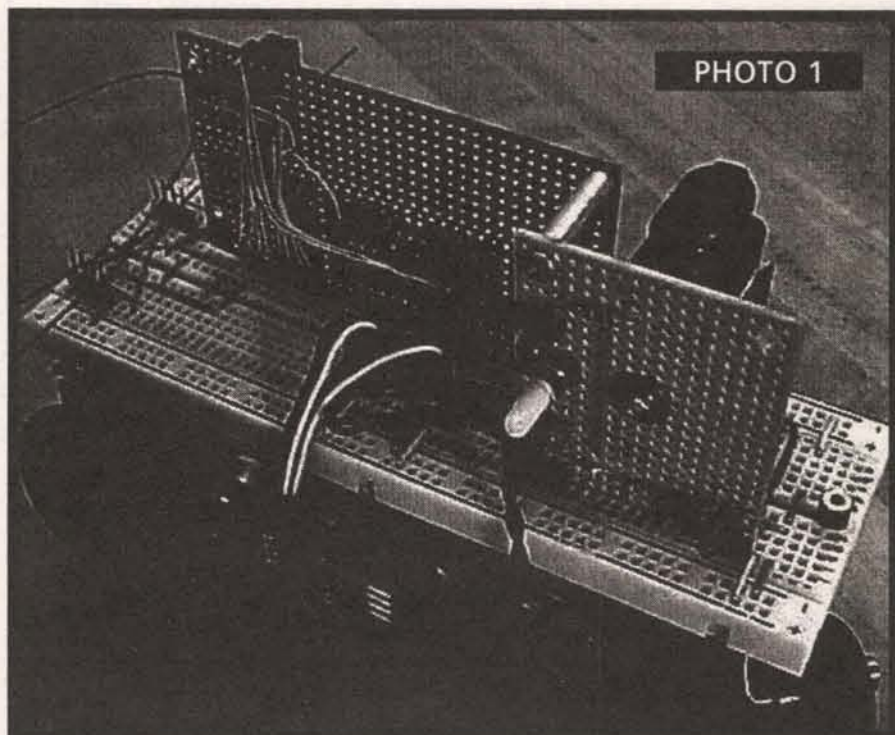


PHOTO 1

When the switch is in the UP position, I can download and test code without fear Breadbot will run away, then when I'm ready to run Breadbot, I flip the switch to the DOWN position and let her rip.

The schematic shows some other nice touches: a power-ON indicator LED and some tantalum decoupling capacitors to suppress noise on the power busses.

### Building the Board

Cut a piece of standard perfboard to the size shown in Figure 2 and drill the holes as shown. The 1/4" hole may require drilling one or two smaller intermediate holes ("step drilling") in order to get a nice clean final hole. For the 1/16" hole, you'll want to use a sharp prick punch to get the drill started

between the regular holes of the perfboard. This hole is for the registration tab of the switch.

Next, use "super glue" (a cyanoacrylate glue) to secure the right angle connectors J2, J3, and J4 to the board. Be sure you don't get any glue on the pins. These connectors are subject to a fair amount of stress, though, so make sure the bonds are strong.

Now install SW1 from the back side as shown in Figure 3. Orient the registration tab so it fits into the 1/16" hole beneath the 1/4" hole and tighten the hex nut on the front side of the board.

Next, test-fit the battery clip with an 1/8" pop rivet to hold it in place. There's not much clearance between the switch body and the

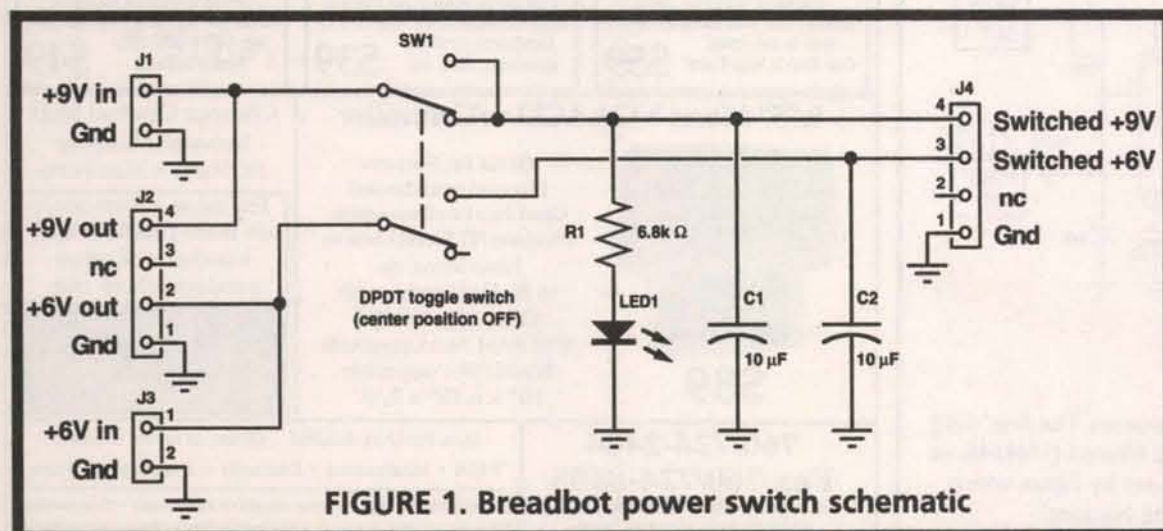


FIGURE 1. Breadbot power switch schematic

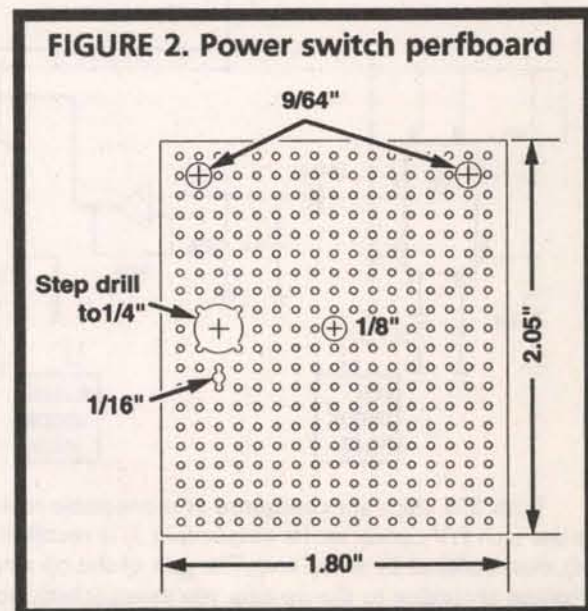


FIGURE 2. Power switch perfboard



clip, so make sure the clip won't be exerting any pressure on the switch when the 9V battery is in place.

Roughen the underside of the metal clip with sand paper to give more "tooth" for the glue to grab onto. Apply the glue to the clip, slip it and the pop rivet back into place on the back side of the board, add a riveting washer on the front side, and rivet the holder clip to the board. Be careful of orientation because you might not get a second chance with the glue. The rivet is to hold the clip securely to the board and the glue is to keep the clip from turning.

Place the remaining components, R1, LED1, C1, and C2, as shown and bend their leads to hold

the connector pins and against the board to provide extra mechanical strength for the connectors.

The capacitors are wired directly between ground and their respective switched voltage output pins on J4. R1 and the anode of LED1 are connected together just by bending their leads parallel to each other and flat to the board. The cathode of LED1 is connected to another run of bare bus wire that ties into the main ground bus. Solder, then trim leads.

## It's a Snap

The rest of the wiring is accomplished in three steps.


are the poles of the DPDT switch, and the upper and lower row lugs — four in all — are the "throws" or contacts of the switch with the lugs lining up in a column representing one half of the switch.

If you use a different switch,

connected so servo power is ON only when the switch is in the DOWN position.

The switch board plugs into Breadbot as shown with a 0.8" long by 1/4" diameter 4-40 threaded aluminum spacer to join it to the

FIGURE 4. The I2C bus

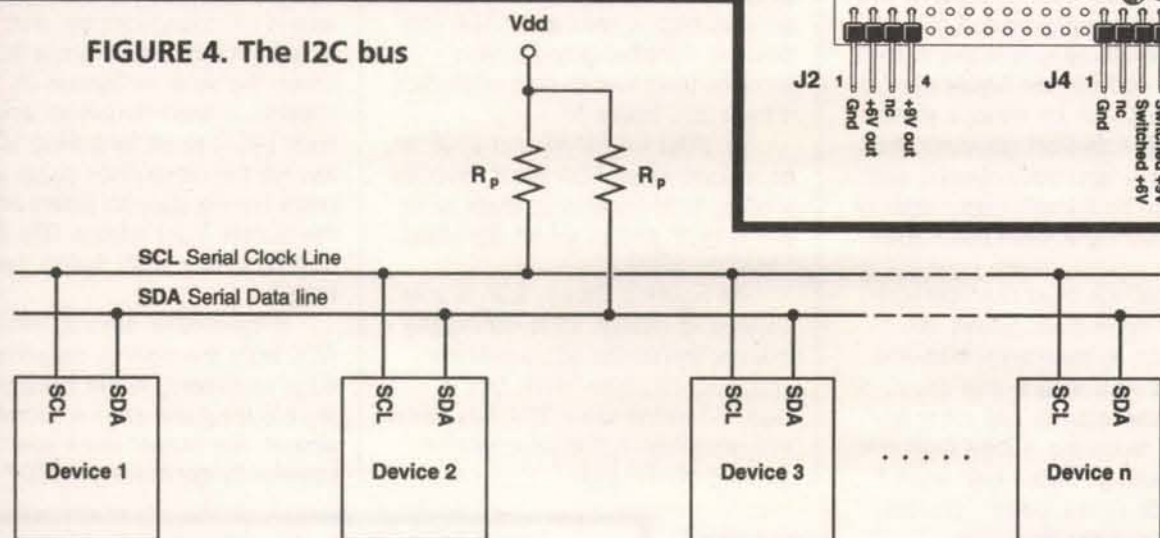

them in place while wiring. I did all ground connections first with 24 gauge bare bus wire on the front side of the board. I refer to this kind of construction as wire "stapling" or "stitching" because the ends of each bus wire run are bent at right angles (like a staple) and fed through the board to make the connections on the back side of the board.

I used needle-nose pliers to tightly form the wire ends around

First, wire the leads of J1 — a 9V battery snap-on connector — to the corresponding pins of J2. The twisted leads of J1 can be dressed to fit between the metal battery clip and SW1, though you may have to temporarily loosen the hex nut holding the switch so the switch can move enough to allow the wires to slip into place.

Second, make the connections to the switch. For the switch specified, the two center row solder lugs

then check with an ohmmeter to find out the proper arrangement of the contacts. The 6V and 9V power inputs are wired to the center lugs, and the switched outputs are taken off the upper and lower row lugs.

Third, wire the switched contacts to their respective switched 9V and 6V outputs on J4. The 9V side of the switch has both switched contacts wired together so 9V is ON in either switch position, while only the upper lug of the 6V side is con-

DT111. I cut my spacer from a longer spacer and filed it to size. In the photos it may appear that the top edges of the switch board and the DT111 aren't parallel as seen from the side. This is because the solderless breadboard chassis of Breadbot itself is curved. It's easy to compensate for this so the mounting holes line up with each other by adjusting how deep you plug J2 into the breadboard.

## Eye-Squared-See?

Last month, I gave a very brief overview of the I2C system. This time and next I aim to give a full introduction but, for the whole story, you'll need to consult various data manuals and appnotes from Philips Semiconductor.

If you find discrepancies between what Philips says and what

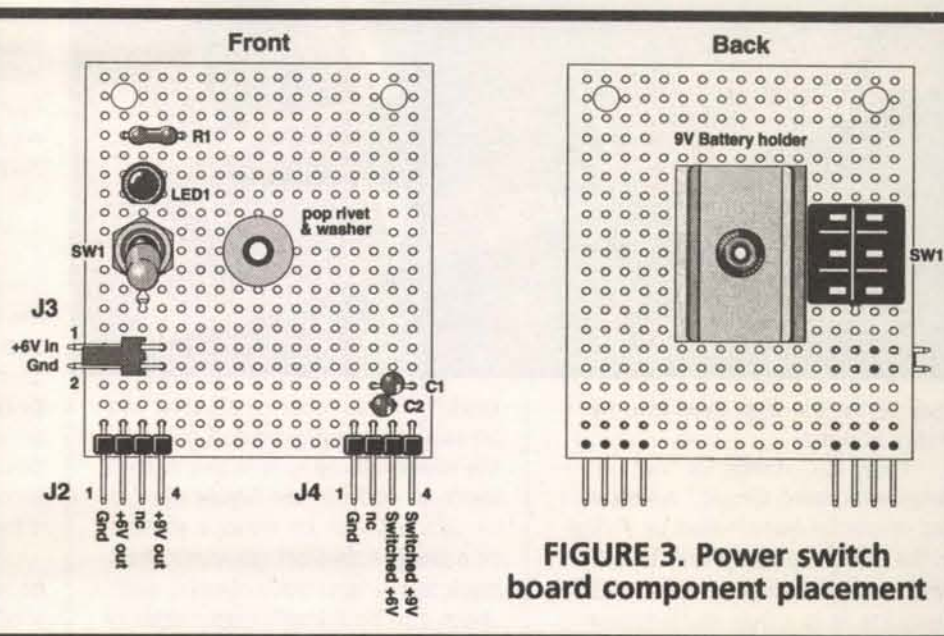


FIGURE 3. Power switch board component placement

## LIGHT WORKS USA™

By Miller Engineering


Electroluminescence  
Experimenters Kit!

\$22.95 plus \$3.00 S&H

This exciting kit is designed just for the experimenter! Kit includes one 1.7"x 3.75" white EL lamp that makes up to 6 EL lamps. Ready to run power supply that runs on two AAA batteries. Six color overlays and complete instructions and ideas on using this space age marvel.

Send To: Miller Engineering, P.O. Box 282,  
New Canaan, CT 06840-0282

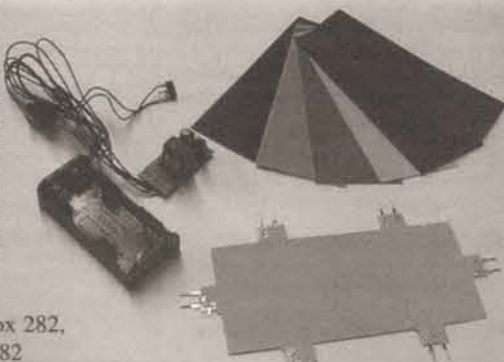Tel. 203-595-0619 Visa & Mastercard accepted. Personal checks must clear first. [www.microstru.com](http://www.microstru.com)



## USB Relay Module

Model JSB-210

Controls 8 to 16 "form C" relays over the USB (Universal Serial Bus). Program the module with simple commands in any program language that supports USB Communications. Driver and sample code provided

J-Works, Inc

12328 Gladstone St., Unit 4  
Sylmar, CA 91342

(818) 361-0787 Voice (818) 270-2413 Fax

### Other Products

RS-485 Remote I/O  
ISA Waveform Generator  
RS-485 to DS-1820  
RS-485 Temperature I/O  
DS-1820 Probe

Visit our Web site for  
Information on all our products  
<http://www.j-works.com>  
E-mail [sales@j-works.com](mailto:sales@j-works.com)



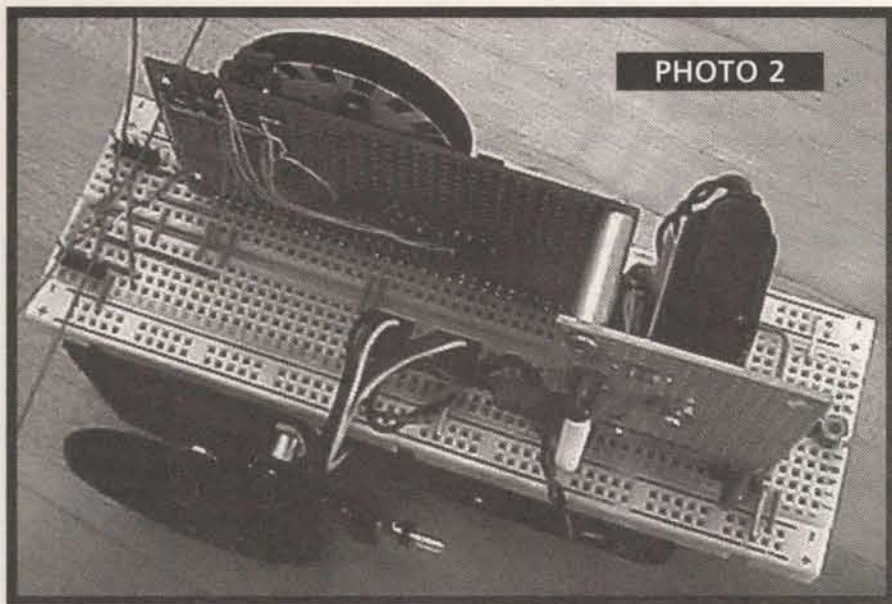


PHOTO 2

I say about the bus, then assume Philips is right.

Okay, I2C stands for "IIC" or "Inter-Integrated Circuit," a simple but powerful bus created by Philips in the 80s as a cheap way to network ICs in consumer electronics products. It is a true multi-master synchronous serial bus. It has collision detection and automatic arbitration to prevent data corruption should two or more masters attempt to transmit on the bus at the same time.

Only two lines are required, SCL (Serial Clock) and SDA (Serial Data). Bidirectional transfers can be made at up to 100 kbps in standard mode and up to 400 kbps in fast mode (I'll be talking only about standard

mode). The number of ICs that can be so networked is limited only by the maximum allowable bus capacitance of 400 pF (see Figure 4).

Each IC can be either a master or a slave — masters generate the clock SCL — and both masters and slaves can be either a transmitter or receiver during a given bus transaction.

All I2C ICs must use open-collector or open-drain drivers, or equivalent, to drive both SDA and SCL lines. This means that any IC on the bus can actively pull these lines low but, to output a logic high level, the IC must go into a high-impedance state so the pullup resistors ( $R_p$ ) can pull the lines high.

SDA and SCL are both bidirec-

tional, so each IC's data inputs are connected to the open-drain outputs. Thus, when an I2C IC reads the status of SDA or SCL, the level read reflects the status of the bus.

If the IC is outputting a logic low, then that's what the input will see, but if the IC is outputting a logic high, then the input will only see a high level if no other IC is asserting a logic low. This is the equivalent of an AND gate; the line will be high only if all the ICs are outputting logic high. Hence, this is often called a "wired AND" configuration.

To signal the beginning of a bus transaction, an IC must first wait for the bus idle state where both SDA and SCL are high for at least 4.7  $\mu$ s. The IC can then signal START by bringing SDA low while SCL remains high. Likewise, a STOP condition is signalled when SDA is brought from low to high while SCL is high (see Figure 5).

In order for START and STOP to be unique, then, SDA must never be allowed to change logic levels while SCL is high, except when signalling START or STOP.

As Figure 6 shows, SDA is only allowed to change state during the low portion of the SCL waveform and must be stable while SCL is high. Whatever value SDA has when SCL goes high is the value of that data bit on the bus.

## Ack! A Datagram

Any number of bytes can be transmitted or received in one datagram, but the simplest possible I2C bus datagram comes when a master reads or writes a single byte to or from a slave. In Figure 7, the top two waveforms in the figure are the data from the master and slave, respectively, that drive SDA, and the SDA waveform below them is the composite of the two open-drain data sources. The master addresses the slave (binary address 0111000), then reads the binary data 0110101 from the slave.

The transaction goes like this: First, the master generates the START condition then acts as a transmitter to send the seven-bit address of the slave. The eighth bit sent is the read/write bit, and the logic high indicates this is a READ. When the slave recognizes its address, it must output an acknowledge (ACK) pulse by pulling SDA low for the ninth clock pulse. In order for the slave to assert ACK, the master must release SDA by outputting a logic high during that time.

If the master doesn't receive an ACK from the slave (a no acknowledge condition), either because the slave is busy and can't respond or is absent, the master must abort the transfer by generating a STOP

FIGURE 5. I2C START and STOP conditions


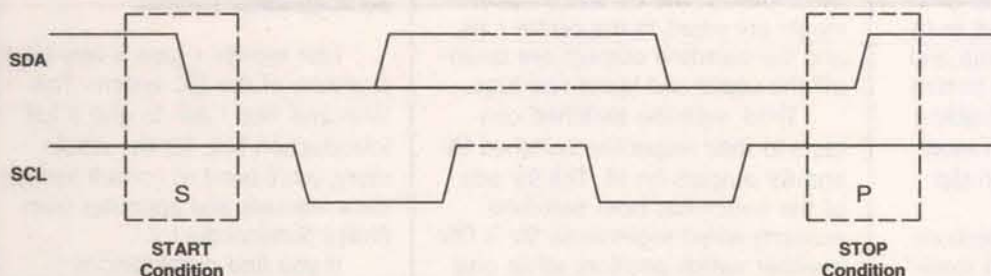


FIGURE 6. Relationship between I2C Data & Clock

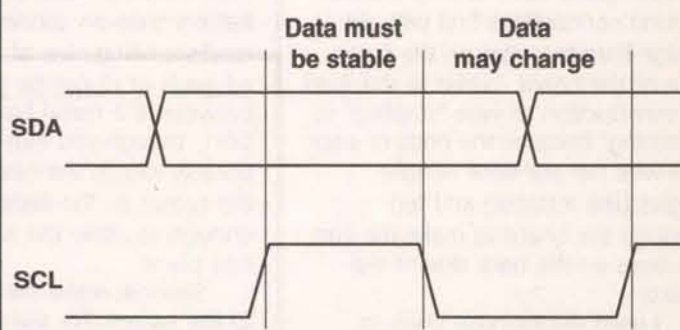

## LASERS & ACCESSORIES

### HELIUM NEON LASERS

- ☒ Complete Systems
- ☒ Plasma Tubes
- ☒ Power Supplies

### ACCESSORIES

- ☒ Optics
- ☒ Electro-Optics
- ☒ IR Viewers
- ☒ Books & More



**MEREDITH**  
**INSTRUMENTS**

### DIODE LASERS

- ☒ Visible / IR
- ☒ Complete Modules
- ☒ Collimating Optics
- ☒ Drive Circuits

### FREE CATALOG

WEB SITE:  
[www.mi-lasers.com](http://www.mi-lasers.com)

Phone: 602-934-9387 • Fax: 602-934-9482

## EZ-EP DEVICE PROGRAMMER - \$169.95

Check Web!! -- [www.m2l.com](http://www.m2l.com)

**Fast** - Programs 27C010 in 23 seconds

**Portable** - Connects to PC Parallel Port

**Versatile** - Programs 2716-080 plus EE and flash (28, 29) to 32 pins

**Inexpensive** - Best for less than \$200

• Correct implementation of manufacturer specified algorithms for fast, reliable programming.

• Easy to use menu based software has binary editor, read, verify, copy, etc. Free updates via bbs or web.

• Full over current detection on all device power supplies protects against bad chips and reverse insertion.

• Broad support for additional devices using adapters listed below.

### Available Adapters


EP-PIC (18C5x, 81, 82x, 71, 84)	\$49.95
EP-PIC64 (18C62-5, 72-4)	\$39.95
EP-PIC12 (12C50x)	\$39.95
EP-PIC17 (17C4x)	\$49.95
EP-51 (8751, C51)	\$39.95
EP-11E (68HC11 E/A)	\$59.95
EP-11D (68HC11D3)	\$39.95
EP-16 (16B EPROMs)	\$49.95
EP-28 (286E02, 3, 4, 6, 7, 8)	\$39.95
EP-SEE2 (93x, 24x, 25x, 85x)	\$39.95
EP-750 (87C750, 1, 2)	\$59.95
EP-PEEL (ICT22v10, 18v6)	\$59.95
EP-1051 (89C1051, 2051)	\$39.95
EP-PLCC (PLCC EPROMs)	\$49.95
EP-SOIC (SOIC EPROMs)	\$49.95
EP-TSOP (TSOP EPROMs)	\$59.95
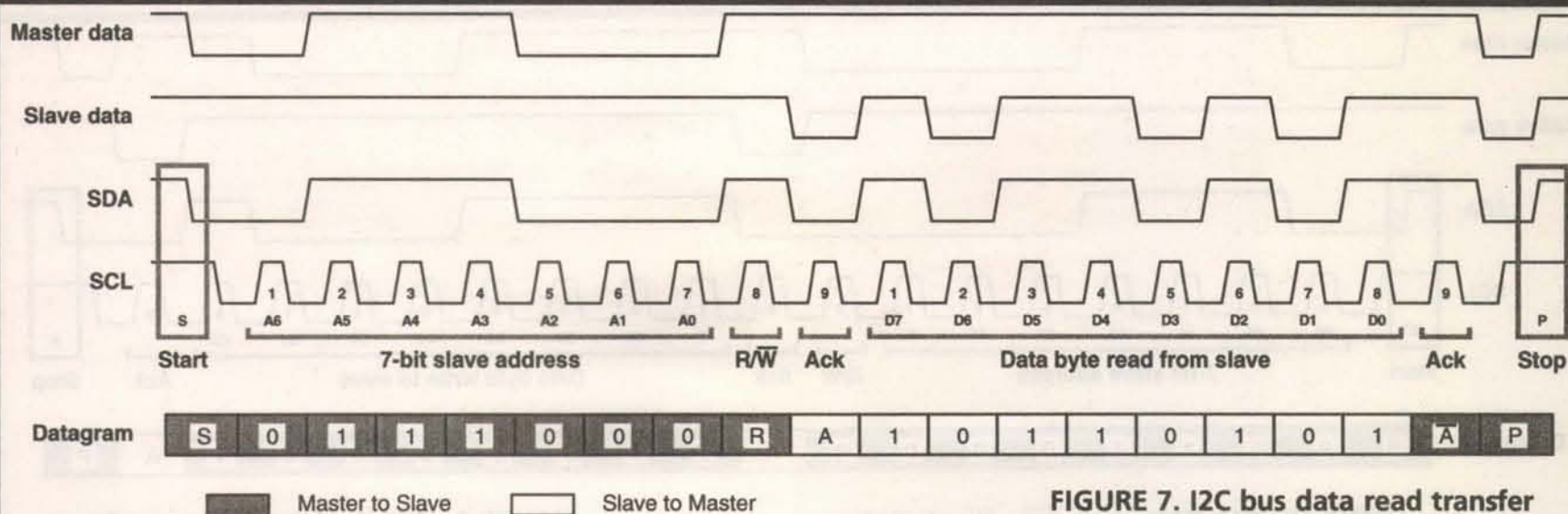
### M<sup>2</sup>L Electronics

970/259-0555  
Fax: 970/259-0777  
250 CR 218  
Durango, CO 81301  
CO orders please add 7% sales tax.  
<http://www.m2l.com>







condition.

Assuming the slave is present and able to respond, though, the slave becomes the transmitter; it ACKs, then drives its data bits onto SDA, and the master clocks them in. Again, the master must release SDA so the slave can drive its data onto the line.

## ACK or NACK?


On the I2C bus, each byte transmitted must be acknowledged by the IC that receives the byte, with the following exceptions: 1) when a slave-receiver cannot receive any more data (its data buffer is full, for instance); or 2) when a master-receiver wants to signal that a read operation is done. In these cases, the receiver generates a not acknowledge (NACK) pulse by releasing SDA to float high during the ACK clock pulse. A slave-receiver in this situation must then release SDA.

Another way of saying this is an acknowledgment of a byte received from a slave is always necessary except on the last byte received. Why? An I2C slave will keep transmitting data unless it's told not to.


If the master generated a normal ACK pulse, the slave would again seize control of SDA to transmit the first bit of the next byte. If that bit happened to be a zero, the master would be unable to generate a STOP condition because the slave would be holding SDA low waiting for the next clock pulse.

But, if during the ACK clock pulse, the master leaves SDA high, then the slave knows it must release SDA and not drive with it with new data after the ACK cycle is over. In this way, the master is free to bring SCL high then bring SDA high to create the STOP condition.

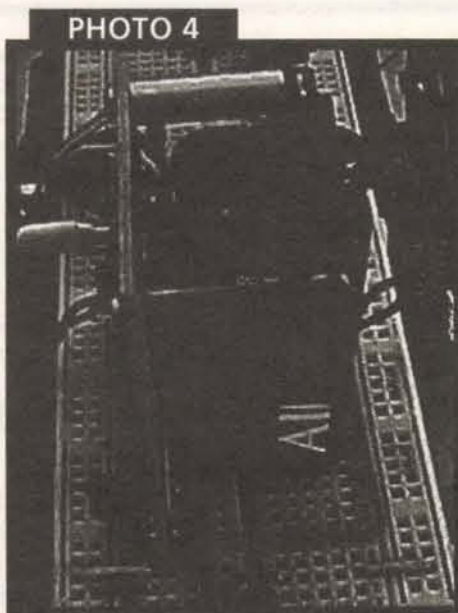Note that NACK is not the same as a no acknowledge condition. Both involve SDA being high during an ACK clock pulse, but NACK is the master telling the slave not to transmit another byte, while no acknowledge is the state of the bus when a slave can't respond to a



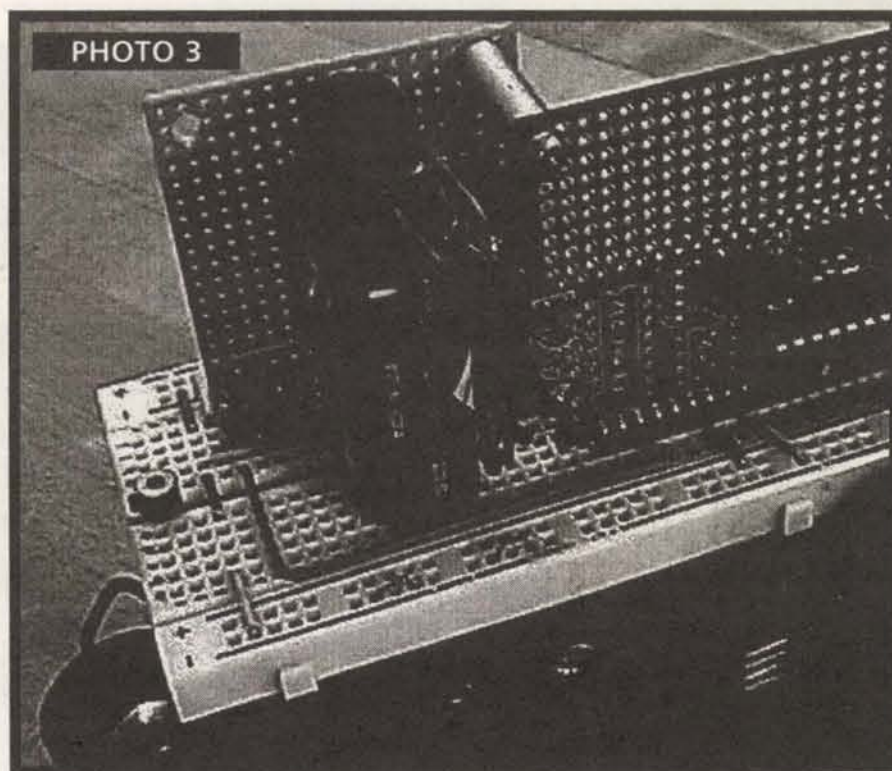master. Because Figure 7 depicts a single-byte read transfer, when that data byte is read, it is, perforce, the last byte, so the master must generate a NACK.



# Honey, I shrunk the COMPUTER!



PicStics are like BASIC Stamps® on steroids. They have more speed, more parallel I/O, more code and data space, and more neat features like a real-time clock, 12-bit ADC, and 12-bit DAC.

**As low as \$29**

**Call for a  
catalog or visit  
our Web site  
today.**

**www.micromint.com**



740 Florida Central Pkwy., Longwood, FL 32750

BASIC Stamp is a registered trademark of Parallax, Inc.

# PRIMECELL

**IF YOU NEED NEW BATTERIES FOR YOUR ELECTRONIC EQUIPMENT  
DON'T PITCH EM' - SEND THEM FOR REBUILDING ! - SAVE \$ \$**

CUNARD ASSOC. INC., 9343 US RT 220, Bedford, PA 15522

- WE INSTALL NEW NI-CAD OR NI-MH BATTERIES INTO YOUR ORIGINAL CASE.
- WE IMPROVE CAPACITY TO BETTER THAN ORIGINAL.
- WE FIX WHAT CAN'T BE FOUND, (OR AFFORDED)
- WE PROVIDE QUICK SERVICE / EXTENDED LIFE FOR OLDER EQUIPMENT
- WE OFFER FREE QUOTES. / FREE RETURN IF QUOTE IS REFUSED.
- WE PROPERLY DISPOSE OF YOUR OLD CELLS BY RECYCLING.
- WE GIVE YOU A 12 MONTH WARRANTY.
- WE WILL BE HERE WHEN YOU NEED US / EST. 1986
- WE SAVE YOU \*\*\*\* MONEY \*\*\*\* \$\$\$





GENERAL ELECTRIC		UNIDEN		RADIO SHACK	
19A704850P(1200mAH)	\$ 34.95	APX650 1050	\$ 29.95	HTX Packs	\$ 29.95
19A704860P(1800mAH)	\$ 39.95	1000 1010 1070	\$ 34.95	New 8.4V pack & charger	\$ 29.95
PL19D429763(777)G1/3	\$ 37.95	1100 1200 Series	\$ 36.95	1500mAH nimh	\$ 34.95
19A705293P 344A4506P	\$ 34.95	BP205 650mAH	\$ 19.95	<b>KENWOOD</b>	
		BP200 1500mAH	\$ 24.95	PB2 / KNB3	\$ 29.95
MAXON SA-1155 1160	\$ 39.95	SC150 1500mAH	\$ 22.95	PB21/H1	\$ 14.95
TAD 1450 1510 1520	\$ 21.95			PB25/H26	\$ 24.95
<b>MOTOROLA</b>		<b>ICOM</b>		<b>CORDLESS DRILLS</b>	
P200 HT600 MT1000		BP2 / BP3 / BP22	\$ 18.95	Any brand 7.2V	\$ 18.95
NTN 4585 4824 5414	\$ 37.95	BP5 / BP23 / 24	\$ 24.95	Any brand 9.6V	\$ 29.95
NTN 5447 5521 5545	\$ 37.95	BP7 / CM7 / BP8	\$ 32.95	Any brand 12.0V	\$ 32.95
NLN 5860 NTN 4327	\$ 39.95	BP180 / CM79	\$ 34.95	Any brand 14.4V	\$ 37.95
<b>MIDLAND</b>		<b>YAesu</b>		Any Brand 18.0V \$ 45.95	
70-B10 B16 B19 B21	\$ 39.95	FNB 3 4 12 14 16	\$ 32.95	<b>COMPUTER PACKS</b>	
B25 B26 B32 B36 B60	\$ 39.95	FNB19 21 26 27 35	\$ 23.95	Send battery for quote	
		FNB 10 11 17 25 35	\$ 29.95		

FOR INFORMATION ABOUT YOUR REQUIREMENTS ..... CONTACT US:  
PHONE OR FAX : (814) 623-7000 E-MAIL TO: PRIMECELL @ AOL.COM  
SEND YOUR PACKS FOR FREE QUOTATION VIA UPS, RPS OR US MAIL  
VISIT OUR WEB SITE <http://members.aol.com/primecell/primecell.htm>

## BATTERY REBUILD SERVICE

MANY OTHERS AVAILABLE - WRITE OR CALL  
**FREE CATALOG**  
ADD \$4.50 SHIPPING & HANDLING PER ORDER

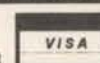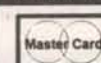



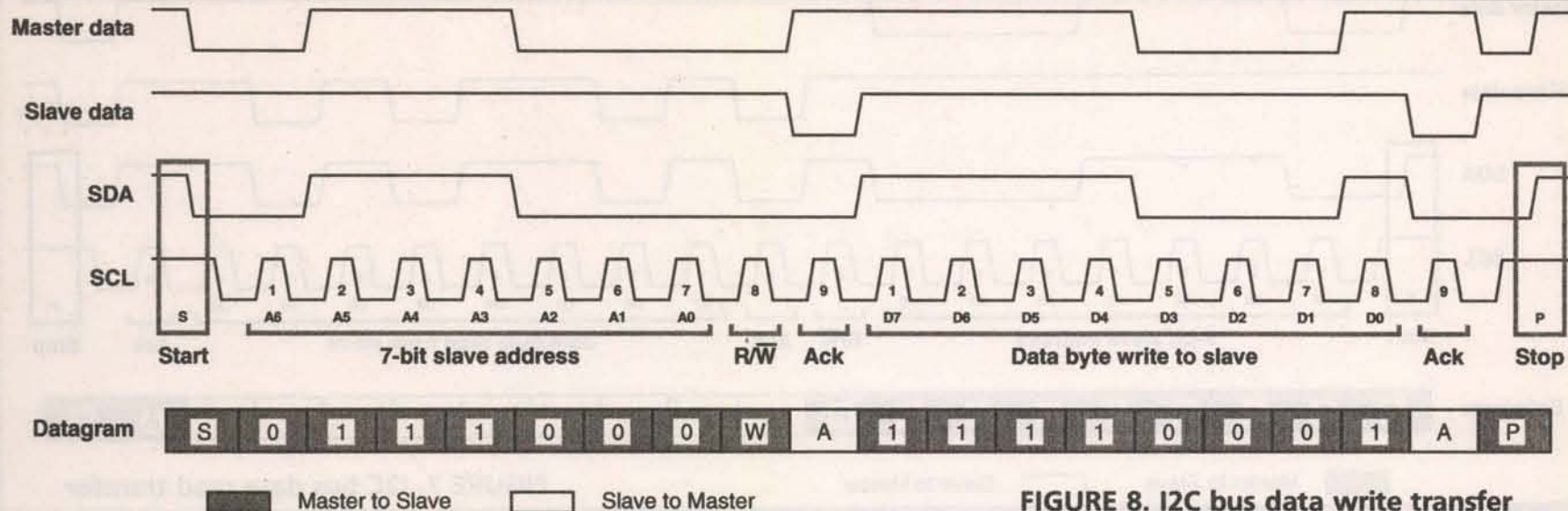


FIGURE 8. I2C bus data write transfer

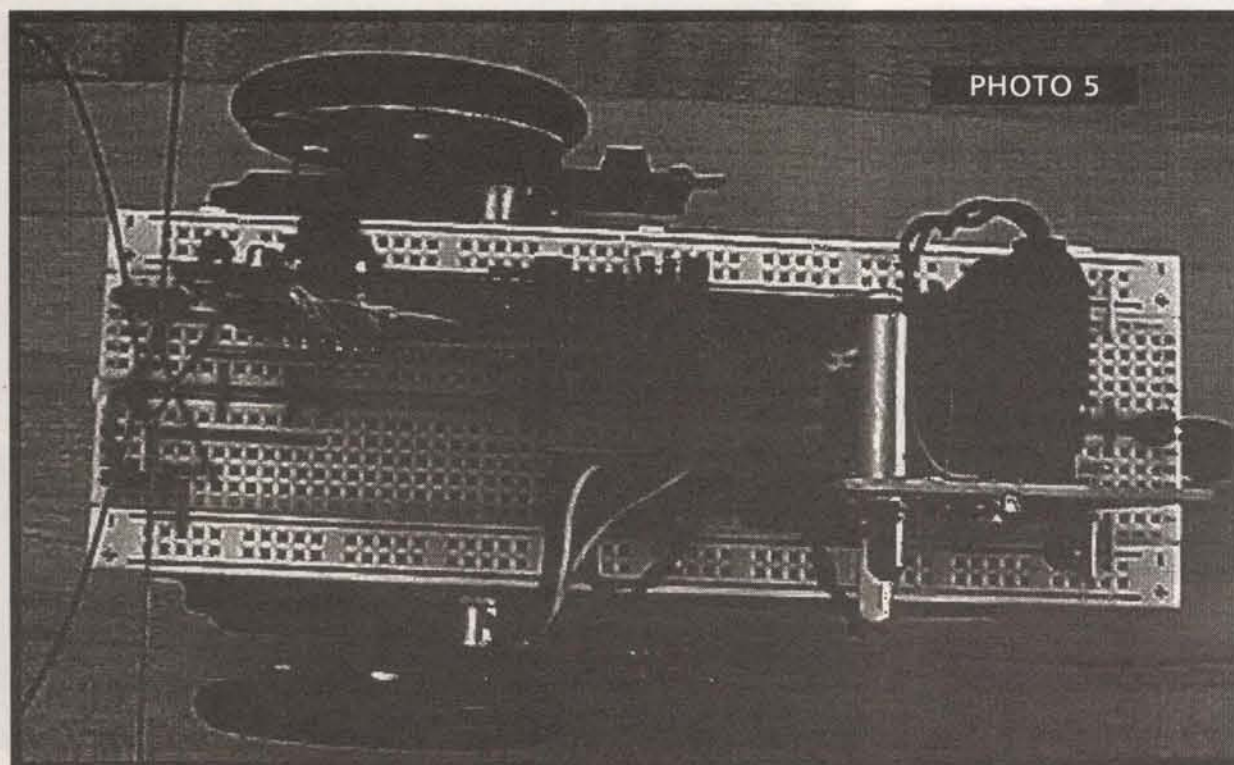


Figure 8 shows a data write operation where the binary data 11110001 is being written to the

same slave as in Figure 7. Since this is a write, the master is in control of SDA except during the ACK cycles

so there is no problem with generating a STOP condition. (If your head isn't ready to

explode yet, then you either already know all about I2C or you weren't paying attention. Go back and reread the above sections a few times until it all makes sense).

Next time, I'll get into the intricacies of multi-master bus arbitration, clock synchronization, and the timing parameters of the SDA and SCL waveforms. Now, though, I'll switch topics to my new ...

### Robot Development System

The beginnings of my robot development system came when I realized about six months ago that I could no longer afford commercial development software. It's not just a matter of money (though that is an issue), but of time and energy expended getting commercial apps to work.


I spend a significant amount of time recovering from application crashes. I'm not talking about experimental, use-at-your-own-risk beta versions, but well-established, supposedly solid commercial programs.

## A DEGREE ON A DISK!

Electro Science Applications Inc.  
EM FORMULARY

File Formulas Conversions Data Search Tables Windows Help

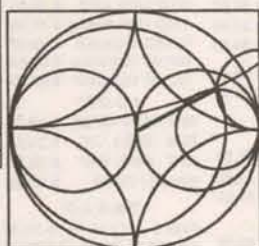smith chart  
smith chart  
solar law  
solar array area  
solenoid B  
solenoid inductance  
solid angle  
space charge current  
space loss  
specific absorption rate  
specific impulse  
sphere capacitance



- 500+ formulas and simulations
- Unit conversions and data tables
- Physical constants
- Electronics, communications, radar
- Antennas, filters, optics
- Physics, math, space science
- Practical and educational

Self-contained and intuitive, you'll be up and running in minutes. Fast menu and hyper-linked access to equations and data. Current version 1.7 works with Windows 3.1, 95, or 98.

ELECTRO SCIENCE APPLICATIONS, INC.  
P.O. BOX 11158, TORRANCE, CA 90510

To order, call (310) 539-2422 or E-Mail esa@earthlink.net  
Send \$29.95 check or money order (CA residents add 8.25% sales tax).  
Foreign orders add appropriate shipping charge.

Electronic and RF design services also available.  
Visit us at <http://www.esap.com>

Weeder Technologies

ON-LINE  
CATALOG  
[www.weedtech.com](http://www.weedtech.com)

Pro-Kit

PO Box 2426, Ft. Walton Beach, FL 32549

Voice/Fax 850-863-5723

### Stackable RS-232 Kits

**Digital I/O** - 12 I/O pins individually configurable for input or output. DIP switch addressable; stack up to 16 modules on same port for 192 I/O points. Turn on/off relays. Sense switch transitions, button presses, 4x4 matrix decoding using auto-debounce and repeat. **\$32**

**Analog Input** - 8 input pins. 12-bit plus sign self-calibrating ADC. Returns results in 1mV steps from 0 to 4095. Software programmable alarm trip-points for each input. DIP switch addressable; stack up to 16 modules on same port for 128 single-ended or 64 differential inputs. **\$49**

**Home Automation (X-10)** - Connects between a TW523 and your serial port. Receive/transmit all X-10 commands with your home-brewed programs. Full collision detection with auto re-transmission. **\$39**

**Caller ID** - Decodes the caller ID data and sends it to your serial port in a pre-formatted ascii character string. Example: \*12/31 08:45 850-863-5723 Weeder, Terry <CR>. Keep a log of all incoming calls. Block out unwanted callers to your BBS or other modem applications. **\$35**

**Touch-Tone Input** - Decodes DTMF tones and sends them to your serial port. Keep a log of all outgoing calls. Use with the Caller ID kit for a complete in/out logging system. Send commands to the Home Automation and/or Digital I/O kits using a remote telephone. **\$34**

### IR Remote Control Receiver

Learns and responds to the data patterns emitted by standard infrared remote controls used by TVs, VCRs, Stereos, etc. Lets you control all your electronic projects with your TV remote. 7 individual output pins can be assigned to any button on your remote, and can be configured for either "toggle" or "momentary" action. **\$32**

### Telephone Call Restrictors

Two modes of operation; either prevent receiving or placing telephone calls (or call prefixes) which have been entered into memory, or prevent those calls (or call prefixes) which have "not" been entered into memory. Use touch-tone phone to program.

Block out selected outgoing calls. Bypass at any time using your password. **\$35**

Block out selected incoming calls. Calls identified using Caller ID data. **\$46**

### Phone Line Transponder

7 individual output pins are controlled with buttons 1-7 on your touch-tone phone. Automatically answers telephone and waits for commands. Monitor room noises with built in mic. "Dial-Out" pin instructs unit to pick up phone and dial user entered number(s). Password protected. **\$49**

### DTMF Decoder/Logger

Keep track of all numbers dialed or entered from any phone on your line. Decodes all touch-tones and displays them on a 16 character LCD. Holds the last 240 digits in non-volatile memory. Connect directly to radio receiver's speaker terminals for off-air decoding of repeater codes, or numbers dialed on a radio program. **\$55**



And I still get hangs and crashes at least three times a week. I've done all the usual stuff with Norton Utilities and have spent countless hours on the phone with the software companies, but none of it helps.

Now, I'm a confirmed Mac user, but I do use DOS and Windows for certain purposes. And, even though I find the Mac easier to use for most jobs, I see no difference at all between my Mac and DOS and Windows machines in the number of application crashes that also crash the OS. Commercial software — especially commercial operating systems — devour too much of my time.

There is out there, though, an OS legendary for almost never crashing, with uptimes measured, not in days, but in months and years.

## Linux.

Individual applications may still crash, but they don't take Linux down with them. And Linux is very low-cost (free if you download it). To understand Linux's extraordinary reliability, take a look at the Linux resource sidebar. In particular, I recommend reading the papers by Eric

S. Raymond. I knew there was something special going on in Open Source software, but I didn't really understand why until I read these papers. Recommended.

There's not much mobile robotics development software commercially out there anyway, Mac or PC, and what there is I can't afford. This points toward leveraging public domain and university AI software and research, and using free software programming tools wherever possible. Most university software is meant to run under some version of Unix, and hence, will run under Linux.

## More Horsepower

On the hardware side, I'll use current generation desktop ATX motherboards to develop code for next generation embedded controllers. Don't worry, I'm abandoning neither Breadbot nor low-end microcontrollers. I want to increase the amount of computing power I can throw at some problems, that's all.

The advantage is that desktop motherboards are dirt-cheap, standardized, and universally available;

Item	Description
C1,C2	10 $\mu$ F, 16V tantalum
J1	2-pin right angle male Waldom connector
J2, J4	4-pin right angle male header
J3	9V transistor battery snap connector
LED1	Red high efficiency LED
R1	6.8k ohm, 1/4 W, 5%
SW1	DPDT switch, 3-position, center OFF (RadioShack #275-1545 or similar)
Misc:	0.8"x1/4" dia. 4-40 threaded aluminum spacer 1.80"x2.05" perfboard, 1/10" hole spacing

PARTS

## I2C links:

[www-us2.semiconductors.philips.com/i2c/](http://www-us2.semiconductors.philips.com/i2c/)  
[www.ping.be/~ping0751/i2cfaq/i2cfaq.htm](http://www.ping.be/~ping0751/i2cfaq/i2cfaq.htm)  
[www.mcc-us.com/i2chowto.htm](http://www.mcc-us.com/i2chowto.htm)

## Linux and Open Source Software links:

### Free Software Foundation

59 Temple Place, Suite 330, Boston, MA 02111-1307  
 Voice: 617-542-5942 • Fax: 617-542-2652  
[www.fsf.org](http://www.fsf.org)  
[www.gnu.org](http://www.gnu.org)

### The Linux Home Page

[www.linux.org](http://www.linux.org)

### The Linux Journal

[www.linuxjournal.com](http://www.linuxjournal.com)  
 (the oldest paper magazine devoted to Linux)

### Linux Magazine

[www.linux-mag.com](http://www.linux-mag.com)  
 (a new upstart paper 'zine)

### The Linux Mail

[www.linuxmail.com](http://www.linuxmail.com)  
 (news source, retailer of cheap Linux distributions, t-shirts, mugs, etc.)

### Open Software Foundation

#### The Open Group

1010 El Camino Real, Suite 380, Menlo Park CA 94025-4345  
 Tel: (650) 323-7992 • Fax: (650) 323-8204  
[www.opengroup.org](http://www.opengroup.org)

### uCLinux:

[ryeham.ee.ryerson.ca/uClinux/](http://ryeham.ee.ryerson.ca/uClinux/)  
 (Small footprint Linux for embedded processors without MMUs)

## Papers by Eric S. Raymond:

### "The Cathedral and the Bazaar"

[www.tuxedo.org/~esr/writings/cathedral-bazaar/](http://www.tuxedo.org/~esr/writings/cathedral-bazaar/)


### "Homesteading the Noosphere"

[www.tuxedo.org/~esr/writings/homesteading/](http://www.tuxedo.org/~esr/writings/homesteading/)

### "The Magic Cauldron"

[www.tuxedo.org/~esr/writings/magic-cauldron/](http://www.tuxedo.org/~esr/writings/magic-cauldron/)

## Any waveform you want!

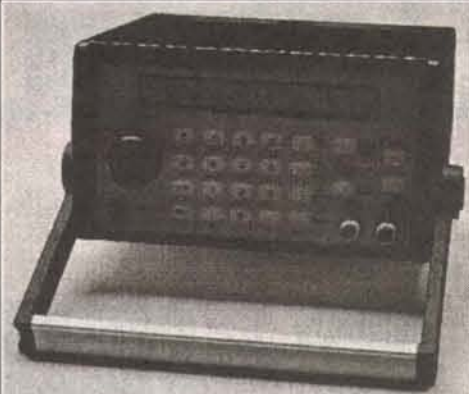

Telulex Inc. model SG-100A

New Features:  
 ✓ 21.5 MHz  
 ✓ .01 Hz steps  
 ✓ multi-unit phaselock

**Telulex Inc.**

### ● Synthesized Signal Generator

Clean sinewaves DC-21.5 MHz with .001% accuracy!  
 .01 Hz steps. DC Offset. RS232 remote control.

### ● Arbitrary Waveform Generator


40 Megasamples/Second. 32,768 points. 12 bit DAC

### ● Function Generator

Ramps, Triangles, Exponentials, Noise & more.  
 0 to 2 MHz in 1 Hz steps. Continuous or Triggered.
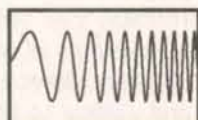
### ● Pulse Generator


Digital waveforms with adjustable duty cycle



DC to 21.5 MHz linear and log sweeps




Int/Ext AM, SSB, Dualtone Gen.

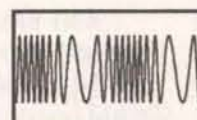


Int/Ext FM, PM, BPSK, Burst




Ramps, Triangles,

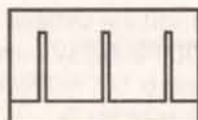


Pulse Generator

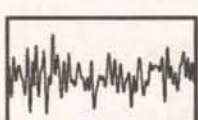

Noise

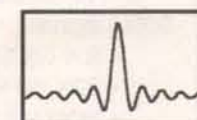

Arbitrary Waveforms

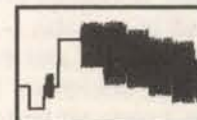

Unlimited Possibilities!

2455 Old Middlefield Way S  
 Mountain View, CA 94043

Tel (650) 938-0240

Fax (650) 938-0241

<http://www.Telulex.com>

Email: [sales@Telulex.com](mailto:sales@Telulex.com)



## A/D CONVERTERS with SERIAL OUTPUT

Tiny (1.75"x1.41") fully assembled and tested printed circuit board includes two 8-bit A/D converters and one digital input. Up to 16 units addressable (DIP switch setting) totalling 32 converters on a single serial port. Output is ASCII encoded bit count (0 to 255) at 2400 BPS via RJ-11 interface. Fully programmed PIC16C71 installed in IC socket. Sample software in BASIC included. Requires 8-28Vdc At 1-2mA. \*\$49.95\*. Optional DC adapter \$19.95. Add \$5.00 shipping.



Tele: 847-891-2584  
Fax: 847-891-2587  
www.glentech-rf.com

## SURPLUS SALE

### 1,000,000 WALL TRANSFORMERS



3VDC/100MA .... CX099 .... \$0.75  
6VDC/100MA .... CS039 .... \$1.45  
9VDC/100MA .... CR314 .... \$1.45  
12VDC/200MA .... CS033 .... \$0.99  
13.5VAC/400MA... CR574 .... \$1.29  
24VDC/500MA ... CR174 .... \$3.40

Min 1000/type -- Call for other types

## SURPLUS TRADERS

PO Box 276,  
Albany, VT 05440  
Tel: (01) 514-739-9328  
Fax: (01) 514-345-8303  
http://www.73.com/w

**FREE CATALOG!**

## PROGRAMMERS OVER 50 MODELS

ADVANTECH EETOOLS NEEDHAMS DATA I/O ICE TECHNOLOGY HILO  
SYSTEM GENERAL CHROMA MODULAR CIRCUIT TECHNOLOGY XELTEK



PROMAX EMP-20 MEGAMAX MEGAMAX4 SIMM/SIP TESTER EMUPA  
CALL ADVANTECH LABTOOL 599 EETOOLS SIMMAX  
629 ICE TECH MICROV 795 CHROMA SIMM/SIP  
650 EETOOLS ALLMAX + 359 MOD-MCT-EMUPA/R  
409 EETOOLS MEGAMAX 279 MOD-MCT-EMUPA/R  
509 EETOOLS MEGAMAX4 49 EPROM 1G TO 512K  
369 XELTEK SUPERPRO II 69 EPROM 1G TO 1MEG  
409 XELTEK SUPERPRO II P 99 EPROM 4G TO 1MEG  
249 XELTEK SUPERPRO L 199 EPROM 1G TO 1MEG  
165 XELTEK ROMMASTER II 89 EPROM 1G TO 8MEG  
479 MOD-MCT-EMUPA 129 EPROM 4G TO 8MEG  
739 STAG ORBIT-32 250 EPROM 8G TO 8MEG



LABTOOL48 MICROMASTER SUPERPRO ALLMAX PLUS ROMMASTER2

**General Device Instruments**

Sales 916-393-1655 Fax 916-392-4949

Web www.generaldevice.com E-Mail icdevice@best.com

## BATTERY — YUASA



Sealed Lead-Acid/Gel-Cell  
12V: 7AH \$19, 2.3/4AH \$16  
18AH \$39, 1.2AH \$13  
6V: 4AH \$9, 10AH \$13

Quantity Discounts Available  
Call for other models

## Aventrade

4518 Temple City Blvd., Temple City, CA 91780  
Tel. 626-286-0118 Fax 626-287-9618  
E-Mail: sales@aventrade.com  
www.aventrade.com

## Serial Port Problems ???

No heavy, aging serial protocol analyzer available? Use Serial to turn your PC into a test tool for asynchronous serial communications. Serial uses your PC serial ports to capture data, control and time stamps to give you what's needed to develop or debug your serial communications.

- Captures Data & Control lines
- Contextual Help
- Autobaud Detect
- Block Transmit
- Millisecond Timing
- Trigger Strings
- Extensive Manual
- Full Duplex Monitoring

Serial with manual US\$99.00  
Full Duplex monitor cable US\$40.00

Allison Technology Corporation  
2006 Finney Valley Rd., Rosenberg, TX 77471  
800-980-9806 or 281-239-8500, Fax: 281-239-8006  
http://www.atcweb.com atc@accesscomm.net

## JUNE SPECIAL SAVE \$10.00

### SHIELDED LOOP RECEIVER

30M, 40M KITS W/ ANTENNA.  
VERY SENSITIVE. HAS HIGH  
IMMUNITY TO QRN & LOCAL  
AM BROADCAST.. \$92.50 PP

### 12/14V PULSE BATTERY TESTER

(LEAD ACID). ATTACH THE BATTERY &  
PUSH THE BUTTON TO DETERMINE IF THE  
BATTERY NEEDS RECHARGING. A MUST  
FOR THE GLIDER SET, BOATERS, ETC.  
BASIC KIT ..... \$55.50 PP  
ASSEMBLED WITH ENCLOSURE \$106.50 PP

### MARCONI ANTENNA 700W 50 Ω

THE BEST "LITTLE" LOW BAND ANTENNA  
80M: 67' OVERALL ..... \$47.45 PP  
160M: 130' OVERALL ..... \$54.45 PP

### CODE PRACTICE OSCILLATOR... \$23.45 PP

SEND FOR FREE CATALOG

1-800 JADE PRO (523-3776)

www.jadeprod.com/

email: jadeprod@jadeprod.com

JADE PRODUCTS E. HAMPSTEAD NH 03826-0368

## CABLE SECRETS!!!

### This ad has been CENSORED!

Want to know why?

Visit us at <http://www.worldwyde.com>

- Find out how "Test" Devices work
- Installation of "Test" Devices
- Descrambling Methods Explained
- Detailed Construction of "Test" Devices

Includes plans and source code

Complete source code ..... \$79.95

Code for individual boxes ..... \$29.95

## DSS SECRETS — Vol. 2

Instructions on programming DSS access  
cards. This is the most current information  
on the market! Includes software, plans, and  
hardware sources. Book & CD-ROM.  
Get this before they censor it too!!

DSS Secrets Vol. 2 ..... \$49.95

VISA • MasterCard • American Express

To order, call Worldwyde • 1-800-773-6698

21365 Randall Street • Farmington Hills, MI 48336

Visit us on the web at [www.worldwyde.com](http://www.worldwyde.com)

## Build Your Electronics Library At A Price You Can Afford!

Check out the  
**HOT DEALS** at the  
**Nuts & Volts Bookstore!!**  
(See ad page 9.)

As a paid subscriber, you'll  
get 10% off the listed price!!

## TV 85 PJ & TV 86 CABLE CONVERTERS VOLUME & NON-VOLUME CONTROL

SALES/SERVICE  
VOICE 1-800-473-0506  
FAX 1-800-488-0525

## FOSS WAREHOUSE DISTRIBUTORS

285 Schenck St.  
N. Tonawanda, NY 14120  
www.fossw.com

## CUSTOM PLASTIC PARTS

- MODELS (WOOD AND RESIN). TO EVALUATE YOUR PARTS BEFORE COMMITTING TO MANUFACTURE A MOLD.
- MOLD DESIGN AND BUILDING.



- PRODUCTION OF INJECTION MOLDED PARTS. NO ORDER TO SMALL OR TO BIG.
- VERY COMPETITIVE ON HIGH LABOR PARTS.

We also have manual low pressure machines for injection molding of very small runs or prototypes of parts up to 2 oz. At a surprisingly low price.

USA Office: V&V Mach. And Equip. Inc.  
Tel. (218) 397-8101, Fax. (218) 397-8220.  
Please send blue prints or samples to:  
Marketing Tech. S.A. • Alamo 93, 4 Pisco • Sta. Monica,  
Tlal. • Eco. De Mexico 54040 • Tel. 011 (525) 361-3351.  
Fax. 011 (525) 361-5996. ATTN: VICTOR M. MCENDOZA  
e-mail: marktech@infocel.net.mx

## PCB's in Minutes From LaserPrint!\*

8 1/2" x 11" Sheets

\* Or Photocopier Use household iron to apply.

## PnP BLUE or PnP WET

For High Precision Professional PCB Layouts

1. LaserPrint
2. Iron-On
3. Peel-Off
4. Etch

Adds an Extra Layer of Resist for Super Fine Lines on Std. Clad Bds


Transfers Laser Printer or Copier Toner as Resist to Std. Clad Bds

205h\$30/405h\$50/1005h\$100 Blue/Wet (No Mix)  
Sample Pack 5 Shets Blue + 5 Shets Wet \$20  
VISA/MC/PO/CH/MO \$4 S&H -- 2nd Day Mail

Techniks Inc. P.O. Box 463 Ringoes NJ 08551  
(908) 788-8249  
100% Money Back Guarantee-Dealer Inquiries Invited
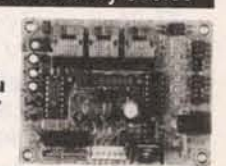
## Convert RS-232 to RS-485 or TTL/CMOS for Only \$49.00

Communicate up to  
4,000 feet, at up to  
1 MEGA-BPS, full  
or half duplex, up to  
32 units on one serial  
link, with 31 jumper  
options for flexible  
configuration, LED  
indicators.



## COMMUNICATIONS CONVERTER

- FULL SCHEMATIC AND DOCUMENTATION
- FULL FAMILY OF MODULAR DESIGNS
- RS-485/RS-422 REMOTE I/O MODULE KITS
- NETWORK SOFTWARE AND SOURCE CODE
- AUTOMATIC OR RTS UNITS AVAILABLE
- RJ-11/12 CONNECTORS OR TERMINAL STRIP
- TURN YOUR PC INTO A DISTRIBUTED DATA ACQUISITION AND CONTROL SYSTEM

## R.E. SMITH

(513) 874-4796  
4311 TYLERSVILLE RD. ■ HAMILTON, OHIO 45011  
www.rs485.com

the disadvantage is that ATX boards are power hungry, consuming 20 to 30W on the DC side of the power supply (less, actually; the 30W typically includes various floppy, CD-ROM and hard drives, and a video card).

By the time my code is debugged and fleshed out, I figure lower-power embedded Pentium systems will be available — say, in PC/104 form factor, and maybe they'll even be affordable. In the meantime, I trade off battery life for more computing horsepower. Plus, I can be secure in knowing that the target controller board is truly identical with my desktop development system.

Okay, so this is my \$1,600.00 budget baseline system:

- ABIT BX6-2 motherboard
- 366 MHz Celeron
- 64 MB of PC-100 ECC SDRAM (expand to 1 GB as memory prices fall)
- AGP video accelerator
- 19" Mitsubishi Diamond Pro 900U monitor
- 8.4 GB IDE hard drive
- 32X CD-ROM
- Upgrade slot 1 CPU to faster Pentium II or III in a year
- ATX mid-tower case, modem, mouse, keyboard, etc.

From what I've read and heard,

ABIT's BX6-2 motherboard is quite stable, even when overclocked. Maybe its best feature, though, is that it incorporates their Softmenu BIOS, which eliminates all on-board jumpers. Softmenu allows varying CPU clock and voltage so I can experiment with power consumption vs. speed tradeoffs:

- CPU voltage variable from 1.30 to 2.30V in 0.05V increments
- Supports bus multipliers of 2-8X in 0.5X increments
- Supports bus speeds from 66 to 133 MHz

All the pieces have arrived. Now all I have to do is put this monster

together. You'll hear more about that, as well as I2C and Breadbot, next time. **NV**

As always, if you have suggestions for improving Breadbot, if you've built a Breadbot, or if you have questions or comments about amateur robotics topics, you can reach me at:

**Robert Nansel**  
69 S. Fremont Ave. #2  
Pittsburgh, PA 15202  
E-Mail: [bnansel@nauticom.net](mailto:bnansel@nauticom.net)





## GPS Design Kit — \$379

The design kit SGM5000KS is a complete and immediately usable means of evaluating the SiGEM GPS receiver module and high performance GPS antenna, which are included in the kit. Software running on the GPS receiver module communicates to a user supplied computer via NMEA 0183 formatted messages. Advanced PC software provides map integration and a demonstration of tracking. Provision has been made for DGPS inputs.

SiGEM Inc.  
50 Hines Road  
Kamela, Ontario  
Canada K2K 2M5  
Tel: (613) 271-1601 (Can)  
(541) 923-3733 (USA)  
Fax: (613) 271-1896

**SiGEM**

Web: [www.sigem.ca](http://www.sigem.ca)  
Email: [info@sigem.ca](mailto:info@sigem.ca)

**PCBs**  
PER SQIN  
**\$100.00 SETUP**  
WE SPECIALIZE IN SINGLE SIDED, 1 OZ, PC75

**9c**

**PCB LAYOUT**  
PER COMPONENT PIN \$100.00 MINIMUM

**59c**


**ENGINEERING DIAGRAMS**  
PER COMPONENT PIN \$100.00 MINIMUM

**39c**

V & V MACH. & EQUIP., INC. (HOUSTON, TX OFFICE)  
PH (281) 397-8101 FAX (281) 397-6220  
MARKETING TECH. S.A. (MEXICO/PLANT)  
PH 011 (525) 361-3351 FAX 011 (525) 361-5996

## SBC2000-074

RS-232

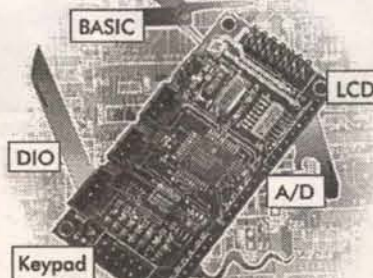


Versatility starting at \$64 each.

Voice: 303.422.8088 Fax: 303.422.9800

[www.sbc2000.com](http://www.sbc2000.com)

Vesta Technology, Inc.
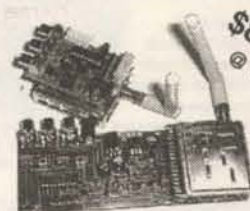
## 2.4 GHz Wireless Transmitter & Receiver



**\$89/pair**  
@ 50 pcs

2.4 GHz ~ 2.48 GHz User Selectable  
Over 700' Range and 4 Chl Auto-scan  
NTSC, PAL, Composite video B/W or Color  
2 Audio Inputs may be used for digital data  
Customizations including battery packs  
and Special Frequencies

**Matco Inc.**

(800)440-0299 or (800)719-9605  
[www.mat-co.com](http://www.mat-co.com)

## Telecom Hardware/Software Developers

STOP using your phone lines to test and demonstrate your telecom devices. Our affordable telephone line simulators offer authentic USA dial tone, busy signals, ringing, and exceptional speech quality.



### RING-IT! TELCO SIMULATOR

- Single Line (two RJ-11 Jacks)
- LED Display
- DTMF Operation
- Automatic Ring-up Mode
- **\$325** (\$149 kit available)

### PARTY-LINE TELCO SIMULATOR

- Six Extensions
- Caller-ID (Name/Nbr)
- Distinctive Ringing
- **\$425** (\$199.95 kit avail)



Digital Products  
**COMPANY**

134 Windstar Circle  
Folsom, CA 95630 USA  
Tel: 916-985-7219  
Fax: 916-985-8460

<http://www.digitalproductsco.com>

## LCD Terminal \$99



Re-Programmable  
LCD 240 x 64 EL Backlit  
RS-232 Port  
1200 Baud Modem  
8051 Compatible Microcontroller  
192k Low Power Static Memory  
Infrared Transmitter  
Nicaid Battery Pack  
QWERTY Keyboard  
FM SCA Data Receiver

**Junkware.com**

<http://www.junkware.com>

## PC BOARD SERVICES

PCB Design Layout

Thru Hole

SMT

Multilayer

PCB FABRICATION

In-house Prototypes

Single and Double Side

Plate Thru Hole

ASSEMBLY

Thru Hole

Small Project Specialists

Serving Engineers and Hobbyists  
for 16 Years

**MIDLAND TECHNOLOGIES**

800-726-8871 Voice

406-586-0300 FAX

This Could Be

# YOUR AD

Read by thousands of  
electronics consumers.

For information, write or call:

**Nuts & Volts Magazine**

430 Princeland Ct., Corona, CA 91719

(909) 371-8497

FAX (909) 371-3052

## GPS Units

Trimble Placer 400 **\$79.95**

6 Chan. & Magnet Mt. Ant.

Trimble SVEsix **\$89.95**

6 Chan w/ Diff. & Mag. Mt. Ant.

Rockwell MicroTracker LP **\$89.95**

5 Chan., Module w/ Differential

& Mag. Mt. Ant.

ACE GPS Mag. Mt. Antenna **\$54.95**

Call for Software Packages

Communications Surplus

713-526-8000 or 1-877-878-6GPS(477)

lshaefer@flash.net Fax to 713-522-6309

## New!

**ActiveWire™ USB**  
**Simple USB Interface**



- Internet Browser Script-able
- 24 MHz CPU core with USB
- Firmware downloadable via USB
- 16 bit parallel I/O
- Expandable add-on boards
- New firmware and scripts available from website

**\$59** plus shipping

**ActiveWire, Inc.**

[www.activewireinc.com](http://www.activewireinc.com)

ph(650) 493-8700 fx(650) 493-2200

## QUALITY KITS

#1 Source for Electronic Kits

Great selection of Hi-Fi AUDIO Kits,  
PSUs, Transmitters, Oscilloscopes,  
PIC Programmers, and much more.

Toll Free Order Line:

**1-888-464-5487**

Secure On-Line Ordering

**[www.qkits.com](http://www.qkits.com)**

Call 613-544-6333 for free catalog

**North American Kit Distributor**

49 McMichael St., Kingston, ON

K7M 1M8, CANADA

## Aviation Components Corp.

28 Hunting Hills Drive  
Landenberg, PA 19350

We buy and sell:

- Relays
- Switches
- RF Components
- All MIL-SPEC
- Resistors
- Circuit Breakers
- Semiconductors
- ICs

Electro-Mechanical

Devices

Home Office (sales)

610-255-3761 • FAX 610-255-3548

Morrisville Office (purchasing)

215-295-3507 • FAX 215-295-8633

E-Mail: [aviationcomp@earthlink.net](mailto:aviationcomp@earthlink.net)

For more info check out our website:

<http://home.earthlink.net/~aviationcomp/>

**Program PICs in Basic**  
Complete kit to get started!

**\$115.95**



Includes:  
Compiler, Programmer, PIC, Cable & Batteries

ORDER

**Electronic Products**

(248) 515-4264 Fax: (413) 825-0377

[www.elproducts.com](http://www.elproducts.com)

**NEED BATTERIES!!**  
**batterystore.com**

TNR Technical, Inc.  
301 Central Park Drive  
Sanford, FL 32771  
1-800-346-0601

## Plans-Kits Unlimited

PLANS KITS PARTS OVER 120,000 PLANS

**LASERS MASERS EMP TESLA**  
**RAIL & COIL GUNS JAMMERS**  
**ULTRASONICS HIGH VOLTAGE**  
**PLASMA & ION GUNS HERF**  
**MIND CONTROL NUCLEAR**  
**PHREAKING BIO-ELECTRONIC**

IF WE DON'T HAVE IT, WE'LL GET IT.

<http://www.plans-kits.com>

AD SPECIAL!!! RUBY & SAPPHIRE SURPLUS RODS  
FOR HIGH POWER CUTTING LASERS. 1/8" x 3" L.  
FLAT ENDS, MATTE FINISHED, SURPLUS MILITARY.  
\$12.00+\$15/M EA. CHECKS, CASH, MONEY ORDER.

PLANS-KITS UNLIMITED: (BASE FOR CATALOG)  
1839-D WEST VISTA WAY #515, VISTA CA 92083

**GREAT**  
FOR TEST FIXTURE  
BUILDING



**LAB-1**  
(1.5" x 2.0" x 0.75")

**FREE!**

PHONE, FAX, WRITE  
OR E-MAIL WITH YOUR  
MAILING ADDRESS  
MUST MENTION  
OFFER "LAB199"

PRE-PUNCHED END PANELS  
ALSO AVAILABLE  
9 BOX SIZES  
25 PREPUNCHED  
END PANELS

ALSO IN STOCK AT:  
JENSEN TOOLS: 800-436-1194  
MCM ELECTRONICS: 800-543-4330  
TECH AMERICA: 800-442-7271

ALL ALUMINUM CONSTRUCTION **LOW COST**  
OFFER GOOD ONLY IN THE 48 STATES. ENDS DECEMBER 20, 1999. LIMIT ONE  
REQUEST PER CUSTOMER. MAILED 1ST CLASS, ALLOW 1-2 WEEKS FOR DELIVERY

ORDERS 800-634-3457 • FAX 800-551-2749  
OFFICE 702-565-3400 • FAX 702-565-4828  
[www.sescom.com](http://www.sescom.com) • [info@sescom.com](mailto:info@sescom.com)  
SES.COM, INC. 2100 WARD DR., HENDERSON, NV 89015  
SES.COM, INC. is not responsible for inadvertent typographical errors  
and prices and specifications are subject to change without notice.



## EMBEDDED DOS Flashlite-V25

- 2 Serial Ports
- 2 DMA Channels
- 2 Timer Channels
- 20 Parallel I/O Lines
- 5 Volt Operation
- 4 Hardware Interrupts
- 8 Analog Comparators
- Low Power Consumption



qty 1 \$119  
qty 100 \$99  
qty 1000 \$65

### Development Kit - \$159 Includes:

- Flashlite V25, 10MHz, 512K Ram/ 512K Flash
- Borland C/C++ 4.52 Development Software on CD
- Telecommunications Program & Sample Programs
- AC Adapter and Cables

www.jkmicro.com

Call 530-297-6073 Fax 530-297-6074

**JK microsystems**

## VIDEO PRODUCTS



CNL-100 \$49 BX-120-P \$59 SX-800 \$79

- 430 TV Lines Resolution
- 9-14 VDC Operation
- Infrared Sensitive
- SX-800 has Audio Output
- A-300 Camera Enclosure also available

**MATCO, INC.**

Schaumburg, IL

1-800-719-9605 • 1-847-619-0852 FAX

E-Mail - info@mat-co.com

Website - www.mat-co.com

## 10&14 Hour Telephone

### Recorders

Starting at \$69  
Times based on a 180 tape  
14 Hour \$89+S/H



120 Tape included!

Automatically starts recording when the phone is picked up and stops when you hang up. Records both sides of the conversation! Printed catalog \$3 (free with order)

Visit our Online Catalog  
www.mscelectronics.com

**MSC Electronics**

PO BOX 461 Jessup, MD 20794

(301) 497-1600

FAX (301) 497-1925

No Checks • US & Canada Only



## EPS

### EPROMS AS LOW AS 25¢

27C256	27C040	27C1024	87C51
27C512	27C400	28F010	8751
2732A	27C4096	28F020	8755
27C32	574000	28F040	MC68HC70
27C128	574200	8749H	5C8A
27C64	27C402	8748H	PIC16C56
2716	27C020	8741	PIC16C54
2708	27C210	8742	PIC16C622
27C512-90	27C010	8744	GAL16V8

### STATIC RAM

HM628128  
62256  
6264  
6116

### PROCESSOR

8255  
8254  
80C31

MEMORY  
D-RAMS  
SIMM

- Many more parts in stock
- All major brands
- All guaranteed

E-Mail: eproms@aol.com

TEL: (818) 774-9444 • FAX: (818) 774-0822

**WE BUY EXCESS INVENTORY**

## FREE SAMPLE COPY! ANTIQUE RADIO CLASSIFIED

Antique Radio's Leading  
Monthly Magazine

Articles - Classifieds - Ads for Parts & Services. Also: Ham Equip. - Books - Telegraph - 40's, 50's & 60's Radios - Early TV - Auction Reports and more...

1-Year: \$39.49 (\$57.95 by 1st Class)

6-Month Trial - \$19.95. Foreign - Write.

A.R.C., P.O. Box 802-G23  
Carlisle, MA 01741  
Call: 978-371-0512 - Fax: 978-371-7129  
Web: www.antiqueradio.com

## TOGGLE SWITCHES - All sizes and types Commercial Quality

FULL SIZE TOGGLE SW. 1/2" DIA.				PRICE
TYPE	MODEL	RATING	LEAD	100-1000
SPST	D125	6A/125V	6" wire	.77 .67
SPST	D128	4A/125V	Solder	.57 .47
DPDT	D126	5A/125V	Solder	.77 .67
DPDT	D127	10A/125V	Solder	1.17 1.06
on-off-on		5A/250V	Screw	
MINIATURE TOGGLE SWITCHES 1/4" DIA.				
SPST	D131	6A/125V	Solder	.57 .47
SPDT	D132	6A/125V	Solder	.61 .51
SPDT	D129	6A/125V	Solder	.77 .67
mom-off-mom		3A/250V	Solder	
SPDT	D134	6A/125V	Solder	.77 .67
on-off-on		3A/250V	Solder	
DPDT	D133	6A/125V	Solder	.77 .67
DPDT	D135	6A/125V	Solder	.92 .82
on-off-on		3A/250V	Solder	
DPDT	D130	6A/125V	Solder	.92 .82
mom-off-mom		3A/250V	Solder	
MOMENTARY PUSHBUTTON SWITCHES 1/4" DIA.				
SPST Nor Open DM1	3A/125V	Solder	.32 .27	
SPST Nor Close DM2	3A/125V	Solder	.32 .27	
ANY ORDERS LESS THAN 100, ADD 20¢ EACH				
LEDS Red, Yellow, Green — \$12.00/100 \$15.00/1000				

ANY ORDERS LESS THAN 100, ADD 20¢ EACH

LEDs Red, Yellow, Green - \$12.00/100 \$10.00/1,000

**DEMAR ELECTRONICS**

P.O. Box 7215, Algonquin, IL 60102

Toll Free 877-655-6433

Fax 847-854-4434

## CABLE BOXES

CUT MANUFACTURING COST!  
WE ACCEPT SMALL ORDERS TOO.


SHEET METAL

20 GAUGE

SILK SCREEN

PRINTED

WITH YOUR CO. NAME

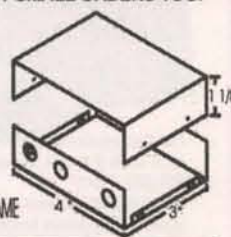

ALSO PCB, SMT, PROTOTYPES, ASSEMBLY,  
PLASTIC MOLDS, INJECTION MOLDING.

USA Office: V&V Mach. & Equipment, Inc.

Ph: (281) 397-8101, Fax: (281) 397-6220.

Mexico Plant: Marketing Tech.

Ph: 011 (525) 361-3351, Fax: 011 (525) 361-5996.

## COVERT CATALOG 2000

### BRAND NEW!

The Latest, Up-to-date, Hands-on  
Supplier and Source Guide for:

- Electronic surveillance equipment
- Covert video cameras and transmitters
- Counter measures gear
- Entry supplies
- Electronic tracking systems
- Computer surveillance and remote viewing

Equipment, exact addresses and ordering info  
from 15 countries!! 220 pages - \$39.95

11 3555 S El Camino Real, San Mateo, CA 94403

Phone 650-513-5549 • fax 650-728-0525 or

www.intelligence.to (no "dot com")

## ASSEMBLY & ENGINEERING

Producible designs since 1970  
Contract Engineering

Embedded Microprocessors  
PCB Layout and Packaging Design  
Analog Including RF to 1 GHz  
Instrumentation  
A/D and D/A

Contract Assembly

High-Speed Fuji Surface Mount  
Through hole  
Turn-key or Kit  
Run sizes one through thousands  
Test and burn-in available

Bilocon Corp.

800-736-5927

425-353-2276

www.bilocon.com

## Stereo Microscopes for Large PC boards



9 in. arm for  
Large boards  
-10X & 30X  
-Dust cover  
-Eye guards  
-5 year warranty  
ST 231P - \$395.00



jlittle@netwizards.

3580 Haven Ave. Redwood City, CA 94063

650/367-8320 Fax 365-5845

## CONTROL • MEASURE • INPUT


### MODEL 40-\$109

- RS-232 interface
- 28 lines digital I/O
- Eight analog inputs
- PWM output
- Three stepper ports


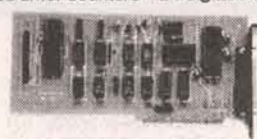
### MODEL 100-\$279

- 12-bit 100KHz A/D • Four analog outputs
- Three timer counters • 24 digital I/O



**PRAIRIE DIGITAL, INC.**

920 SEVENTEENTH ST., INDUSTRIAL PARK

PRAIRIE DU SAC, WI 53578

TEL: (608) 643-8599 • FAX: (608) 643-6754

## dmdsystems.com

[electronic test & mfg]

[test]

[measurement]

[rf/microwave]

[specialized equipment]

[computers]



**DMD SYSTEMS RECOVERY, INC.**

**602 305-8485**

fax 602 305 8490 • email info@dmdsystems.com

## ASTRO TOO

Surplus/Electronics Equipment

Web Site: AstroToo.Com

E-Mail: Astro@AstroToo.Com

2854 Sarno Road  
Melbourne, FL 32935

(407) 253-3371  
Fax: (407) 727-1546

When visiting Central Florida,  
come see us!  
I-95, Exit 72

## SOLAR ELECTRICITY

All manner of photovoltaics and  
solar electronics available here.

www.planetarypower.com

120 Watts  
Panel  
\$589

64 Watts  
Panel  
\$319

**P.V. Power Corp.**

Inverters, Controllers, Racks,  
Meters, Shunts, Fans, Pumps

**(877) SOLAR PV**

## softwarecloseouts.com

DOS - Windows - Win95  
UNIX - MAC - Upgrades  
Secure on-line ordering

softwarecloseouts.com

Corel Office 7 \$29  
Norton Anti-Virus 2 \$5  
Windows WGP 3.11 \$39  
Office 4.2upg \$39

Up to 85% off titles by Symantec!

softwarecloseouts.com

New Arrivals Weekly!  
Hard-to-find a specialty ...  
We buy your surplus software.

softwarecloseouts.com

## Doctor GB card / Xchanger for Professional Game Developers

Doctor GB card is a  
Gameboy compatible ROM  
emulator FlashROM  
cartridge. It has built-in  
SRAM and supports MBC1,  
MBC2 and MBC5 standard.



GameBoy

The advanced design of the  
Doctor GB card and Doctor GB  
Xchanger makes it easy for  
programmers and coders to  
burn a ROM file to the Doctor  
GB card. To transfer data into  
the Doctor GB card, the only  
requirements are the Doctor  
GB Xchanger, PC and our  
customized software. No need  
for expensive and difficult to  
use EEPROM burners.

www.UpstateGames.com

E-mail: sales@upstategames.com Fax: (716) 442-7223

P.O. Box 40184 Rochester, NY 14604 U.S.A.



capacitor of the second 555 timer (right), which generates the sweep needed for the scope display. Be aware that this is just an expanded block diagram (I've never built it) and the values listed are only ballpark figures — values that you can start with, but will have to tweak to match your scope's and car's needs. If you run into problems using an inductive pickup, I suggest an NE2H neon lamp coupled to a homemade optical sensor using shrink tubing.

### I-Worm.ExploreZip Cures — Free!

A new Internet Worm virus, called I-Worm.ExploreZip (I've seen it spelled many different ways), is hitting corporate networks and end-user PCs around the world at an extremely rapid pace. Once a PC is infected it will reply using MAPI to every E-Mail received by that PC. The reply E-Mail contains a copy of the worm and reads as follows:

oHi "name of recipient" !  
oI received your email and I shall send you a reply ASAP.  
oTill then, take a look at the attached zipped docs.  
oSincerely

I-Worm.ExploreZip contains a very malicious payload. It uses Microsoft Outlook or Microsoft Exchange's MAPI to mail itself out by replying to the messages you receive. It attaches a file called "ZIPPED\_FILES.EXE" that, upon execution, infects the recipient's PC. Unknowingly, users execute the attachment since it has the familiar icon of a Winzip file and it apparently comes from a known source or friend.

Fortunately, it's not a very destructive virus in that lost data can be recovered. Unfortunately, some companies are capitalizing on this malady, to the tune of hundreds of dollars. I did a search of the web — with the help of <http://www.internetwork.com> — and found three top-notch companies that are willing to fix the problem for free. Here they are.

- **Emergency Undelete**, a free utility originally developed to recover accidentally deleted files from Windows NT network disks, is being used by companies all over the world to help recover data destroyed by the ExploreZip worm. It can be downloaded free at <http://www.undelete.com>.

- **GFI**, leading developer of E-Mail security and management software, offers a freeware version of Mail essentials for Exchange/SMTP that's able to protect a corporate E-Mail system from the dangerous data-destroying E-Mail virus, Worm.ExploreZip. Other anti-spam features in the freeware Mail essentials version include checking for incorrect "From" headers and addresses in the E-Mail body, real-time black hole list support and more. The freeware anti-spam version can be downloaded from: <http://www.gficomms.com/mesindex.htm>. The download contains all the Mail essentials features, valid for 60 days; however, the anti-spam feature does not expire and remains fully functional.

- **Panda Software** has added detection and disinfecting of this extremely dangerous Internet worm to their software programs, and has posted free "good-riddance" software on its website at <http://www.pandasoftware.com>.

TJ Byers  
Q & A Editor

### MAILBAG

Dear TJ:

Regarding your May '99 answer for the reader wanting a VGA cable for his Macintosh IIsi, the IIsi and earlier Macs don't do VGA. They have only a couple of scan modes and VGA isn't one of 'em. The IIsi does 640 x 480 at Apple's own 67 Hz rate. The first Macs to do VGA, at 60 Hz, were the LCIII — the model released after the IIsi. So, while your info about how to build a VGA cable for Mac is correct, it won't be helping the particular reader who requested it. I suspect that some SVGA monitors can handle this, but none that I have in house. Also make sure to tell the reader to wire the cable for 640 x 480 mode.

Fred Martin  
via Internet

Response:

I wasn't aware that the scan rate changed somewhere between models. Neither did my sources, who sell this adapter cable. In case you missed the answer, here is the pinouts of the adapter again — corrected for SVGA monitors that can do 640 x 480 at 67 Hz. Thanks Fred!

TJ Byers  
Q & A Editor

Mac IIsi	SVGA monitor	Function
Pin 1	6	Red GND
2	1	Red
3	--	Composite TTL sync
4	--	Monitor sense 2
5	2	Green
6	7	Green GND
7	--	Monitor sense 1
8	--	not used
9	3	Blue
10	--	Monitor sense 0
11	--	GND
12	14	Vertical sync
13	8	Blue GND
14	10	Horizontal sync GND
15	13	Horizontal sync

Dear TJ:

I read with interest your remarks on GR Variacs in the June '99 issue, but was sorry you did not remark on the real novelty of the Variac design: the use of a graphite brush which made contact with several turns of the winding at once, but had enough resistance to not load the nearly shorted turns too much. This feature provides a smoothly adjustable voltage rather than steps as would have been the case of a metallic contact moving from turn to turn, and not touching two at once.

Bob Meade  
via Internet

### SOLAR POWERED SPACE EXPLORER KIT

Do you want to have the ultimate go-anywhere solar powered educational car? If so, this is the one for you. This car is the "Sport Utility" type of solar cars, able to slowly rumble like a tank over grass, small stones or obstacles, and up slopes (40° or less)! This easy to assemble solar car has a high torque gear box, a tank type drive mechanism, and decals to customize your vehicle. Includes many fun and exciting experiments and a brief history of space exploration! Perfect for summer fun or as an introduction to solar power. No special tools are required to assemble this car and all of the soldering is already done for you! Size of the space explorer is approximately 8" L x 4 1/4" W. Can operate on 2 AA batteries (not included) or it can operate without batteries with its efficient Solar Panel (included).

G1492 \$29.95 ea.

### ROBOTICS/GENERATOR GEAR DRIVE PLUS MOTOR KIT

High torque motor and gear drive assembly consists of a small efficient DC motor, a black snap to gether housing, 4 plastic gears, 1 plastic pinion gear for the motor, a 3 5/8" Long hexagonal steel shaft, a small steel shaft, and an orange plastic crank. Comes with a simple diagram to put together the gear box motor assembly. After assembly you can use the unit to generate electricity to light LEDs, recharge 2.4V nicad packs, etc or remove the crank and attach your wheels to the shaft and you'll have a powerful drive train capable of providing forward or backward motion for robots, small tanks, etc, or anything that high torque and low speed is a requirement. The motor/gearbox can operate from the solar module (above, center G1496) or any voltage from 1.5V to 3VDC. Brand new and in kit form.

G1509 \$8.95

### ROBOT WHEELS AND AXLE

Set of two 1 1/2" Dia. bright orange wheels which press onto the above hexagonal shaft and a set of two 1 1/2" Dia orange wheels that press onto a 3 5/8" Dia round shaft (for use on the front of your robot or other application). You get a total of 4 wheels and 1 front axle/shaft with this set.

G1521 \$2.00/set

### POWERFUL SOLAR MODULE

Compact module consists of 3 amorphous silicon solar cells connected in series, mounted on a glass epoxy board and then coated with a clear epoxy. Size only 4 1/2" x 2 5/8" x 1/16" but produces an incredible 1.6V open circuit voltage and up to 400ma short circuit current. These are great for powering small DC motors to make hundreds of unique solar powered cars, boats, fans, & electronic projects.

G1496 \$14.95 ea.

SOLAR!

### SMALL EFFICIENT MOTOR & FAN BLADE

Works perfectly with the solar panel sold above, this motor features solder tinned connection posts and small 2" overall dia. push on fan blade.

G1495 \$2.75

### 15VDC 400MA ADAPTER

Special Adapter made for Sega Channel. Plugs into standard 120VAC outlet and features a 5mm female barrel plug with center (+). Has built in ferrite bead RF interference filter. Special blowout price.

G1357M 99¢ ea.

### CDS CELL BLOWOUT

Light sensitive CDS cell varies resistance according to ambient light. Perfect for thousands of light sensitive alarms, robots, automatic door sensors, etc. Resistance in darkness is over 1 meg, and less than 200 in light. Brand new!

G1479 5/\$1.00 • 1000/\$150.00 • 10,000/\$1200.00

### TEST LEADS WITH CLIPS

Package of 10 test leads with clips. You get 10 total test leads (2 red, 2 black, 2 green, 2 yellow, and 2 white). Each has a clip on each end and is 13 1/2" long.

G1498 Package of 10 \$2.49

Wow!

ELECTRONIC GOLDMINE  
WE ALSO OFFER OVER 150 DIFFERENT ELECTRONIC KITS  
ELECTRONIC GOLDMINE  
PO Box 5408  
Scottsdale, AZ 85261

<http://www.goldmine-elec.com>

NOTE: All items subject to prior sale; All prices expire 10-01-99

For Phone Orders Call: 800-445-0697

or Fax Your Orders to: (602) 661-8259

For a Free Catalog Call: (602) 451-7454

Foreign catalog request: send \$5.00

Minimum Order: \$10 (plus min. \$5 Shipping and Handling). We accept MasterCard, Visa and personal checks, however, we cannot accept personal checks on orders outside the U.S. Minimum Foreign Order Amount: \$50 (plus a minimum \$10 S&H)

### CORDLESS PHONE BATTERY

This 3 cell nicad button pack is rated 3.6V@280mAh. Size is 1" Tall x 1" Dia. has blue vinyl sleeve, flexible color coded wires and small female connector. Prime brand new. Sold for up to \$9.00 each elsewhere.

G1508 \$1.49 ea. • 5 for \$7.00

### GIANT ROUND FAN

When you have a major cooling job, you need this giant 6 3/4" Dia. x 2" Thick metal case fan. Brand new type TA600DC Nidec BETA V™ model A33400-29 provides a tremendous volume of air. Reliable heavy duty design. Requires 36VDC @ .70amp. No finger guard so be careful when operating. Prime and worth much more than our low price!

G1522 \$10.95 ea.



# Servos, Steppers, and Optical Encoders — Part I

by TJ Byers

Which one works best in your robotic or R/C project?

Here's everything you need to know.

Whether you play with robots, model planes, or boats, there are motors inside which supply the muscles and habits that make them go. Choosing the right motor for your project, though, can be a daunting experience. Motors that provide locomotion aren't the same as those that move robotic arms or guide a plane.

Basically, controller motors come in three flavors: servos, steppers, and encoders. Each operates differently and each performs a specific task. In this discussion, I explain the differences between the three and their application. I'll also show you the control circuitry needed to make them perform as expected.

Unfortunately, the length of my discoveries ran a lot longer than I originally planned, and longer than the editor is willing to put up with in a single issue, so I've broken it up. The first part deals with servos. It includes all the theory you ever wanted to know about servos, and were sorry you asked. It also includes the circuitry needed to make your servo jump through hoops.

The next installment is on stepper motors — which aren't servos! Steppers spin, and servos actuate. So, with that in mind, let's take a look at servos.

## Servos

The term "servo" actually defines any system where a small force controls a larger one,

and encompasses both mechanical and electrical controllers. In the electronics and hobby world, the word servo usually means an R/C (remote control) servo motor — the kind typically found in model airplanes and RadioShack cars.

Of course, they find widespread use in robotics, too. This is the type of servo I'll focus on in this article.

Unlike what most of us think of as a motor, a servo motor isn't free running. That is, it doesn't spin like motors used to drive the wheels of a robot or R/C race car. Instead of spinning round and round, the output of a servo motor simply assumes a position and holds it. There's a position encoder attached to the motor's shaft that reports the absolute position of the shaft back to a controller.

If there's an error in the position, the servo takes corrective action to twist the shaft to the proper position. Most servos have a span of 180 degrees from full left to right, but this can vary from 90 degrees to 270 degrees, depending on the servo.

Servos are generally used where back-and-forth motion is required, in applications like:

- Robotic arms and grippers
- Sweep scanning for robotic sight and sound sensors
- R/C airplane elevator, rudder, and throttle
- R/C car steering and throttle
- Pan and tilt for security cameras

## Servo Construction

Servos are constructed from three basic elements: a motor, a feedback device, and a feedback loop (Figure 1).

## Servo Motors

For hobby and robotic applications, DC motors are preferred over AC motors because they generate greater torque for their size and weight. The output from the motor's shaft is connected to a gearbox (usually called a gearhead) that reduces the motor's speed to a usable output speed. The gearhead ratio between the RPM speed of the drive motor and the output shaft determines the response time and the torque of the servo.

The torque is measured in inch ounces, usually listed as oz-in or oz/in. The listed torque is the maximum force the servo will exert on an object one inch from the shaft. The farther away from the shaft you go, the less torque is available. The formula is simple:


$$\text{Torque} = \text{Distance} \times \text{Force}$$

Let's say the servo is rated at 100 oz-in. This means it can lift a 100-ounce weight when the weight is attached one inch from the shaft. Move that point out to two inches, and the force drops to 50 ounces. Three inches is 33 ounces, and so forth. Most servos have a torque that falls somewhere between 10 oz-in and 300 oz-in, with the popular hobby models within the 20 oz-in to 150 oz-in range.

The higher the input-to-output gearhead ratio, the greater the output torque — but the lower the output RPM. The slower the shaft turns, the more time it takes for the servo to respond to changes in shaft position. Depending on the servo, the response time can be anywhere between 0.10 and 1.5 seconds. The faster ones are used for airplane surface controls and the slower ones, which usually have higher torque, are used in sailing ships to raise the sail.

The construction of the gearhead is critical to servo life. Most of the hobby models use plastic gears that often wear out after 100 hours of use. If the servo is energized but not moving, as in a holding state, that time doesn't count — just the motion time. Adding to the longevity problem of these low-end servos is the shaft bearing which is plastic, too. Medium-priced servos have metal gears and a metal bearing that stand up

FIGURE 1

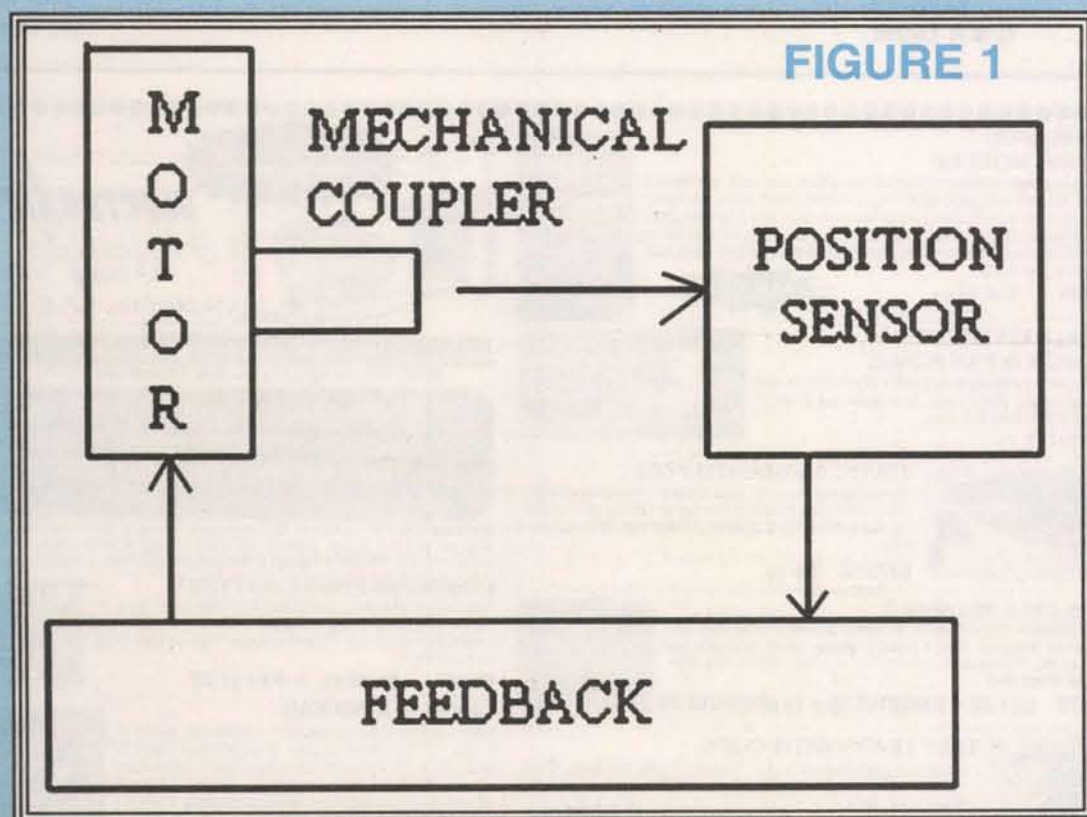



# Servos, Steppers, and Optical Encoders — Part I

better under heavy use. At the top of the line, you'll find heavy-duty gear-heads with ball-bearing bushings.

## Servo Feedback

Critical to servo operation is a position sensor: a device that monitors the angle of the shaft and feeds it back to the controller. In virtually every case, the sensor is a potentiometer (variable resistor) wired in a ratiometric feedback configuration (Figure 2).

In this configuration, the wiper of the potentiometer is tied to the positive input of an error op amp. The top of the potentiometer is connected to Vcc (typically +5 volts) and the bottom is returned to GND. The potentiometer shaft is physically attached to the output shaft using a 1:1 ratio gear so that the potentiometer is in step with the output shaft.

The negative input of the error amp is connected to a reference volt, the value of which is set by the pulse width on the signal wire. (More on that later.) This voltage sets the position of the servo shaft. When the voltage across the potentiometer wiper equals that of the reference voltage, the control circuit stops the motor and locks the shaft into position.

For the sake of argument, let's set Vcc at +5 volts (typically Vcc servo voltages range from 4 to 6 volts). This means that a reference of 2.5 volts will set the shaft position to exactly one-half of the servo's full sweep. Likewise, 1.25 volts is one-quarter of the sweep, and 3.75 volts is three-quarters of the sweep — plus all of the increments in between.

Like the gearhead, the potentiometer is a source of potential failure — and inaccuracy. In many cheap servos, the potentiometers are made of plastic, which get gritty, and wear out rather quickly. What happens is that the servo will jitter or hunt for an exact position. Not surprisingly, the lifetime of the gearhead is matched to that of the potentiometer. Both wear out at just about the same time. Medium-priced servos generally have sealed potentiometers to keep the

dust out and make the potentiometer last a lot longer. Again, the quality of the metal gears is paired with the potentiometer for an equal lifetime.

## Servo Control

Now that you're totally bored with servo motor theory, here's some real hands-on stuff. Specifically, what does it take electronic-wise to make the servo shaft turn?

Surprisingly, not a lot; a single 555 timer chip makes an excellent servo controller.

As explained above, it's a changing reference voltage that positions the shaft. This reference voltage is derived from an input pulse to the signal or control wire (typically white). The reference voltage is derived from the width of the signal input pulse, not the repetition rate. The range is between 0.5 mS and 2.5 mS, depending on the particular

servo, with 1.5 mS defined as mid range — halfway through the sweep regardless of the sweep arc.

Put in the scenario above, if the input pulse is 1.5 mS, then the reference voltage is 2.5 volts, and the shaft's rotation is resting at half rotation. Assuming that we have a typical 180-degree servo with a 1 mS to 2 mS pulse width range, a 1 mS pulse sets the servo shaft position at 0 degrees and a 2 mS pulse twists the dial to 180 degrees; 1.5 mS puts it at 90 degrees.

This timing is independent of the servo's Vcc or rotational range: 1.5 mS always sets the sweep at mid scale. Keep in mind, though, that the minimum and maximum pulse widths will vary from servo to servo, and should not be exceeded. If you try to command the servo to a position beyond its physical limits, it will hum, jitter, and eventually burn out.

However, servos will not hold their position forever. The signal pulse must be repeated periodically for the servo to stay in position. The maximum amount of time that can pass before the servo will stop holding its position is called the command repetition rate, usually every 10 mS to 40 mS — about 20 Hz to 80 Hz. You can repeat the pulse more often than this, but not less often. If the repetition rate drops below 50 mS, the servo ceases to be a servo and, instead, becomes a "98-pound weakling" that can be shoved around.

## Servo Drivers

Okay, here's the circuit you've been waiting for (Figure 3). The 10k position potentiometer adjusts the pulse width between 1 mS and 2 mS, the range typically used in small hobby (40 oz/in) servos, with the center setting generating a 1.5 mS pulse width. The pulse repeats every 20 mS, for a repetition rate of 50 Hz. The 1N34A is a pulse shaping diode that sharpens the fall time. The red and black servo leads are +6 volts (Vcc) and GND, respectively, and the white lead from the servo is the control wire.

Trust me. This circuit works all the time — done it, been there. If you need a bigger sweep, you can try stretching the pulse width limits by increasing the value of the 68k resistor. But at the first sound of chatter, back off. You've hit the limit.

## Not Done Yet!

No, there's a lot more to come. Just remember that servos actuate — move like limbs — and steppers rotate — like fan motors. With that in mind, we'll continue this discussion next time.

Next time, I'll serve up a full platter of stepper motor theory and circuits. **NV**

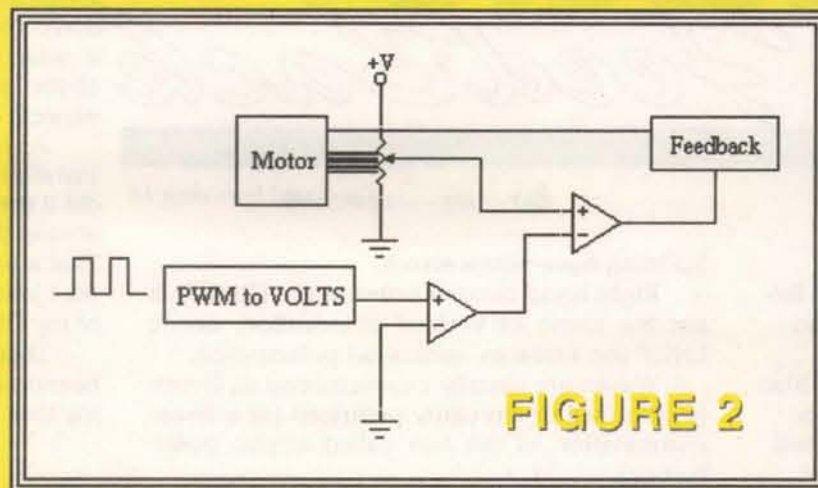


FIGURE 2

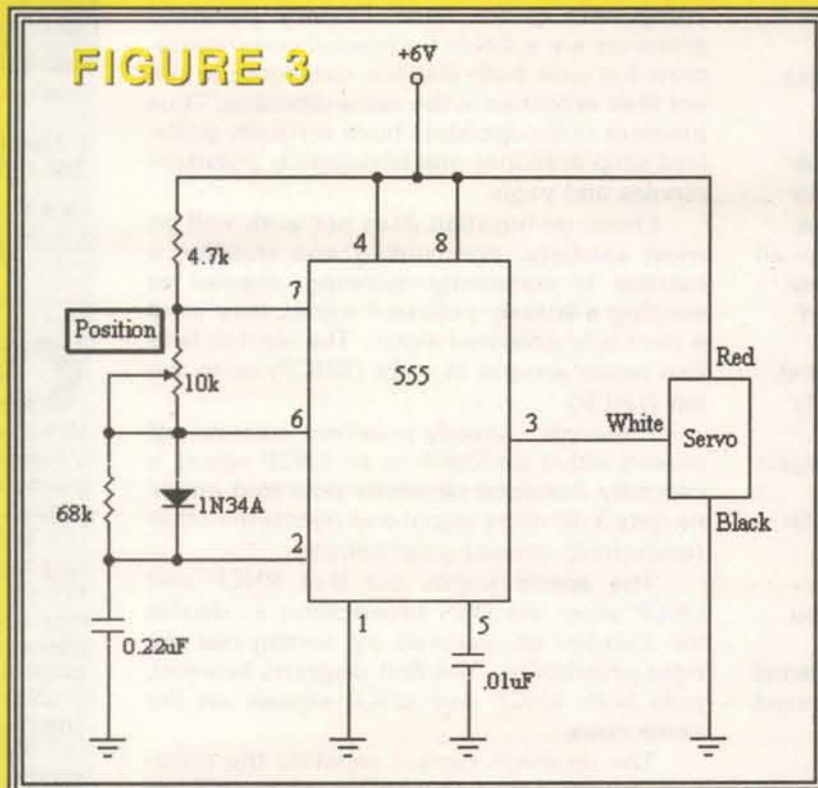


FIGURE 3

Table 1. Wire colors for popular servo motors

Mfg	Positive (+)	Negative (-)	Signal
Airtronics	Red	Black	Brown
Sanwa	Red	Black	Black stripe
Futaba J	Red	Black	White
KO Propo	Red	Black	Blue
Pulsar Kyosho	Red	Black	Yellow
Japan Radio(JR)	Red	Brown	Orange



# Reader Feedback

Continued from page 16

Also, since crystals cannot easily be made for very high frequencies, it will be followed by a multiplier chain which will then double or triple the output frequency.

Along with that information, you will also have to know if it is series or parallel resonant, how much capacitance the crystal will be working with in the oscillator, and the required frequency tolerance.

In short, you need to know all of what the designer of the radio knew when the original crystal was specified, and that was much more than just crystal frequency.

Rather than try to engineer your own crystal, the easiest path is to call up a custom crystal grinder and order one for your specific radio and frequency. They keep a database of the necessary information, so all you need to do is to tell them what receive frequency you want and they take care of the rest.

A good Internet source can be found at [www.geocities.com/CapeCanaveral/8701/mega/xtals.htm](http://www.geocities.com/CapeCanaveral/8701/mega/xtals.htm)

Listed on that page are two of the largest and oldest custom crystal makers: JAN Crystals, Ft. Myers, FL 33906-6017, 1-800-526-9825; and ICM, Oklahoma City, OK 73126-0330, 1-800-426-9825. Give these folks a call and they can probably get you what you need in a week or so.

**Dave Sarraf**  
Via Internet

## Dear Nuts & Volts:

The bridge circuit offered by TJ Byers in the April '99 issue (page 77), and the "corrected" circuit given in July '99 (page 34), have dangerous short circuits across the power line.

In the July circuit, the lower quad's NW diode and the upper quad's SW diode short the power line on positive excursions. The negative excursion is shorted by the upper SW and lower NW diodes. The circuit is dangerous and should not be used. The short circuits are present because the circuit is trying to connect the 115 VAC line across the upper and lower capacitors at the same time.

Reasonable simple circuits are a 160V full-wave single supply (using four diodes) or a  $\pm 160V$  half-wave supply (using two diodes). Since the application uses a transformer, there is no need for a 320V supply, making a 160V full-wave supply a good bet.

Be careful when working with the power line. The schematic should have a fuse in the power lead to guard against shorts caused by wiring or design errors. When testing power line circuits, keep one hand in your pocket and use a GFCI.

**Gerald Roylance**  
via Internet

## Dear Nuts & Volts:

TJ Byers' comments about DSS Signal

Splitting have some errors.

Right hand circular polarization (RHCP) is not the same as vertical polarization, nor is LHCP the same as horizontal polarization.

Waves are usually characterized as linearly polarized or circularly polarized (or a linear combination of the two called elliptic polarization).

The direction refers to the electric field component of the wave. Linearly polarized antennas are suitable for ground communications because both stations can agree to orient their antennas in the same direction. Thus amateur radio operators have vertically polarized whip antennas and horizontally polarized dipoles and yagis.

Linear polarization does not work well on most satellites. For cooling and stability, a satellite is constantly spinning. Instead of sending a linearly polarized signal, they send a circularly polarized signal. The electric field can rotate around to right (RHCP) or to the left (LHCP).

Although a linearly polarized antenna will receive either an RHCP or an LHCP signal, a correctly designed circularly polarized antenna gets 3 dB more signal and rejects the other (undesired) circular polarization.

The article points out that RHCP and LHCP allow the DSS broadcaster to double the number of channels by sorting out the right polarization. The first diagram, however, puts both RHCP and LHCP signals on the same coax.

The receivers cannot separate the polarizations (that was the LNB's job!), so both receivers will produce trash.

There is another reason why a splitter isn't a good idea, and Mike Quinn guessed it when he thought the signals might be too weak. Signal-to-noise ratios are important for DSS broadcasters, and using a passive splitter will lower the SNR by at least 3 dB. A lower SNR means more bit errors, so your MPEG decoder will generate more trash, especially when it rains.

That aside, there are DSS splitters for sale, and they skirt the DC signaling voltage fights by putting a DC block in one leg. Ordinary TV splitters (50-500 MHz) don't have the frequency range for satellite signals (1-2 GHz).

The bottom line is you need a dual LNB for complete independence of the set-top boxes. When you get to three set-top boxes, there are multiplexers that connect to a dual LNB and provide three DSS ports.

Some of these multiplexers will even combine the signal from a local TV antenna so you don't need to run two cables (one satellite TV, one ordinary TV) to each receiver.

**Gerald Roylance**  
via Internet

## Response:

Right hand circular polarization (RHCP) is not the same as vertical polarization, nor is LHCP the same as horizontal polarization. I know the difference between polar, vertical, and horizontal polarization. The people at the Good Guys don't. That's why my answer was worded the way it was. Many sales people don't even know about polarization, much less the technical aspects of circular vs. polar.

As to the block diagram, that came from an installation manual. BTW, the reader who asked, did it the way I suggested, and it works. I always answer the question online before printing them. That's not to say I don't make mistakes, 'cause I do; I just try to minimize them. Check out some of my DSS answers in earlier columns.

Thanks for your input, and look forward to hearing from you in the future. You keep me on my toes.

**TJ Byers**

## Newsbytes

Continued from page 16

E-Mail: [info@softapproach.com](mailto:info@softapproach.com). Voice 1-800-268-9898, 416-499-0594. Fax: 416-490-8993.

### FULL SERVICE FOR YOUR PC

Continuing in its tradition of producing superior PC utilities, Iolo Technologies announces a new set of tools for Windows 95, 98, and NT. System Mechanic 3.0 is a complete suite of 10 utilities, providing the essential preventative maintenance today's PCs require.

System Mechanic delivers the tools necessary to search for, diagnose, and solve the modern problems with today's computers. As well as reacting to existing issues, System Mechanic allows the user to conveniently and preemptively maintain their computer in order to prevent problems from reoccurring, increase speed, and ensure reliability.

"Computers are not appliances like microwave ovens or washing machines — an automobile is a much better comparison," says Noah Rowles, president of Iolo Technologies. "All computers need regular maintenance and similar to your car, will begin to run poorly or even break-down if not routinely serviced. System Mechanic is a product built around extensive research into the most common PC problems and the result is a complete set of tools that allow you to comprehensively maintain your computer system."

System Mechanic 3.0 allows you to

- Find and remove junk and obsolete files.
- Ensure your privacy.
- Repair Windows shortcuts.
- Remove invalid uninstaller information.
- Remove duplicate files and drivers.
- Clean and optimize the registry.
- Manage the items that start when Windows does.
- Track and report critical system changes.
- Schedule unattended system maintenance.
- Keep comprehensive logs and statistics.

System Mechanic 3.0 will be available in June 1999 directly from Iolo Technologies for \$59.95. It requires Windows 95, 98, or NT with at least 8 MB of RAM and 2 MB of free disk space. A 30 day trial version is available at [www.iolo.com](http://www.iolo.com). For more information, contact Iolo Technologies at 626-793-3993 or 877-239-IOLO or visit [www.iolo.com](http://www.iolo.com).



# SUBSCRIBE TO NUTS & VOLTS TODAY!

Just fill out this card  
and drop it in the mail.

Or call

**1-800-783-4624**

Or fax to

**909-371-3052**

Or E-Mail to

**subscribe@nutsvolts.com**

Or visit our Web site at **http://www.nutsvolts.com**

You can also order a subscription directly  
through our Web site with "secure" encrypted  
transactions to protect your credit card information.  
*Check it out and take advantage of  
our special subscription offer!*


When using your Visa or MC, it is advisable to  
enclose the card in an envelope.

Use this FREE Reader Service  
card to get more information  
on products or services  
advertised in this issue.

Write in the number on the  
card that corresponds with the  
ad and mail, fax, or E-Mail it to  
the numbers listed above.

If you use E-Mail or a form  
other than this card, be sure to  
include all the information  
on the card including the  
ad number in the upper  
right corner. *Without it, we  
cannot process your request!*

0899

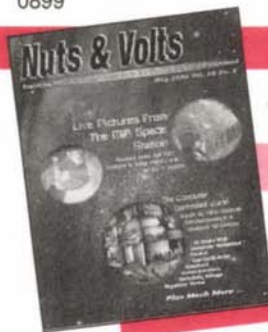

## Subscribe Today And Receive 54% Off The Newsstand Price

**Yes!** Enter my subscription for one year at \$19\*  
and save me 54% off the newsstand price!

☐ Payment Enclosed ☐ BILL ME

\*Offer available in US only. ☐ 2-Year US only Subscription \$35 for 24 issues.

☐ 3-Year US only Subscription \$51 for 36 issues. ☐ Canada/Mexico USD \$37.

All other foreign countries (12 issues) ☐ USD \$50 Surface; ☐ USD \$100 Airmail.

Are you active in electronics in:

- ☐ your profession  
☐ your hobby  
☐ both

Would you classify your level of  
experience in electronics as:

- ☐ beginner  
☐ intermediate  
☐ advanced

Do you use the internet?

- ☐ Yes ☐ No

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE \_\_\_\_\_ ZIP \_\_\_\_\_

VISA/MC# \_\_\_\_\_ EXP. DATE \_\_\_\_\_

NAME AS IT APPEARS ON CARD \_\_\_\_\_

## Reader Service Card

Your Name \_\_\_\_\_

Company Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

Zip \_\_\_\_\_ Phone # \_\_\_\_\_

Account Number \_\_\_\_\_

### Please enter a subscription to Nuts & Volts.

☐ \$19.00 - 1 Year ☐ \$35.00 - 2 years

☐ \$51.00 - 3 Years ☐ Payment enclosed ☐ Bill me

0899

Are you active in electronics in:

- ☐ your profession ☐ your hobby ☐ both

Would you classify your level of experience in  
electronics as:

- ☐ beginner ☐ intermediate ☐ advanced

Do you use the internet?

- ☐ Yes ☐ No

Which subjects and features interest you in  
reading NUTS & VOLTS? Check all that apply.

- |   |  |
|---|--|
| <input type="checkbox"/> COMPUTERS        | <input type="checkbox"/> TECHNICAL ARTICLES    |
| <input type="checkbox"/> AMATEUR RADIO    | <input type="checkbox"/> KITS & PROJECTS       |
| <input type="checkbox"/> AMATEUR ROBOTICS | <input type="checkbox"/> ADVERTISING RESOURCES |
| <input type="checkbox"/> MICROCONTROLLERS | <input type="checkbox"/> PRODUCT REVIEWS       |
| <input type="checkbox"/> NEW TECHNOLOGY   | <input type="checkbox"/> EVENTS CALENDAR       |
| <input type="checkbox"/> LASERS           | <input type="checkbox"/> TECH FORUM            |
| <input type="checkbox"/> SCANNERS         | <input type="checkbox"/> Q & A                 |
| <input type="checkbox"/>                  | <input type="checkbox"/>                       |


**VOID AFTER  
October 1999**





NO POSTAGE  
NECESSARY  
IF MAILED  
IN THE  
UNITED STATES

**BUSINESS REPLY MAIL**

FIRST-CLASS MAIL PERMIT NO. 316 CORONA, CA

POSTAGE WILL BE PAID BY ADDRESSEE

***Nuts & Volts***

430 PRINCELAND COURT  
CORONA CA 91719-9938



PLACE  
STAMP  
HERE

***Nuts & Volts***

430 PRINCELAND COURT  
CORONA CA 91719-1300





# Build an LED Digital Thermometer

by Fred Blechman

**The LED Digital Thermometer — which can be assembled from an under-\$38.00 kit or from scratch — can measure temperatures in all kinds of environments from -040 degrees to +100 degrees Centigrade or (with modification) from -040 degrees to +212 degrees Fahrenheit.**

**Designed with a probe for dipping in liquids, it can also be used for ambient temperature measurements. Three large seven-segment LED digital displays provide visibility in darkness.**

## Background

Several types of measuring "instruments" are in common use. For example, most homes use measuring cups to measure volume, scales to measure weight, clocks to measure the passage of time, and thermometers to measure temperature. Modern technology has provided digital readouts for many of these devices.

Initially, light emitting diodes (LEDs) using seven-segment digital displays were used. These were easily readable in the dark, but difficult to read in daylight. More recently, liquid crystal displays (LCDs) — unreadable in the dark without a special "backlight" — have become popular. LED digital clocks and digital weighing scales are still common, but LED digital thermometers — readable in the dark — are relatively rare or very expensive.

## Measuring Temperature

The most common (and least expensive) thermometer consists of a closed glass tube filled with a colored organic liquid — such as alcohol — of known thermal expansion. The expansion is small, being about one thousandth of the original volume per degree Centigrade for alcohol. The more expensive (and more accurate) thermometers use mercury as the liquid, such as in clinical thermometers used to measure body temperature. The "height" of the liquid column in relation to an engraved calibrated scale indicates temperature.

Another common thermometer is the wall-mounted type with a large circular dial. Some of these consist of a spiral capillary tube with either liquid or gas that changes state or phase with temperature. The changing pressure or the volume in the

system activates gears and levers to move a pointer above the circular scale. Others — such as common wall thermostats — typically use a spiral bimetallic strip that depends on the differential thermal expansion of two dissimilar metals. As the temperature changes, the spiral strip curls or uncurls, resulting in movement of the pointer (or mercury switch) by mechanical coupling.

None of the above thermometers lend themselves to electronic temperature measurement beyond "on" or "off." However, many metals, semiconductors, and ceramics change their electrical resistance with temperature in a known and reproducible manner.

This change in resistance results in a change of current or voltage, so it can be measured and then displayed in an analog or digital fashion. This is the basis for the digital thermometer assembled in this construction project.

## Digital Thermometer

The CEKIT K-038 Digital Thermometer — which can be assembled from a kit or from scratch — can measure temperatures in all kinds of environments from -040 degrees to +100 degrees Centigrade, or with modification, from -040 degrees to +212 degrees Fahrenheit.

The temperature sensor can be mounted at the end of a cable or probe for dipping in liquids, or it can be used for ambient temperature measurements. For example, in repairing electronic equipment, the probe could be used to monitor the temperature of an electronic component suspected of overheating.

Three .56-inch-high red LED seven-segment digital displays provide visibility in darkness. Although designed for short-time portable battery use, we include the simple

changes to allow use with plug-in external power that disconnects the battery, allowing constant operation.

Although originally designed for measuring temperature in Centigrade (where 000-degrees is freezing, and 100-degrees is the boiling point of water), we describe the few changes to have it read in Fahrenheit (where 032-degrees is freezing and 212-degrees is the boiling point of water). We also include a temperature conversion table and formulas.


It should be mentioned at this

may be available only from National Semiconductor distributors; we could not find a mail-order source or price.


On the other hand, the K-038 kit includes ALL parts and solder, plus a silkscreened etched and drilled printed circuit board, for a kit price of \$37.95.
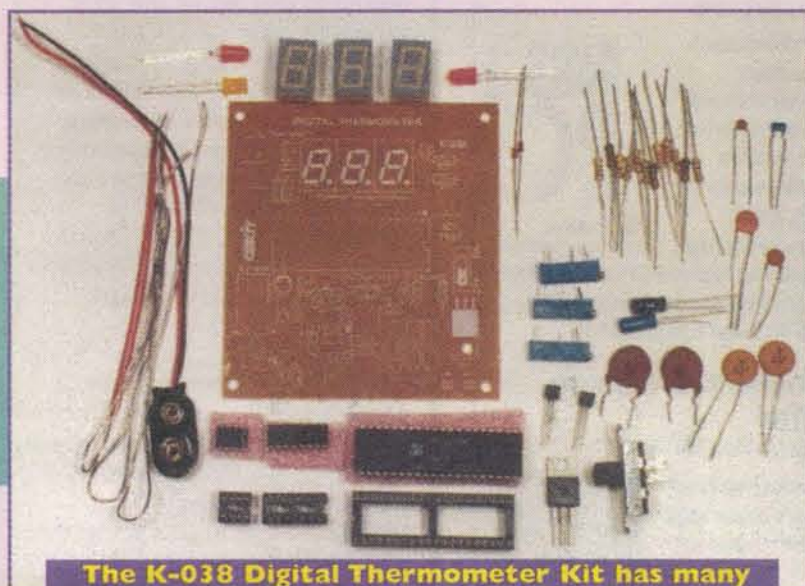
## Circuit Operation

For an overview of how the K-038 works, look at its block diagram, Figure 1. A known reference voltage



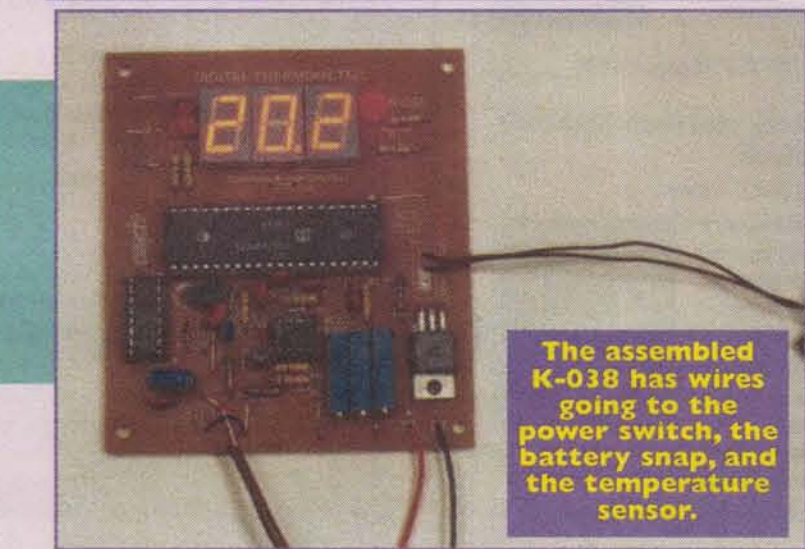**The K-038 Digital Thermometer Kit has many parts, including a fairly complex silkscreened printed circuit board.**



**The assembled K-038 has wires going to the power switch, the battery snap, and the temperature sensor.**

point that some of the parts necessary for this project may be difficult to find, or expensive. For example, we checked the price of the 40-pin ICL7107CPL 3-1/2-digit A/D converter 40-pin DIP integrated circuit from Thompson Consumer Electronics (their stock number SK10279) — \$25.00! Mouser has it for under \$7.00. The three seven-segment displays cost about \$2.00 each — if you can find them! And the LM335 temperature sensor integrated circuit

is provided by IC4. This is amplified and adjusted by IC3 and fed to one input of the analog/digital converter, IC1. At the same time, the temperature sensor, IC5, feeds a voltage that depends on temperature to the other voltage input of IC1.

IC1 is designed to compare the two voltage inputs and, using internal dual-slope conversion and drive circuitry, provides the appropriate outputs to light common-anode seven-segment LED displays.



## Great Books for Hobbyists, Students, Engineers . . .

### Simple, Low-Cost Electronics Projects

by Fred Blechman

Learn electronics with Fred Blechman's exciting new book. Begin with simple designs and progress to more sophisticated projects. Each project comes with a complete discussion of circuit theory and parts list, as well as information on troubleshooting and testing. Build voltmeters and multimeters, inductance and semiconductor testers, variable frequency audio oscillators, a photoelectric counter, and much more!

1-878707-46-9/224 pages/\$19.95



### Controlling the World with Your PC

by Paul Bergsman

PC Disk Included! Connect your computer to the real world and make it do useful work like controlling stepper motors, turning appliances on and off, or monitoring fluid levels. PC disk contains software files in ready-to-use form.

1-878707-15-9/208 pages/\$35.00



### The Forrest Mims Engineer's Notebook

by Forrest Mims III

This revised edition of Forrest's classic book includes hundreds of useful circuits built from integrated circuits and other parts available from convenient sources.

1-878707-03-5/156 pages/\$19.95



### The Integrated Circuit Hobbyist's Handbook

by Thomas R. Powers

Covers the major types of integrated circuit devices—linear, TTL, and CMOS—and provides complete details and theory about their operation. Contains lots of useful application circuits—an essential reference for every hobbyist.

1-878707-12-4/256 pages/\$19.95



Order on the Web!

For these and other great books  
on electronics, visit:

[www.LLH-Publishing.com](http://www.LLH-Publishing.com)

or

call 1-800-247-6553 to use a  
major credit card, or send check or  
money order to:

**LLH**

Technology Publishing  
3578 Old Rail Road  
Eagle Rock, VA 24085

## LED Digital Thermometer

The schematic (Figure 2) shows the complete circuit, and allows a more complete description of exactly how all this occurs. Obviously, the heart of the entire device is IC1, an ICL7107CPL 40-pin plastic dual-inline-pin (DIP) integrated circuit.

The pinouts of IC1 are shown in Figure 3. IC1 is designed to operate from a +5V and -5V supply. However, to operate from a single +5V supply, a negative supply can be generated from OSC 3 pin 38 of IC1 with two diodes, two capacitors, and an inexpensive IC. As shown in Figure 2, IC2—a 16-pin CD4049B hex inverter—C6, C7, D1, and D2 perform this function, and provide a DC voltage to pin 26, the V<sub>-</sub> pin of IC1.

Internal IC1 circuitry connected to pins 38, 39, and 40 is used with capacitor C1 and resistor R7 to create an oscillator operating at about 48kHz as a "clock" used in the dual-slope conversion process. This provides about three readings per second. (See *Nuts & Volts*, March '98, "Build the Elenco \$20.00 Digital Multimeter Kit," for a more complete explanation of the dual-slope conversion process.)

Capacitors C2, C3, C4, C5, and resistor R11 are external components required for proper IC1 operation. Pin 1 of IC1 receives a regulated +5V from a 9V DC battery or power supply feeding VR1, an LM7805 voltage regulator, together with filtering capacitors C8 and C9, with IC1 pin 21 as the ground return.

The voltage at pin 36 compared to the voltage at pin 35 of IC1 determines the scale at which IC1 measures input voltage. This is determined by the setting of multi-turn potentiometer R8, fed by resistor R9 from the regulated +5 volt supply, as you'll see during "Calibration."

Two input voltages are provided

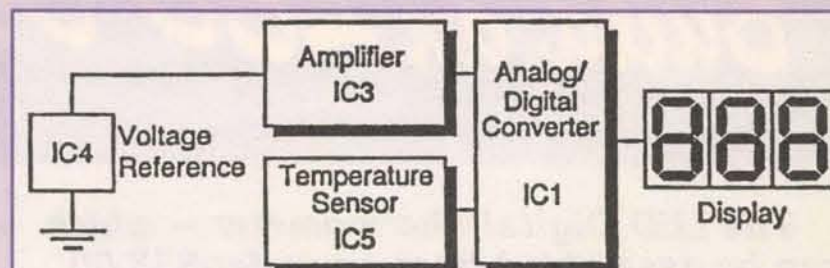


Figure 1: K-038 Digital Thermometer Block Diagram

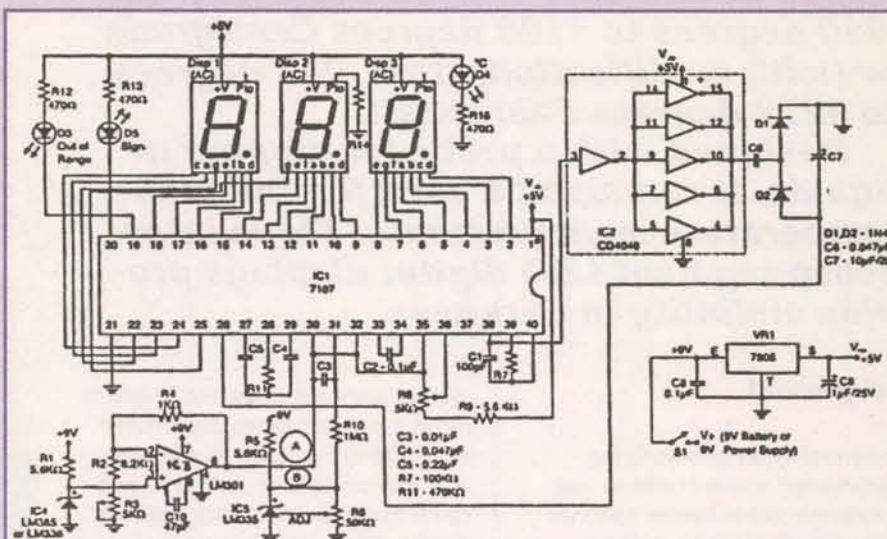


Figure 2: K-038 Digital Thermometer Schematic

to IC1 at pins 30 and 31. One is stable, the other varies with temperature, and IC1 measures this difference and converts this measurement to light the appropriate digital numbers on the display.

The voltage fed to IN LO pin 30 of IC1 comes from the pin 6 output of IC3, an LM301 operational amplifier eight-pin integrated circuit. IC4, an LM336 2.5-volt zener diode is fed from the 9V supply through resistor R1. Its zener action provides 2.5 volts to pin 3 of IC3. However, the other input of IC3, pin 2 is adjusted (as you'll see during "Calibration") by means of multi-turn potentiometer R3, R2, and feedback resistor R4, to provide a specific stable IC3 output

voltage to pin 30 of IC1. We'll call this Voltage A. This voltage sets the temperature range to be read.

The voltage fed to IN HI pin 31 of IC1 comes from a network composed of resistors R5 and R10, multi-turn potentiometer R6, and adjustable temperature sensor IC5, an LM335.

IC5 is shown in Figure 4. This three-pin temperature sensor looks like a transistor, but is actually an integrated circuit with 16 transistors, two capacitors, and 10 resistors! The voltage across its output is adjustable by the voltage seen at the ADJ pin. Once adjusted, the positive terminal then increases in 10-millivolt (0.01 volt) increments with each positive

### K-038 Digital Thermometer Parts List

All resistors 1/4-watt 5% carbon

R1, R5, R9 - 5.6K  
R2 - 8.2K  
R3, R8 - 10-turn 5K potentiometers  
R4 - 1K  
R6 - 10-turn 50K potentiometer  
R7 - 100K  
R10 - 1 megohm  
R11 - 470K  
R12, R13, R14, R15 - 470-ohm

Capacitors are 50V ceramic disc unless otherwise specified

C1 - 100pF  
C2, C8 - 0.1mF  
C3 - 0.01mF  
C4, C6 - 0.047mF  
C5 - 0.22mF  
C7 - 10mF 25V electrolytic  
C9 - 1mF 25V electrolytic or tantalum  
C10 - 47pF  
D1, D2 - 1N4148 signal diode  
D3, D4 - Red 5mm round LED  
D5 - Yellow flat LED  
IC1 - ICL7107CPL 3-1/2 digit A/D converter  
IC2 - CD4049B hex inverter

IC3 - LM301 operational amplifier  
IC4 - LM336 2.5-volt zener diode  
IC5 - LM335 temperature sensor  
VR1 - LM7805 5-volt regulator  
DISP1,2,3,4 - .56-inch 7-segment high-efficiency red common-anode display (MAN6960 or equivalent)  
S1 - SPST slide switch  
**Miscellaneous:** Printed circuit board etched, drilled, and silk-screened; nine-volt battery snap; three IC sockets (eight-pin, 16-pin, and 40-pin); hookup wires; solder.


Optional parts for Fahrenheit conversion:

R16 - 2.2K  
R17 - 10K  
R3 - 50K multi-turn potentiometer
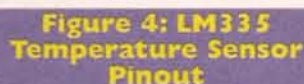
### Source

A complete kit of all parts above (possibly even including the optional parts by the time you read this) is available as the CEKIT K-038 Digital Thermometer Kit from **Centerpointe Electronics, Inc.**, 5241 Lincoln Avenue, Suite A6, Cypress, CA 90630. The price \$37.95 plus \$5.00 shipping and handling. California residents add 7.75% sales tax. Phones: (800) 272-2737 or (714) 821-1100. Fax: (714) 828-0282. Call or fax for their FREE 14-page Educational Electronic Kits Catalog. Internet: <http://www.cpcare.com>.






As mentioned earlier, some of the parts required for this project may be difficult to find, or expensive. Although you could build this project from the information provided, we will assume you are assembling the K-038 from the kit described under "Source."

You might also give thought to packaging (discussed later) in which case, you might wish to mount the power switch, SI, off the board. The voltage regulator, VRI, gets pretty hot in extended operation, and you might want to add a heatsink to the tab, bearing in mind that the tab is connected internally to the GROUND pin of VRI.

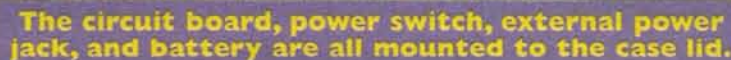The next adjustment is made to R3, which is set to read exactly 2.73 volts between output pin 6 and



To aid you in converting from Centigrade to Fahrenheit temperatures, see Table 1. The formulas for

**CONVERGENT, INC.**  
1-888-577-7285, 716 River Crest, Leander, TX 78641  
[www.convergentinc.com/radio](http://www.convergentinc.com/radio)



# Serial in, graphics out. Almost too easy.

These serial displays take RS-232 at 2400 or 9600 baud and produce stunning text and graphics on a supertwist LCD screen. See our complete line at [www.seetron.com](http://www.seetron.com). All models are in stock for immediate delivery.

## G12032 120x32-pixel LCD

SGX-120L \$99.00  
Same size as 2x16 text LCD  
Editable font(s) in 4 sizes  
Up to 6 screens in EEPROM  
Easy terminal protocol



(3.2 x 1.4 in.)



(3.7 x 2.8 in.)

## G12864 128x64-pixel LCD

BGX-128L-I \$199.00  
Large, sharp LCD  
Editable font(s)  
Up to 14 screens in flash  
Separate text, graphics layers  
DB9 connector built in  
AC adapter jack built in  
Easy terminal protocol

[www.seetron.com](http://www.seetron.com)

Scott Edwards Electronics, Inc. ph 520-459-4802 fx 520-459-0623 nnv@seetron.com

Write in 109 on Reader Service Card.

## E-Math Pro Windows version!


E-Math is the Essential Formula Tool for Engineers, Technicians, and Students.

### Features

- Over 300 formulas
- Ability to rotate equations.
- Solve for any variable.
- Help for each equation.
- Win95, Win98, NT compatible

### Formula Categories:

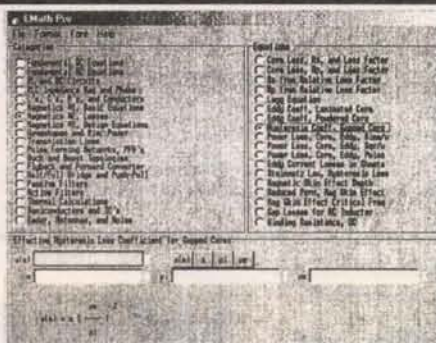- (A) Fundamental DC Formulas
- (B) Fundamental AC Formulas
- (C) RL and RC Circuits
- (D) RLC Impedance Magnitude and Phase
- (E) L's, C's, R's and Conductors
- (F) Magnetism #1, Basic Equations
- (G) Magnetism #2, Losses
- (H) Magnetism #3, Design Equations
- (I) Waveforms and Miscellaneous Power
- (J) Transmission Lines
- (K) Pulse Forming Networks
- (L) Buck and Boost Topologies
- (M) Flyback and Forward Converters
- (N) Half/Full Bridge and Push-Pull Topologies
- (O) Passive Filters
- (P) Active Filters
- (Q) Thermal Calculations
- (R) Semiconductors and Integrated Circuits
- (S) Radar, Antennas and Noise



E-Math Pro Windows v1.0  
\$49.95

Bytech Services  
[www.bytechservices.com](http://www.bytechservices.com)  
US Toll-free: 1-888-422-7521  
Voice/FAX (360) 422-7520

Dealer and Distributor  
inquiries - YES



Bytech Services

## LED Digital Thermometer

conversion are:

Fahrenheit Degrees =  
(1.8 times Centigrade Degrees)  
+ 32  
Centigrade Degrees =  
(Fahrenheit Degrees - 32)  
times .5555

### Troubleshooting

If the displays don't come on when you apply power, check for approximately +9V DC at the input pin of VRI (right pin looking down on PC board with displays at the top of the board) and +5V DC at the output (left) pin. The center pin and metal tab are ground.

Once you have power, the displays should come on. Connect +5V briefly to TEST pin 37 of IC1 to assure that all segments (but not all decimal points) light. Looking at Figure 5, you'll see how the segments are identified (A-G). The schematic (Figure 2 and Figure 3) shows you which pins on IC1 drive each segment of each display. If a segment doesn't light during TEST, check the solder connections at IC1 and the display.

Any other problems can probably be traced to a bad solder joint, an incorrect part location, improper orientation of a polarity-sensitive part, or an IC plugged in "backwards." Troubleshooting is more of an art than a science, and takes patience, as well as thought.

### Modifications

As this is being written, the manufacturer of the K-038 kit is planning to modify the circuit board

Pin No.	Function	Pin No.	Function
1	Cathode E	6	Cathode B
2	Cathode D	7	Cathode A
3	Anode	8	Anode
4	Cathode C	9	Cathode F
5	Cathode D,P	10	Cathode G

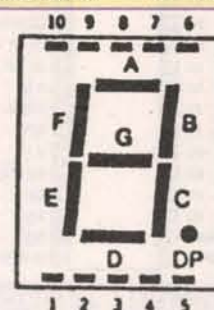


Figure 5: Seven-Segment Display Pinout

and provide the additional parts to allow you to build the kit for either Centigrade or Fahrenheit readout. If your kit has this option, follow the kit instructions.

However, if you are building from scratch with the circuit and PC board shown, then there are only some small changes needed. For one thing, since your displays will now read in full digits (-032 to +212 and beyond), the decimal point is no longer needed, so remove resistor R14.

Resistors R16 (2.2K) and R17 (10K) are added to the circuit as shown in Figure 8. This is most easily done at the bottom of the printed circuit board.

Remove Jumper 7, noting the top and bottom solder pads from which it is removed. Now solder one end of R16 to the pin 3 pad of IC3. Solder one end of R17 to the bottom pad from which Jumper 7 was removed. Next, connect the free ends of R16 and R17 to the top

°C	°F	°C	°F	°C	°F	°C	°F
100	212.0	63	145.4	26	78.8	-11	12.2
99	210.2	62	143.6	25	77.0	-12	10.4
98	208.4	61	141.8	24	75.2	-13	8.6
97	206.6	60	140.0	23	73.4	-14	6.8
96	204.8	59	138.2	22	71.6	-15	5.0
95	203.0	58	136.4	21	69.8	-16	3.2
94	201.2	57	134.6	20	68.0	-17	1.4
93	199.4	56	132.8	19	66.2	-18	-0.4
92	197.6	55	131.0	18	64.4	-19	-2.2
91	195.8	54	129.2	17	62.6	-20	-4.0
90	194.0	53	127.4	16	60.8	-21	-5.8
89	192.2	52	125.6	15	59.0	-22	-7.6
88	190.4	51	123.8	14	57.2	-23	-9.4
87	188.6	50	122.0	13	55.4	-24	-11.2
86	186.8	49	120.2	12	53.6	-25	-13.0
85	185.0	48	118.4	11	51.8	-26	-14.8
84	183.2	47	116.6	10	50.0	-27	-16.6
83	181.4	46	114.8	9	48.2	-28	-18.4
82	179.6	45	113.0	8	46.4	-29	-20.2
81	177.8	44	111.2	7	44.6	-30	-22.0
80	176.0	43	109.4	6	42.8	-31	-23.8
79	174.2	42	107.6	5	41.0	-32	-25.6
78	172.4	41	105.8	4	39.2	-33	-27.4
77	170.6	40	104.0	3	37.4	-34	-29.2
76	168.8	39	102.2	2	35.6	-35	-31.0
75	167.0	38	100.4	1	33.8	-36	-32.8
74	165.2	37	98.6	0	32.0	-37	-34.6
73	163.4	36	96.8	-1	30.2	-38	-36.4
72	161.6	35	95.0	-2	28.4	-39	-38.2
71	159.8	34	93.2	-3	26.6	-40	-40.0
70	158.0	33	91.4				
69	156.2	32	89.6				
68	154.4	31	87.8				
67	152.6	30	86.0				
66	150.8	29	84.2				
65	149.0	28	82.4				
64	147.2	27	80.6				

Table 1:  
Temperature  
Conversion  
Chart



# ELECTRONIC TEST EQUIPMENT BOUGHT & SOLD

90 DAY WARRANTY PARTS & LABOR • 10 DAY RIGHT OF RETURN, OPEN ACCOUNTS

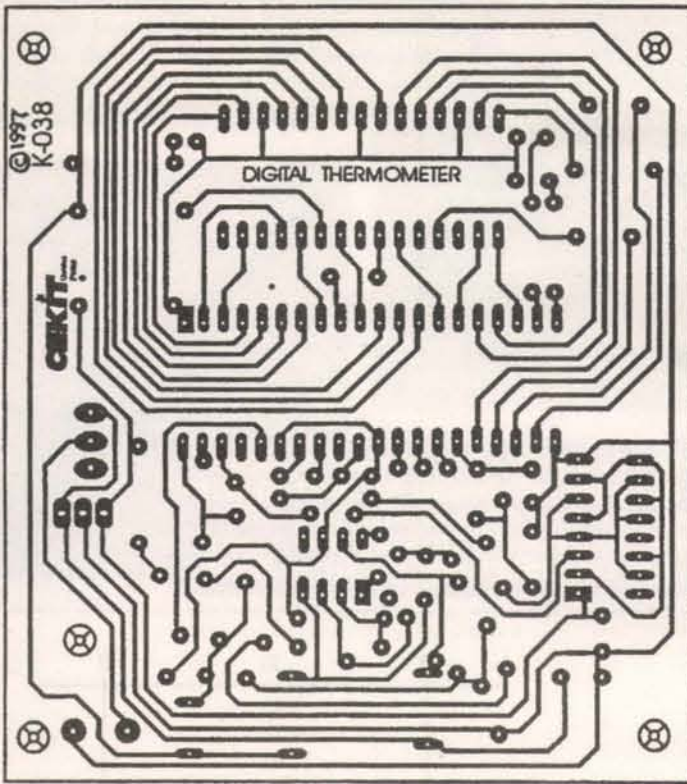


Figure 6: K-038 Printed Circuit Board Layout

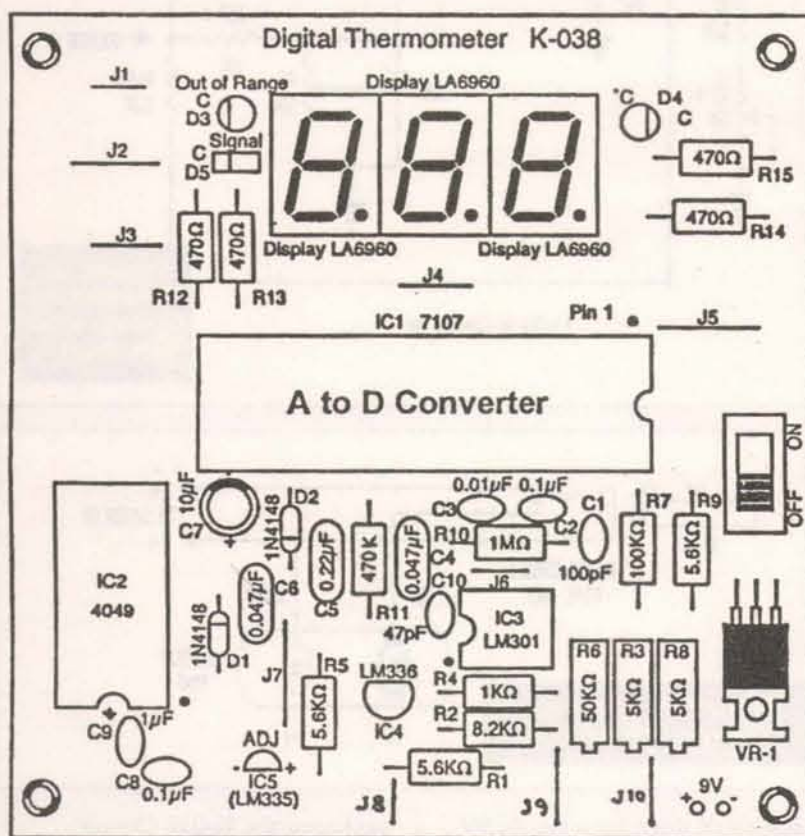


Figure 7: K-038 Parts Layout

point where Jumper 7 was removed. Note that Voltage B is now at the intersection of R10, R16, and R17.

One other change is required. Unsolder 5K potentiometer R3 and replace it with a 50K multi-turn potentiometer. This completes the changes, but now you must recalibrate. Set potentiometer R8, as before, to one volt between pins 36 (positive) and 35. This allows an analog input voltage range of zero to two volts, the same as with Centigrade readings.

Set the replaced potentiometer R3 to a new voltage of 2.554 volts from output pin 6 and ground pin 4

of IC3, the LM301 operational amplifier. This sets Voltage A (pin 30 of IC1) so that when Voltage A and Voltage B are identical, the display will read 000. With the new resistor network connected to IC5, the Voltage A to Voltage B difference is one millivolt (0.001 volts) for each one degree Fahrenheit change in sensor temperature.

Now adjust potentiometer R6 so the display reads the actual sensor Fahrenheit temperature, and you are finished with the conversion.

When operated on battery power, the K-038 uses about 200 millamperes, which is well beyond

Ailtech 360D11, Frequency Syn.	\$800	HP 86601A, RF Plug-In, 110MHz.	\$300
Ailtech Type 32, Precision Attenuator, 0-100dB	\$300	HP 86602A, RF Plug-In, 1300MHz.	\$500
Argosystems AS210, Frequency Calibration System	\$2,000	HP 86603A, RF Plug-In, 2600MHz.	\$1,000
Austron 2100R, Loran-C Frequency Monitor	\$500	HP 8697A, RF Plug-In, 26.5-40GHz.	\$250
Bird 4381, RF Power Analyst, Opt. 832	\$200	HP 8743A, Reflection Transmission Test Set, 18GHz	\$300
Boonton 82AD, Modulation Meter	\$450	HP 8750A, Storage Normalizer, Includes Cable	\$250
Boonton 92BD, Digital RF Millivolt Meter	\$250	HP 8753B, Network Analyzer, Opt. 002,006,010	\$8,000
Boonton 102B, Signal Generator, 45-520MHz.	\$500	HP 8756A, Scalar Network Analyzer	\$1,500
Boonton 518-A4, O Standard	\$100	HP 8901A, Modulation Analyzer	\$1,000
Boonton 2500, DC Range Calibrator	\$250	HP 8903B, Audio Analyzer, Opt. 001	\$2,000
Boonton 4G, Power Meter Sensor, .01-26.5GHz.	\$200	HP 8920D, Dual-Mode Cellular Mobile Test System	\$8,000
Boonton 4200, Power Meter w/4G Sensor, Cable	\$500	Opt. 002,008,014	\$250
Boonton 4220/51013, Power Meter with Sensor	\$600	HP E3617A, DC Power Supply, 0-40V, 1A	\$250
Boonton 4300, Power Meter, 2 Channel	\$1,200	HP P486A, Power Sensor, 12.4-18GHz.	\$100
Brüel & Kjær 1612, Bandpass Filter	\$250	HP X486A, Power Sensor, 8.2-12.4GHz.	\$100
Calif. Inst. 101T, AC Power Source	\$400	Hughes 8010H, TWT Amplifier, 3-8GHz	\$1,000
Eaton 380K11, Frequency Synthesizer, 1-2000MHz	\$2,000	Huntron HTR 1005B, Tracker Component Tester	\$200
EIP 371, Source Locking Microwave Counter, 18GHz	\$1,000	Huntron 5100DS, Computer Controlled Troubleshooting	\$1,200
EIP 578, Source Locking Microwave Counter, 26.5GHz	\$2,200	System	\$1,200
EIP 931, Microwave Source, .01-18.6GHz, Opt. 9320	\$6,000	Keithley 192, Programmable DMM, 6.5 Digits, HP/IB	\$600
ESI 296, Auto LCR Meter	\$800	Keithley 195A, Digital Multimeter	\$300
Fluke 515A, Portable Calibrator	\$800	Keithley 614, Electrometer	\$700
Fluke 540B, Thermal Transfer Standard	\$500	Krohn-Hite 3202, Filter, LP, HP, BP, Unused	\$350
Fluke 5450A, Programmable Resistance Calibrator	\$1,000	Leeds & North 1091, Capacitor Decade, .001uF-1uF	\$150
Fluke 6010A, Frequency Synthesizer, 10Hz-11MHz	\$300	Micronetics NSI-S2640W, Noise Source, 26.5-40GHz.	\$350
Fluke 6080A/AN Frequency Syn., 5-1024MHz	\$4,000	Micro Sciences ICT-101, IC Tester	\$300
Fluke 8520A, Digital Multimeter	\$250	Ming HT-21, Handy IC Tester	\$100
Fluke 8922A, True RMS Voltmeter	\$250	Narda 5082, High Directivity Bridge, 2-18GHz	\$300
Fluke A55, Thermal Converter	\$200	Narda 5292 Directional Coupler, 1-18GHz	\$200
FTS 1150/001, Frequency Standard	\$400	Racal Dana 1515, Delay Pulse Generator	\$500
General Microwave 478A, Peak Power Meter	\$700	Racal Dana 1992, Frequency Counter, High Stab.	\$500
General Radio 1557, Vibration Calibrator	\$400	Racal Dana 9082P, Signal Gen. 1.5-520MHz	\$400
Gigatronics 600/6-12, Frequency Synthesizer	\$1,000	Simco A300, Aerostat Anti-static	\$100
Gigatronics 600/10-18, Frequency Synthesizer	\$1,500	Tek 134, Probe Amplifier for P6021 & P6022	\$100
Gigatronics 910, Frequency Synthesizer, .05-26GHz, Opt. 03/06	\$8,000	Tek 1470, NTSC Color Sync & Test Sig. Generator	\$500
Guideline 9154C, Transvolt Standard Cell	\$300	Tek 1502, TDR, Opt. 4, Chart Recorder	\$1,000
Guideline 9577, Precision DMM, 7.5 Digits	\$300	Tek 1502C, TDR	\$3,500
Hitachi V-212, Scope, 20MHz, Dual Trace	\$200	Tek 1503/01/05, TDR, Scale in Meters	\$1,000
HP 1122A, Probe Power Supply	\$200	Tek 178, Linear IC Test Fixture, For 577	\$150
HP 11590A, Bias Network	\$250	Tek 1730D, Digital Waveform Monitor	\$500
HP 11604A, Universal Extension	\$100	Tek 2246, Oscilloscope, 4-Channel, 100MHz, Cursors	\$1,200
HP 11605A, Flexible Arm	\$100	Tek 2432, Scope, Digital, 300MHz, 4 Channel, HP/IB	\$2,000
HP 11638A, Calibration Kit, Type N	\$100	Tek 2445A, Scope, 150MHz, 4 Channel	\$1,200
HP 11665B, Modulator	\$250	Tek 2445B, Scope, 150MHz, 4 Trace, HP/IB	\$1,500
HP 11713A, Attenuator Switch Driver	\$400	Tek 2465, Scope, 300MHz, 4 Channel	\$1,500
HP 11869A, Adaptor for Plug-In 8350A/B	\$350	Tek 305DMM, Scope, 10MHz, Dual Trace, DMM, battery	\$500
HP 11970A, Harmonic Mixer, 26.5-40GHz	\$800	Tek 318, Logic Analyzer w/pds	\$500
HP 11970K, Harmonic Mixer, 18-26.5GHz	\$800	Tek 464, Scope, 100MHz Dual Trace, Storage	\$400
HP 11970Q, Harmonic Mixer, 33-50GHz	\$800	Tek 492, Spectrum Analyzer, Opt. 01/02	\$4,500
HP 1600A, Logic Analyzer w/pds	\$400	Tek 492/02, Spectrum Analyzer	\$4,000
HP 1630D, Logic Analyzer w/pds	\$500	Tek 492BP, Spectrum Analyzer	\$8,500
HP 16530A/16531A, Digital Scope Card, 16500A System	\$500	Tek 492P, Spectrum Analyzer, Opt. 01,02	\$5,000
HP 214B, Pulse Generator	\$1,000	Tek 576, Curve Tracer	\$2,000
HP 33102A, Microwave Switch, 100MHz-18GHz	\$100	Tek 604, XY Monitor	\$100
HP 3314A, Function Generator, Opt. 001	\$1,500	Tek 7D20, Programmable Digitizer PI	\$600
HP 3325A, Function Generator	\$1,000	Tek 7S11, Sampling Unit w/S4 Head, DC-14GHz	\$800
HP 3325A/01/02, Function Gen., Opt. 01/02	\$1,500	Tek AM503/A6302, Current Probe, Amp & Power Supply	\$800
HP 33322H, Programmable Attenuator, DC-18GHz	\$250	Tek DC503, Universal Counter Timer TM500	\$100
HP 339A, Distortion Analyzer	\$900	Tek DM502A, Autoranging DMM	\$150
HP 3400A, RMS Voltmeter, 10Hz-10MHz	\$200	Tek FG501, Function Generator, 1MHz	\$100
HP 3403C, True RMS Voltmeter	\$200	Tek FG502, Function Generator, 1Hz-11MHz	\$250
HP 3456A, Digital Multimeter	\$600	Tek P6046, Differential Probe	\$300
HP 3468A, Multimeter, 5.5 Digits	\$400	Tek P6201, FET Probe Kit, 900MHz	\$400
HP 35689A, S-Parameter Test Set for 3589A	\$1,400	Tek P6202A, FET Probe, 500MHz unused	\$300
HP 3582A, Spectrum Analyzer, .02-25.5KHz	\$1,800	Tek P6602, Temperature Probe for DM5110, DM511	\$150
HP 4140B, Picoammeter, DC Source	\$2,000	Tek PG506, Scope Cal System w/TS501, SG503,	\$1,500
HP 4274A, Multi-frequency LCR Meter, Opt. 001,002,003	\$3,000	New Style	\$1,500
HP/IB, includes Test Fixture	\$300	Tek PG508, Pulse Generator, 50MHz	\$300
HP 435B, Power Meter	\$350	Tek PS503A, Dual Power Supply	\$150
HP 436A/022, Power Meter, HP/IB	\$800	Tek SC502, Scope, 15MHz, Dual Trace	\$200
HP 438A, Power Meter	\$2,600	Tek SG502, Sig. Gen. 5Hz-50KHz	\$200
HP 5005B, Signature Multimeter	\$350	Tek TDS410, Digitizing Oscilloscope, 150MHz	\$2,800
HP 5006A, Signature Analyzer	\$300	Tek TDS410A, Digitizing Scope, 200MHz, Opt. 13,1F	\$3,000
HP 5316A, Universal Counter, Opt. 004	\$200	Tek TG501, Time Mark Generator	\$200
HP 5334A/020, Universal Counter w/DVM	\$600	Tek TM503, 3 Slot Power Module	\$100
HP 5335A/010, Frequency Counter	\$600	Tek WM490A, Waveguide Mixer, 26.5-40GHz.	\$800
HP 5335A/030, Frequency Counter, 1300MHz	\$800	Tek WM490K, Waveguide Mixer, 18-26.5GHz.	\$800
HP 5340A, Frequency Counter, 18GHz	\$600	Texscan SSG2000, Freq. Syn., 100KHz-2GHz,	\$1,800
HP 5340A, Frequency Counter w/01/02/011	\$800	AM, FM	\$1,800
HP 5342A, Microwave Counter	\$1,000	Ungar 4624, Solder, Desolder Station	\$250
HP 5345A, Frequency Counter, Opt. 012	\$400	Valhalla 2000, Auto Digital Watt-Ammeter	\$200
HP 5350A/010/002, Microwave Frequency Counter	\$2,000	Vu-Data 5110, Semiconductor Tester, In/out Circuit	\$150
HP 54100D, Digital Scope, 1GHz	\$2,000	Wavetek 178, 50MHz Programmable Waveform Syn.	\$1,000
HP 54200A, Digital Storage Scope	\$800	Wavetek 180, Sweep/Function Generator	\$200
HP 54601A, Digital Scope, 100MHz, 4 Channel	\$1,600	Wavetek 185, Sweep Function Gen., .0001-5MHz	\$400
HP 6112A, Power Supply, 0-40V, 0.5A	\$200	Wavetek 188, 5MHz Phase Lock Generator	\$200
HP 8015A, Pulse Generator, 1Hz-50MHz, 30V	\$500	Wavetek 1084, Signal Gen. Sweeper, 3.5-4.5GHz	\$300
HP 8165A, Programmable Signal Source, .0001-50MHz	\$1,000	Wavetek 1910, XY Monitor, Dual Trace	\$400
HP 8165A, Programmable Signal Source, Opt. 02/03	\$1,200	Wavetek 452, Filter, Dual Hi/Low, 1Hz-10KHz	\$450
HP 8350B, Sweep Oscillator Mainframe	\$2,000	Wavetek 7530A, FFT Spectrum Analyzer 0-100KHz	\$500
HP 83540A, RF Plug-In, 2-8.4GHz	\$1,200	Wavetek 907, Signal Generator, 7-11GHz	\$600
HP 83545A, RF Plug-In, 5.9-12.4GHz	\$1,200	Wavetek 955, Micro Source, 7.5-12.4GHz, AM, FM,	\$1,000
HP 8410C/8412B, Network Analyzer	\$800	Sweep	\$1,000
w/8411A/Opt. 18, 18GHz	\$250	Wiltron 560-7K50, RF Detector, 10MHz-40GHz	\$400
HP 8411A, Frequency Converters	\$250	Wiltron 6100, Sweeper Mainframe	\$250
HP 8414A, Polar Display	\$100	Wiltron 6213D, RF Plug-In, 10MHz-4.2GHz	\$400
HP 8444A, Tracking Generator	\$650	Wiltron 6219D, RF Plug-In, 2-8GHz	\$200
HP 8445B, Spectrum Anyz., Automatic Pre-Selector	\$300	Wiltron 6223D, RF Plug-In, 4-12.4GHz	\$250
HP 8447E, Amplifier, 1-1300MHz, Gain 22dB	\$600	Wiltron 6229D, RF Plug-In, 7.9-18.5GHz	\$300
HP 8481H, Power Sensor, 18GHz, 3 watts	\$400	Wiltron 62FF75, VSWR Bridge, 10-1000MHz	\$150
HP 8501A, Storage Normalizer, w/cable	\$800	Wiltron 6NFS0, Autotester, 1-1500MHz, for 640	\$100
HP 85033C, 3.5mm Calibration Kit	\$1,000	Wiltron 7B50, Detector, 1-1500MHz, for 640	\$100
HP 8505A, Network Anyz. w/8501A & 8503A, Opt. 05	\$4,000		
HP 85021B, Directional Bridge, 10MHz-26.5GHz	\$1,200		
HP 8557A/180TR, Spectrum Analyzer, .01-350MHz	\$1,000		
HP 8558B, Spectrum Analyzer, .1-1500MHz	\$1,300		
HP 8559A, Spectrum Analyzer, .01-21GHz	\$2,000		
HP 8559A/853A, Spectrum Analyzer, Digital, .01-21GHz	\$3,000		
HP 8565A, Spectrum Analyzer, .01-22GHz, Opt. 100	\$3,500		
HP 8569A, Spectrum Analyzer, 10MHz-22GHz	\$5,000		
HP 86220A, RF Plug-In, 10-1300MHz	\$500		
HP 86241A, RF Plug-In, 3.2-6.5GHz	\$400		
HP 86260A, RF Plug-In, 12.4-18GHz	\$400		
HP 86290A, RF Plug-In, 2-18GHz	\$1,200		
HP 86290B, RF Plug-In, 2-18GHz	\$1,400		
HP 8643A, Synthesized Frequency Generator	\$6,000		
HP 8656B, Signal Generator, 1-990MHz, AM/FM	\$1,500		
HP 8660C, Freq Syn w/86603A & 86635A, 2.6GHz	\$2,500		

**MONTHLY CLEARANCE SALE**  
HP 3325A PROGRAMMABLE FREQUENCY SYNTHESIZER,  
.001Hz-21MHz, 11 DIGIT DISPLAY, HP/IB PROGRAMMABLE,  
OUTPUT 1mV-10V INTO 50Ω. **\$795**

## PHELPS INSTRUMENTS

2631 Hillside Ave., Norco, CA 91760  
909-279-7347 • FAX 909-279-7323





# TECH FORUM

Continued from page 32

engine speed for 60N. It should read from 50 CPM to 65 CPM.

A dirt cheap and simple way to measure the frequency output of your engine-driven generator is to use a clock! Yes, a clock! Older style clocks used a synchronous motor that relied on the 60 Hz stability of the power line to determine time.

It is important to use a motor driven clock, preferably with a sweep second hand. Adjust the speed of the engine up or down to make a "minute" of indicated clock time equal to a true minute, as determined say by your wristwatch.

Michael Mruzek  
via Internet

## ANSWERS TO #6996 - JUNE 1999

According to a dairy farmer friend who owns a PTO-driven generator, measuring generator speed is done with the instrumentation already on the tractor and generator.

Since the PTO is connected to the engine through a fixed-ratio gear reducer, the engine's tachometer will indicate PTO speed after dividing the reading by the gearbox ratio.

Some tractor tachometers have the PTO speed already on them as a secondary calibration, much like car speedometers that are calibrated for MPH and KPH. Also, PTO-driven generators almost always have a frequency meter as part of their instrument set.

When running the generator, my farmer friend relies on this instead of the tractor's tachometer.

If you don't have either of these instruments, you have a few options. The first — and perhaps the simplest — would be to install a tach on the tractor. Find out the gear ratio between the engine and the PTO, then divide the tach reading by this ratio to get the PTO speed.

Since almost all implements, including generators, are designed for a PTO speed of 540 RPM, just open up the throttle to a speed just a little faster, then apply the load to the generator. You can find your PTO gearbox ratio by inspection — crank the engine by hand (does yours have a hand starter on the front?) and count. How many turns the engine makes for one turn of the PTO.

If you don't want to or can't install a tach, you have several low-cost options. The first is to build a frequency meter. Install several magnets on the PTO shaft and a Hall sensor to measure PTO rotation. Feed that signal to a frequency-to-voltage converter such as a one-shot, a dedicated V-F chip, or a PLL, then connect the output of that circuit to an indicator such as a bargraph or a meter.

Another method would be to monitor the output of the generator with a frequency counter. Use a step-

down transformer to both reduce the voltage of the signal and to provide isolation. A simple bell transformer would do. Finally, check with Fair Radio Sales [www.fairradio.com](http://www.fairradio.com) to see if they have any surplus vibrating reed frequency meters.

These were used extensively by the military because they were rugged and reliable. They fell out of favor largely because they became much more expensive to manufacture than modern electronic indicators.

As a final word, check the generator carefully prior to using it on a critical or expensive load. Make sure it keeps its output voltage within a reasonable range under full, partial, and no-load conditions, and check that it is properly fused and grounded.

David B. Sarraf  
via Internet

## ANSWER TO #7992 - JULY 1999

I need information on building a variable frequency drive for a single phase motor. I would like to build one to adjust the speed on a wood turning lathe.

Single phase motors are wound for a given frequency, due to their impedance. Altering the frequency will overheat the windings. What you want is one of two methods of altering the voltage while keeping the current the same.

One method is to use a "auto transformer" commonly referred to as a "variac."

The other method uses a "chopper" which is used readily as a "light dimmer."


The light dimmer is sold at most hardware stores for around \$5.00 and it works quite well, but it has some flaws. As you lower the voltage very low on a motor, the "chopped" pulses are noticeable on the lathe and cause pulsing in the motor which can affect the finish of the cut. At medium to high speed, there is no noticeable pulsing.

The other method — the Variac — is the best and most reliable method of total control over a motor's speed. It consists of two transformers in one that move in relationship to each other keeping the current totally constant while lowering the output side of the secondary transformer in voltage only.



This method not only has zero pulsing, but it is electronically quieter in terms of radio noise. I prefer the transformer over the chopper, but either works well.

A 600 watt variac sells for around \$20.00 to \$40.00 used, while a new one can cost anywhere from \$50.00 to over \$100.00. The chopper sells for \$5.00 and that is always a consideration.

Chris  
Bieber, CA

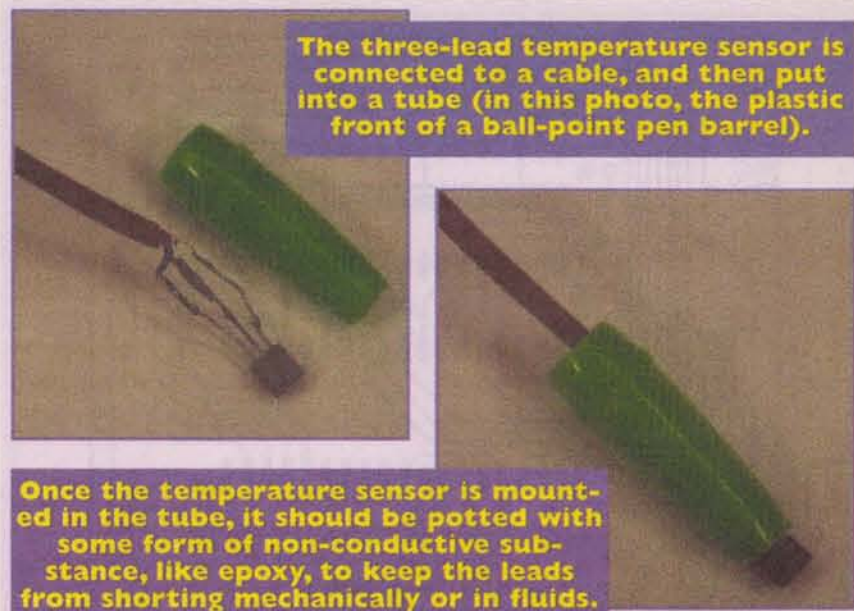

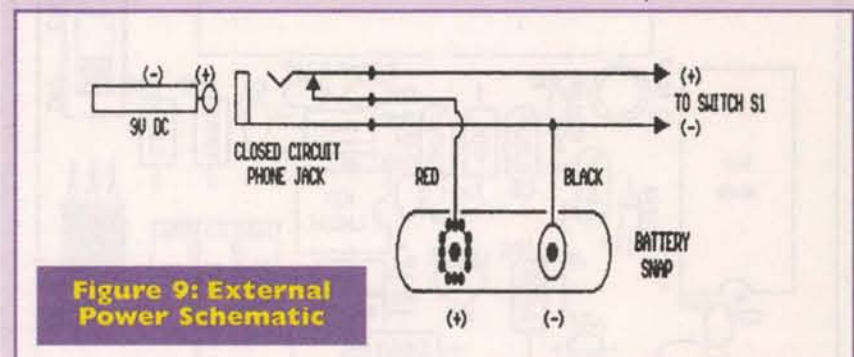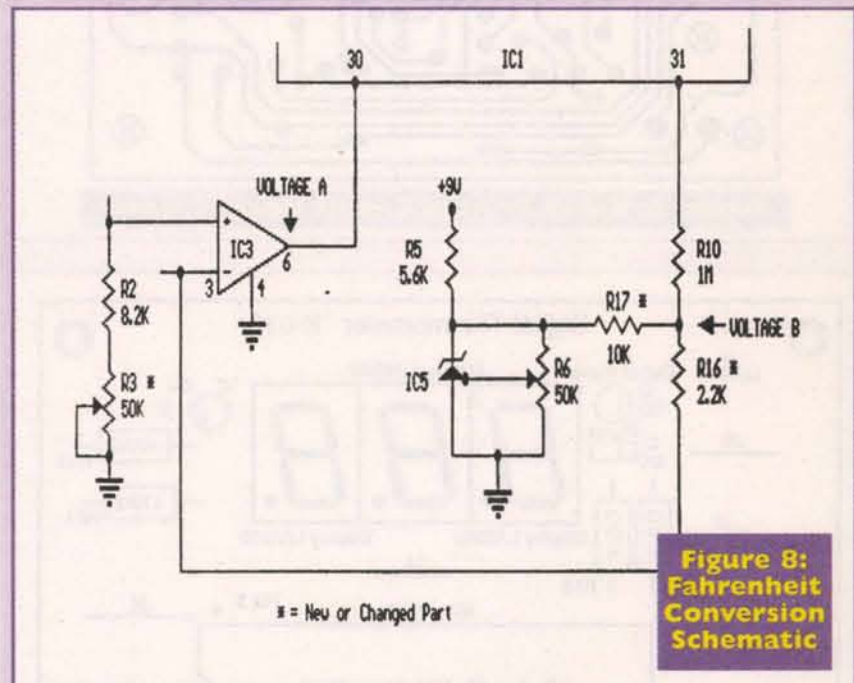Once the temperature sensor is mounted in the tube, it should be potted with some form of non-conductive substance, like epoxy, to keep the leads from shorting mechanically or in fluids.



the suggested drain for a typical 9V radio battery. As soon as the voltage drops below about seven volts, the K-038 readings become erratic. If you wish to add the capability of powering the K-038 externally, any common wall-plug transformer DC power supply can be used, as long as it supplies about nine volts at 250 milliamperes or more.

Figure 9 shows how a standard closed-circuit phone jack can be wired to disconnect the battery when external power is used. If you use external power, be certain it is DC, and that the polarity of the external power is proper.

## Packaging

As shown in the photos, we

packaged the K-038 Digital Thermometer in an empty translucent case designed to hold a video cassette. Since it was made of thin plastic, it was relatively easy to cut access holes and a "window" to view the digital display.


The printed circuit board was mounted display-up in the cover of the case using four screws and nuts. The switch and external power jack were also mounted on the cover, and the battery was held inside the cover with double-sided tape.

The sensor cable and probe come out through a notch in the bottom of the case.

Labels were made using a desktop publishing computer program, and pasted to the cover. **NV**



# New Product News

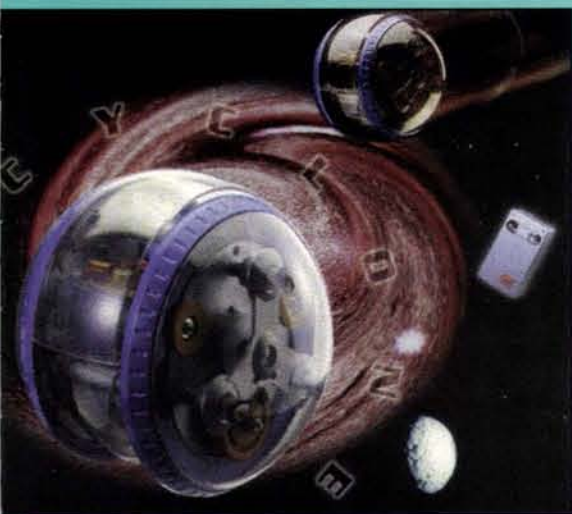

## CYCLONE ROBOT KIT

Powered by a wireless remote radio controller, Cyclone responds instantly to commands of 'spin,' 'swivel,' 'forward,' 'backward,' 'left,' or 'right.' Six different frequency settings offer a multitude of challenges, including speed races or timed, maze competitions. Control sticks afford the user complete control even as Cyclone swivels wildly from left to right.

Cyclone possesses a certain mystery and stands


apart from other MOVIT family members. Its unique design includes domes that protrude from the sides of two parallel wheels and see-through membrane that permits interior viewing to engage the eye. Engineers also will be intrigued by: a motion system based upon drive wheels and concentric discs that allow the user to propel its movement and, a ballast created by the batteries' weight to keep Cyclone's center upright.

Cyclone provides basic knowledge of wireless remote controllers and principles of gear mechanism. Suggested retail price: \$74.95.
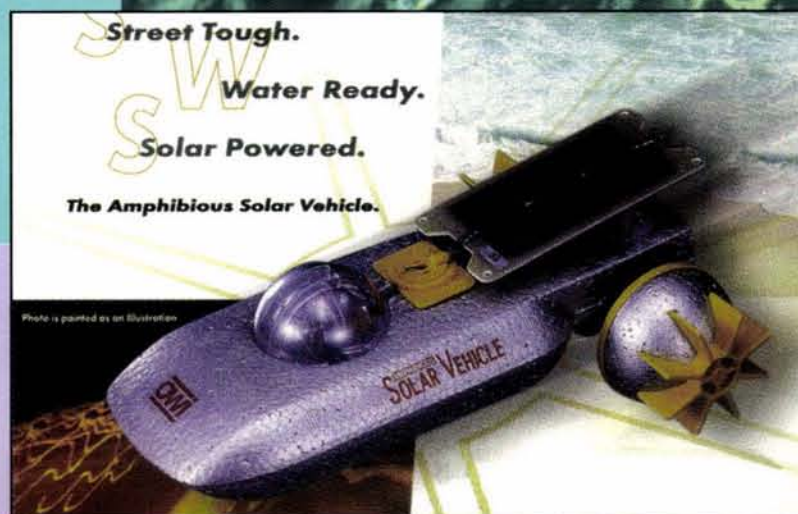
## AMPHIBIOUS SOLAR VEHICLE

This kit teaches and introduces the fundamentals of solar power through hands-on experiments. The sun or any intense mobile light can power the solar battery. The multiple function switch (solar or battery) allows this kit to be energized day or night, indoors or outdoors.

Its scientifically structured catamaran design reduces water resistance and makes capsizing more



difficult.

The user can explore different types of energy and energy conversion with this land and water vehicle.

Discover the world of alternative energy by learning what materials solar batteries are made from, characteristics of solar batteries, advantages and disadvantages of solar.

Suggested selling price: \$39.95.

For more information, contact:

**OWI, INC. OWI, INC.**  
17141 KINGSVIEW AVE., DEPT. NV  
CARSON, CA 90746  
310-515-1900 FAX: 310-515-1606  
E-MAIL: [owi@ix.netcom.com](mailto:owi@ix.netcom.com)  
WEB: <http://owi-inc.com> <http://owirobot.com>



## IC-T81A TRANSCEIVER

Icom America announces their newest handheld, the IC-T81A. This radio has it all with four bands, excellent audio, 124-memory channels, water resistant construction, and Icom durability.

The IC-T81A is only 2.3" in width by 4.2" in height and 1.1" thick, weighing only 9.9 oz. This slim, yet powerful radio covers the 6M, 2M, and 400 MHz at 5

watts output power and 1 watt on the 1.2 GHz band.


The IC-T81A boasts a five-position "joy stick" control for easy control of set mode, tone, duplex, volume, operating band, scanning and more, as well as an alphanumeric display for memory channel naming.

For more information, contact:

**ICOM AMERICA, INC.**  
2380 116TH AVE. N.E., DEPT. NV  
BELLEVUE, WA 98004  
425-454-8155 FAX: 425-454-1509  
WEB: [www.icomamerica.com](http://www.icomamerica.com)

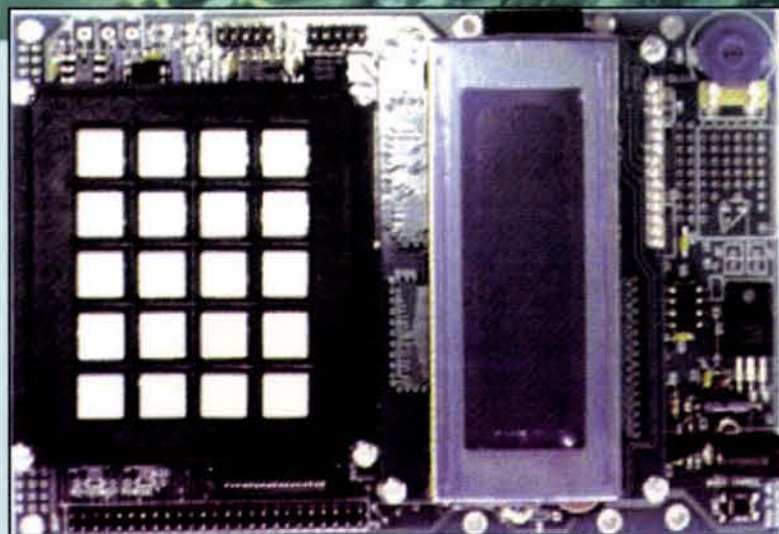**Showcase your New Products here! Send all press releases or information/photos to:**

**Nuts & Volts Magazine**  
New Product News  
430 Princland Court,  
Corona, CA 91719  
or E-Mail to  
[newproducts@nutsvolts.com](mailto:newproducts@nutsvolts.com)



## CP-550 HIGH-SPEED 8051 CARD

The CP-550 is a high-speed 8051 card featuring an optional LCD display and keypad. It uses the recently introduced 87C550 MPU.

The LCD display option supports two configurations: two lines of 20 characters, or four lines of 20 characters.

The microcontroller used on the CP-550 is the 87C550, which is an enhanced 8051 family derivative. It offers an eight-channel, 10-bit A/D converter, 8K bytes

of on-chip EPROM, 1K bytes of on-chip SRAM, PWM outputs, up to 55 digital I/O lines, optimized instruction execution, up to 33 MHz clock speed, two full-duplex serial ports, dual data pointers, power-fail reset, watchdog timer, 16 interrupt sources, and enhanced STOP and IDLE operations.

Other board features include RS-232 buffering on serial port 0, optional RS-232 or RS-485 buffering on serial port 1, and optional DS1286 calendar/clock chip.

The CP-550 comes with system monitor debugger software installed in the 87C550's EPROM. During development, this debugger allows user code to be downloaded in two battery-backed RAM, and then tested. Once

tested, user software can be burned into the available board EPROM.

For more information, contact:

**ALLEN SYSTEMS**  
2346 BRANDON RD., DEPT. NV  
COLUMBUS, OH 43221  
614-488-7122  
E-MAIL: [allensys@aol.com](mailto:allensys@aol.com)  
WEB: <http://members.aol.com/allensys>

## BA-1 BALUN BOX

LDG Electronics announces the introduction of the BA-1 Balun Box.

The 4:1 BA-1 provides an easy interface of ladder line and long-wire antennas to radio transceivers requiring an output impedance of 50 to 75 ohms.

This device is also the perfect complement to the AT-11, microprocessor controlled automatic antenna tuner.

The BA-1 is sold in kit and assembled form. The kit assembles in about 20 minutes and requires only minimal soldering skills. The BA-1 ships with an enclosure so there is nothing else required to complete the kit. The finished kit measures only 4.7 in. x 6.1 in. x 1.2 in. and weighs only 6 oz. Frequency coverage is 1.8 to 30 MHz and peak input power is 200 watts.

The BA-1 Balun kit retails for \$25.00 plus shipping. The assembled BA-1 retails for \$30.00.

For more information, contact:

**LDG ELECTRONICS, INC.**  
1445 PARRAN RD., DEPT. NV  
ST. LEONARD, MD 20685  
410-586-2177 FAX: 410-586-8475  
E-MAIL: [ldg@ldgelectronics.com](mailto:ldg@ldgelectronics.com)  
WEB: <http://www.ldgelectronics.com>



**Fantastic DMM Offer!**

Don't let this price fool you. This meter is a digital multimeter designed for engineers and hobbyists. Equipped with 5 functions and 19 ranges. Each test position is quickly and easily selected with a simple turn of the FUNCTION/RANGE selector rotary switch. **Rubber Boot Included!** Display: 3-1/2 Digit LCD, 21mm Figure Height with Automatic Polarity. Overrange Indication: 3 Least Significant Digits Blank. Temperature for Guaranteed Accuracy: 23°C ±5°C RH<75%. Temperature Ranges: Operating: 0°C to 40°C (32°F to 104°F) Storage: -10°C to 50°C (14°F to 122°F) Power: 9V Alkaline or Carbon-Zinc Battery (NEDA 1604) Low Battery Indication: BAT on Left of LCD Display Dimensions: 188mm(L) x 87mm(W) x 33mm thick Net Weight: 400g **Get All the Specs From Our Web Site**



**ONLY \$19**

**True RMS DMM**

- Full Sized, 4 1/2 Digit
- Frequency Range to 20 KHz
- Capacitance Ranges from 2000 pF to 20 uF
- hFe, Audible Continuity, 20A max 1000VDC/20A max & 700VAC max
- Selectable Data Hold Function

**CSi-980 DMM**  
More DMMs On Our Web Site



**ONLY \$69**

**Removable Hard Drive Rack**

For IDE/Ultra DMA Hard Drives

**We Sold Over 14,000 in 1998!**

This product can be used with any 3-1/2 IDE hard drive up to 1" high. It includes an electronic keylock for safe removal and insertion. Made of ABS 707 fireproof plastic. Use this product to protect sensitive hard drive data, take your hard drive between work and home or even set up different users with their own hard drives that they physically insert every time they use a PC. Other models available from C.S.I. include RH10 series and RH20 series, which are interchangeable within the same interface design (IDE or SCSI). **Other Models are Available. See www.web-tronics.com under "hard drive and accessories" for more details and pictures.**



**ONLY \$14.95**  
any qty.

**RH-10C-IDE**

**Our Most Sophisticated DMM**

**We Sold Over 700 Last Year!**  
with RS-232 Interface & Software, 3-3/4 Digit, 4000 Count, Auto-Ranging with Analog Bargraph

- True RMS Mode
- 10MHz Frequency Counter
- Time Mode with Alarm, Clock, and Stop Watch
- Dual Display
- 10 Location Memory
- Min, Max, Avg and Relative Mode
- Decibel Measurement
- Cap and Ind. Measurement
- Temperature Mode (C/F)
- K Type Temperature Probe Included
- Pulse Signal for Logic &



**PROTEK 506**

**SALE \$139**  
Reg. \$169

**Auto-Temp Solder Station with Ceramic Element**

- With Ceramic Heating Element for More Accurate Temp Adjustment
- 3 Conductor Grounded Power Cord
- 250°C-480°C (470°F-900°F)
- Fast Heating Feature

**SR-976** Extra Tip Options Available. See Web!



**ONLY \$39**

CTRL - D to bookmark this site

**www.web-tronics.com**

Don't forget the dash

**Circuit Specialists Inc.**

In Business Since 1971

- Easy to Navigate
- Includes a Search Engine That Really Works
- New Items Added Constantly

**CCD B&W Board Cameras**

- ASIC CCD Area Image Sensor
- Extremely Low Power Consumption
- 0.5 Lux Min Illumination
- Built-In Electronic Auto Iris for Auto Light Compensation

Detailed Specs on the Web



**VM1030PA-B**  
30mmx30mmx25mm, Pinhole lens with audio, 12V  
**\$49.00** any qty.



**VMCB21**  
44mmx38.5mmx28mm with 6 infra-red LEDs, 12V  
**\$49.00** any qty.



**VM1035A**  
42mmx42mmx25mm Standard lens with audio, 12V with back light compensation  
**\$59.00** any qty.



**VM1030A**  
30mmx30mmx26mm Standard lens with audio, 12V  
**\$49.00** any qty.



**VM1036A**  
32mmx32mmx25mm Standard lens with audio, 12V, reverse mirror image feature  
**\$59.00** any qty.

**Bullet CCD Cameras**

**B&W and Color**

- Smart Rugged Metal Housing
- Extremely Low Power Consumption
- 12 Volt
- CCD Area Image Sensor for Long Camera Life
- Built-In Electronic Auto Iris for Auto Light Compensation
- No Blooming, No Burning
- 0.1 Min Lux Illumination (B&W), 1 Lux Min Lux Illumination (color)



**VMBLT3025W**  
Digital Color, Weatherproof 20mm(D)x83mm(L)  
**\$189.00** any qty.



**VMBLT1020W**  
B&W Weatherproof 21mm(D)x58.5mm(L)  
**\$79.00** any qty.



**VMBLT1020A**  
B&W with audio 21mm(D)x55mm(L)  
**\$69.00** any qty.

Detailed Specs on the Web

**Protek**

**Series 6500 Deluxe 20MHz/40MHz/60MHz/100MHz Dual-Trace Oscilloscopes**

- Alternate Trigger
- Internal Sync Separator Circuit
- Alt-Mag Sweep
- Delay Sweep (6510)

**LATEST DESIGNS!**



**#6502 - 20MHz**  
**\$289**

**#6504 - 40MHz**  
**\$569**

**#6506 - 60MHz**  
**\$689**

**#6510 - 100MHz**  
**\$799**

**new! Mini CCDs (B/W & Color)**

**Sensational NEW Design for Small Observation Cameras. Smaller and Better!**

- Ultra Miniature Design
- Black & White Versions Only 25mm x 25mm
- Color Versions Only 32mm x 32mm Available in Standard Lens or Pinhole Lens
- All Include Audio
- All Include Pre-Wired Cable Harness for Audio, Video & Power
- 12V Regulated Power Supply Required (120mA typical power consumption)
- 0.1 LUX Rating (B/W), 1 LUX (color)
- CCD Area Image Sensor for Long Camera Life
- Back Light Compensation Circuit
- Built-In Electronic Auto Iris Lens



**VMPS-718A**  
25mmx25mmx30mm, B/W CCD with standard lens, pre-wired cabling for video/audio, 12V DC Power Input  
**\$69.00** \$59.00 5 or more



**VMCW-H11A**  
32mmx32mmx30mm, Color CCD with standard lens, pre-wired cabling for video/audio, 12V DC Power Input  
**\$149.00** \$139.00 5 or more



**VMCW-H12A**  
32mmx32mmx19mm, Color CCD with pinhole lens, pre-wired cabling for video/audio, 12V DC Power Input  
**\$149.00** \$139.00 5 or more



**VMPS-250A**  
25mmx25mmx15mm, B/W CCD with pinhole lens, pre-wired cabling for video/audio, 12V DC Power Input  
**\$69.00** \$59.00 5 or more

**new! Removable Hard Drive Rack with Auto Door And Cooling Fan**

- For 3,600 RPM - 5,400 RPM HDD
- Auto door on the outer frame
- ABS material of outer frame, High efficiency cooling fan
- Worldwide patent pulling function handle
- CE Approved
- Coating iron bottom cover
- For IDE interface
- For 1" high 3.5" HDD
- Not compatible with our RH10 & RH20 series. Compatible with our RH17-IDE model.



**#MR-27**

**ONLY \$18.95**  
any qty.

Details at www.web-tronics.com




**BOTH SINGLE AND DUAL  
DRIVE MODELS AVAILABLE.**

**INTERNAL A/V HARD DRIVE  
STORES DISC IMAGES FOR MULTIPLE  
COPIES, AND CUSTOM AUDIO DISCS.**

**EXTERNAL SCSI-II PORT WORKS  
LIKE A STANDARD CD WRITER  
FOR CREATING CUSTOM DISCS.**

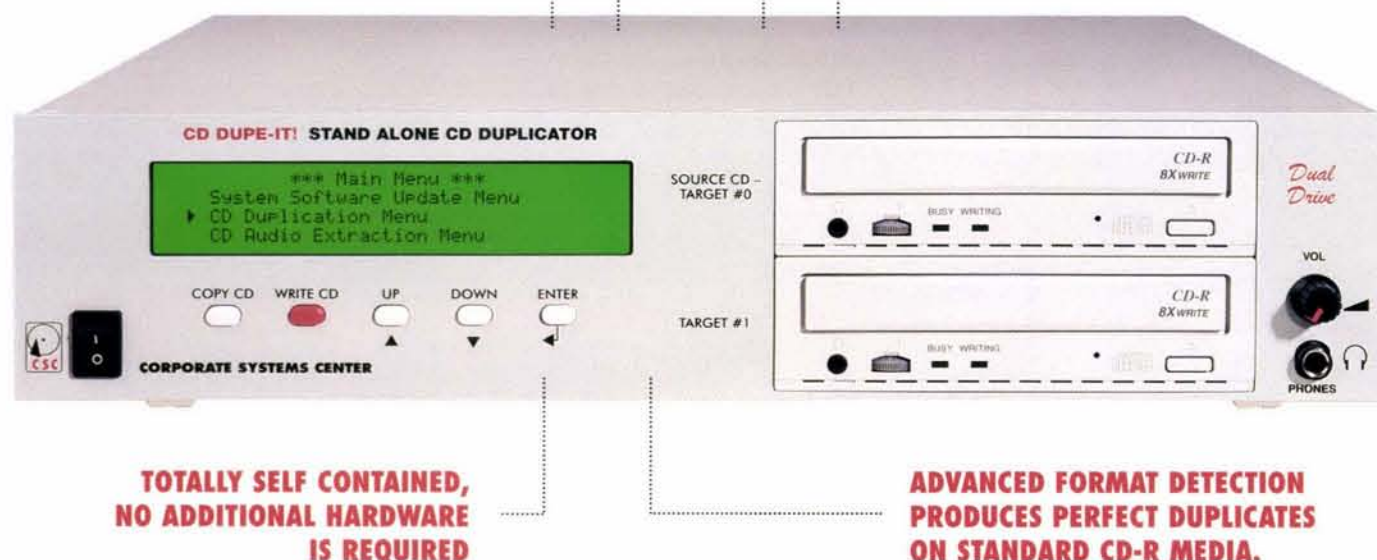**MAKE CUSTOM DISCS WITH  
JUST THE MUSIC YOU LIKE.**



**TOTALLY SELF CONTAINED,  
NO ADDITIONAL HARDWARE  
IS REQUIRED**

**ADVANCED FORMAT DETECTION  
PRODUCES PERFECT DUPLICATES  
ON STANDARD CD-R MEDIA.**

# COPY ANY CD NOW. NO PC REQUIRED.

## DUPE-IT!

Instantly copy music and CD-ROM compact discs. Make backup copies of your favorite music and software on rugged, permanent CDs. Produce compact discs quickly and economically. No mastering or multimedia experience is required.

Insert your original CD and press "start." The multimedia processor quickly copies any disc to the internal A/V hard drive. Insert blank CDs and make as many copies as you like. You'll produce perfect duplicates. The system is totally self contained — no additional hardware is required.

**FROM \$595!**

**100 BLANK CDs \$169!  
408 330-5524**

Just plug in the power cord and press "start"—it's that easy.

You can even make your own custom music CD without a PC! Insert your original CD's, select the tracks you want, and Dupe-It will copy them to the internal hard drive. Built in amplified stereo speakers allow you to preview the music before recording a CD. Then insert a blank CD, and you'll have a custom music CD with just the songs you want.

With the included CD mastering software, Dupe-It will work overtime as your personal CD design system. Just attach a SCSI cable to your PC or Mac, and you're ready to design and create your own original CD's. Similar systems used in duplication houses cost over \$5,000. Now you can easily copy CDs yourself for a fraction of the price.



**CORPORATE SYSTEMS CENTER**  
3310 WOODWARD AVE., SANTA CLARA, CA 95054  
**WWW.DUPEIT.COM**

Musicians—ask about our pro-audio CD recorders. Software publishers—ask about our high-volume multi-drive duplication systems. Dupe-It is sold and intended for backup and in-house design purposes only. Copyright laws must be observed. Dual 8x20 model is pictured above.




# BACK TO SCHOOL

With Parallax BASIC Stamps<sup>®</sup> and the Stamps in Class<sup>®</sup> educational program!
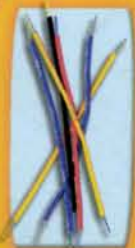
## Learn how to program the BASIC Stamp from our free resources!

If you're a hobbyist, consulting engineer, or student we're making it easier to learn how to program microcontrollers. We've spent a significant portion of 1999 with some specialists in robotics (Chuck Schoeffler, University of Idaho), environmental earth measurements (Tracy Allen, EME Systems), and the basics of programming (Matt Gilliland, I-Four). This resulted in a load of free microcontroller training material. Our curriculum and documentation is **free** for download at <http://www.stampsinclass.com>.

The Stamps in Class curriculum will show how to build a robot from your Board of Education, read temperature data from a DS1620 digital thermometer, calibrate a sensor, build circuits from schematics, and efficiently wire a breadboard. The curriculum can take somebody with no experience and bring them to the point where they can write their own source code. It's built around the BASIC Stamp, but the concepts apply to many types of microcontrollers.



**WWW.STAMPSINCLASS.COM**

RECOMMENDED  
AGES 16+

### What's a Microcontroller?

Introduction to microcontroller interfacing. Learn how to light LEDs on the Board of Education, and program the BASIC Stamp to make them blink. Projects include a servo activated by a photoresistor (grocery store door) and conclude with a manual and digital potentiometer.

### Earth Measurements

Learn the BASIC Stamp for control as it relates to the earth, ocean, space, or factory. Covers data collection, math conversion between C and F, and storing this data in EEPROM. Interface a light sensor with piezo speaker feedback. Create a feedback loop to control the level of water in a cup using a battery powered pump.

**PARALLAX**

toll free 888.512.1024  
info [www.parallaxinc.com](http://www.parallaxinc.com)

BASIC Stamp and the Parallax logo are registered trademarks of Parallax, Inc. Stamps in Class, the Board of Education, and Stampie are trademarks of Parallax, Inc.

## See new Parallax products at five Fall 1999 Trade Shows!

Complete information and tickets to these shows is shown at <http://www.parallaxinc.com>

**Sensors Expo**  
Cleveland, Ohio  
September 14-16, 1999  
Booth 825



**Embedded Systems Conference**  
San Jose, California  
September 26-30, 1999  
Booth 5031, right at the entrance!

**Robo Expo**  
San Francisco, California  
October 2-3, 1999



**Vintage Computer Festival**  
Santa Clara, California  
October 2-3, 1999  
Booth 1, right at the entrance!



**COMDEX Fall '99**  
Las Vegas, Nevada  
November 15-19, 1999



Write in 194 on Reader Service Card.

**NUTS & VOLTS MAGAZINE**  
430 PRINCELAND COURT  
CORONA, CA 91719

ADDRESS SERVICE REQUESTED

BULK RATE  
U.S. POSTAGE  
PAID  
PERMIT No. 49  
LONG BEACH CA

